 


VHDL for half subtractor [data flow style]

A	B	diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

It can subtract two binary numbers. It has two inputs & two outputs.

$$\text{diff} \leq (A \text{ XOR } B)$$
$$\text{Borrow} \leq ((\text{NOT } A) \text{ AND } B);$$



library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity and-gate is

Port (A, B: in std_logic;

Diff, Borrow: out std_logic);

end and-gate;

Architecture and_arch of and-gate is

begin


diff <= (A XOR B);

Borrow <= ((NOT A) AND B);

end and_arch;

function in digital computer

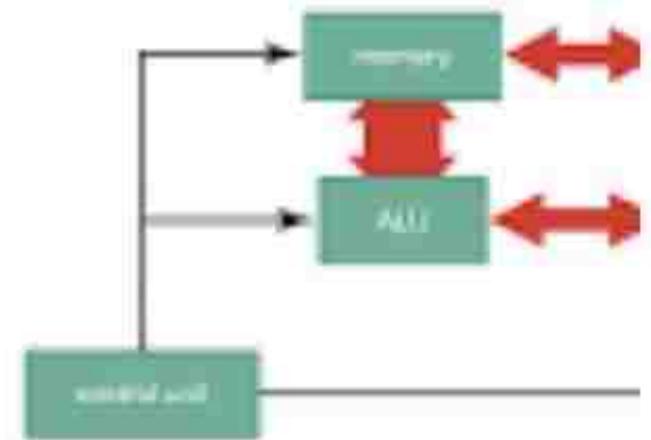The ALU performs **simple addition, subtraction, multiplication, division, and logic operations, such as OR and AND**. The memory stores the program's instructions and data.




© Engstrom & Jones, Inc.

operation	Inputs			Outputs
	S2	S1	S0	F
clear	0	0	0	F=0000
B-A	0	0	1	B-A
A-B	0	1	0	A-B
ADD	0	1	1	A+B+CIN
XOR	1	0	0	A XOR B
OR	1	0	1	A OR B
AND	1	1	0	A AND B
PRESET	1	1	1	F=1111

Disadvantages of Ripple Carry Adder-

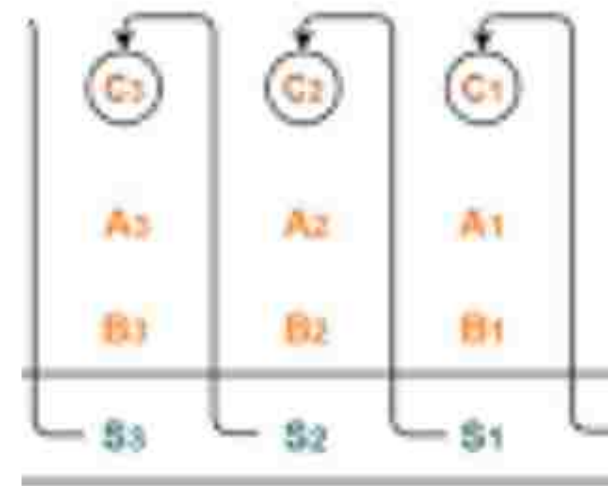- Ripple Carry Adder does not allow to use all the full adders simultaneously.
- Each full adder has to necessarily wait until the carry bit becomes available from its adjacent full adder.
- This increases the propagation time.
- Due to this reason, ripple carry adder becomes extremely slow.



Adding two 4-bit Numbers

BCD to 7 segment decoder

library IEEE;

use IEEE-STD-LOGIC-164.all;

Entity codeconverter is

Port (bcd : in std-logic-vector (3 downto 0));

leds : out std-logic-vector (6 downto 0);

end codeconverter;

Architecture codeconverter_arch of codeconverter is

begin

Process (bcd)

begin

case bcd is

when "0000" => leds <= "1111110";

when "0001" => leds <= "0110000";

when "0010" => leds <= "1101101";

when "0011" => leds <= "111001";

when "0100" => leds <= "0110011";

when "0101" => leds <= "1011011";

when "0110" => leds <= "0111111";

when "0111" => leds <= "1110000";

when "1000" => leds <= "1111111";

when "1001" => leds <= "1111011";

when others => leds <= "-----";

end case;

end process;

end code_converter_arch;

VHDL Code For 4 to 1 Multiplexer

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux_4to1 is
    port(
        A,B,C,D : in STD_LOGIC;
        S0,S1: in STD_LOGIC;
        Z: out STD_LOGIC
    );
end mux_4to1;

architecture bhv of mux_4to1
is
begin
process (A,B,C,D,S0,S1) is
begin
    if (S0 = '0' and S1 = '0')
then
        Z <= A;
    elsif (S0 = '1' and S1 =
'0') then
        Z <= B;
    elsif (S0 = '0' and S1 =
'1') then
        Z <= C;
    else
        Z <= D;
    end if;
end process;
end bhv;
```

VHDL Code for 1 to 4 Demux

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity demux_1to4 is
  port(
    F : in STD_LOGIC;
    S0,S1: in STD_LOGIC;
    A,B,C,D: out STD_LOGIC
  );
end demux_1to4;

architecture bhv of
demux_1to4 is
begin
  process (F,S0,S1) is
  begin
    if (S0 = '0' and S1 = '0')
  then
    A <= F;
    elsif (S0 = '1' and S1 = '0')
  then
    B <= F;
    elsif (S0 = '0' and S1 = '1')
  then
    C <= F;
    else
    D <= F;
    end if;
  end process;
end bhv;
```


Circuit Design of 4 to 16 Decoder Using 3 to 8 Decoder

A decoder circuit of the higher combination is obtained by adding two or more lower combinational circuits. 4 to 16 decoder circuit is obtained from two 3 to 8 decoder circuits or three 2 to 4 decoder circuits.

When two 3 to 8 Decoder circuits are combined the enable pin acts as the input for both the decoders. When enable pin is high at one 3 to 8 decoder circuits then it is low at another 3 to 8 decoder circuit.

VHDL Code for 4 to 2 encoder using logic gates

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity encoder2 is
  port(
    a : in STD_LOGIC_VECTOR(3
downto 0);
    b : out STD_LOGIC_VECTOR(1
downto 0)
  );
end encoder2;

architecture bhv of encoder2
is
begin

b(0) <= a(1) or a(2);
b(1) <= a(1) or a(3);

end bhv;
```

VHDL Code for 2 to 4 decoder using logic gates

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity decoder2 is  
  port(  
    a : in STD_LOGIC_VECTOR(1  
downto 0);  
    b : out STD_LOGIC_VECTOR(3  
downto 0)  
  );  
end decoder2;
```


```
architecture bhv of decoder2  
is  
begin
```

```
b(0) <= not a(0) and not  
a(1);  
b(1) <= not a(0) and a(1);  
b(2) <= a(0) and not a(1);  
b(3) <= a(0) and a(1);
```

```
end bhv;
```

b) Draw the circuit and explain the operation of binary adder subtractor.

Ans.

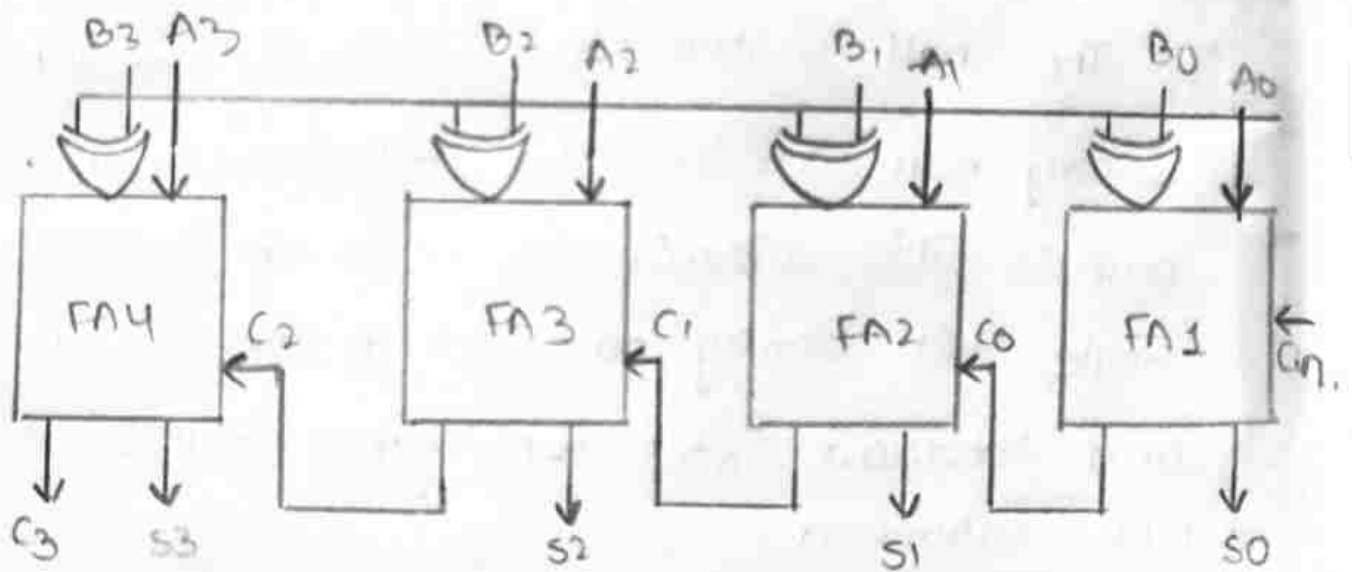

A Binary Adder subtractor is one which is capable of both addition and subtraction of binary numbers in one circuit itself. The operation being performed depends upon the binary value the control signal holds. It is one of the components of the ALU.

This circuit requires XOR gate, full adder, Binary addition and subtraction.

• As shown in fig, the first full adder has control line directly as its input (C_{in}). The input A_0 is directly input in FA 1. The 3rd input is the XOR of B_0 and m . The two outputs produced are S_0 and C_0 .

If the value of m is 1 the output of $B_0 \oplus B_0'$ is 1. Thus the operation would be $A + (B_0')$. Now 2's comp

subtraction for two numbers A & B is given by $A + B'$.

This suggests that when $k=1$, the operation being performed on the four bit numbers is subtraction.

parallel Binary Adder/Subtractor

library IEEE;

use IEEE.STD_LOGIC_1164.all;

Entity PBAS is

Port (A: in std_logic_vector (0 to 3);

B: in std_logic_vector (0 to 3);

Cin, m: in std_logic;

S: out std_logic_vector (0 to 3);

C: out std_logic_vector (0 to 3));

End PBAS;

Architecture PBAS_arch of PBAS is

signal D0, D1, D2, D3, D4, D5, D6, D7: std_logic;

component FA

Port (I0, I1, I2: in std_logic;

sum, carry: out std_logic);

End component;

component XOR

Port (I3, I4: in std_logic;

I5: out std_logic);

End component;

begin

L1: XOR portmap (B(0), D0, D1);

L2: XOR portmap (B(1), D2, D3);

L3: XOR portmap (B(2), D4, D5);

L4: XOR portmap (B(3), D6, D7);

L5: FA portmap (A(0), D1, (Cin, S(0), C(0)));


L6: FA portmap (A(1), D3, C(0), S(1), C(1));

L7: FA portmap (A(2), D5, C(1), S(2), C(2));

L8: FA portmap (A(3), D7, C(2), S(3), C(3));

End PBAS_arch;

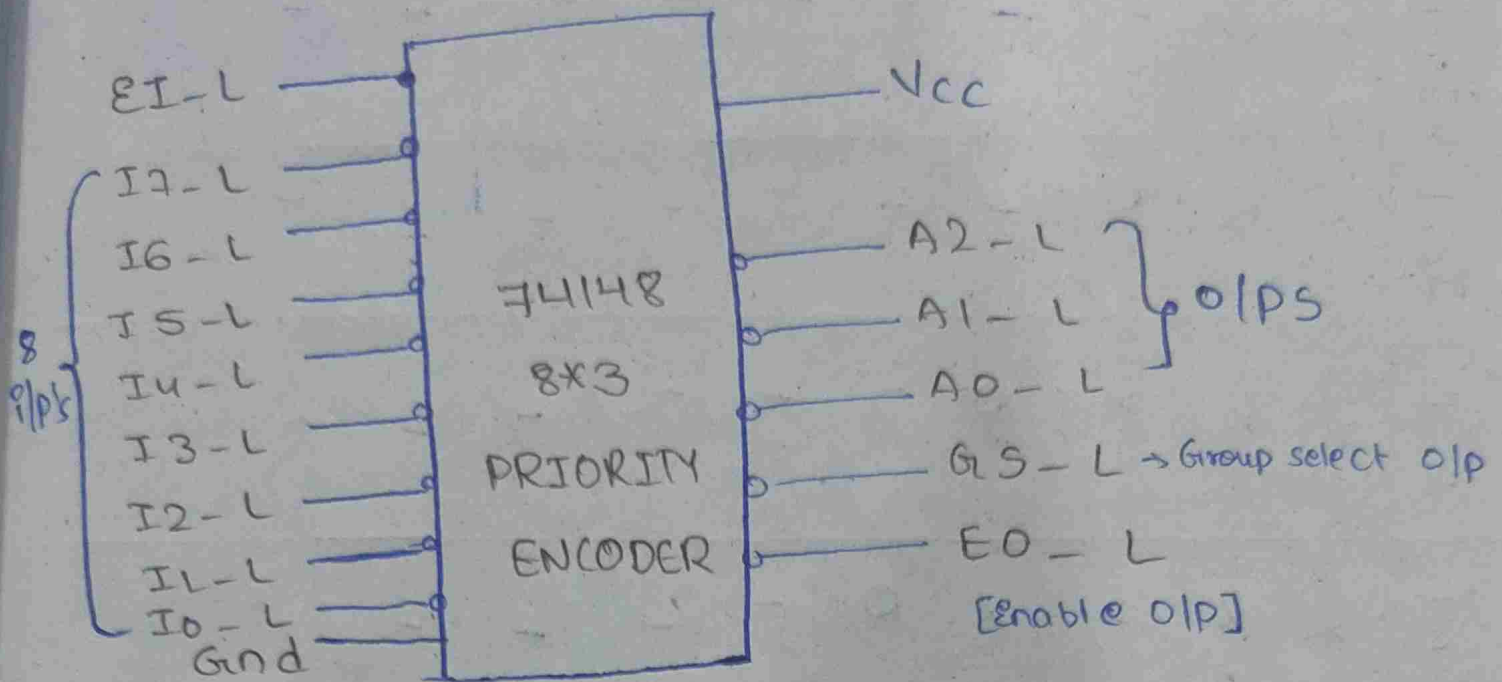74148 [PRIORITY ENCODER] $\rightarrow (8 \times 3)$



GS-L [when more than 1 i/p is asserted]

$$M_7 = I_7$$

$$M_6 = I_6 \cdot I_7'$$

$$M_5 = I_5 \cdot I_6' \cdot I_7'$$

$$M_4 = I_4 \cdot I_5' \cdot I_6' \cdot I_7'$$

$$M_3 = I_3 \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$$

$$M_2 = I_2 \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$$

$$M_1 = I_1 \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$$

$$M_0 = I_0 \cdot I_1' \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$$

$$A_2-L = M_4 + M_5 + M_6 + M_7$$

$$A_1-L = M_2 + M_3 + M_6 + M_7$$

$$A_0-L = M_1 + M_3 + M_5 + M_7$$

library IEEE;

use IEEE.STD_LOGIC_1164 all;

entity priority_encoder is

Port (I_L: in std_logic_vector (7 downto 0);

EI_L: in std_logic;

A_L: out std_logic_vector (2 downto 0);

GS_L, EO_L: out std_logic);

end priority_encoder;

Architecture priority_encoder_arch of priority_encoder is

signal EI, EO, GS: std_logic;

signal A: std_logic_vector (2 downto 0) := "000";

signal I: std_logic_vector (7 downto 0);

begin

EI <= (not EI_L);

I <= (not I_L);

EO <= '1';

GS <= '0';

if EI = '0' then EO <= '0';

else

for j in 7 downto 0 loop

if I(j) = '1' then

GS <= '1';

EO <= '0';

A <= conv_std_logic_vector (j, 3);

exit;

end if;

end loop;

end if;

EO-L <= (not EO);

GS-L <= (not GS);

A-L <= (not A);

end process;

end priority. Encoded arch,

$P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$

Program: 4-BIT CLA Program

Library IEEE;

Use IEEE-STD-LOGIC-1164 all;

Entity cla_block is

Port (P, G : in std_logic_vector (3 down to 0);

 Cin : in std_logic;

 C : out std_logic_vector (4 down to 0));

end cla_block;

Architecture cla_arch of cla_block is

begin

C(0) <= Cin;

C(1) <= ((P(0) AND C(0)) OR G(0));

C(2) <= ((P(1) AND P(0) AND C(0)) OR (P(1) AND G(0))

OR G(1));

C(3) <= ((P(2) AND P(1) AND P(0) AND C(0)) OR ((P(2) AND P(1) AND G(0)) OR (P(2) AND G(1)) OR G(2));

$$C(4) \leftarrow (P(3) \text{ AND } P(2) \text{ AND } P(1) \text{ AND } P(0) \text{ AND } C(0))$$

$$\text{OR } (P(3) \text{ AND } P(2) \text{ AND } P(1) \text{ AND } B(0)) \text{ OR}$$

$$(P(3) \text{ AND } P(2) \text{ AND } G(1)) \text{ OR } (P(3) \text{ AND } G(2))$$

$$\text{OR } G(3);$$

4-CLA ADDER PROGRAMS

A	[A3	A2	A1	A0	S
B	[B3	B2	B1	B0	Cout
Co						

library IEEE;

use IEEE.STD-LOGIC-1164.all;

entity adder is

Port (A, B : in std_logic_vector(3 downto 0);

Co : in std_logic;

s : out std_logic_vector(3 downto 0);

Cout : out std_logic);

end adder;

Architecture adder_arch of adder is

signal P, G : std_logic_vector(3 downto 0) := "0000";

signal C : std_logic_vector(4 downto 0) := "0000";

Component cla_block

Port (P, G : in std_logic_vector(3 downto 0);

Co : in std_logic;

C : out std_logic_vector(4 downto 0));

end component;

begin

$P \leftarrow (A \text{ XOR } B);$

$G \leftarrow (A \text{ AND } B);$

L1: clb-block port map (P, G, Co, C);

$S \leftarrow (P \text{ XOR } C \text{ (3 down to 0)});$

$\text{Cout} \leftarrow C(4);$


end adder_4bit;

a) 2-INPUT 4-BIT MULTIPLEXER

The MSI, 74X157 is a 2-input, 4-bit Multiplexer. This multiplexer has two sets of 4-bit inputs. It also has 4-bit outputs. The single select input line allows the first set of four inputs or the second set of 4-inputs to be connected to the output. Thus four-bits of data from two sources are routed to the output. The function table and the circuit of the multiplexer are shown. table 18.1, figure 18.1

The multiplexer has two sets of 4-bit active-high inputs 1A, 2A, 3A, 4A and 1B, 2B, 3B, 4B respectively. The multiplexer has 4-bit active-high outputs 1Y, 2Y, 3Y 4Y. The single select input allows either the 4-bit input A or the 4-bit input B to be connected to the 4-bit output Y. The G active-low pin enables or disables the Multiplexer.

74157 [MULTIPLEXER]

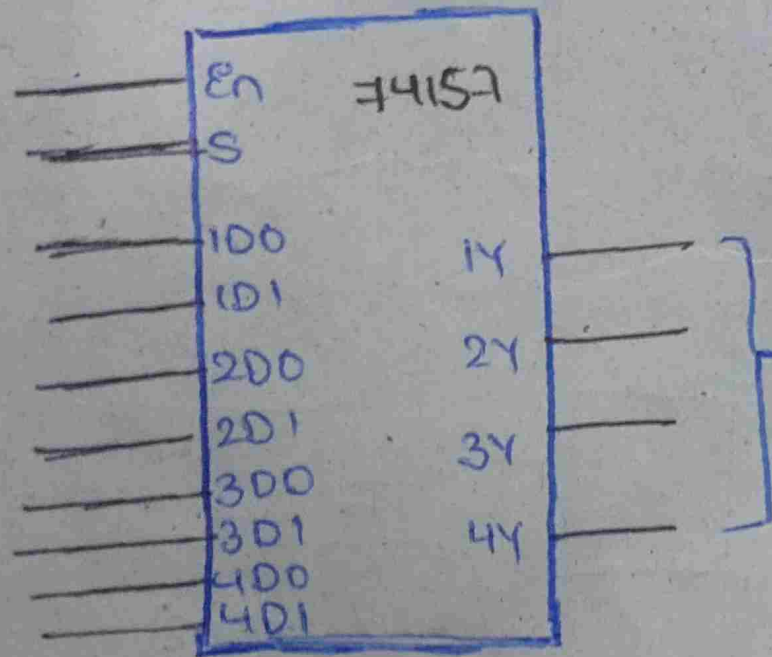

Y [4-bits]

Inputs		Output			
En-1	S	1Y	2Y	3Y	4Y
1	X	0	0	0	0
0	0	1D0	2D0	3D0	4D0
0	1	1D1	2D1	3D1	4D1

Assessted as $\rightarrow [1D0 \ 2D0 \ 3D0 \ 4D0] \rightarrow [A_3 \ A_2 \ A_1 \ A_0]$

$[1D1 \ 2D1 \ 3D1 \ 4D1] \rightarrow [B_3 \ B_2 \ B_1 \ B_0]$



$Y \rightarrow [Y(3) \ Y(2) \ Y(1) \ Y(0)]$
 $\rightarrow [1Y \ 2Y \ 3Y \ 4Y]$

```

library IEEE;
use IEEE.STD-LOGIC-1164.all;
entity mux is
Port (en_1 : in std_logic;
      s : in std_logic;
      Y : out std_logic_vector(3 downto 0);
      A, B : in std_logic_vector(3 downto 0));
end mux;
Architecture mux_arch of mux is
signal k : std_logic_vector(3 downto 0);
begin
with s select
    k <= A when '0';
    B when '1';
    '0' when others;
Y <= k when en_1 = '1' else Y <= "000";
end mux;

```


74820 [9-bit parity Generator]:

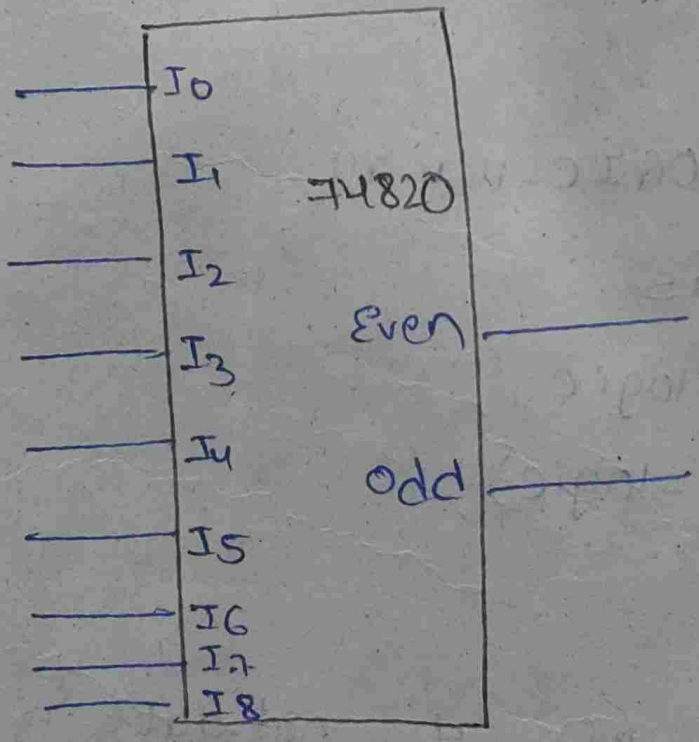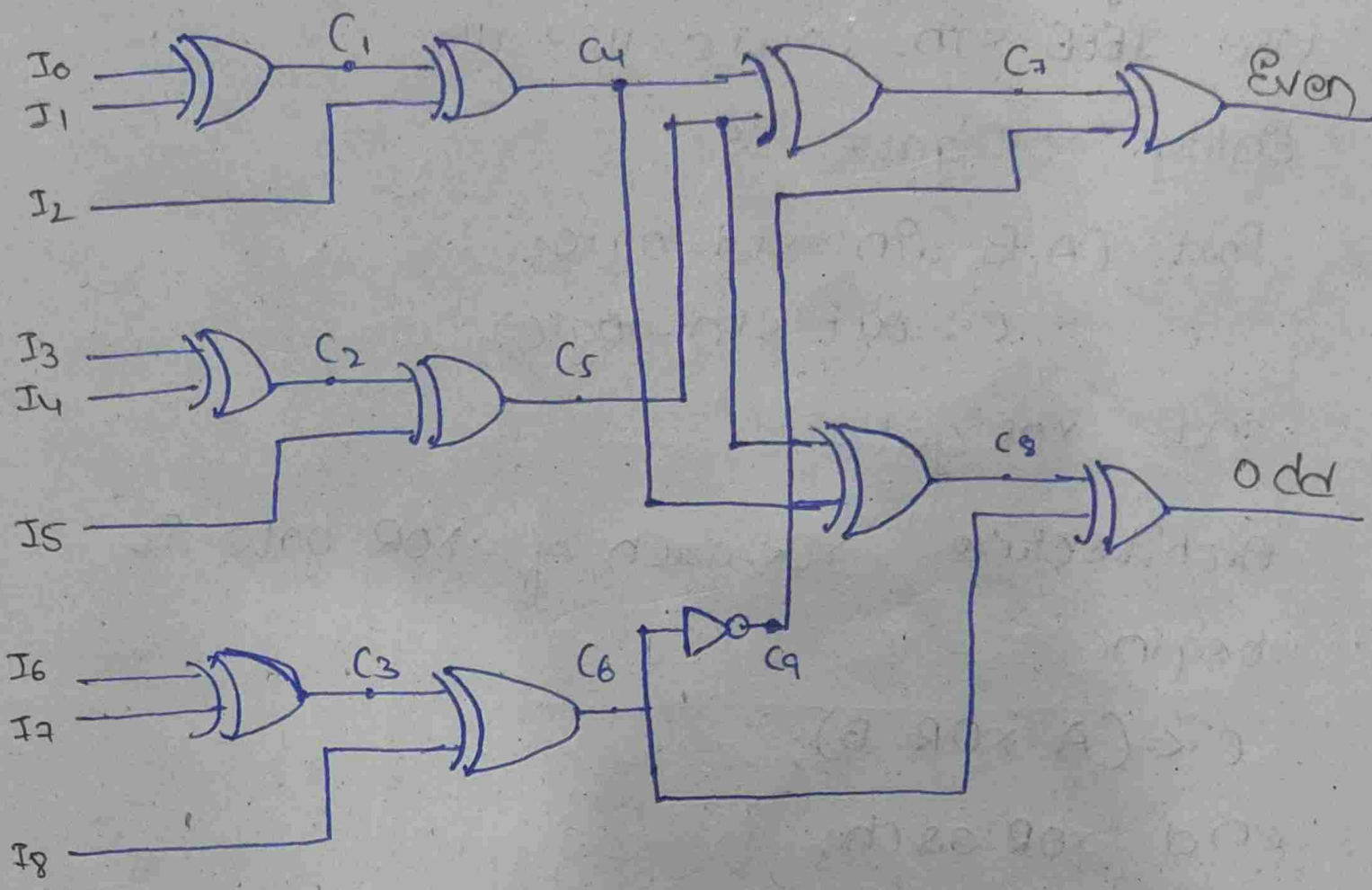

XOR Gate

library IEEE;

use IEEE.STD-LOGIC-1164.all;

Entity XOR-gate is

Port (A, B : in std-logic;

C : out std-logic);

end XOR-gate;

Architecture XOR-arch of XOR gate is

begin

C <= (A XOR B);

end XOR-arch;

NOT gate

library IEEE;

use IEEE.STD-LOGIC-1164.all;

Entity NOT-gate is

Port (D : in std-logic;

Y : out std-logic);

end NOT-gate;

Architecture NOT-arch of not-gate is

begin

Y <= (NOT D);

end NOT-arch;

library IEEE;

use IEEE.STD_LOGIC_1164.all;

Entity 9-bit parity is

Port (I: in std_logic_vector (8 downto 0);

Even, odd: out std_logic);

end 9-bit parity;

Architecture parity_arch of 9-bit parity is

signal c: std_logic_vector (9 downto 0);

component xor_gate

Port (A, B: in std_logic;

c: out std_logic);

end component;

component NOT_gate

Port (D: in std_logic;

y: out std_logic);

end component;

begin

L1: XOR1 port map (I(0), I(1), c(1));

L2: XOR2 port map (I(3), I(4), c(2));

L3: XOR3 port map (I(6), I(7), c(3));

L4: XOR4 port map (c(1), I(2), c(4));

L5: XOR5 port map (c(2), I(5), c(5));

L6: XOR6 port map (c(3), I(8), c(6));

L7: XOR7 port map (c(4), c(5), c(7));

L8: XOR 8 port map (c(4), c(5), c(8));

L9: NOT 1 port map (c(6), c(9));

L10: XOR 9 port map (c(7), c(9), even);

L11: XOR 10 port map (c(8), c(6), odd);

end parity_aech;

VHDL Code for 2 to 4 decoder using case statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder is
port (
a : in STD_LOGIC_VECTOR(1
downto 0);
b : out STD_LOGIC_VECTOR(3
downto 0)
);
end decoder;
architecture bhv of decoder
is
begin

process (a)
begin
case a is
when "00" => b <= "0001";
when "01" => b <= "0010";
when "10" => b <= "0100";
when "11" => b <= "1000";
end case;
end process;

end bhv;
```

