

10/01/19
Tuesday

UNIT - IV

ACTIVE FILTERS

- Filter is nothing but separation and gives desired comp. quantities matter. It separates unwanted particles from desired particles.
- power supply is nothing but converter of AC signal into pure DC signal.
- Here the characters of signal are frequency, phase, amplitude. Here signals are separated from based on frequencies.

Filters are 3 types they based on components. they are
 (i) passive and active filter.
 based on signal

(ii) analog and digital filter.


Based on frequency range

(i) audio & radio frequency filters.
 (20-20K) (>20KHZ)


→ Here filters are mainly of active and passive filters. If the filter is constructed by resistor, inductor, transistor, capacitor then it is called passive filter and the filter is constructed by op-amp, resistor and capacitor then it is called active filter.

→ If we use inductor, at lower frequencies we use want high value of inductance this increases the winding and resulting it increases size & power dissipation. Now this is one drawback in passive filters.

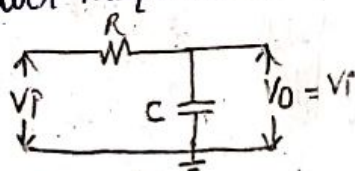→ In passive low pass filter it allows lower frequencies and (gain is maximum) and rejects lower frequencies.



$X_C = \frac{1}{\omega C}$

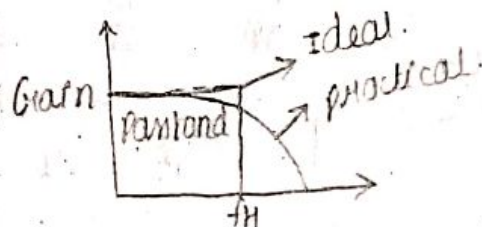

$f_H = \frac{1}{2\pi RC}$

In ideal output is same as input at lower frequencies but in practical, output has some drops and output is gradually reduces after cut-off frequency.


→ Here Gain is also not adjusted in passive filter. These are another drawbacks of passive filter. → Here for ideal characteristics, the output must be nearly reduce its gain. Here so we want high gain roll-off for high gain which we use want to increase number of orders.



So if we use number of orders then drop across each element and leads to decrease in output voltage. So the o/p is decreased then it leads to loading effect.

Drawbacks of passive filters:

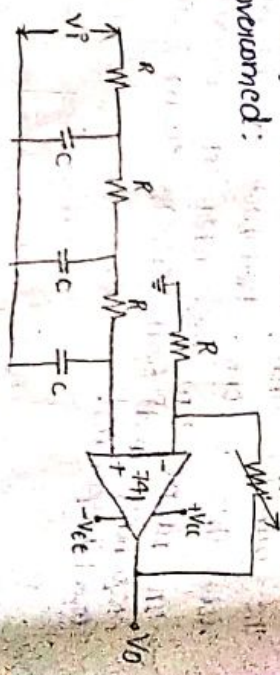1. Start size is increases.
 2. Power dissipation is large.
 3. Practical characteristics are doesn't match with the ideal characteristics.
 4. Loading effect is occurs.
 5. Impedance is mismatched.
- By using active filters the above all drawbacks are overcome.



In the above circuit, the power dissipation and size are decreased because we didn't use any inductor coil. Hence so the first two drawbacks are overcome.

And here the output characteristics are nearly ideal characteristics. So the third drawback is also overcome. For op-amp the input impedance is very large i.e. infinity. So for any low amount of input the circuit can able to drive the load. So the fourth drawback is also overcome.


Here the output impedance is low so we can easily connected to load so the impedance is matched to drive the load. Hence in drawback is overcome. In the above circuit we use one rheostat by changing the rheostat position we can adjust the gain of the circuit. So the 6th drawback is also overcome.

Types

- The mostly used filters are
- (i) Lowpass
 - (ii) Highpass
 - (iii) Bandpass
 - (iv) Band rejection
- First order low pass active filter:

Here we use buffer with approximation lead-lag.

Uses: for analysis purpose.

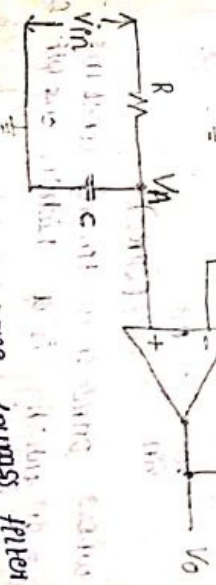

Here we use only one lowpass filter and the phase non-inverting terminal and the phase difference

between output and input & On.

- To know the whether the ckt. acts as LP or not we must know its frequency response
- To know frequency response we know Gain change with respect to frequency.
- To know Gain we know about output voltage.
- Here the input for op-amp is V_i and output is V_o . And this is a non-inverting amplifier. So Gain is $1 + \frac{R_f}{R_1}$ the overall Gain of the ckt is $\frac{V_o}{V_i}$.

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_i$$

$$A_f = \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_1}\right) \rightarrow \text{Gain}$$

By using voltage division rule we can measure V_i

$$V_i = \frac{V_o \frac{R_1}{R_1 + R_f}}{R_1 + R_f}$$

$$V_o = \frac{V_i (R_1 + R_f)}{R_1}$$

from (1); $V_o = A_f \frac{V_i}{1 + \frac{R_f}{R_1}}$

$$\frac{V_o}{V_i} = \frac{A_f}{1 + \frac{R_f}{R_1}}$$

$$\frac{V_o}{V_i} = \frac{A_f}{1 + \frac{R_f}{R_1}}$$

$$\frac{V_o}{V_i} = \frac{A_f}{1 + \frac{R_f}{R_1}}$$

where $\frac{R_f}{R_1}$ is a frequency constant. $\frac{1}{1 + \frac{R_f}{R_1}}$ = frequency cut-off frequency.

So $\frac{1}{2\pi RC} = f_H$ where f_H is a higher cut-off frequency.

$$\frac{V_o}{V_i} = \frac{A_f}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{A_f}{\sqrt{1 + (f/f_H)^2}}$$

$$\phi = -\tan^{-1} \left(\frac{f}{f_H} \right)$$

f	Gain	Gain in dB
0	Af	Af
1Hz	Af	Af
100Hz	Af	Af
f = fH	Af/√2	(Af) - 3dB
f > fH	Gain & decreases.	




* Design a LPF with cut-off frequency 10kHz and Gain is 2. Draw the frequency response

Q: Design a ckt $\left| \frac{V_o}{V_i} \right| = \frac{A_f}{\sqrt{1 + (f/f_H)^2}}$

Given $A_f = 2$ and $f_H = 10\text{kHz}$

$$\left| \frac{V_o}{V_i} \right| = \frac{2}{\sqrt{1 + (f/10k)^2}}$$

f	Gain	Gain in dB
0	2	6.0205
10Hz	1.999	6.0201
100Hz	1.999	6.02
500Hz	1.9975	6.009
1kHz	1.9907	5.98
5kHz	1.7889	4.5051
10kHz	1.4142	3.0102
20kHz	0.8944	-0.969
30kHz	0.6324	-3.979
50kHz	0.3922	-8.1291

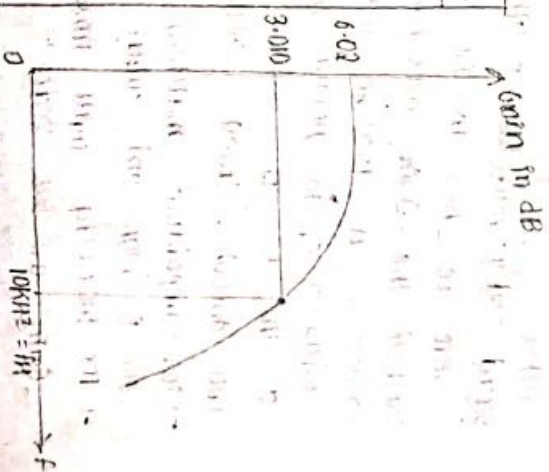

13/01/19

After cut-off frequency we want maximum atten. and no here we have 1 decade ft reduces 20 db gain only

$$\left| \frac{V_o}{V_i} \right| = \frac{AF}{\sqrt{1+(f/f_H)^2}}$$

if $f > f_H$, neglect 1 then

$$\left| \frac{V_o}{V_i} \right| = \frac{AF}{(f/f_H)}$$

$$\left| \frac{V_o}{V_i} \right|_{dB} = 20 \log \left(\frac{AF}{(f/f_H)} \right)$$

$$20 = 20 \log (AF (f_H)^{-1}) \quad [f = 10k \ \& \ f_H = 1k]$$

$$\left| \frac{V_o}{V_i} \right|_{dB} = -20 \log (\text{constant gain})$$

no for every 1 decade of frequency gain reduces (roll off) by 20db.

→ so here the ideal and practical characteristics are not matched due to not having any sharp cutting reduction of gain.

so we have to go for second order active low pass filter.

second order Butterworth filter:


Here we have increase chosen order at input to roll off the gain maximum gain.

→ here we use two RC sections. If we connect the capacitor C_1 to ground the input of the impedance of the circuit is reduced due to minimum current flow through lowest resistance path.

→ For impedance matching the input resistance of circuit is high and output resistance is small.

→ For increasing input impedance and for better gain we use feedback from C_1 to output.


when the circuit becomes.

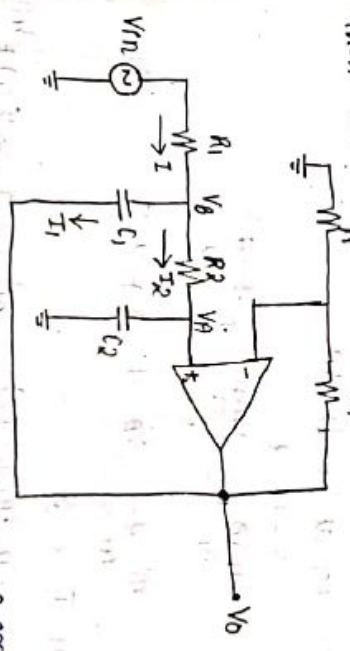

Analysis: here we have to calculate frequency response to know whether the circuit acts as LPF or not. For frequency response, we have to calculate output gain changes with respect to frequency V_o .

$$V_o = AF V_i$$

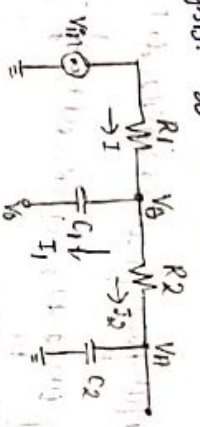→ For gain we have to calculate output voltage V_o .



By voltage division rule

$$V_i = V_o \left(\frac{R_2 + \frac{1}{j\omega C_2}}{R_1 + R_2 + \frac{1}{j\omega C_2}} \right)$$

$$V_i = \frac{V_o \left(\frac{1}{j\omega C_2} \right)}{R_2 + \left(\frac{1}{j\omega C_2} \right)}$$

$$V_i = \frac{V_o}{1 + sR_2C_2}$$

$$V_o = V_i (1 + sR_2C_2)$$

[Here directly finding V_o is difficult so we have to apply superposition theorem. No we calculate it

through V_A]

Apply KCL at node V_B

$$I = I_1 + I_2$$

$$\frac{V_B - V_0}{R_1} + \frac{V_B - V_A}{R_2} = \frac{V_B - V_0}{sC_1} + \frac{V_B - V_A}{R_2}$$

$$\frac{V_B - V_0}{R_1} = (V_B - V_0)(sC_1) + \frac{V_B - V_A}{R_2} \quad \rightarrow \textcircled{1}$$

Exam ① & ②

$$\textcircled{2} \Rightarrow \frac{V_B - V_A (1 + sR_2C_2)}{R_1} = (V_A (1 + sR_2C_2) - V_0)(sC_1) + \frac{V_B - V_0}{R_2}$$

$$\frac{V_B - V_A - V_A sR_2C_2}{R_1} = sC_1 V_A + V_A sR_2C_2 sC_1 - V_0 sC_1 + \frac{V_B - V_0}{R_2}$$

$$\frac{V_B - V_A - V_A sR_2C_2}{R_1} = sC_1 V_A + V_A sR_2C_2 sC_1 - V_0 sC_1 + \frac{sR_2C_2 V_B}{R_2}$$

$$\frac{V_B - V_A - V_A sR_2C_2}{R_1} = sC_1 V_A + V_A sR_2C_2 sC_1 - V_0 sC_1 + \frac{sR_2C_2 V_B}{R_2}$$

$$\frac{V_B - V_A - V_A sR_2C_2}{R_1} = sC_1 V_A + V_A sR_2C_2 sC_1 - V_0 sC_1 + \frac{sR_2C_2 V_B}{R_2}$$

$$\frac{V_B}{R_1} + V_0 sC_1 = -V_A (1 + sR_2C_2) + sC_1 V_A + V_A sR_2C_2 sC_1 + sC_2 V_B$$

$$\frac{V_B}{R_1} = V_A \left[\frac{(1 + sR_2C_2)}{R_1} + sC_1 + V_A sR_2C_2 sC_1 + sC_2 V_B \right] - V_0 sC_1$$

$$V_A = \frac{\frac{V_B}{R_1} + sC_2 V_B}{\frac{(1 + sR_2C_2)}{R_1} + sC_1 + sR_2C_2 sC_1 + sC_2 R_1 - \frac{V_0 sC_1 R_1}{V_B}}$$

$$V_A = \frac{V_B + sC_2 R_1 V_B}{(1 + sR_2C_2) + sR_1 C_1 + sR_2C_2 sC_1 R_1 - \frac{V_0 sC_1 R_1}{V_B}}$$

$$V_B = V_A \left\{ (1 + sR_2C_2) + sR_1 C_1 + sR_2C_2 sC_1 R_1 - \frac{V_0 sC_1 R_1}{V_B} \right\}$$

$$V_B = V_A \left\{ 1 + sR_2C_2 + sR_1 C_1 + sR_2C_2 sC_1 R_1 - \frac{V_0 sC_1 R_1}{V_B} \right\}$$

$$\left[\because \frac{V_0}{V_A} = \frac{V_0}{V_A} \right]$$

$$V_B = \frac{V_0}{AF} [1 + sR_2C_2 + sR_1 C_1 + sR_2C_2 sC_1 R_1 + sC_2 R_1 - \frac{V_0 sC_1 R_1}{V_B}]$$

$$\frac{V_0}{V_B} = \frac{AF}{sR_2C_2 C_2 + sR_1 C_1 + R_1 C_2 + R_2 C_2 - AF R_1 C_1} + 1 \quad \rightarrow \textcircled{3}$$

Divide with $\frac{V_0(s)}{V_B(s)}$

$$\frac{V_0(s)}{V_B(s)} = \frac{AF}{s^2 + s(R_1 C_1 + R_2 C_2) - AF R_1 C_1} + \frac{1}{sR_2C_2} \quad \rightarrow \textcircled{4}$$

the standard form of any 2nd order system is

$$\text{Given by } \frac{V_0(s)}{V_B(s)} = \frac{A}{s^2 + 2\zeta \omega_n s + \omega_n^2} \quad \rightarrow \textcircled{5}$$

$\zeta \rightarrow$ damping, natural frequency here ω_n (higher cut off frequency)

$\omega_n \rightarrow$ natural frequency here ω_n (higher cut off frequency)

compare eqns ④ & ⑤ then

$$\omega_n^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega_n^2 = \frac{1}{R_1 R_2 C_1 C_2} \quad \rightarrow \textcircled{6}$$

$$(\omega_n F_n)^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$F_n = \frac{1}{(\omega_n)^2 R_1 R_2 C_1 C_2}$$

$$F_n = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$ then

$$F_n = \frac{1}{2\pi \sqrt{R^2 C^2}}$$

$$F_n = \frac{1}{2\pi RC}$$

and Eqn ③ becomes,

$$\frac{V_0(s)}{V_B(s)} = \frac{AF}{s^2 RC^2 + sRC(3 - AF) + 1}$$

From (3); $\omega_H^2 = \frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{RC^2}$

$\Rightarrow RC^2 = \frac{1}{\omega_H^2}$ and $s = j\omega$

$\frac{V_O(s)}{V_I(s)} = \frac{AF}{\left(\frac{j\omega}{\omega_H}\right)^2 + \left(\frac{j\omega}{\omega_H}\right) (3-AF) + 1}$ $\rightarrow (3)$

here we consider the better pole response.

-match techniques for better pole response. The standard form of Butterworth approximation for second order is

$\frac{V_O(s)}{V_I(s)} = \frac{A}{s^2 + \sqrt{2}s + 1}$ $\rightarrow (4)$

Comparing (3) & (4) we get


$3-AF = \sqrt{2}$

From (3); $\frac{V_O(s)}{V_I(s)} = \frac{AF}{\left(\frac{j\omega}{\omega_H}\right)^2 + \sqrt{2} \frac{j\omega}{\omega_H} + 1}$

$\frac{V_O(s)}{V_I(s)} = \frac{AF}{1 - \left(\frac{j\omega}{\omega_H}\right)^2 + \sqrt{2} \frac{j\omega}{\omega_H}}$


$\left| \frac{V_O(s)}{V_I(s)} \right| = \frac{AF}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_H}\right)^2\right]^2 + \left[\sqrt{2} \left(\frac{\omega}{\omega_H}\right)\right]^2}}$

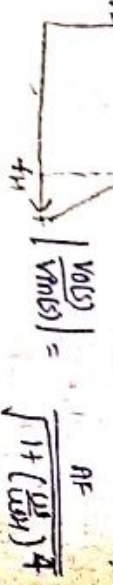$= \frac{AF}{\sqrt{1 + \left(\frac{\omega}{\omega_H}\right)^4 - 2\left(\frac{\omega}{\omega_H}\right)^2 + 2\left(\frac{\omega}{\omega_H}\right)^2}}$



here the Gain roll off is 40dB because in denominator we have 4th degree. So here gain is reduces better than first order active low pass filter.

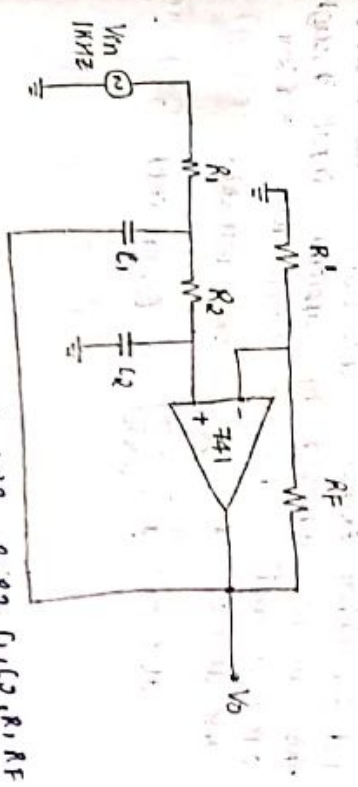* Design a second order active lowpass filter with cut-off frequency $f_H = 1kHz$. $3-AF = \sqrt{2}$



Here we have to calculate $R_1, R_2, C_1, C_2, R_1, R_2$

$f_H = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$ then

$f_H = \frac{1}{2\pi RC}$

Let $C = 0.01\mu F$ then

$R = \frac{1}{2\pi(1k)(0.01\mu)} = 15.91k\Omega$

$R \approx 15k\Omega$

We know that

$3-AF = \sqrt{2}$

$AF = 3-1.414$

$AF = 1.586$

$\frac{R_F}{R_I} = AF \Rightarrow 1.586 = \frac{R_F}{R_I}$

$0.586 R_I = R_F$, assume $R_I = 1k\Omega$

$R_F = 0.586 \times 15k = 8.79k\Omega$

$R_F \approx 8.79k\Omega$

$R_F \approx 8.79k\Omega$


$R_F \approx 586\Omega$

$R_1 = R_2 = R = 15k\Omega$ and $R_F = 10k\Omega, R_I = 1k\Omega$

$C_1 = C_2 = C = 0.01\mu F$


$R = 15k\Omega$

$R = 15k\Omega$

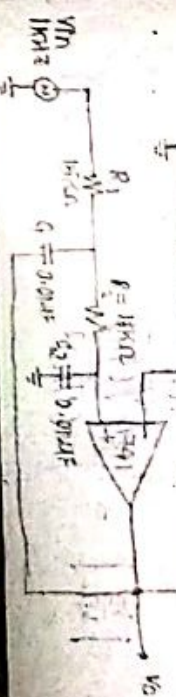

1st

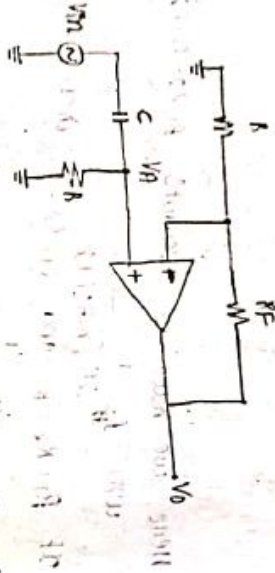First order high pass filter:
 For lower frequencies, the gain is minimum and for higher frequencies, the gain is maximum. This can be achieved by applying input through capacitor and output is taken across resistor.
 At $f=0$; $X_C = \frac{1}{\omega C} = \infty$ (open ckt). (Gain = 0)
 At $f=\infty$; $X_C = \frac{1}{\omega C} = 0$ (short ckt). (Gain = ∞)



Analysis:
 Here we have to calculate gain for frequency response. For gain, we should calculate V_0 .
 $V_0 = A_F V_A$

For V_0 , we calculate V_A

$$V_A = \frac{V_m R}{R + \frac{1}{j\omega C}}$$

$$V_A = \frac{V_m j\omega RC}{1 + j\omega RC}$$

$$V_0 = A_F \left[\frac{V_m j\omega RC}{1 + j\omega RC} \right]$$

$$V_0 = A_F \left[\frac{V_m j\omega RC}{1 + j\omega RC} \right]$$

where RC is time constant. If $f = f_c$, so produces one frequency i.e. f_c (because of HPF).

$$V_0 = A_F \left[\frac{V_m j \left(\frac{f}{f_c} \right)}{1 + j \left(\frac{f}{f_c} \right)} \right]$$


$$\left| \frac{V_0}{V_m} \right| = \frac{A_F \left(\frac{f}{f_c} \right)}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}}$$

$$\left| \frac{V_0}{V_m} \right| = \frac{A_F \left(\frac{f}{f_c} \right)}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}}$$

$$\phi = -\tan^{-1} \left(\frac{f}{f_c} \right)$$

$$\text{Let } f_c = 1 \text{ kHz}$$

HPF Freq. (f)	Gain
0	0
10	≈ 0
100	≈ 0
1k	$A_F/2$
10k	Gain maintains constant (A_F)

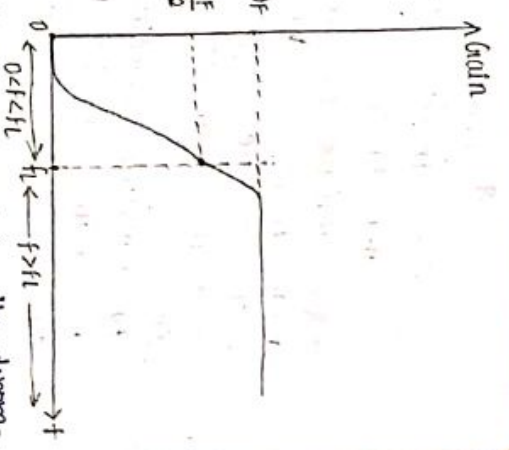

After f_c i.e. $f > f_c$, the denominator increases with frequency, so gain & maintains a constant value as A_F (neglect 1 in denominator).
 $\left| \frac{V_0}{V_m} \right| = \frac{A_F \left(\frac{f}{f_c} \right)}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}} = A_F$

* Bandpass filter:

It allows the certain range of frequencies and rejects all other frequencies. So we have two stop bands and one passband. Pass band allows frequencies and stop bands means the rejected low and high frequencies before passband and after passband respectively.


Bandpass filters are two types

$$\text{Factor } Q = \frac{f_c}{B.W.}$$

$Q > 10$; then it is narrowband pass filter.

$Q < 10$; then it is wideband pass filter.

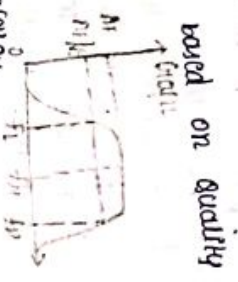- (1) wideband pass filter ($Q \leq 10$).
- (2) narrow bandpass filter ($Q > 10$).



$$Q = \frac{f_M}{B.W.}$$

B.W. = upper cut-off frequency - lower cut-off frequency

$$B.W. = f_H - f_L$$

→ For calculate f_M we didn't use arithmetic mean because of varying components with respect to time we didn't use arithmetic mean so we use geometric mean for time varying factors.

By calculating geometric mean for f_H and f_L we obtain f_M . here f_H and f_L are only two factor so $f_M = \sqrt{f_H f_L}$

$$f_M = \sqrt{f_H f_L}$$

now we determined both f_M and B.W. so we easily calculate quality factor and for from Q we easily said whether the filter is wide (or) narrow band filter.

$$Q = \frac{f_M}{B.W.}$$

$$Q = \frac{\sqrt{f_H f_L}}{\sqrt{f_H - f_L}} = \frac{\sqrt{f_H f_L}}{f_H - f_L}$$

→ In wideband pass filter we allow more frequencies are allowed to output so we simply select some frequencies. so it is a less selective circuit.
 → For narrowband pass filter the selection is difficult to select some of the frequencies only. so it is a more selective circuit.

Widepass

wideband pass filter:




wideband pass filter is constructed by using HPF and LPF. highpass filter followed by lowpass filter is wideband pass filter.

→ By selecting proper values of components, we

fix the cut-off filter frequency f_L . From f_L onwards the HPF allows the frequencies. If f_L is 500 then HPF allows all frequencies greater than 500 and rejects upto 500.

Now this output is given to lowpass filter and by proper values of R and C we fix f_H . let f_H is 5k then LPF allows all frequencies upto 5k and rejects above 5k frequencies.

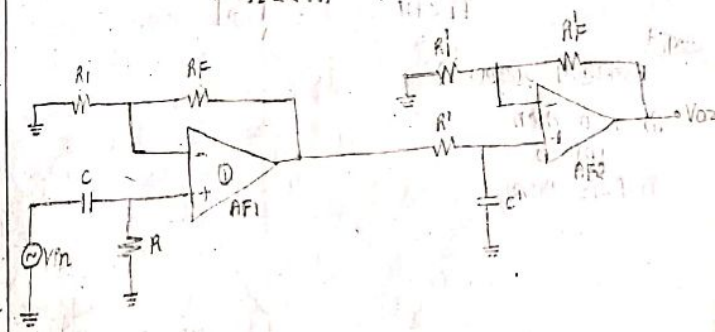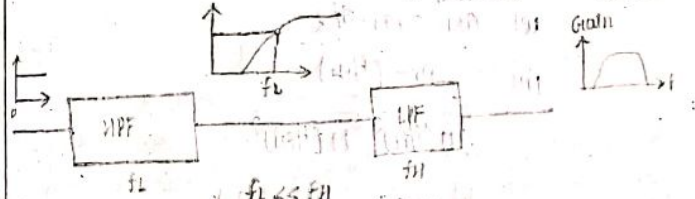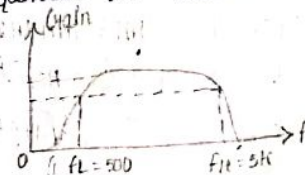The output of LPF contains only 500 to 5k frequencies because below 500 frequencies are rejected by HPF and above 5k frequencies are rejected by LPF then the response is equivalent to wide bandpass filter.



Outputs:
High pass filter:

$$f_c = \frac{1}{2\pi RC}$$

$$A_H = H \frac{R_F}{R_I}$$

$$|M_1| = \left| \frac{V_{O1}}{V_{in}} \right| = \frac{R_F (f/f_c)}{\sqrt{1+(f/f_c)^2}}$$

Outputs:
Low pass filter:

$$f_c = \frac{1}{2\pi RC}$$

$$A_L = 1 + \frac{R_F}{R_I}$$

$$|M_2| = \left| \frac{V_{O2}}{V_{O1}} \right| = \frac{R_F}{\sqrt{1+(f/f_c)^2}}$$

Here, both HPF and LPF are in cascaded connection. So total gain is the multiplication of individual gains.

$$|M| = |M_1| |M_2|$$

$$= \frac{R_F (f/f_c)}{\sqrt{1+(f/f_c)^2}} \cdot \frac{R_F}{\sqrt{1+(f/f_c)^2}}$$


Let $A_{HP} = R_F / R_I$, $A_{LP} = 1 + R_F / R_I$

$$|M| = \frac{A_{HP} A_{LP} (f/f_c)}{\sqrt{1+(f/f_c)^2} \sqrt{1+(f/f_c)^2}}$$

$f_c < f_H$

25/01/19
Frequency response:

- (i) $f = 0$ then $|M| = 0$.
- (ii) $f < f_c$ then

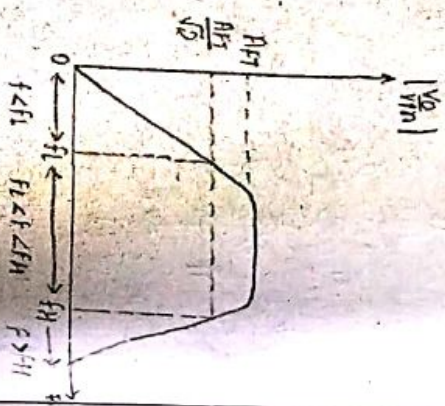


Band rejection (or) Band Elimination (or) Band stop filter: It has 2 passbands and one stopband. It rejects the certain band of frequencies and is used in biomedical applications.

There are two types based on quality factor: (i) wide band rejection filter (WBPF) ($Q < 10$) (ii) narrowband rejection filter (NBPF) ($Q > 10$)

Wideband rejection filter: Method 1:

In this we use reject more number of frequencies and have use less selection.

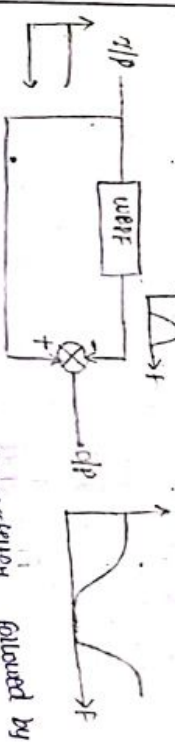Wideband rejection filter is constructed by using a WBPF and subtractor.




So here we require one act lowpass filter followed by

highpass filter and one subtractor. Here we have to use for subtraction, the for negative terminal we have to apply WBPF output and for positive terminal we apply the input which has all frequencies.

Then subtractor subtracts WBPF o/p from all pass frequencies then the output response becomes the WBPF response.


For WBPF we use WBPF and for NBPF we use NBPF.

Method 2:

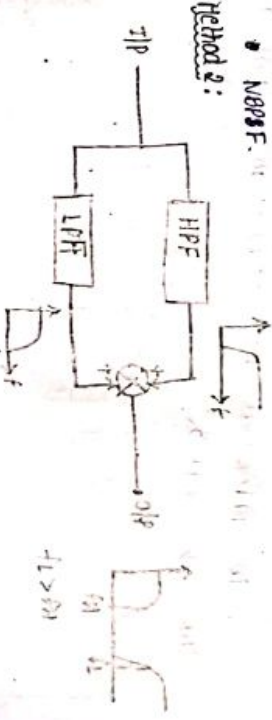

If we want to construct a BPF by using LPF and HPF then we should make $f_L > f_H$. For such cases $f_H > f_L$.
 In BPF, we require one adder provided to make add the responses of LPF and HPF. Then the output response is the response of BPF.

General diagram for method 2:

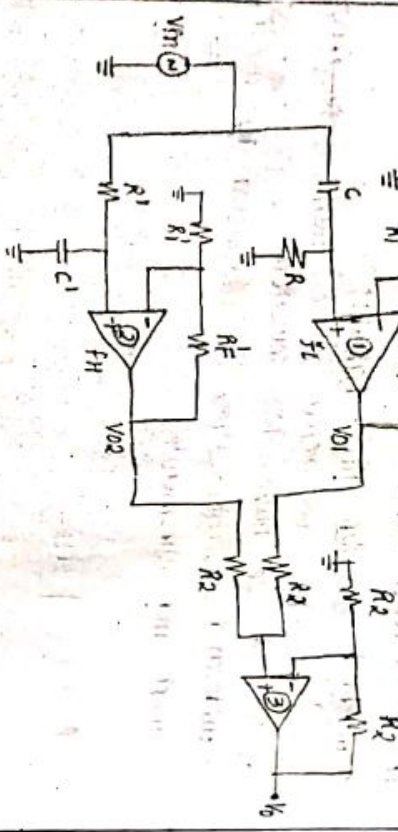

$$f_L = \frac{1}{2\pi R_1 C}$$

$$f_H = \frac{1}{2\pi R_1' C}$$

$$f_L > f_H$$

$$A_f = 1 + \frac{R_f}{R_1}$$

$$V_{01} = \frac{V_m A_f \left(\frac{f}{f_L} \right)}{1 + \left(\frac{f}{f_L} \right)^2}$$

$$V_{02} = \frac{V_m A_f}{1 + \left(\frac{f}{f_H} \right)^2}$$


For adder, all the resistors are same, so

$$V_0 = V_{01} + V_{02}$$


Hint

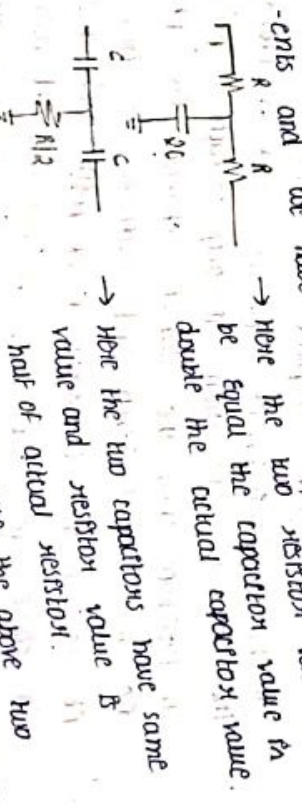(ii) Narrow band rejection filter (or) notch filter:
 It is constructed by using twin T followed by voltage follower (or) notch filter is implemented by cascading connection of twin T and voltage follower.

Here T-shape is implemented by passive components and we have follow some rules.



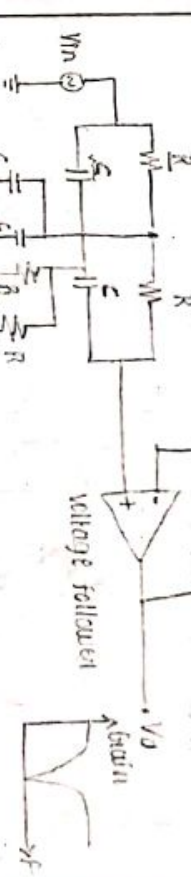→ Here the two resistor values must be equal the capacitor value. In double the actual capacitor value.
 → Here the two capacitors have same value and resistor value is half of actual resistor.




Let $f_H = 500\text{Hz}$



→ Here the R and C acts as lowpass filter. Except f_H .
 then upto f_H it allows all frequencies. Let $f_L = 500\text{Hz}$
 → And R and C acts as highpass filter. Except f_H then after f_H it allows all frequencies. In above so in overall response 500Hz is rejected. Hence it is only one frequency is rejected. Hence it is called as narrow band rejection filter.

superfluous filter:


It allows all frequencies i.e. the signal strength is maximum at all frequencies, any device the signal strength is constant
 → in general without using any device the signal strength is constant
 → all pass filter are also called as phase compensator
 (any) phase delay (any) phase associated
 → in the transmission of sig we want to transmit that in frequency then if any obstacle is present in frequency then the signal continues the transmission
 in frequency then the signal continues the transmission i.e. the signal bends and changes the phase and received at receiver the transmitted sig phase and received sig phase are not same. No we use all pass filter at receiver. this filter doesn't change amplitude and frequency but it produces corresponding phase to make signals equal.

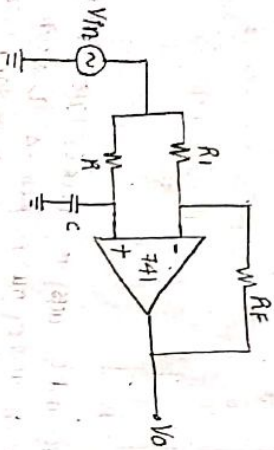

Analysis:

Here we have to prove the above circuit has unity gain and because it didn't change the amplitude and frequency.

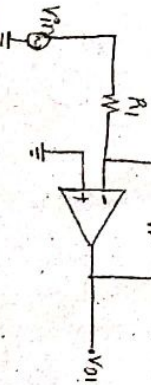we have both inverting and non-inverting terminals so we use superposition theorem
 case 1: inverting terminal is active




$$V_{O1} = \left(-\frac{R_f}{R_1} \right) V_m$$

If $R_f = R_1$ then

$$V_{O1} = -V_m$$

case 2: non-inverting terminal is active

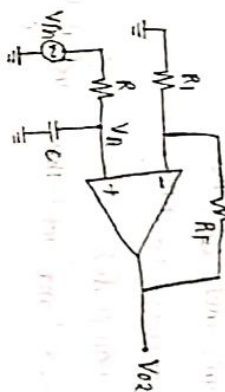

$$V_{O2} = \left(1 + \frac{R_f}{R_1} \right) V_m$$

If $R_f = R_1$ then

$$V_{O2} = 2V_m$$

where $V_A = \frac{V_m \left(\frac{R_f}{R_1} \right)}{R_1 + \left(\frac{R_f}{R_1} \right)}$

$$V_A = \frac{V_m}{1 + \frac{R_f}{R_1}}$$

$$V_{O2} = 2 \left[\frac{V_m}{1 + \frac{R_f}{R_1}} \right]$$

total output voltage $V_O = V_{O1} + V_{O2}$

$$V_O = -V_m + 2V_m$$

$$V_O = -V_m + \frac{2V_m}{1 + \frac{R_f}{R_1}}$$

$$V_O = V_m \left[-1 + \frac{2}{1 + \frac{R_f}{R_1}} \right]$$

$$\frac{V_O}{V_m} = \left[\frac{2 - (1 + \frac{R_f}{R_1})}{1 + \frac{R_f}{R_1}} \right]$$

$$\frac{V_O}{V_m} = \frac{2 - \frac{R_f}{R_1}}{1 + \frac{R_f}{R_1}}$$

$$\left| \frac{V_O}{V_m} \right| = \frac{\sqrt{1 + \left(\frac{R_f}{R_1} \right)^2}}{\sqrt{1 + \left(\frac{R_f}{R_1} \right)^2}}$$

$$\left| \frac{V_o}{V_m} \right| = 1$$

here output voltage is equal to input voltage
 so it acts as an pass filter.

$$\phi = \tan^{-1}(-\omega RC) - \tan^{-1}(\omega RC)$$

$$\phi = -\tan^{-1}(\omega RC) - \tan^{-1}(\omega RC)$$

$$\phi = -2\tan^{-1}(\omega RC)$$

and $\omega = 2\pi f$ and let $f = 1\text{kHz}$ and $R = 1\text{k}\Omega$ and $C = 0.1\mu\text{F}$. then

$$\phi = -2\tan^{-1}(2\pi \times 1\text{k} \times 1\text{k} \times 0.1\mu)$$

$$\phi = -64.28$$

By choosing the proper values of R and C
 we can change the phase angle
 → here we get lagging phase if you want leading
 phase then we can just interchange R and C
 in this manner we can control the phase
 angle by changing R and C and interchanging
 also.

→ let us consider the phase angle is -90° then
 the input and output waveforms be [let V_{in} is
 sinusoidal sig]

→ here we didn't change
 the amplitude and
 frequency but we only
 phase is changes.

