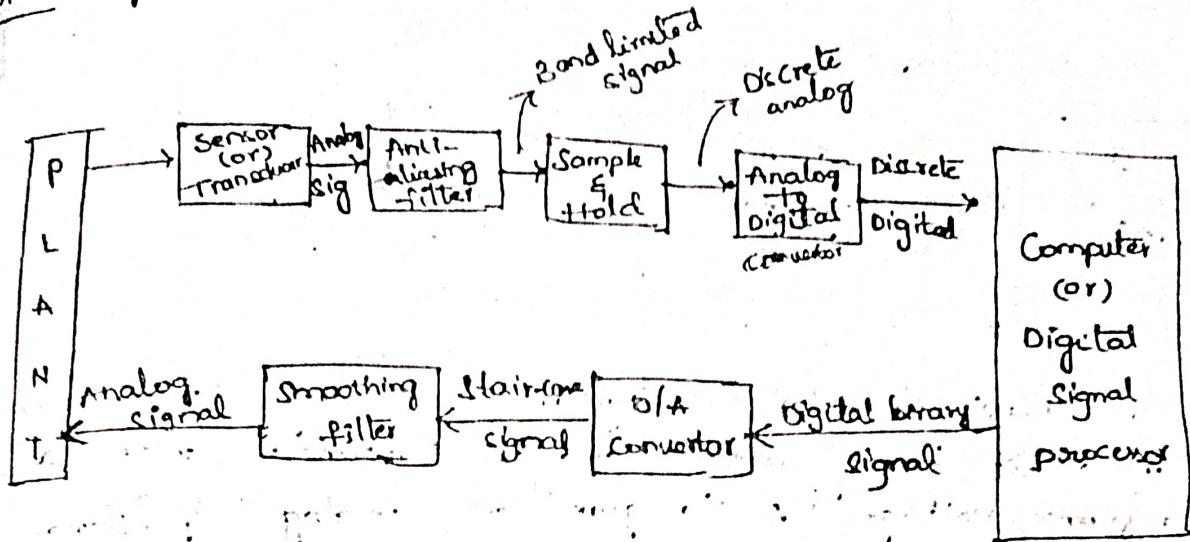



D/A & A/D Converters

Block diagrams :-



From the Block diagram it uses the physical quantities like voltage, current, temperature, pressure and time etc which is applied as a i/p reference signal for the sensor (or) transducer which senses the particular i/p signal and it will produce the analog signal. This analog signal is applied to the anti-aliasing filter which reduces aliasing effect i.e., the overlapping of many signals and which gives the band limited signal only and it can be sampled and sometimes it is in hold state then the discrete analog signal is produced. This discrete analog signal is applied to analog to digital converter which gives the o/p of discrete digital response. This response is applied to a mini computer or DSP which accepts only the binary i/p signal and that digital info applied to the D/A converter which gives the staircase response signal this signal is applied to the smoothing filter which reduces unwanted noise then the o/p is analog signal.

 Basics of DAC Techniques (Digital to Analog Converter) :-



The basic principle for a digital to analog converter is an n -bit binary word and is combined with a reference voltage V_R to give an analog output signal.

The output of DAC may be voltage or current the DAC converter is mathematically expressed as

$$V_o = k V_{FS} [d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + \dots + d_n 2^{-n}] \quad \text{--- (1)}$$

where, k is the scaling factor always adjusted to unity i.e. $k=1$, V_{FS} is "full scale voltage",

d_1, d_2, \dots, d_n = digital binary word.



d_1 = most significant bit (MSB) with weightage of $\frac{V_{FS}}{2}$

d_n = least significant bit (LSB) with weightage of $\frac{V_{FS}}{2^n}$

There are 3 types of DAC techniques to implement the above eqⁿ those are

- ① Binary weighted resistor DAC
- ② R-2R ladder network DAC
- ③ Inverted R-2R DAC

Binary weighted Resistor DAC :

 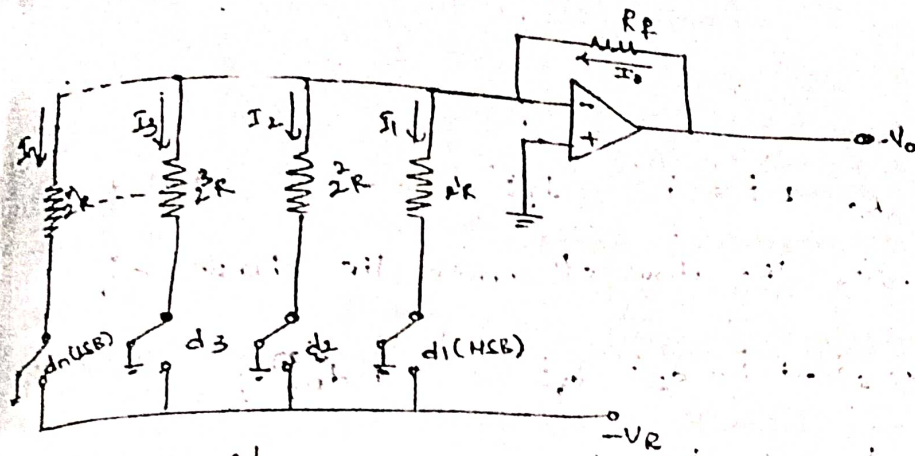

Binary weighted Resistor method uses n electronic switches. $d_1, d_2, d_3, \dots, d_n$ controls the i/p binary word. From the dt the switches are Single pole double through switches (SPDT). If the binary i/p is one the switch is connected to the reference voltage V_R and if the binary i/p is zero the switch is connected to ground.

From the fig the o/p current I_0 is calculated by using

$$I_0 = I_1 + I_2 + I_3 + \dots + I_n$$

$$= \frac{V_R}{2R} d_1 + \frac{V_R}{2^2 R} d_2 + \frac{V_R}{2^3 R} d_3 + \dots + \frac{V_R}{2^n R} d_n$$

$$I_0 = \frac{V_R}{R} \left[d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + \dots + d_n 2^{-n} \right]$$

From the fig

$$V_0 = I_0 R_f$$

$$= \frac{V_R}{R} \cdot R_f \left[d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + \dots + d_n 2^{-n} \right]$$

By the comparison the above eqⁿ with the basic eqⁿ

$$V_0 = k V_{FS} \left[d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + \dots + d_n 2^{-n} \right]$$

From both the eqⁿs $R_f = R$

then $k = 1$

$$V_{FS} = V_R$$

Disadvantages :-

The only dis is for a BWR is "The circuit complexity is more".

R-2R Ladder Network DAC :-



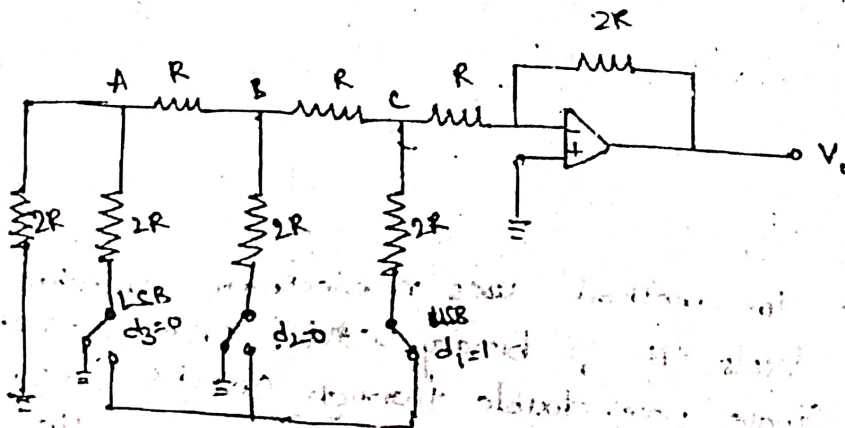


fig (a)

 

(c) Equivalent ckt at node c

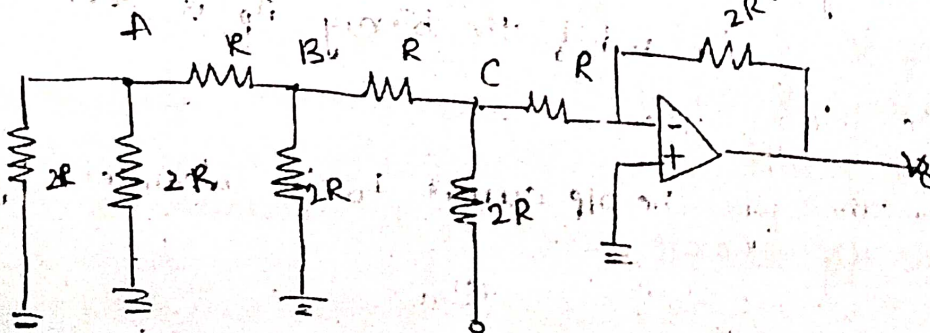

(b) Equivalent of ckt fig (a)


the wide range of resistors are required in Binary weighted resistor DAC. This problem can be avoided by using R-2R DAC by using only two values of resistors with the range of ϕ 2.5k Ω to 10k Ω . The simple understanding purpose. Consider a 3-bit DAC where the switch positions d_1, d_2, d_3 as 100. This can be simplified by using the fig(b) and finally the voltage at node c can be easily calculated by using fig(c) i.e., voltage at node c

$$= \frac{\frac{2}{3}R \times 2R}{\frac{4R}{3} + 2R} (-V_R)$$

$$= \frac{\frac{4R^2}{3}}{\frac{10R}{3}} (-V_R)$$

$$= \frac{\frac{2}{3}R (-V_R)}{2R + \frac{2}{3}R}$$
 
$$= \frac{-3V_R}{4} \quad \left[V_C = \frac{-V_R}{4} \right]$$



$$V_o = \frac{-R_1}{R_1} V_{in}$$



Then from the fig the o/p voltage $V_o = \frac{-2R}{R} \left(\frac{-V_R}{4} \right)$

$$V_o = \frac{V_R}{2}$$

Disadvantages:

1. The current flow in the resistors changes as the i/p data changes
2. More power consumption causes heating which produces non-linearity DAC


Inverted R-2R ladder network :-

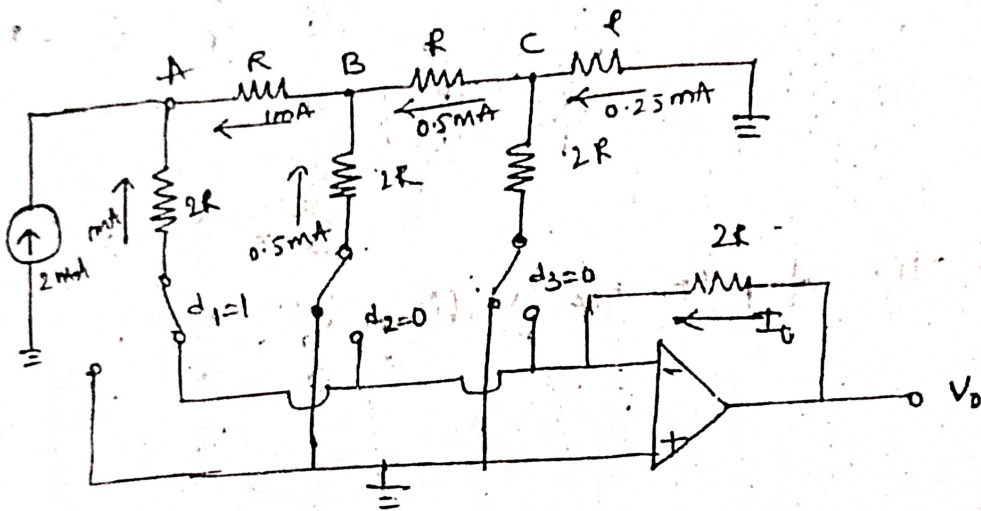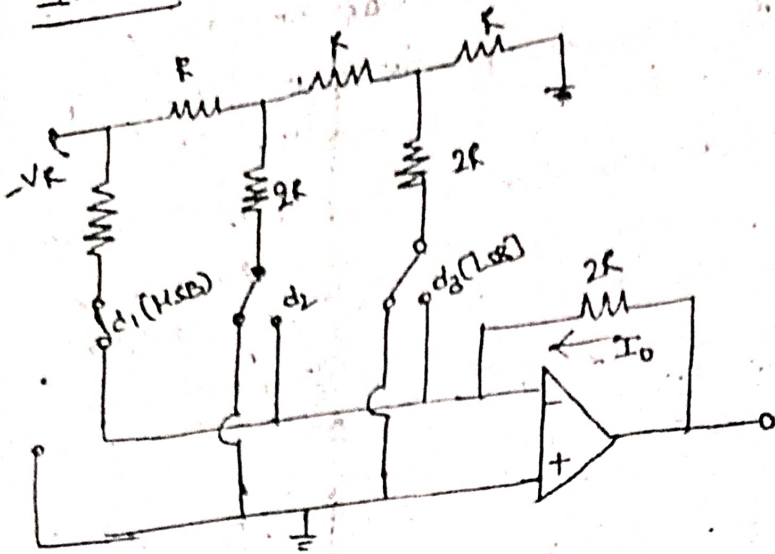


The drawbacks of BWR and R-2R ladder DAC was overcome by using inverted whose switch positions was interchanged from previous ckt. so it is called as inverted R-2R ladder N/W.

From fig (b) consider the reference current has 2mA. This was equally divided at node A as 1mA. Similarly this 1mA equally divided at node B as 0.5mA and also at node C. it is 0.25mA


Monolithic IC 1408 DAC:-

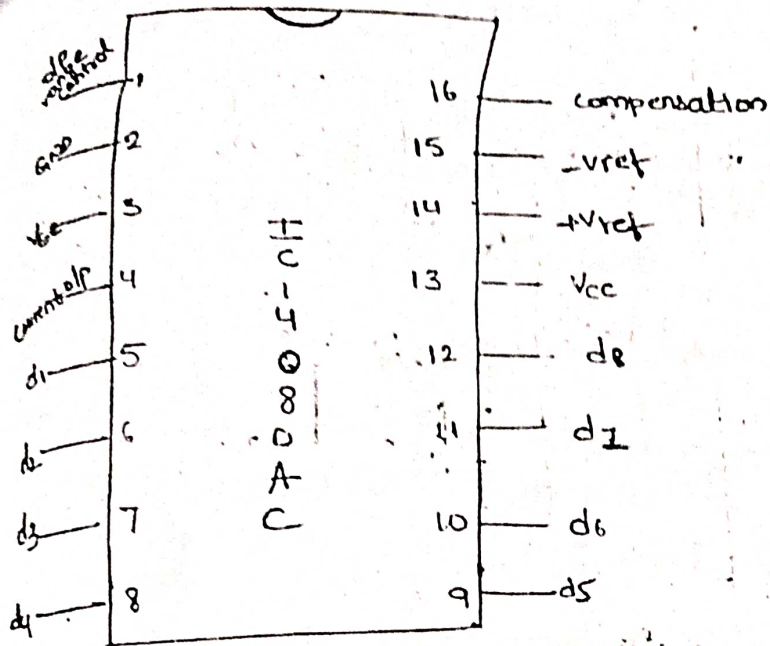

unipolar range ckt:-

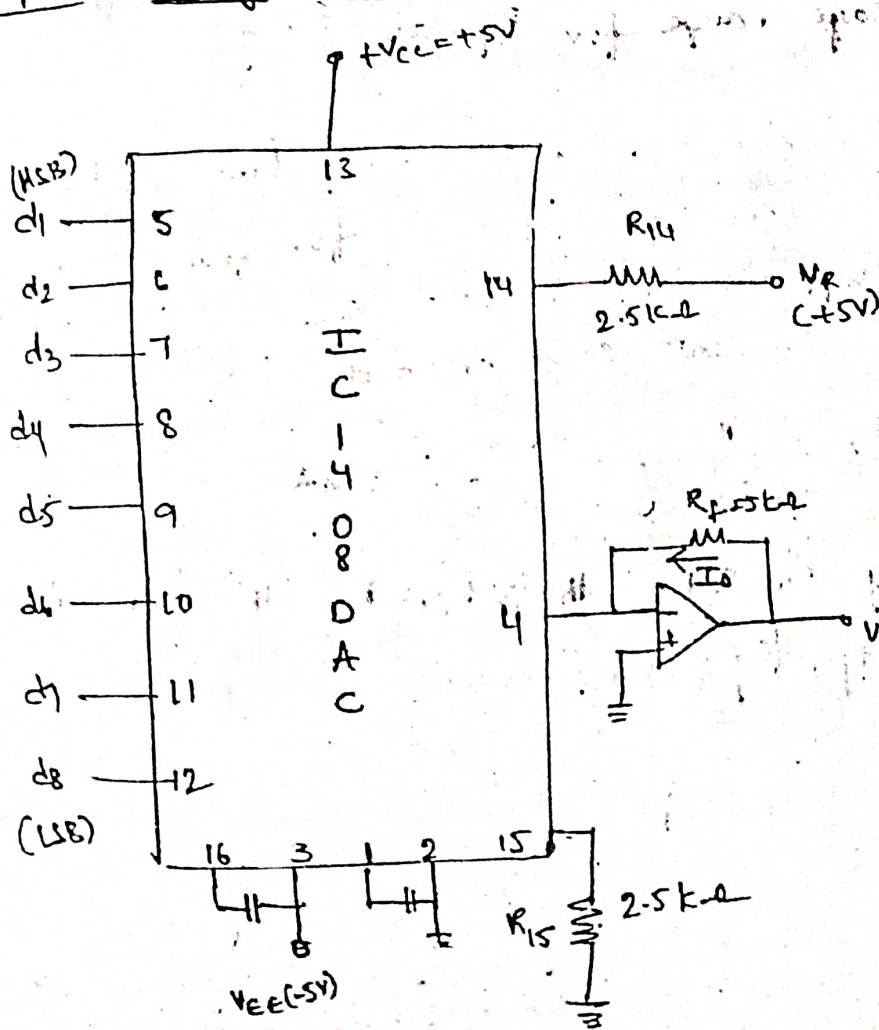

a) o/p voltage in unipolar range

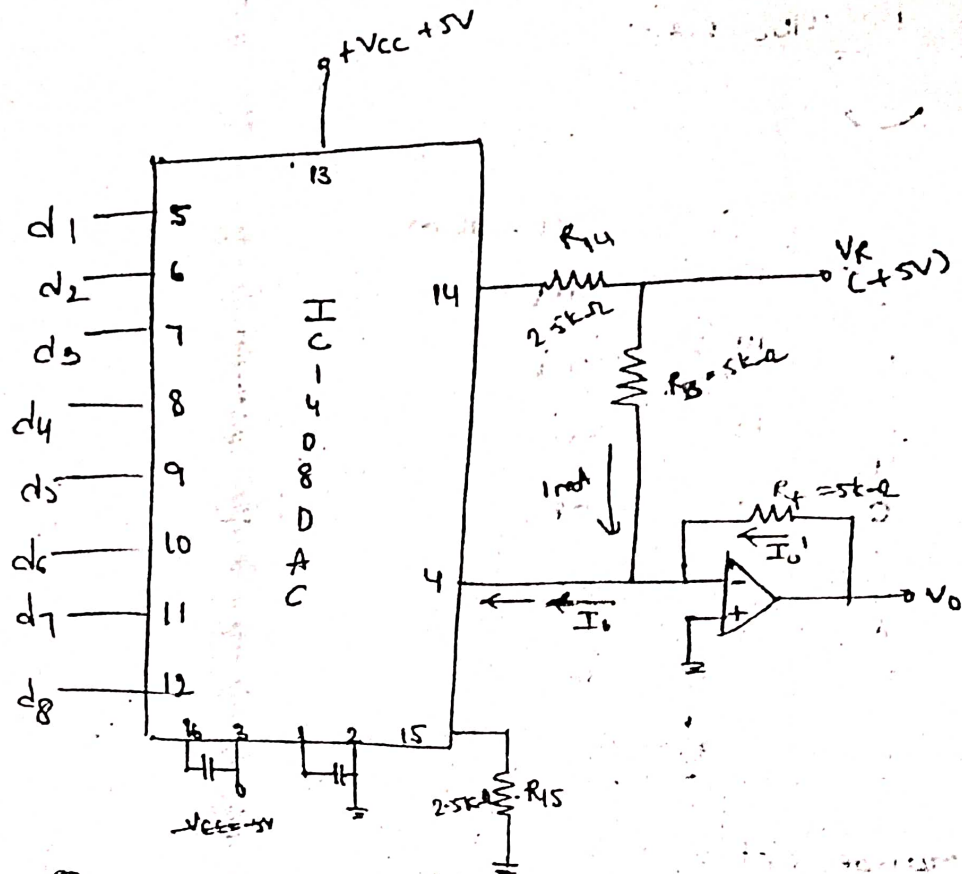

(b) o/p voltage range for Bipolar Range

A typical 8-bit IC1408 DAC has 8-bit data lines d_1 to d_8 . It requires 2mA reference current for full scale. If and two power supplies $V_{CC} = 5V$ and $V_{EE} = -5V$, then the total reference current is determined by the resistor

Using R_{14} i.e.
$$I_R = \frac{V_R}{R_{14}} = \frac{5V}{2.5} = 2mA$$

from the fig R_{14} & R_{15} is $R_{14} = R_{15}$ then I_0 is calculated by using fig (a) i.e.

$$I_0 = \frac{V_R}{R_{14}} \left(\sum_{i=1}^8 d_i \frac{1}{2^i} \right)$$

$$= \frac{V_R}{R_{14}} \left[d_1 \frac{1}{2^1} + d_2 \frac{1}{2^2} + d_3 \frac{1}{2^3} + d_4 \frac{1}{2^4} + d_5 \frac{1}{2^5} + d_6 \frac{1}{2^6} + d_7 \frac{1}{2^7} + d_8 \frac{1}{2^8} \right] \quad \text{--- (1)}$$

For unipolar range

consider all digital i/p's as 1

i.e. d_1 to $d_8 = 11111111$ then from eqⁿ ①

$$I_0 = \frac{5}{2.5k\Omega} \left[1 \times 2^{-1} + 1 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4} + 1 \times 2^{-5} + 1 \times 2^{-6} + 1 \times 2^{-7} + 1 \times 2^{-8} \right]$$

$$I_0 = \frac{5}{2.5k\Omega} \left[\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{64} + \frac{1}{128} + \frac{1}{256} \right]$$

$$= I_0 \approx 1.99 \text{ mA} \quad | \quad V_0 = I_0 R_f$$
$$= 1.99 \times 10^{-3} \times 5 \times 10^3$$

$$V_0 = 9.96 \text{ V}$$

For bipolar range

Consider range from -5V to $+5\text{V}$ by adding a resistor

$R_B = 5k\Omega$ in b/w V_R and pin 4. From fig ⑥ the

bipolar operation o/p current $I_0' = I_0 - \frac{V_R}{R_B}$

$$I_0' = \frac{V_R}{R_{14}} \left[d_1 2^{-1} + d_2 2^{-2} + \dots + d_8 2^{-8} \right] - \frac{V_R}{R_B} \quad \text{--- ②}$$

$$I_0' \text{ \& o/p voltage } V_0 = I_0' R_f \quad \text{--- ③}$$

Let us consider the digital i/p d_1 to $d_8 = 00000000$

$$\text{from ② } I_0' = 0 - \frac{5}{5k\Omega} = -1 \text{ mA}$$

$$\text{eqⁿ ③ } V_0 = -1 \times 10^{-3} \times 5 \times 10^3 = -5 \text{ V}$$

Let us consider the digital i/p d_1 to d_8 as 10000000

$$\text{from ② } I_0' = \frac{V_R}{R_{14}} \left[1 \times 2^{-1} + 0 + 0 + 0 + 0 + 0 + 0 + 0 \right] - \frac{V_R}{R_B}$$

$$= \frac{5}{2.5 \times 10^3} \times \frac{1}{2} - \frac{5}{5 \times 10^3} = 0$$

$$\text{from ③ } I_0' = 0$$
$$\text{from } V_0 = 0$$

Let us consider the digital i/p d_1 to d_8 is 11111111

Then from eqⁿ (2)

$$I_0 = \frac{V_R}{R_A} \left[d_1 \bar{2}^1 + d_2 \bar{2}^2 + \dots + d_8 \bar{2}^8 \right] - \frac{V_R}{R_B}$$

$$I_0 = \left[1.99 \times 10^{-3} - \frac{5}{5k\Omega} \right]$$

$$= 0.99 \text{ mA}$$

from eqⁿ (3) $V_0 = I_0 R_f$

$$V_0 = 0.99 \times 10^{-3} \times 5 \times 10^3$$

$$V_0 = 4.95 \approx 5 \text{ V}$$

problem:

- (1) An 8 bit DAC has an o/p voltage range 0 to 2.55 Volts. Define its resolution and calculate % of resolution.

Resolution is defined as the ratio of full scale voltage (V_{FS}) to the least bit of n-bit DAC ($2^n - 1$) i.e.,

$$\text{resolution} = \frac{V_{FS}}{2^n - 1}$$

$$= \frac{2.55}{2^8 - 1} = 0.01$$

- (2) The LSB of a 10 bit DAC is 20 mV calculate its
 (i) % of resolution (ii) full scale range (iii) o/p voltage for 1011001101

$$\% \text{ Resolution} = \frac{V_{FS}}{2^n - 1}$$

$$= \frac{20 \times 10^{-3}}{2^{10} - 1} = 0$$

$$\% = 1.95 \approx 2\%$$

(ii) Full scale range is

$$V_{OFS} = \text{Fullscale} - \% \text{ resolution}$$

$$= 20 \times 10^{-3} - \frac{2}{100} [20 \times 10^{-3}]$$

$$= 20 \times 10^{-3} - 0.02$$

$$= 0.002 - 0.02$$

$$= 0$$

Then the range is 0 to 20 mV.

(iii) o/p voltage

$$V_o = K V_{FS} [d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + d_4 2^{-4} + d_5 2^{-5} + d_6 2^{-6} + d_7 2^{-7} + d_8 2^{-8} + d_9 2^{-9} + d_{10} 2^{-10}]$$

$$V_o = 1 \times 20 \times 10^{-3} [1 \times 2^{-1} + 1 \times 2^{-3} + 1 \times 2^{-4} + 1 \times 2^{-7} + 1 \times 2^{-8} + 1 \times 2^{-10}]$$

$$V_o = 20 \times 10^{-3} [$$

(3) How many bits are required to design a D/A converter that can have a resolution of 5 mV with 8 V full scale.

(4) Resolution = $\frac{V_{FS}}{2^n - 1}$

$$5 \times 10^{-3} = \frac{8}{2^n - 1}$$

$$\Rightarrow 2^n - 1 = \frac{8}{5 \times 10^{-3}}$$


$$2^n = \frac{8}{5} \times 10^3 + 1$$

$$2^n = 1601$$

$$2^n = 2$$

$$\underline{(n = 11)}$$

Basics of ADC Techniques :-

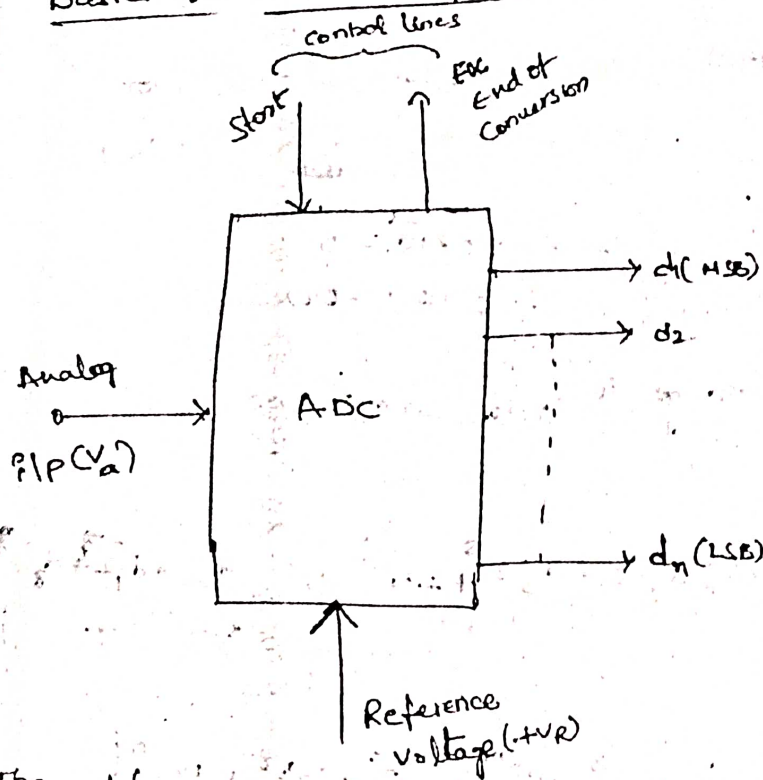


The A/D converter is exactly opposite to Digital to Analog Converter which produces the output as digital mode i.e.

$$D = (d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n})$$

In this A/D converter when the conversion is started it is executed by start control line and when the conversion is completed the end of conversion (EOC) control line is used.


Classification of ADC :-

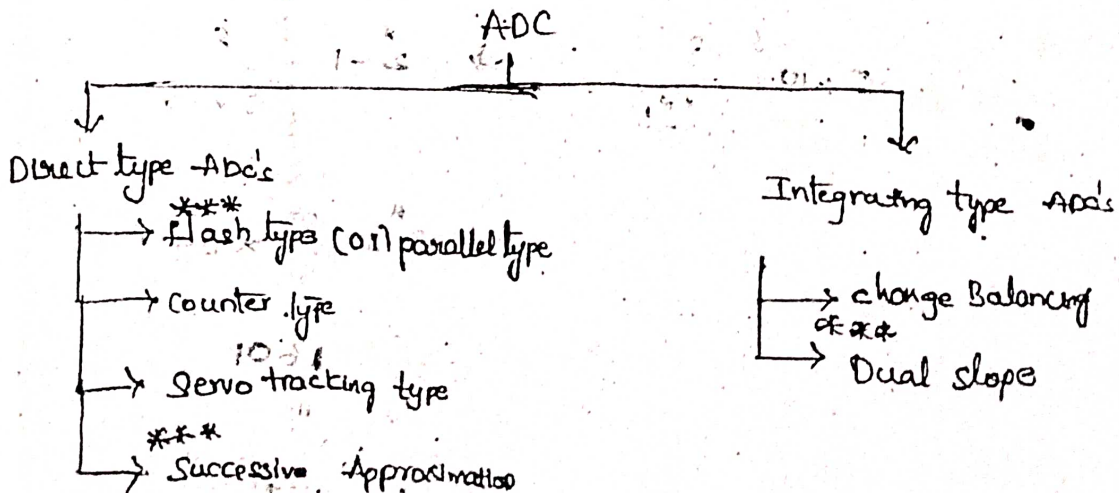

Direct type
Flash type (or)

Direct type ADC's

① Flash type (or) parallel type :

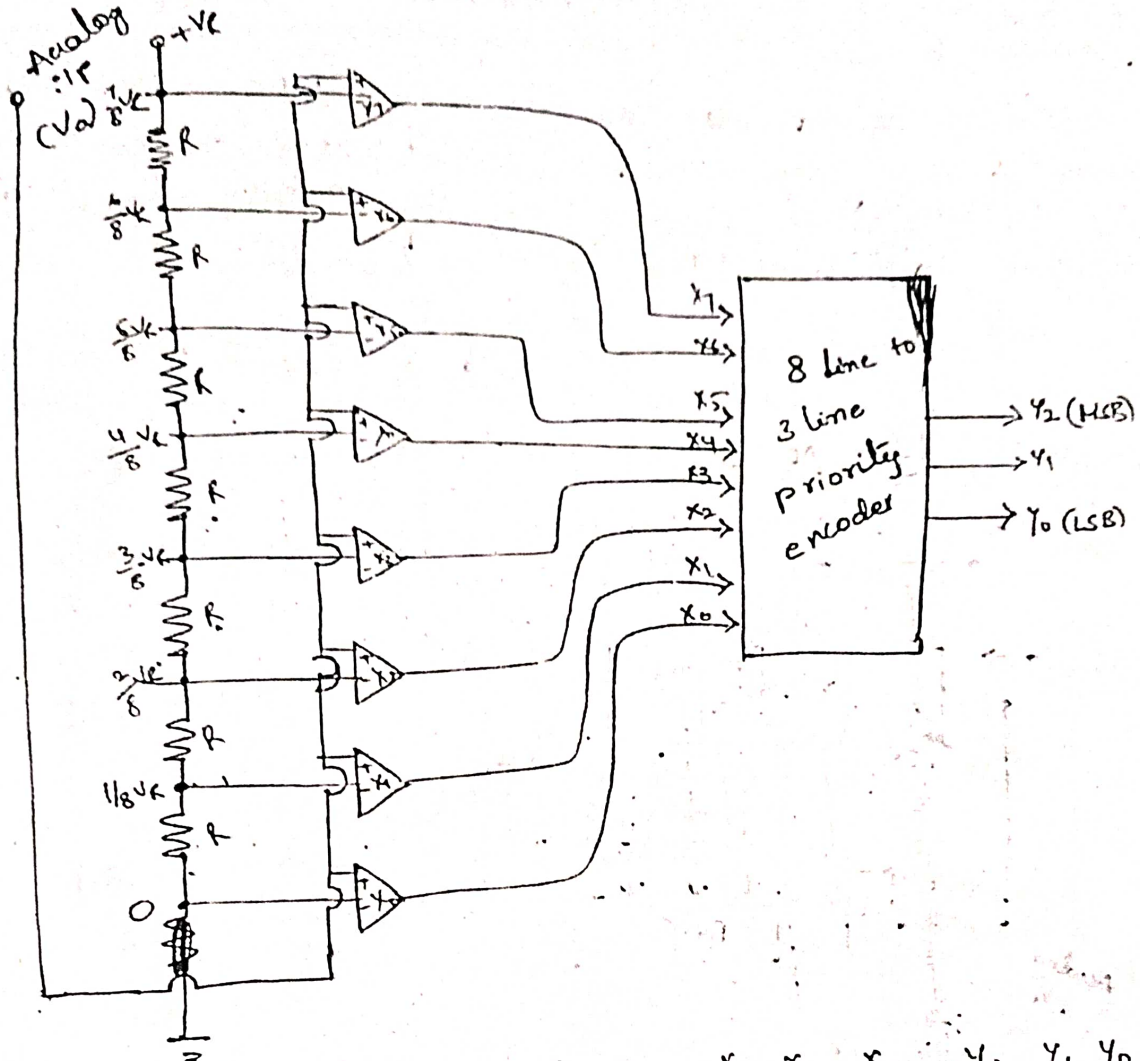


Input voltage	X_7	X_6	X_5	X_4	X_3	X_2	X_1	X_0	Y_2	Y_1	Y_0
0 to $\frac{VR}{8}$	0	0	0	0	0	0	0	1	0	0	0
$\frac{VR}{8}$ to $\frac{2VR}{8}$	0	0	0	0	0	0	1	0	0	1	0
$\frac{2VR}{8}$ to $\frac{3VR}{8}$	0	0	0	0	0	1	1	1	0	1	0
$\frac{3VR}{8}$ to $\frac{4VR}{8}$	0	0	0	0	1	1	1	1	1	0	0
$\frac{4VR}{8}$ to $\frac{5VR}{8}$	0	0	0	1	1	1	1	1	1	0	1
$\frac{5VR}{8}$ to $\frac{6VR}{8}$	0	0	1	1	1	1	1	1	1	1	0
$\frac{6VR}{8}$ to $\frac{7VR}{8}$	0	1	1	1	1	1	1	1	1	1	1
$\frac{7VR}{8}$ to VR	1	1	1	1	1	1	1	1	1	1	1

Scanned with CamScanner

In this flash type A/D converter is the fastest technique and most expensive. The ckt consists of a resistive divider network, 8 op-amp comparators and ~~8~~ priority encoder is used.

This type of converter has the disadvantage that no. of op-amps requires almost doubles. If the analog I/P $V_a > V_R$ then it gives the higher value otherwise it gives lower value i.e., $V_a > V_R \Rightarrow V_o = 1$
 $V_a < V_R \Rightarrow V_o = 0$
 $V_a = V_R \Rightarrow V_o = 0(00)1$

② Counter type ADC's :-


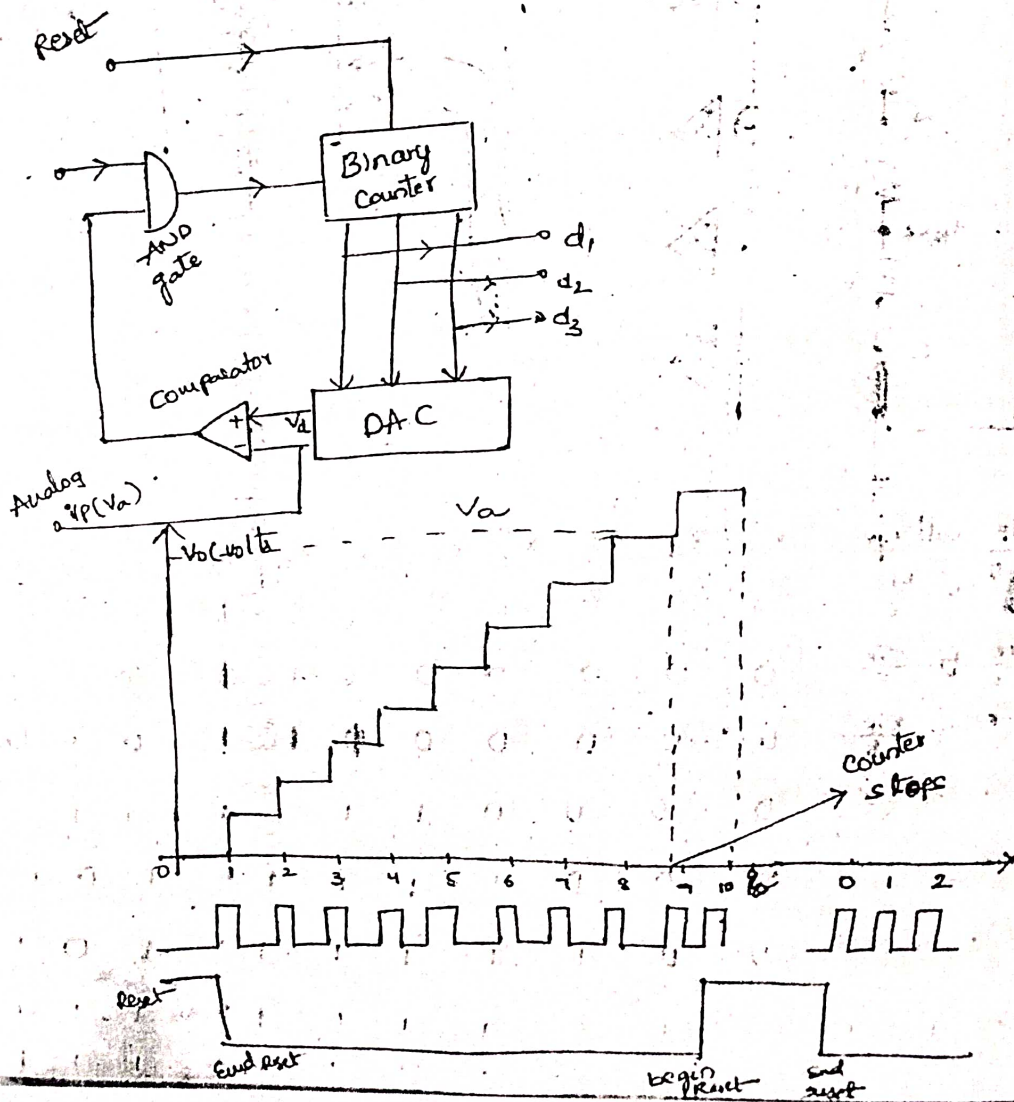


This is based on 'n' width counting principle. The counter is reset to zero by the reset pulse, when the reset was released the clock pulses were counted by the binary counter. These pulses go through an AND gate which is enabled by the Voltage Comparator high o/p.

If the analog i/p (V_a) is greater than DAC conversion (V_d) comparator becomes high and the AND gate is enabled to allow Txision of clk pulses to the counter.


If $V_a < V_d$ the o/p of comparator becomes low and AND gate is disabled and the counter stops counting when $V_a \leq V_d$ then the end of reset and counting begins again.

3. Servo tracking type A-D-C :-

 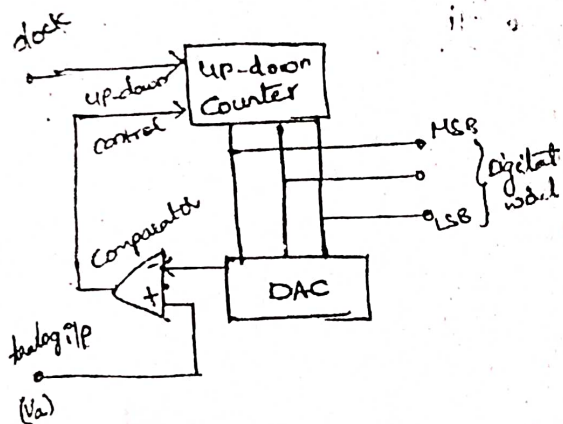



The Servotracking ADC consists of up-down counter to count the no. of clock pulses of up-down. If the i/p $V_a > V_d$ the op of the comparator goes high and counter is counts only up pulses the digital to analog Converter o/p increases with each incoming clk pulses and then if $V_a < V_d$ the counter counts only the down pulses. The advantage of this ADC is very simple and the drawback is more time it takes for the conversion.

④ Successive Approximation ADC :-

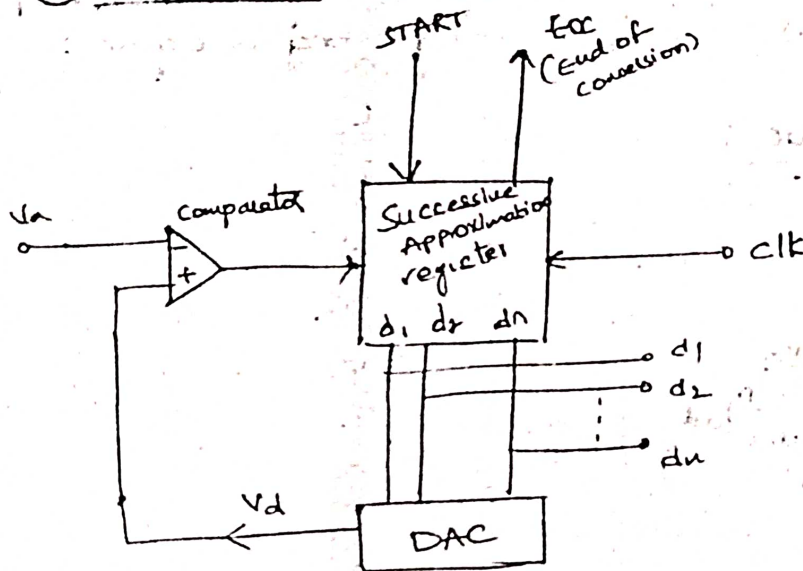

The Successive Approximation method is a n-bit of conversion in just n-clk pulses the ckt uses Successive Approximation register (SAR) to find the required value of each bit by trial and error method. The ckt operates with the arrival of START command. The best example is the weighing machine whenever the weights are applied as the analog i/p for one side as 5.2 kg and other side is to increase the weightages like 1kg, 3kg, 5kg & 7kg. Then if $V_a > V_d$ the Successive approximation register and comparator produces a high value, otherwise low value i.e., 0.

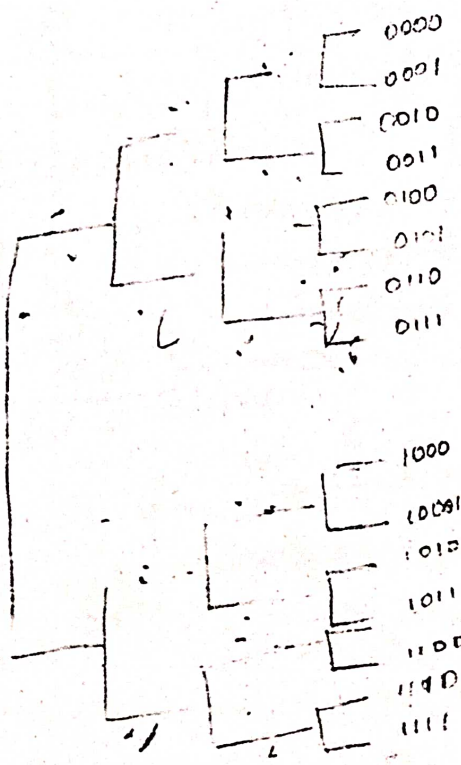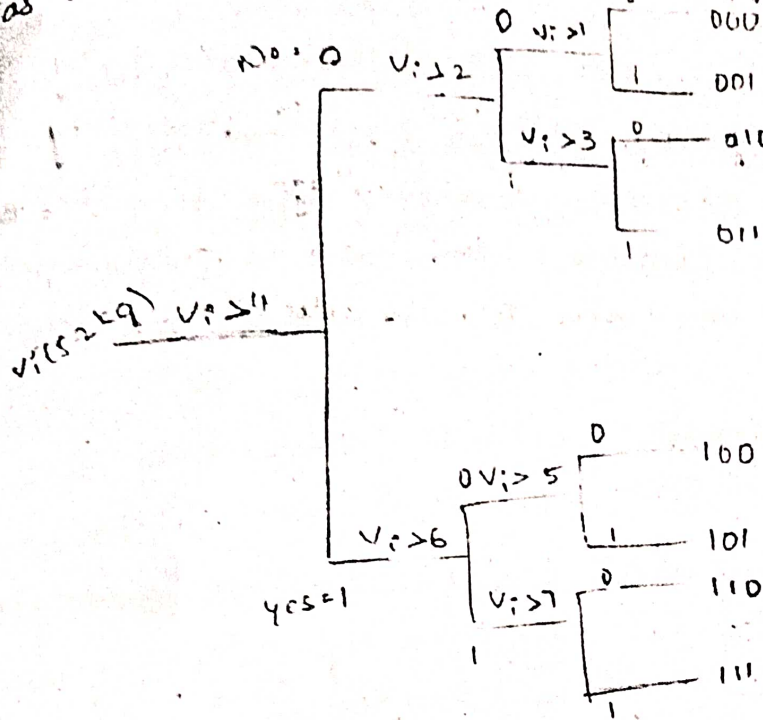Let us consider Analog i/p as, 5.2 kg. The ckt operates as follows.





Integrating type ADC's :-

Charge balancing ADC :

The charge balancing ADC is used for ① Integrating the I/P signal to frequency by using voltage to frequency counter which is a converter & converted into o/p is proportional to the analog I/P i.e. $f = \frac{1}{T}$. This ADC is also called as SINGLE SLOPE ADC

Dual slope ADC :-

 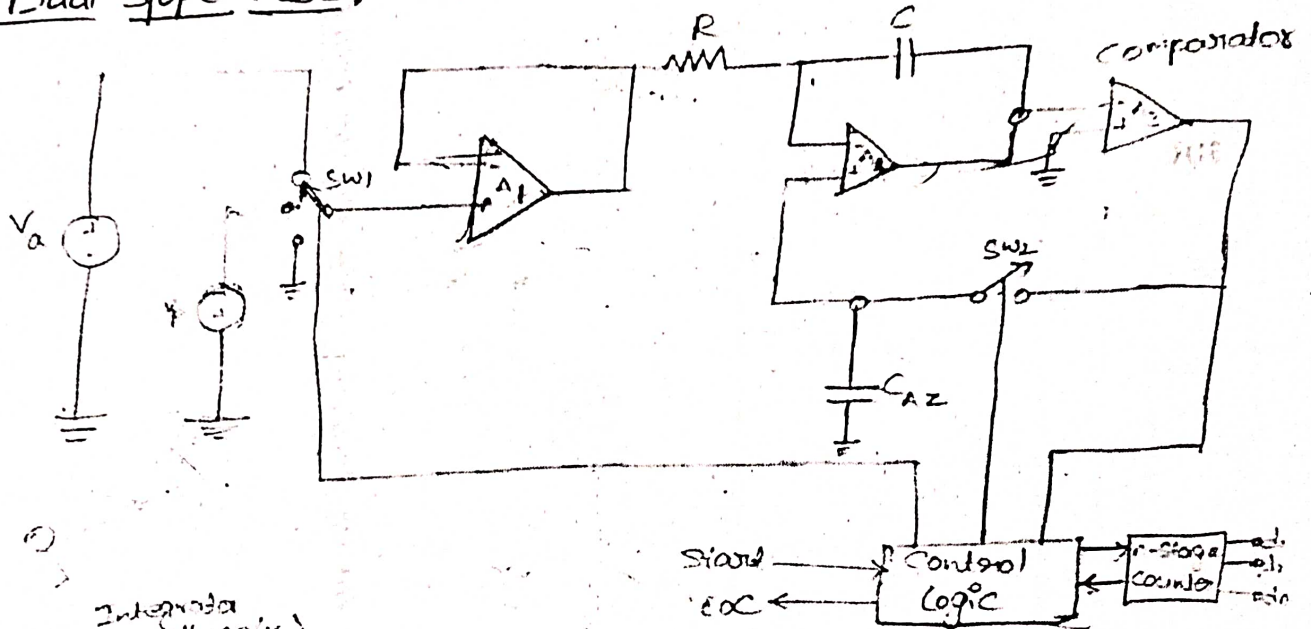

the dual slope ADC consists of a high i/p ^{related} impedance buffer (A_1), precision integrator (A_2), voltage comparator (A_3). The converter first integrates analog i/p signal V_a after that it integrates its reference voltage ($+V_R$) with n - no. of clock cycles and analog voltage integrates 2^n clk cycles.

Before start command arrives switch-1 connects to ground and switch-2 closed. Any ~~offset~~ offset voltage ~~present~~ present in the A_1, A_2, A_3 the voltage appears across the capacitor (C_{AZ}) (Auto zero capacitor) which provides automatic compensation for the i/p offset voltages for all op-amp's.

After start command arrives at $t = T_1$, switch 2 opens by the control logic & switch 2 connects to V_R and enables the counter starting from 0. the ckt uses n stage counter and results to 0 after counting 2^n pulses. the analog voltage (V_a) is integrated for a fixed no of 2^n counts of clk-pulses. If the clk period is T then the integration takes place for a time $T_1 = \frac{n}{2} T$ & the o/p is ramp going downwards.

The counter resets itself to 0 at the end of interval T & switch 1

From Fig. $T_1 = t_2 - t_1 = \frac{2^n \text{ clk. pulses}}{\text{clk. period}} = \frac{2^n}{2} T$ — (1)

and

$$t_3 - t_2 = \frac{\text{Digital Count (N)}}{\text{clk. period}} = NT$$
 — (2)

For an integrator the o/p voltage is $\Delta V_0 = \frac{-1}{RC} V(\Delta t)$

where $V_0 = V_1$ at time $T = t_2$ then it integrates the analog i/p voltage then

$$V_1 = \frac{-1}{RC} \int V_a(t_2 - t_1)$$
 — (3)

If the -ve Reference voltage was integrated then

$$V_1 = \frac{-1}{RC} \int (-V_R)(t_3 - t_2)$$
 — (4)

Now substitute the values of eqⁿ (1) & (2) in eqⁿ (3) & (4)

~~$$V_1 = \frac{-1}{RC} \int V_a \frac{2^n T}{2} = \frac{-1}{RC} \int V_a \frac{2^n T}{2}$$~~

$$V_1 = \frac{-1}{RC} \int -V_R NT$$

$$\therefore \frac{-1}{RC} \int V_a \frac{2^n T}{2} = \frac{-1}{RC} \int -V_R NT$$

$$V_a = -V_R \frac{N}{2^n}$$

From this above eqⁿ if the V_R is constant then

$$V_a = \frac{N}{2^n}$$

From this eqⁿ we observe that if

- (i) if V_R and N are constant the analog voltage is proportional to N ($V_a \propto N$)
- (ii) Dual slope ADC integrates i/p signal at 2^n times of T which rejects the noise.

main disadvantage it takes long conversion time.


DAC / ADC Specifications

- Resolution, ② Linearity, ③ Accuracy, ④ Monotonicity, ⑤ Settling time, ⑥ Stability.

① Resolution: It is defined as the smallest change in voltage which may be produced at the dp of the converter i.e.,

$$\text{Resolution} = \frac{V_{FS}}{2^n - 1}$$

 ② Linearity: The linearity of an A/D & D/A converter is an important parameter of its accuracy and linearity tells how close the converter o/p but when ever one i/p increased the respective o/p increases as linearly.



③ Accuracy: The absolute accuracy is defined as the max deviation b/w actual converter o/p & ideal converter o/p.

④ Monotonicity: It is defined as when the i/p is also or constant o/p was produced. It is called as Monotonicity.

⑤ Settling time: It is defined as the time taken for settle with in the specified band $\pm 1/2$ LSB of its final value.

⑥ Stability: The performance of the converter changes with age, power supply variations, all relevant parameters such as gain error, linearity error, Monotonicity all these values are stable with any changes was produced.

problems

1. The basic step of a 9-bit DAC is 10.2 mV. If 00000000 represents 0 volts what is the o/p for 10110111.

Sol: $V_0 = k V_{FS} [d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + d_4 2^{-4} + \dots + d_9 2^{-9}]$

$$= 1 \times 10.2 \times 10^{-3} [1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + \dots + 1 \times 2^{-9}]$$

$$V_0 = 7.38 \text{ mV}$$

2. calculate the value of LSB, HSB & full scale o/p for an 8 bit DAC with in 0 to 10V range.

$$V_0 = k V_{FS} [d_1 2^{-1} + d_2 2^{-2} + \dots + d_8 2^{-8}]$$

$$= V_{FS} \left[\frac{d_1}{2} + \frac{d_2}{2^2} V_{FS} + \frac{d_3}{2^3} + \dots + \frac{d_8}{2^8} V_{FS} \right]$$

$$\text{LSB} = \frac{V_{FS}}{2^8} = \frac{10}{256} = 0.39 \text{ V}$$

$$\text{HSB} = \frac{V_{FS}}{2^1} = \frac{10}{2} = 5 \text{ V}$$

Full scale o/p voltage = full scale range - LSB

$$= 10 - 0.39 = 9.61 \text{ V}$$

3. what is the o/p voltage produced by D/A converter whose o/p voltage range is (0-10)V & whose i/p binary number is

(i) 10 (2 bit DAC)

(ii) 0110 (4 bit DAC)

(iii) 10111000 (8 bit DAC)

(i) 10 (2 bit DAC)

$$V_0 = k V_{FS} [d_1 2^{-1} + d_2 2^{-2}]$$

$$= 1 \times 10 [1 \times 2^{-1} + 0 \times 2^{-2}]$$

$$= 10 \left(\frac{1}{2} \right)$$

$$= 5 \text{ V}$$

(ii) 0110

$$\begin{aligned}V_0 &= kV_{FS} [d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} + d_4 2^{-4}] \\&= 1 \times 10 [0 \times 2^{-1} + 1 \times 2^{-2} + 1 \times 2^{-3} + 0 \times 2^{-4}] \\&= 3.75V\end{aligned}$$

(iii) 1011100

$$\begin{aligned}&= 1 \times 10 [1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4} + 1 \times 2^{-5} + 1 \times 2^{-6} + 0 \times 2^{-7} + 0 \times 2^{-8}] \\&= 7.34V\end{aligned}$$