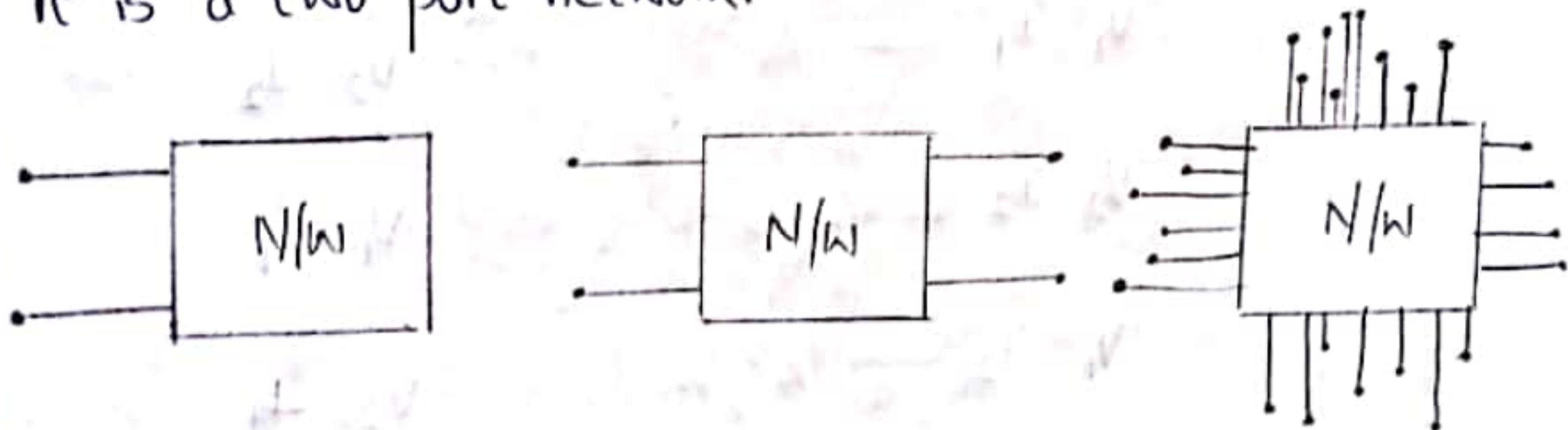


5. Two Port Networks


Port:

A pair of terminals at which signal can enter or leave a network is known as port.

If there is only 1-pair port then it is single port network and if there are 2-pair ports then it is a two port network.



TWO PORT NETWORK :-

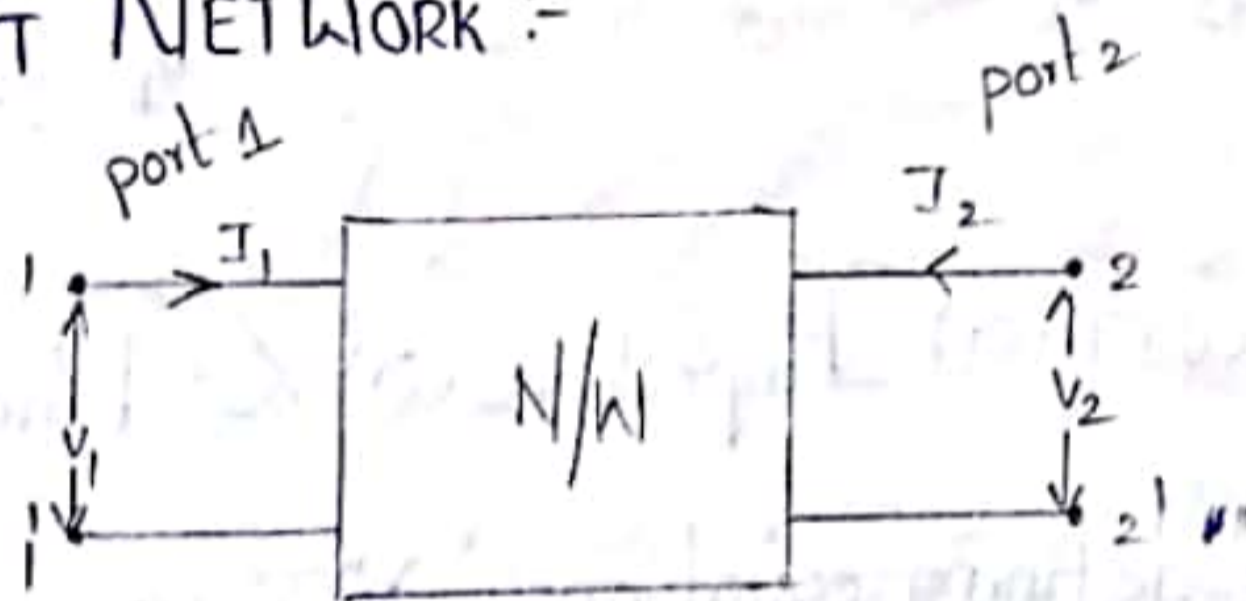

V, I are interrelated and their relationships is explained (or) expressed by Parameters, is known as N/W parameters.

$1, 1'$: port 1 Sending end point

$2, 2'$: port 2 Receiving end point

V_1, I_1 : Voltage and current at port 1

V_2, I_2 : voltage and current at port 2

The voltages and current at these ports are interrelated and their relationships are expressed in terms of parameters is known as Network Parameters.

The variables of the network are V_1, I_1, V_2, I_2 , Out of these 4 variables only 2 are independent and the other 2 are dependent. The dependent variables are expressed

interms of independent variables and network parameters.

Out of these we have 6 combination. They are:

Dependent Variables

Independent Variables

$$V_1, V_2 \text{ --- Z parameters } I_1, I_2$$

$$I_1, I_2 \text{ --- Y parameters } V_1, V_2$$

$$V_1, I_1 \text{ --- ABCD parameters } V_2, I_2$$


$$V_2, I_2 \text{ --- Inverse ABCD parameters } V_1, I_1$$

$$V_1, I_2 \text{ --- H parameters } V_2, I_1$$

$$V_2, I_1 \text{ --- Inverse H parameters } V_1, I_2$$

Open CIRCUIT (or) Impedence (or) Z-Parameter:-

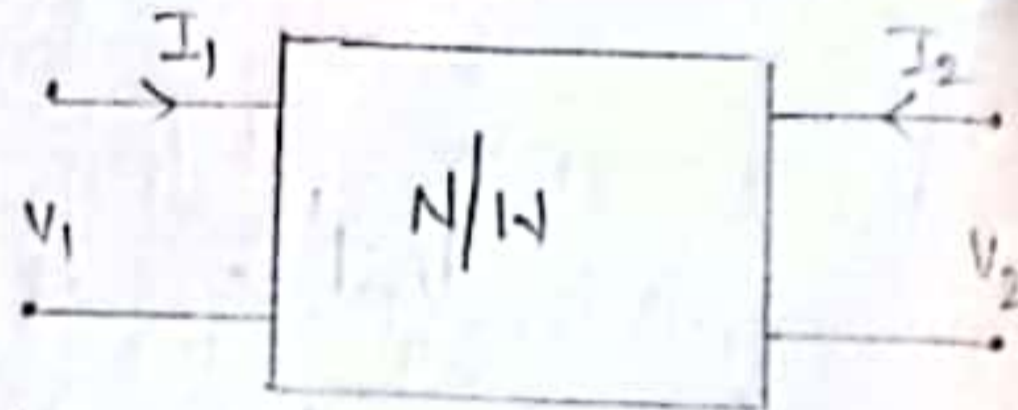The defining equations can be written by considering any two independent variables and network parameters. The independent variables are V_1 and V_2 and network parameter is impedance i.e. Z .



Therefore the defining equation is

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

In Matrix form:-

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Dependent Network param Indep Variables.

Determination Of Z parameters:-

If I_2 is made equal to zero i.e. port 2 is open circuited we can determine Z_{11} and Z_{21} .

$$\therefore V_1 = Z_{11} I_1 + 0.$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0.}$$

port 2 o.c
 $\Rightarrow I_2 = 0$

$$V_2 = Z_{21} I_1 + 0.$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0.}$$

If I_1 is made equal to zero i.e. port 1 is open circuited we can determine Z_{12} and Z_{22} .

port 1 o.c $\Rightarrow I_1 = 0$

$$V_1 = 0 + Z_{12} I_2$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0.}$$

$$V_2 = 0 + Z_{22} I_2$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0.}$$

Where Z_{11} : Driving point Impedence. (DPI)


Z_{21} : forward transfer impedance. (FTI)

Z_{12} : Reverse Transfer impedance. (RTI)

Z_{22} : Driving point Impedence. (DPI).

Short Circuit (or) Admittance (or) Y-Parameter:-

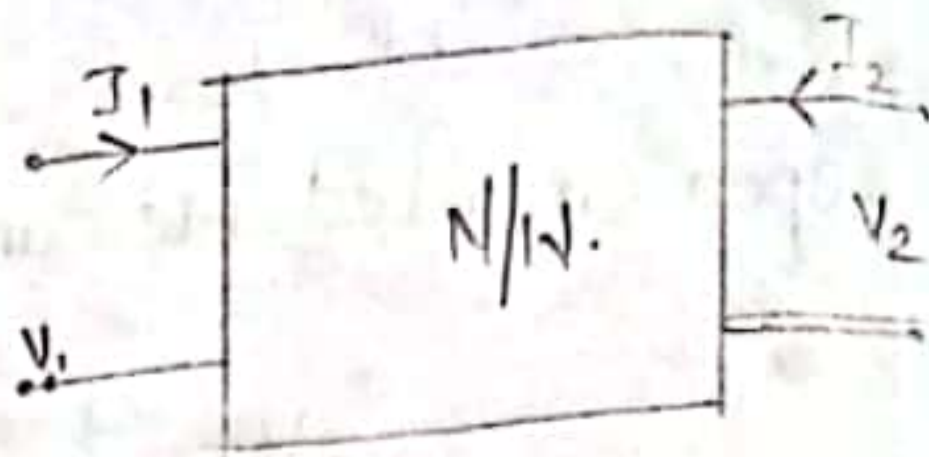The defining equations can be written by using



(or) considering any two independent variables and network parameters. The independent variables are V_1 and V_2 and network parameter is Admittance i.e., $Z = Y = \frac{1}{Z}$.

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Determination Of Y-Parameters:-

If V_2 is made equal to zero i.e., port 2 is short circuited we can determine Y_{11} and Y_{21}

$$I_1 = Y_{11} V_1 + 0$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$I_2 = Y_{21} V_1 + 0$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

If V_1 is made equal to zero i.e. port 1 is short circuited. We can determine Y_{21} and Y_{22} .

$$I_1 = 0 + Y_{12} V_2$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$I_2 = 0 + Y_{22} V_2$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

Y_{11} : Input Admittance


Y_{12} : Forward Transfer Admittance

Y_{21} : Reverse Transfer Admittance.

Y_{22} : Output Admittance.

TRANSMISSION LINES (OR) ABCD PARAMETERS:-

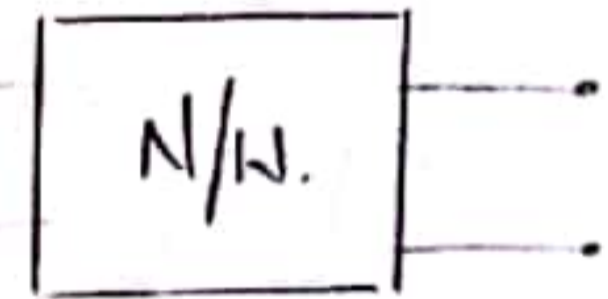In this voltage and current at the transmission end will be expressed with the voltage and current at the receiving end.



Generally, in power system engineering these parameters are used to study the performance of transmission lines.

The defining equations are

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$-I_2$ is considered instead of $+I_2$ because the current direction of I_2 is opposite to I_1 ; the -ve sign is only for indicating the reversal of direction of current but not to the network parameters.

Determination Of ABCD Parameters:-

If I_2 is made equal to zero i.e. \rightarrow port 2 is open circuited we can determine A and C.

$$\text{port 2 is o.c.} \Rightarrow I_2 = 0.$$

$$V_1 = AV_2 - 0 \quad I_1 = CV_2 - 0$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \quad C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

If V_2 is made equal to zero i.e. \rightarrow port 2 is short circuited we can determine B and D.

$$\text{port 2 is s.c.} \Rightarrow V_2 = 0$$

$$A \quad V_1 = 0 - BI_2 \quad I_1 = 0 - DI_2$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \quad D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

A = Open circuit voltage

C = Open circuit transfer admittance

B = Short circuit transfer impedance.

D = Short circuit current

INVERSE ABCD PARAMETERS [A'B'C'D']:

These parameters gives the relationship as follows:

The sending end voltage and currents are expressed in terms of receiving end voltage and current.

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

Determination Of A'B'C'D' Parameters:-

If $I_1 = 0$ is made equal to zero i.e., port 1 is open circuited we can determine A' and C'

port 1 is o.c $\Rightarrow I_1 = 0$.

$$V_2 = A'V_1 - 0$$

$$I_2 = C'V_1 - 0$$

$$A' = \left. \frac{V_2}{V_1} \right|_{I_1=0}$$

\rightarrow forward voltage ratio

$$C' = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$

If V_1 is made equal to zero i.e., port 1 is short circuited we can determine B' and D'

port 1 is s.c $\Rightarrow V_1 = 0$.

$$V_2 = 0 - B'I_1$$

$$I_2 = 0 - D'I_1$$

$$B' = -\frac{V_2}{I_1}$$

$$D' = \left. \frac{I_2}{-I_1} \right|_{V_1=0}$$

A' : forward voltage ratio.

B' : Transfer impedance

C' : Transfer Admittance.

D' : forward current ratio.

HYBRID PARAMETERS. (OR) H PARAMETERS:

These parameters gives the relationship between sending end voltage and receiving end current in terms of send ending end current and receiving end voltage.

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Determination Of H-PARAMETERS:-

If V_2 is made equal to zero i.e., port 2 is short circuited we can determine h_{11} and h_{21}

port 2 is s.c. $V_2 = 0$.

$$V_1 = h_{11} I_1 + 0$$

$$I_2 = h_{21} I_1 + 0$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

If I_1 is made equal to zero i.e., port 1 is open circuited we can determine h_{12} and h_{22}

Port 1 is O.C $\Rightarrow I_1 = 0$.

$$V_1 = 0 + h_{12} V_2 \quad I_2 = 0 + h_{22} V_2$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

h_{11} : short circuit impedance

h_{12} : reverse voltage gain

h_{21} : forward current transfer ratio.

h_{22} : Open circuit Output admittance.

H-parameters are useful in analysing the transistor characteristics

INVERSE HYBRID PARAMETERS (or) H^{-1} PARAMETER :-

These parameters gives the relationship between sending end current and receiving end voltage in terms of sending end voltage and receiving end current.

$$I_1 = g_{11} V_1 + g_{12} V_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

Determination of H⁻¹ Parameters:-

open If V_2 is made equal to zero i.e. port 2 is short circuited we can determine g_{11} and g_{21}

port 2 is o.c, $I_2 = 0$

$$I_1 = g_{11} V_1 + 0 \quad V_2 = g_{21} V_1 + 0$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

If V_1 is made equal to zero i.e. port 1 is short circuited we can determine g_{12} and g_{22}

port 1 is s.c $V_1 = 0$

$$I_1 = 0 + g_{12} I_2 \quad V_2 = 0 + g_{22} I_2$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} \quad g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

g_{11} : Impedence conductance.


g_{12} : reverse current ratio

g_{21} : open circuited forward voltage gain

g_{22} : Impedence

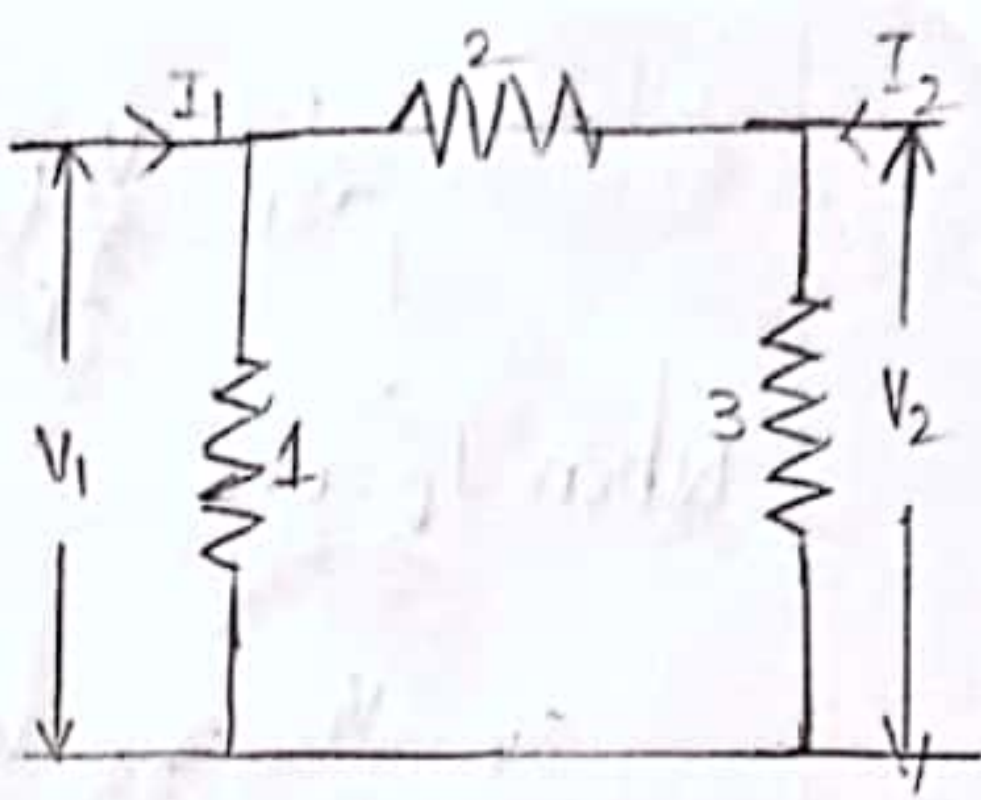9)

Find the Z-parameters for the given network.



sol: N.K.T


$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

When $I_2 = 0$ O.C


$$Z_{11} = \frac{V_1}{I_1} \quad \& \quad Z_{21} = \frac{V_2}{I_1}$$

I_2 is open circuited.

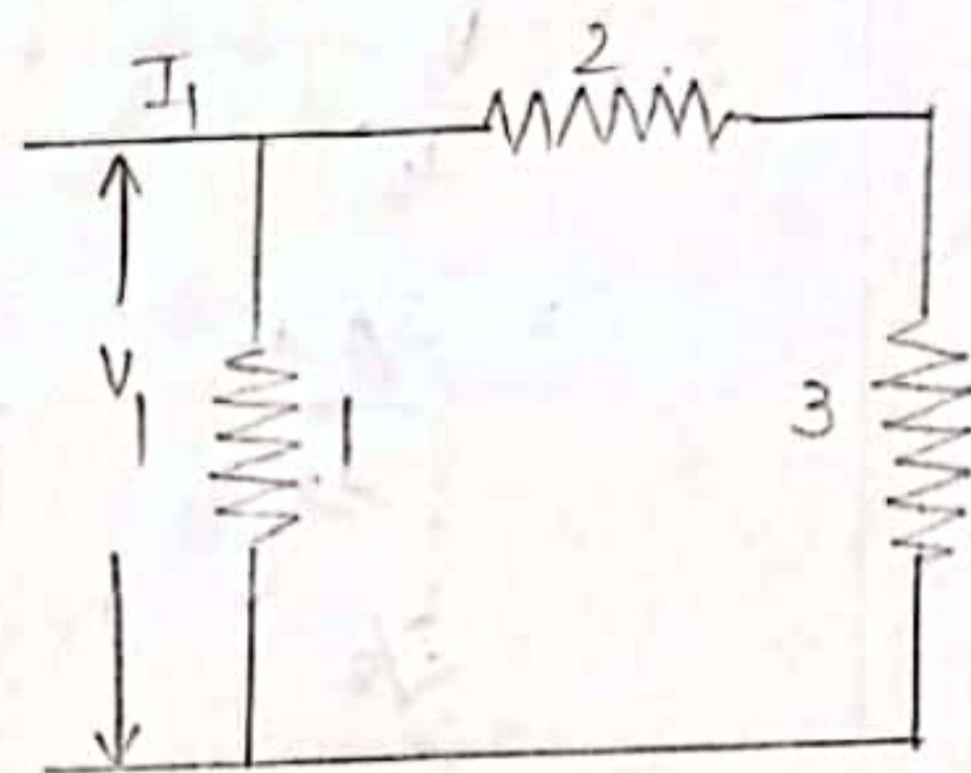

$$V_1 = Z_{eq} \cdot I_1$$

$$= \frac{5}{6} \cdot I_1$$

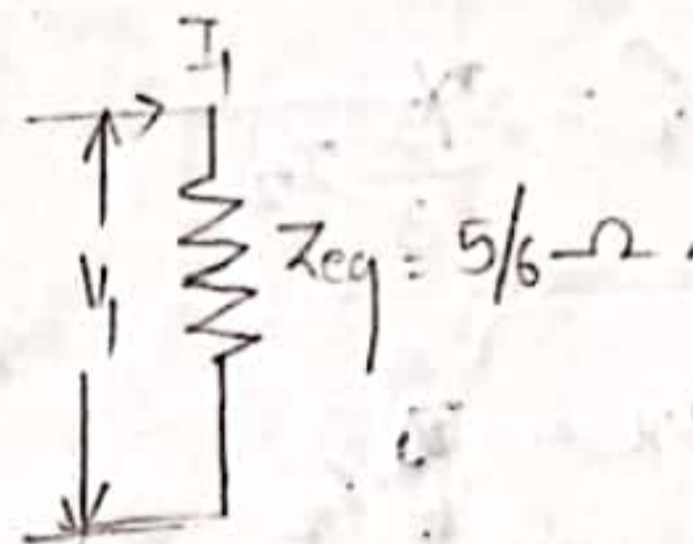


Now, $Z_{11} = \frac{5/6 \cdot I_1}{I_1}$
 $= \frac{5}{6} \Omega$

$$I_x = \frac{1}{6} I_1$$

$$V_{3\Omega} = \frac{1}{6} I_1 \times 3$$

$$= \frac{1}{2} I_1$$

$$V_{3\Omega} = V_2 = \frac{1}{2} I_1$$

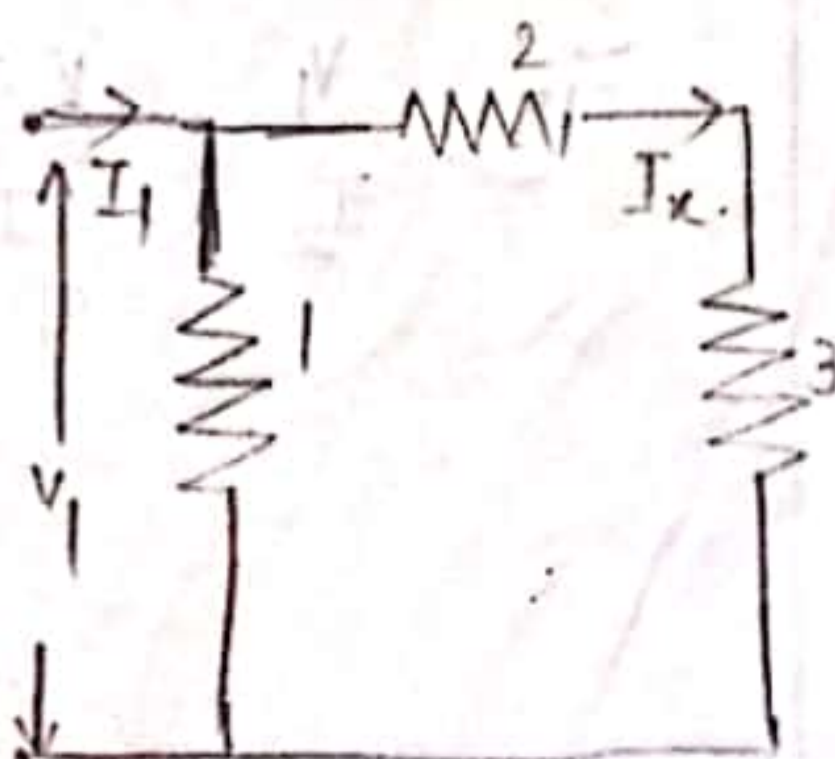


$$Z_{21} = \frac{V_2}{I_1} = \frac{V_2 I_1}{I_1} = \frac{V_2}{I_1}$$

When $I_1 = 0$.


$$Z_{12} = \frac{V_1}{I_2} \quad Z_{22} = \frac{V_2}{I_2}$$

$$V_2 = \frac{3}{2} I_2$$

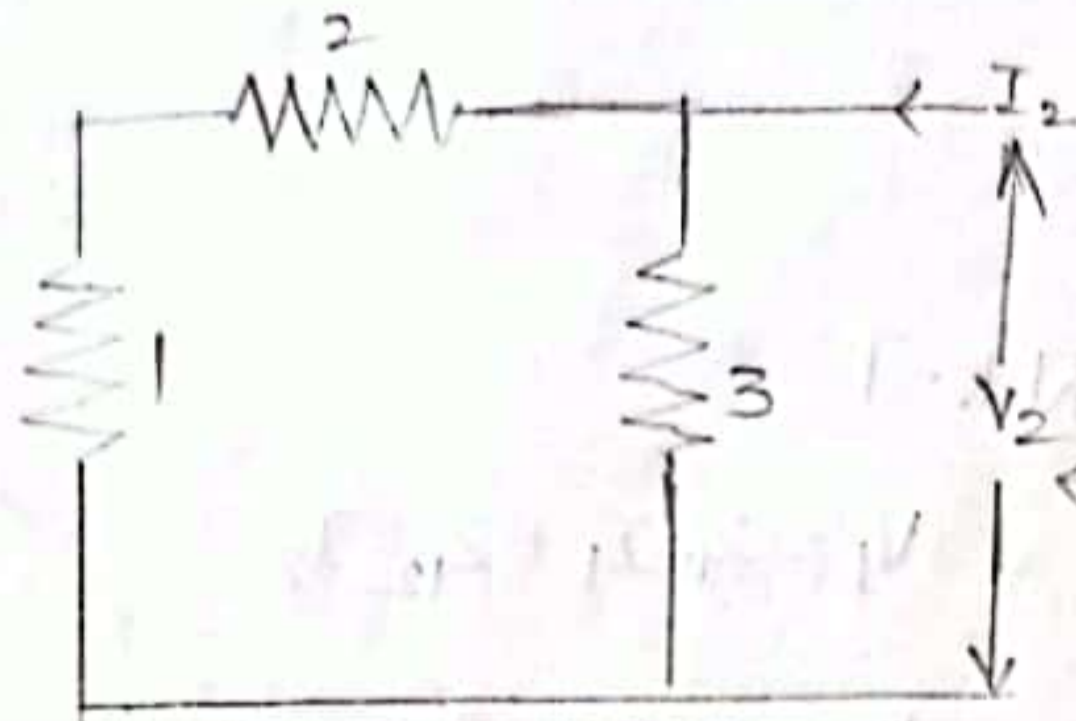

Now,
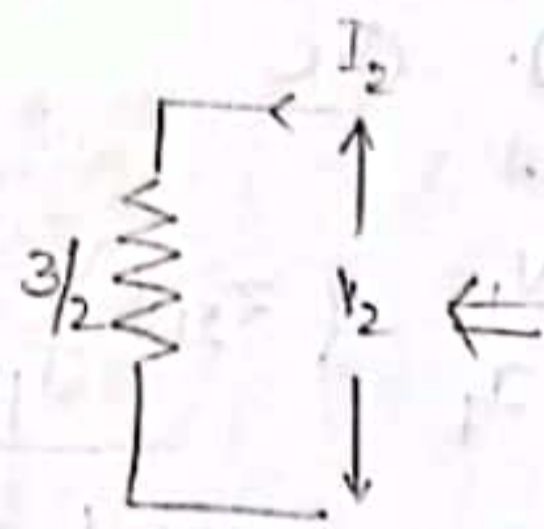
$$\begin{aligned} Z_{22} &= \frac{V_2}{I_2} \\ &= \frac{3/2 I_2}{I_2} \\ &= 3/2 \end{aligned}$$




$$I_x = \frac{2 \times 3}{3} I_2$$

$$I_x = \frac{1}{6} I_2$$


$$\begin{aligned} I_x &= \frac{1}{6} I_2 \\ &= \frac{1}{2} I_2 \end{aligned}$$

$$V_{1\Omega} = \frac{3}{6} I_2 \times 1 = \frac{1}{2} I_2$$
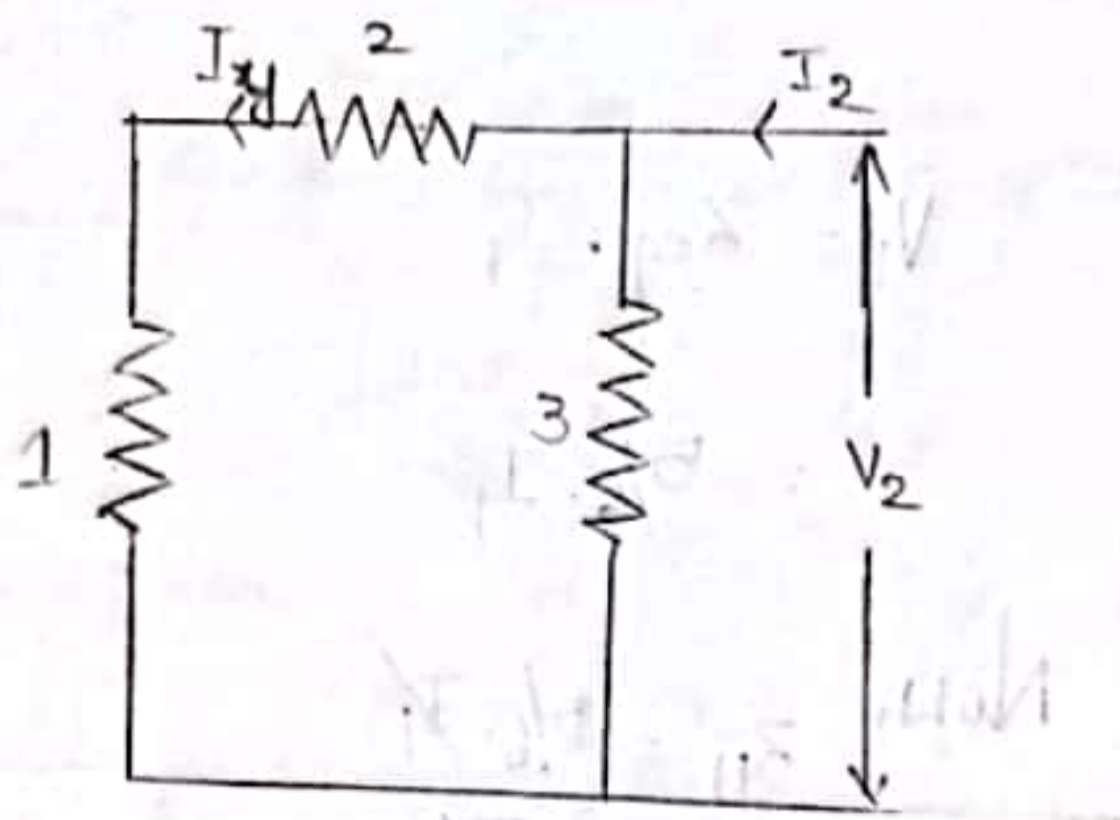
$$Z_{12} = \frac{V_1}{I_2} = \frac{1/2 I_2}{I_2} = \frac{1}{2}$$



Q)

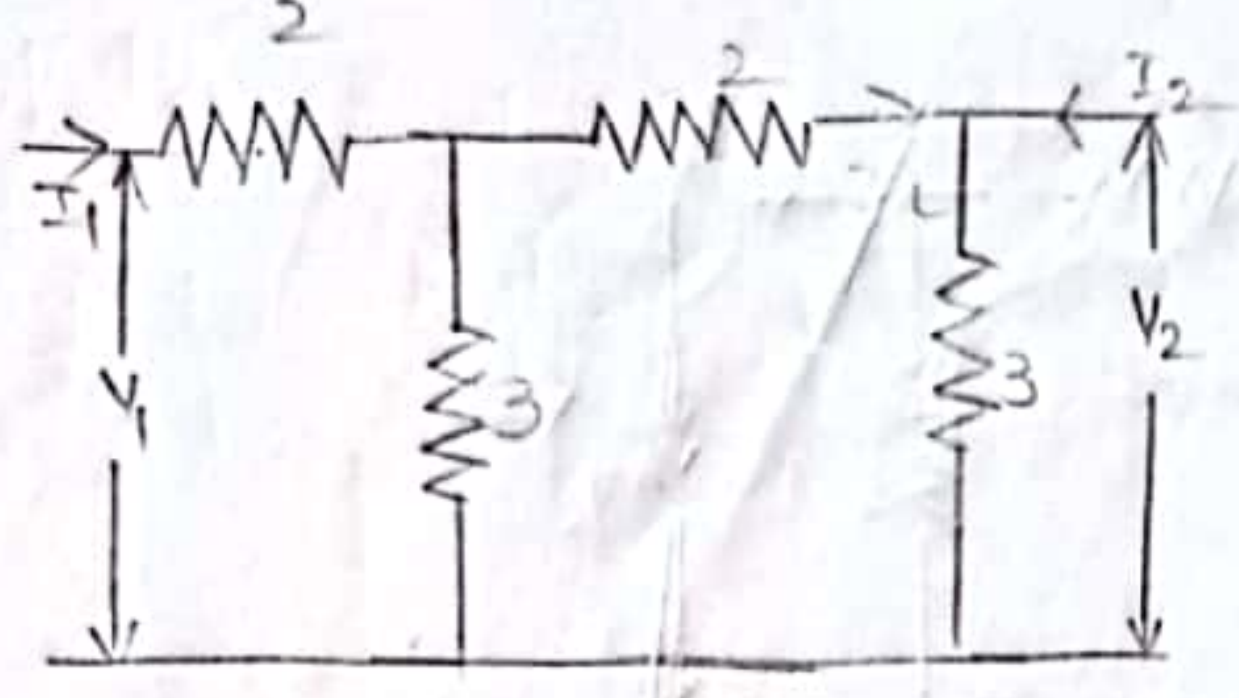


Ans:-

When $I_2 = 0$.

$$Z_{11} = \frac{V_1}{I_1} \quad \& \quad Z_{21} = \frac{V_2}{I_1}$$


I_2 is open circuit

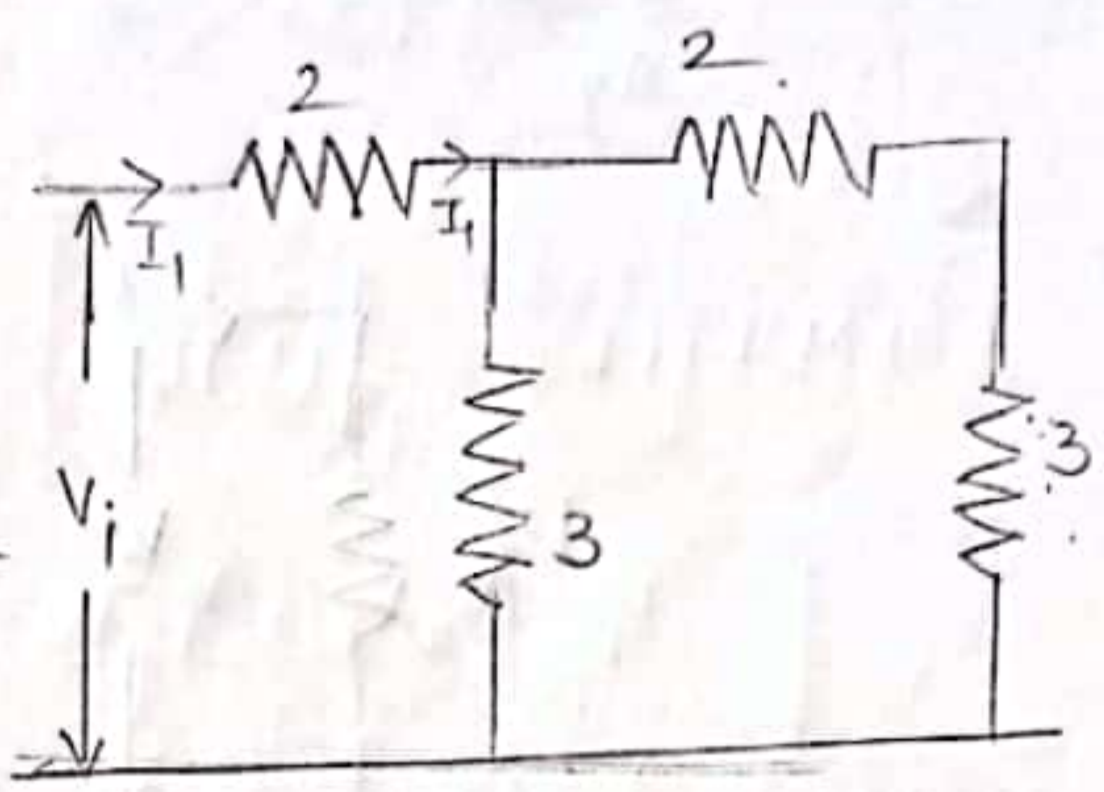

$$V_1 = \frac{31}{8} I_1$$

$$Z_{11} = \frac{\frac{31}{8} I_1}{I_1}$$


$$Z_{11} = \frac{31}{8}$$

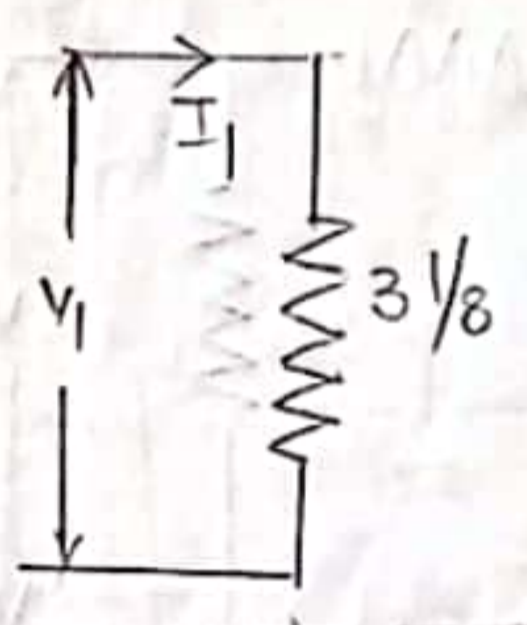



$$I_x = \frac{3}{8} I_1$$

$$V_{3-2} = \frac{3}{8} I_1 \times 3 = \frac{9}{8} I_1 = V_2$$
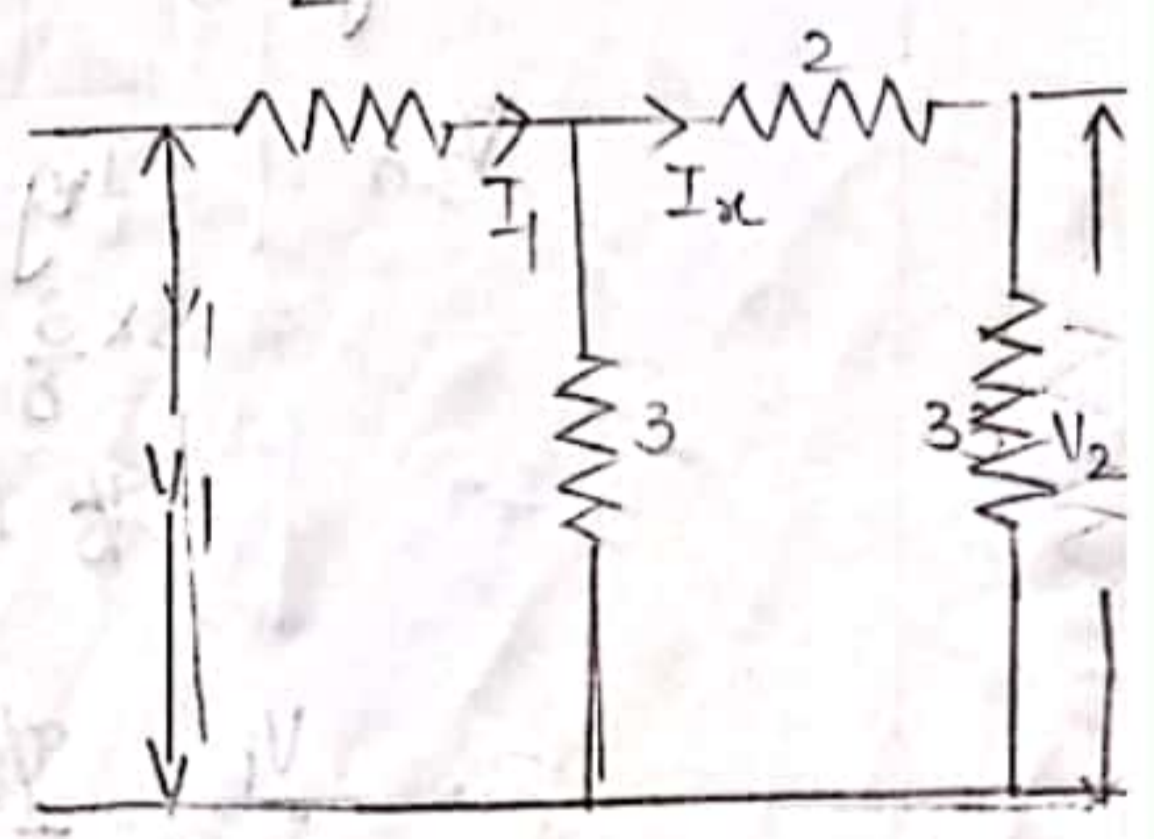
$$Z_{21} = \frac{V_2}{I_1} = \frac{\frac{9}{8} I_1}{I_1} = \frac{9}{8}$$




When I_1 is open

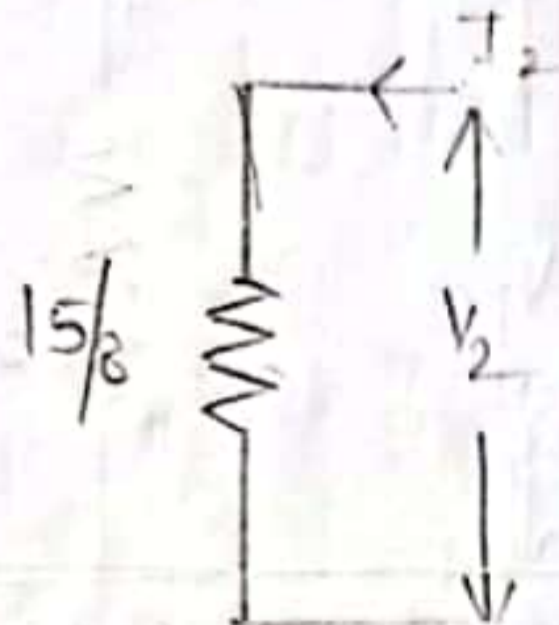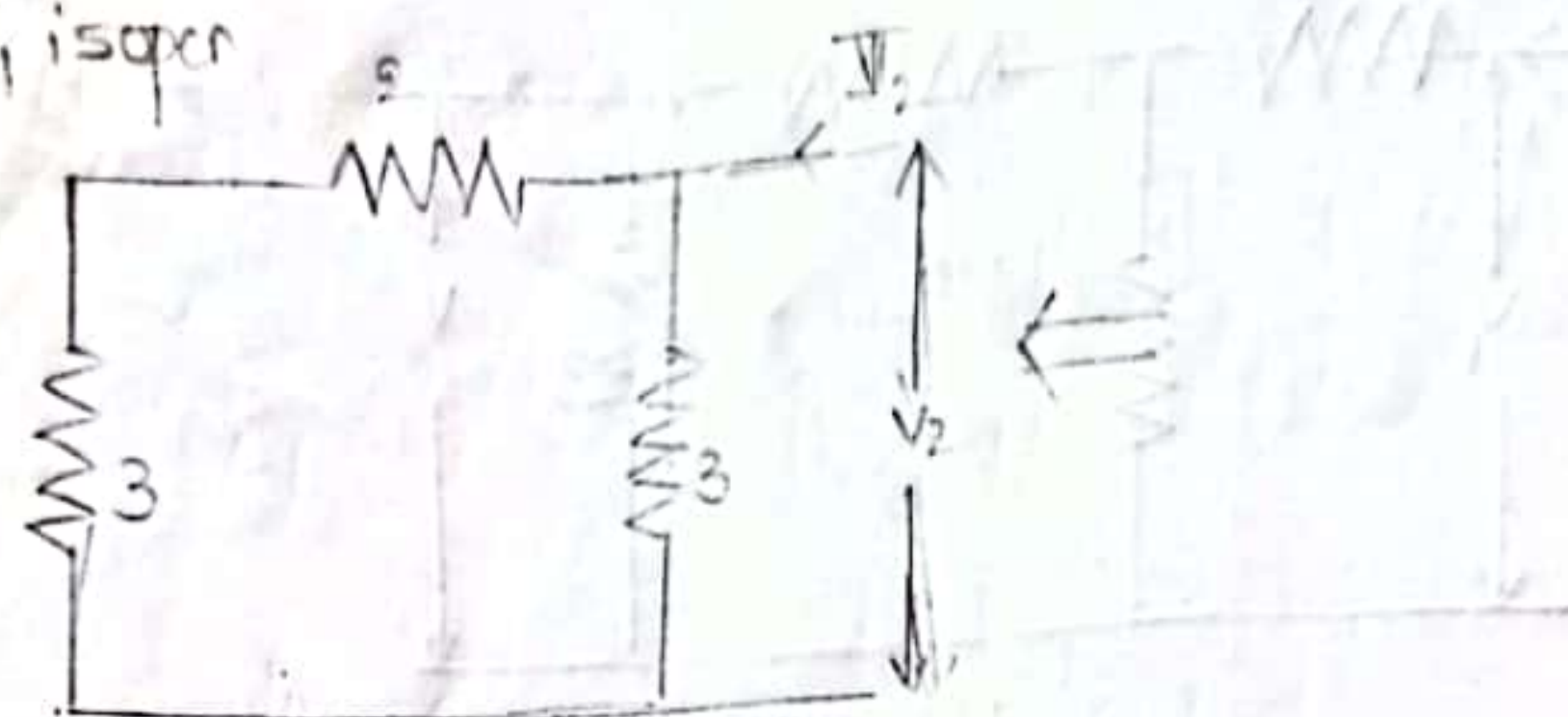

$$\frac{V_2}{I_2} = 15/8 \Omega$$

$$Z_{22} = 15/8 \Omega$$

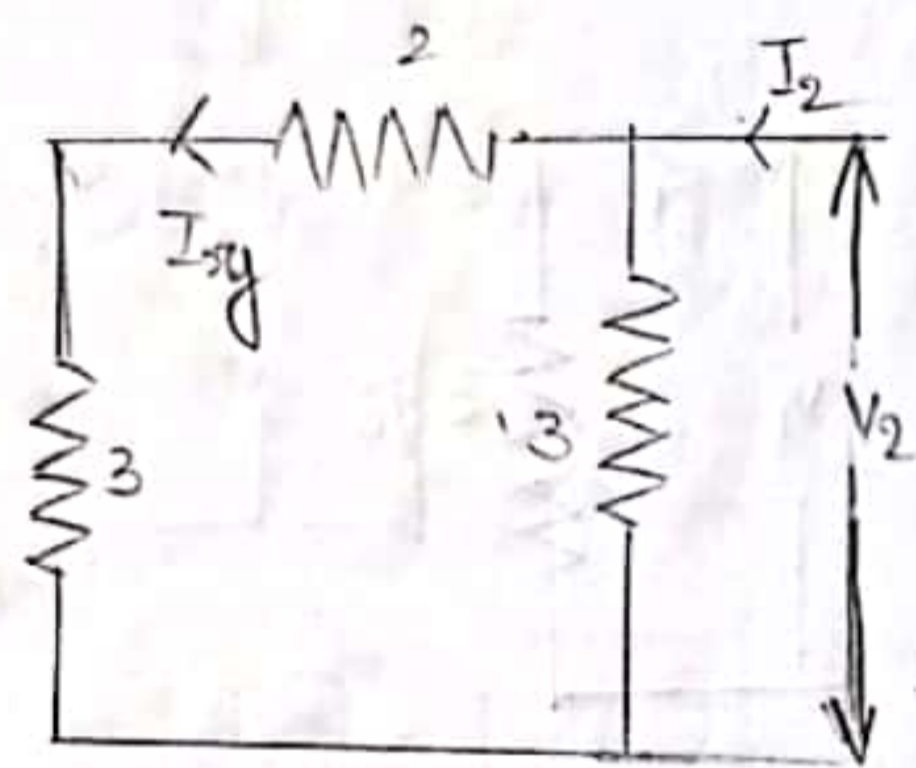

$$I_{xy} = \frac{3}{8} I_2$$

$$I_{xy} = \frac{3}{8} I_2$$

$$V_{3\Omega} = 3 I_{xy}$$

$$= 3 \times \frac{3}{8} I_2$$

$$= \frac{9}{8} I_2 = V_1$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{9/8 I_2}{I_2}$$

$$= 9/8 \Omega$$

Relation SHIPS:

Z - PARAMETERS INTERMS OF Y PARAMETERS:-

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\Delta Y = \begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix} = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$\Delta Y_1 = \begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix} = Y_{22} I_1 - Y_{12} I_2$$

$$\Delta Y_2 = \begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix} = Y_{11} I_2 - Y_{21} I_1$$

$$V_1 = \frac{\Delta Y_1}{\Delta Y} = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y} \quad \text{--- (3)}$$

$$V_2 = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y} \quad \text{--- (3)}$$

$$V_2 = \frac{\Delta Y_2}{\Delta Y} = \frac{Y_{11} I_2 - Y_{21} I_1}{\Delta Y}$$
$$= \frac{Y_{11}}{\Delta Y} I_2 - \frac{Y_{21}}{\Delta Y} I_1 \quad \text{--- (4)}$$

from ①, ②, ③ & ④.

$$Z_{11} = \frac{V_{22}}{\Delta y} \quad Z_{21} = \frac{-V_{21}}{\Delta y}$$

$$Z_{12} = \frac{-V_{12}}{\Delta y} \quad Z_{22} = \frac{V_{11}}{\Delta y}$$

Y-PARAMETERS IN TERMS OF Z-PARAMETERS.

$$\left[\begin{array}{l} I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- ①} \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- ②} \end{array} \right.$$

$$Z_1 \quad V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Now,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta Z = \begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix} = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$\Delta Z_1 = \begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix} = V_1 Z_{22} - V_2 Z_{12}$$

$$\Delta Z_2 = \begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix} = Z_{11} V_2 - Z_{21} V_1$$

$$I_1 = \frac{\Delta Z_1}{\Delta z} = \frac{V_1 Z_{22} - V_2 Z_{12}}{\Delta z} \quad \text{--- (3)}$$

$$I_2 = \frac{\Delta Z_2}{\Delta z} = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta z} \quad \text{--- (4)}$$

Comparing (1), (2) with (3), (4) respectively, we get,

$$Y_{11} = \frac{Z_{22}}{\Delta z} \quad Y_{12} = \frac{-Z_{12}}{\Delta z}$$

$$Y_{21} = \frac{-Z_{21}}{\Delta z} \quad Y_{22} = \frac{+Z_{11}}{\Delta z}$$

Z-PARAMETERS IN TERMS OF H-PARAMETERS:-

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

From (2)

$$V_2 = \frac{I_2 - h_{21} I_1}{h_{22}} \quad \text{--- (3)}$$

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1$$

put (3) in eqn (1).

$$\begin{aligned}V_1 &= h_{11} I_1 + h_{12} \left[\frac{I_2 - h_{21} I_1}{h_{22}} \right] \\&= h_{11} I_1 + \frac{h_{12}}{h_{22}} I_2 - \frac{h_{12} h_{21}}{h_{22}} I_1 \\&= \left[\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right] I_1 + \frac{h_{12}}{h_{22}} I_2.\end{aligned}$$

$$V_1 = \frac{\Delta h}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2. \quad \text{--- (4)}$$

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \quad \text{--- (5)}$$

Comparing z & h parameters we get.

$$Z_{11} = \frac{\Delta h}{h_{22}} \quad Z_{12} = \frac{h_{12}}{h_{22}}$$

$$Z_{21} = -\frac{h_{21}}{h_{22}} \quad Z_{22} = \frac{1}{h_{22}}.$$

H - PARAMETERS IN TERMS OF Z - PARAMETERS:-

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$V_2 = h_{21} I_1 + h_{22} V_2.$$

$$V_1 = Z_{11} I_1 + Z_{12} V_2. \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$I_2 = \frac{V_2 - Z_{21} I_1}{Z_{22}} \quad \text{--- (3)}$$

Substitute (3) in (1)

$$V_1 = Z_{11} I_1 + Z_{12} \left[\frac{V_2 - Z_{21} I_1}{Z_{22}} \right]$$

$$= Z_{11} I_1 + \frac{Z_{12} V_2}{Z_{22}} - \frac{Z_{12} Z_{21} I_1}{Z_{22}}$$

$$= \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right] I_1 + \frac{Z_{12}}{Z_{22}} V_2$$

$$\therefore V_1 = \frac{\Delta Z}{Z_{22}} I_1 + \frac{Z_{12}}{Z_{22}} V_2 \quad \text{--- (4)}$$

$$I_2 = \frac{1}{Z_{22}} V_2 - \frac{Z_{21}}{Z_{22}} I_1 \quad \text{--- (5)}$$

Comparing equation (5) & (4) with h-parameters

$$h_{11} = \frac{\Delta Z}{Z_{22}} \quad h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = \frac{-Z_{21}}{Z_{22}} \quad h_{22} = \frac{1}{Z_{22}}$$

H-PARAMETERS IN TERMS OF Y-PARAMETERS:-

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

from (3)

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$V_1 = \frac{I_1 - Y_{12} V_2}{Y_{11}} \quad \text{--- (5)}$$

Put substitute (5) in (4)

$$I_2 = Y_{21} \left[\frac{I_1 - Y_{12} V_2}{Y_{11}} \right] + Y_{22} V_2.$$

$$= \frac{Y_{21}}{Y_{11}} I_1 - \frac{Y_{21} Y_{12} V_2}{Y_{11}} + Y_{22} V_2$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 + V_2 \left[\frac{Y_{11} Y_{22} - Y_2 Y_{21}}{Y_{11}} \right] \quad \text{--- (6)}$$

$$(5) \Rightarrow V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2$$

Comparing (5) & (6) with (1) & (2). we get,

$$h_{11} = \frac{1}{Y_{11}} \quad h_{12} = \frac{-Y_{12}}{Y_{11}}$$

$$h_{21} = \frac{Y_{21}}{Y_{11}} \quad h_{22} = \frac{\Delta Y}{Y_{11}}$$

Y-parameters in terms of H-parameters:-

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (4)}$$

From (3).

$$I_1 = \frac{V_1 - h_{12} V_2}{h_{11}}$$

$$= \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \quad \text{--- (5)}$$

Substitute (5) in (4)

$$I_2 = h_{21} \left[\frac{V_1}{h_{11}} - \frac{h_{12} V_2}{h_{11}} \right] + h_{22} V_2$$

$$= \frac{h_{21}}{h_{11}} V_1 - \frac{h_{12} h_{21}}{h_{11}} V_2 + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + V_2 \left[\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} \right] \quad \text{--- (6)}$$

$$\text{(5)} \Rightarrow I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2$$

Comparing (5) & (6) with (1) & (2) we get,

$$Y_{11} = \frac{1}{h_{11}} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad Y_{22} = \frac{\Delta h}{h_{11}}$$

* Relation between A, B, C, D, Z, And Y-Parameters:-

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\text{When } I_2 = 0 \quad A = \frac{V_1}{V_2}$$

$$V_1 = Z_{11} I_1$$

$$V_2 = Z_{21} I_1$$

$$A = \frac{V_1}{V_2} = \frac{Z_{11} I_1}{Z_{21} I_1}$$

$$= \frac{Z_{11}}{Z_{21}}$$

$$A = \frac{Z_{11}}{Z_{21}} = \frac{[Y_{22}/\Delta Y]}{[-Y_{21}/\Delta Y]} = -\frac{Y_{22}}{Y_{21}}$$

$$\therefore A = \frac{Z_{11}}{Z_{21}} = -\frac{Y_{22}}{Y_{21}}$$

$$C = \frac{I_1}{V_2} = \frac{I_1}{Z_{21} I_1} = \frac{1}{Z_{21}}$$

$$C = \frac{1}{Z_{21}} = \frac{1}{-\frac{Y_{21}}{\Delta Y}} = -\frac{\Delta Y}{Y_{21}}$$

$$\text{When } V_2 = 0 \quad B = -\frac{V_1}{I_2}$$

$$Y_{21} = \frac{I_2}{V_1} \Rightarrow V_1 = \frac{I_2}{Y_{21}}$$

$$\text{Now, } B = -\frac{V_1}{I_2} = -\frac{I_2/Y_{21}}{I_2}$$

$$B = -\frac{1}{Y_{21}}$$

$$\therefore B = -\frac{1}{Y_{21}}$$

$$D = -\frac{I_1}{I_2} = -\frac{Y_{11}}{Y_{21}} = \frac{-Z_{22}/\Delta Z}{-Z_{21}/\Delta Z} = \frac{Z_{22}}{Z_{21}}$$


$$* A = \frac{Z_{11}}{Z_{21}} = -\frac{Y_{22}}{Y_{21}}$$

$$* B = -\frac{1}{Y_{21}}$$

$$* D = \frac{-Y_{11}}{Y_{21}} = \frac{Z_{22}}{Z_{21}}$$

$$* C = -\frac{\Delta Y}{Y_{21}}$$

Series Connection:-

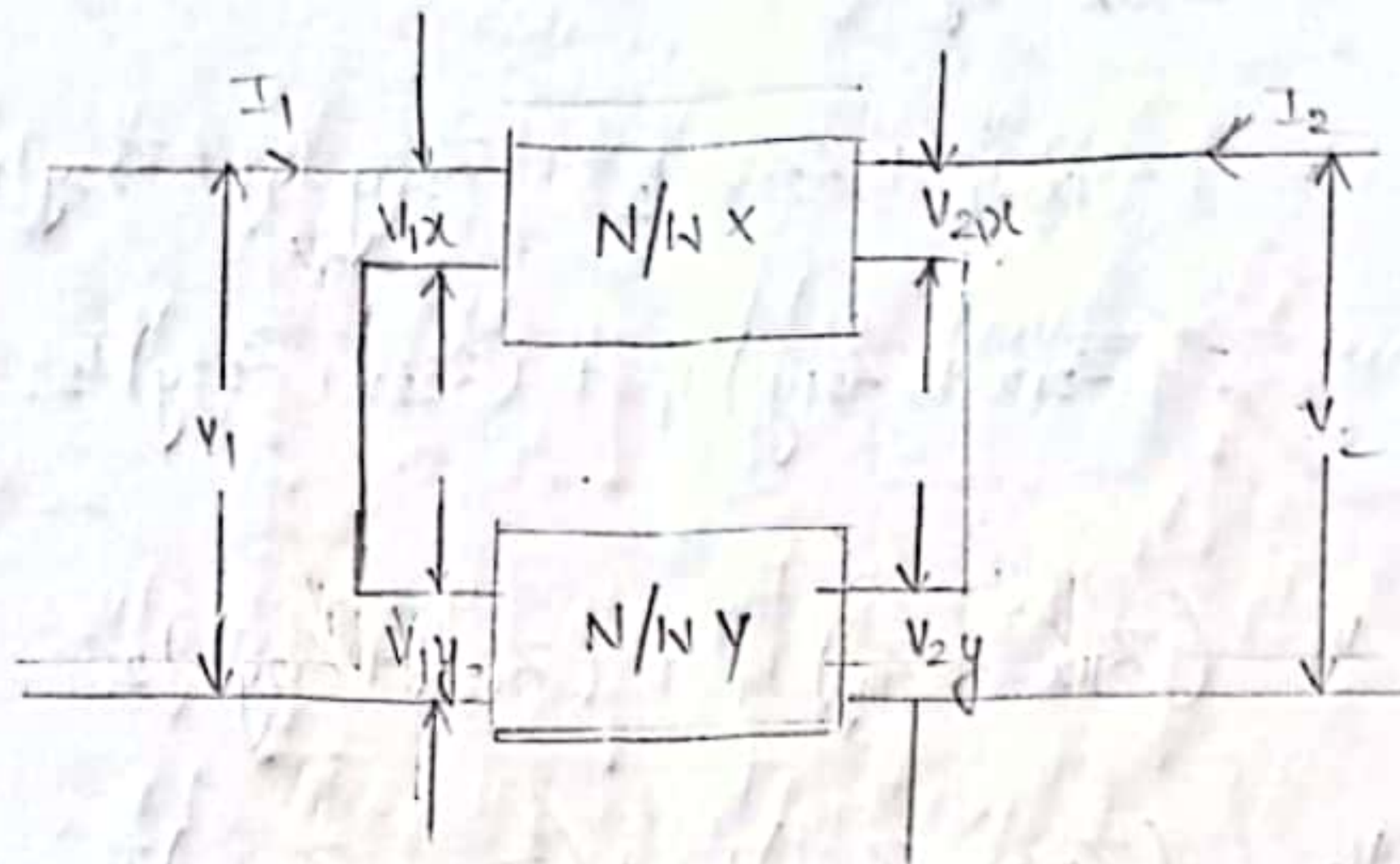

When the 2 two ports networks are connected in series then,

$$V_{1x} = Z_{11x} I_1 + Z_{12x} I_2$$

$$V_{2x} = Z_{21x} I_1 + Z_{22x} I_2$$

for N/W Y.

$$V_{1y} = Z_{11y} I_1 + Z_{12y} I_2$$

$$V_{2y} = Z_{21y} I_1 + Z_{22y} I_2$$

Voltage across V_1 is $V_1 = V_{1x} + V_{1y}$

across V_2 is $V_2 = V_{2x} + V_{2y}$

Now

$$V_1 = V_{1x} + V_{1y}$$

$$= Z_{11x} I_1 + Z_{12x} I_2 + Z_{11y} I_1 + Z_{12y} I_2$$

$$= (Z_{11x} + Z_{11y}) I_1 + (Z_{12x} + Z_{12y}) I_2$$

$$V_2 = V_{2x} + V_{2y}$$

$$= Z_{21x} I_1 + Z_{22x} I_2 + Z_{21y} I_1 + Z_{22y} I_2$$

$$= (Z_{21x} + Z_{21y}) I_1 + (Z_{22x} + Z_{22y}) I_2$$

$$V_1 = (Z_{11x} + Z_{11y}) I_1 + (Z_{12x} + Z_{12y}) I_2$$


$$V_2 = (Z_{21x} + Z_{21y}) I_1 + (Z_{22x} + Z_{22y}) I_2$$

$$Z_{11} = Z_{11x} + Z_{11y} \quad \left| \quad Z_{21} = Z_{21x} + Z_{21y}$$

$$Z_{22} = Z_{22x} + Z_{22y} \quad \left| \quad Z_{12} = Z_{12x} + Z_{12y}$$

From the above expressions we can say that, the impedance is equal to the individual impedances of x and y.

PARALLEL CONNECTION:-

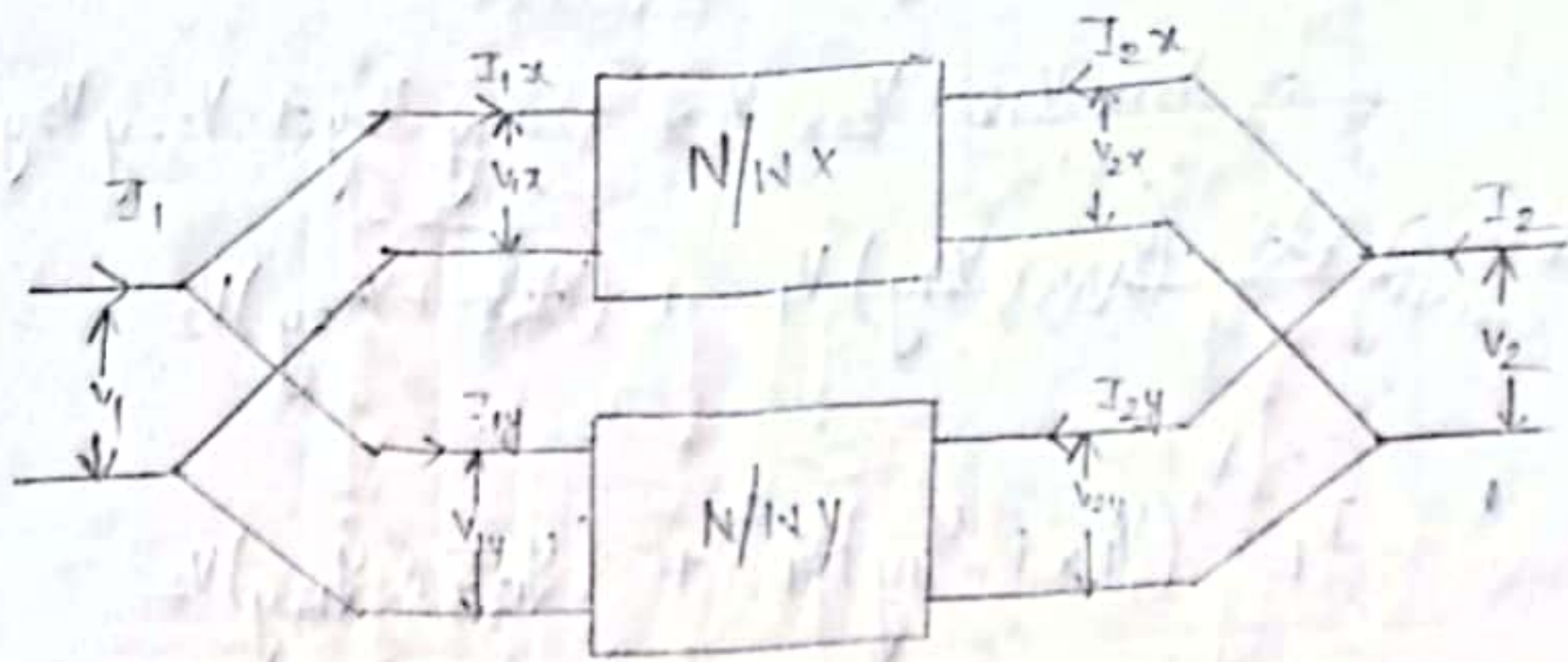

When the 2 two ports networks are connected in parallel, then

$$\begin{cases} I_1 = I_{1x} + I_{1y} \\ I_2 = I_{2x} + I_{2y} \end{cases} \quad \left| \quad \begin{cases} V_1 = V_{1x} = V_{1y} \\ V_2 = V_{2x} = V_{2y} \end{cases} \right.$$

from \$N_1/N_x\$.

$$I_{1x} = Y_{11x} V_{1x} + Y_{12x} V_{2x}$$

$$I_{2x} = Y_{21x} V_{1x} + Y_{22x} V_{2x}$$

from \$N_1/N_y\$

$$I_{1y} = Y_{11y} V_{1y} + Y_{12y} V_{2y}$$

$$I_{2y} = Y_{21y} V_{1y} + Y_{22y} V_{2y}$$

Now,

$$I_1 = I_{1x} + I_{1y}$$

$$= Y_{11x} V_{1x} + Y_{12x} V_{2x} + Y_{11y} V_{1y} + Y_{12y} V_{2y}$$

$$= (Y_{11x} + Y_{11y}) V_1 + (Y_{12x} + Y_{12y}) V_2$$

$$I_2 = I_{2x} + I_{2y}$$

$$= Y_{21x} V_{1x} + Y_{22x} V_{2x} + Y_{21y} V_{1y} + Y_{22y} V_{2y}$$

$$= (Y_{21x} + Y_{21y}) V_1 + (Y_{22x} + Y_{22y}) V_2$$

$$I_1 = (Y_{11x} + Y_{11y}) V_1 + (Y_{12x} + Y_{12y}) V_2$$

$$I_2 = (Y_{21x} + Y_{21y}) V_1 + (Y_{22x} + Y_{22y}) V_2$$


$$Y_{11} = Y_{11x} + Y_{11y}$$

$$Y_{21} = Y_{21x} + Y_{21y}$$


$$Y_{12} = Y_{12x} + Y_{12y}$$

$$Y_{22} = Y_{22x} + Y_{22y}$$


CASCADE CONNECTION:-

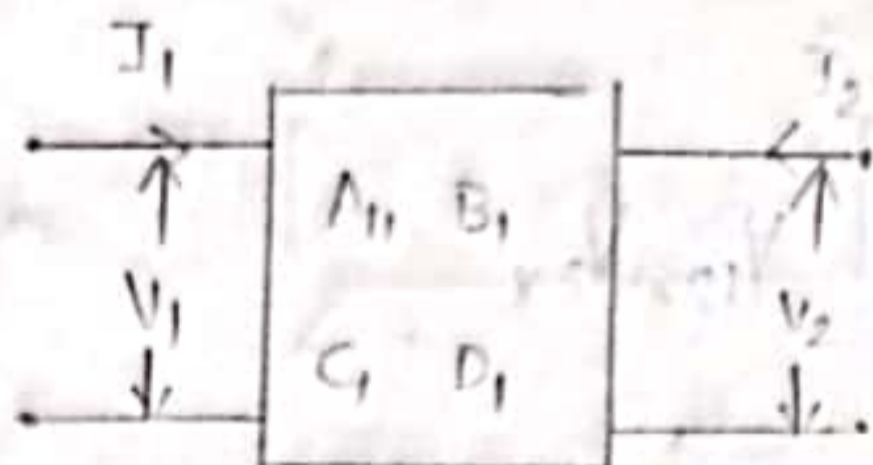
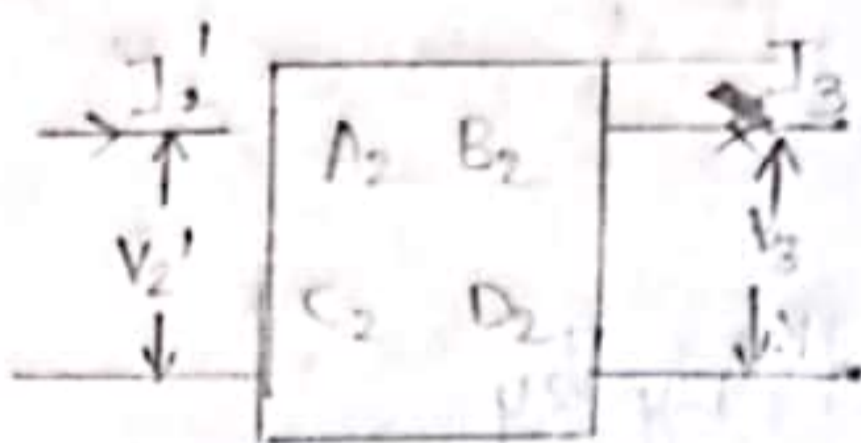
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


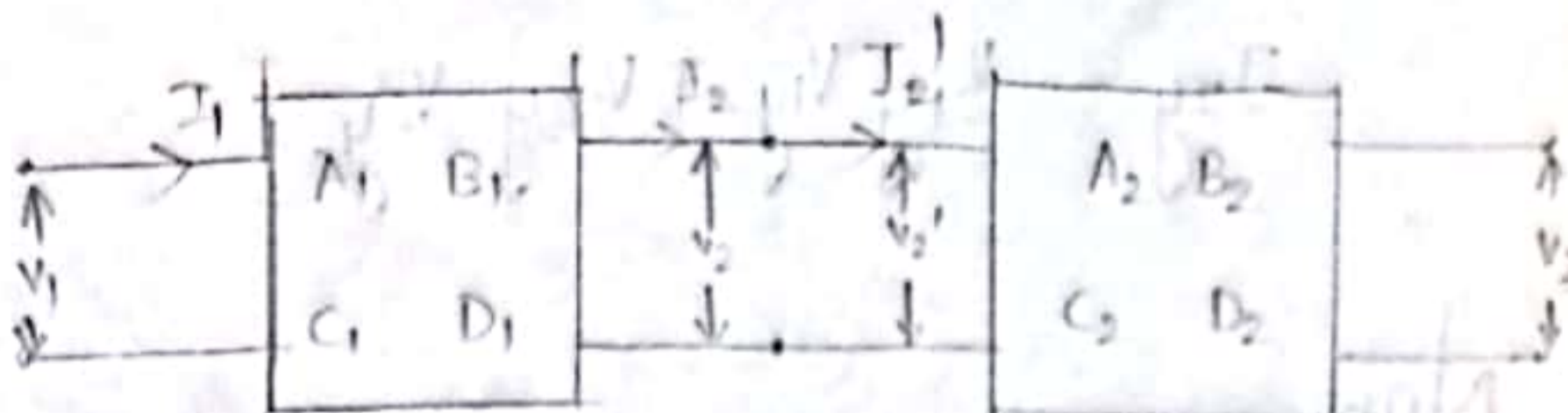
$$\begin{bmatrix} V_2' \\ I_2' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$



From figure, $I_2 = I_2'$

$$V_2 = V_2'$$

Now,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & B_2 C_1 + D_1 D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

comparing above Matrix with

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$


$$A_3 = A_1 A_2 + B_1 C_2$$

$$B_3 = A_1 B_2 + B_1 D_2$$

$$C_3 = C_1 A_2 + D_1 C_2$$

$$D_3 = B_2 C_1 + D_1 D_2$$

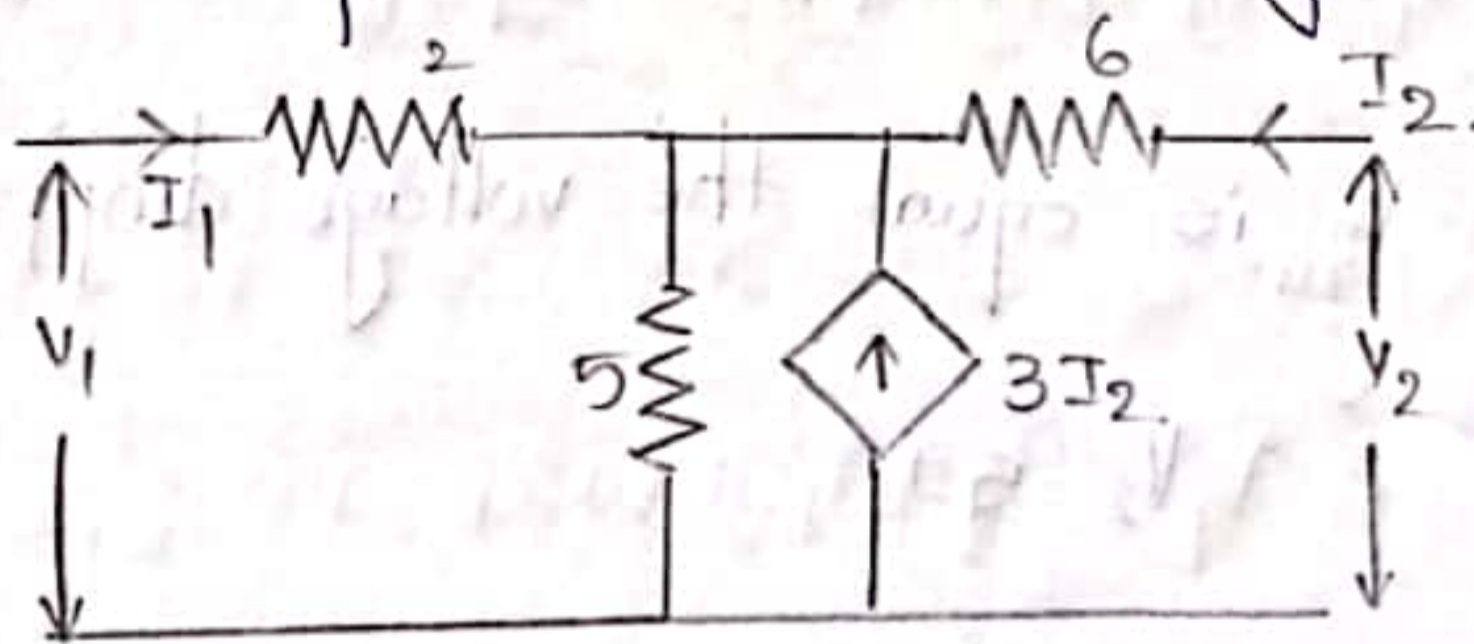1. Find the z-parameters for the given network.



Ans.


W.K.T

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

When port₂ is open circuited. $I_2 = 0$
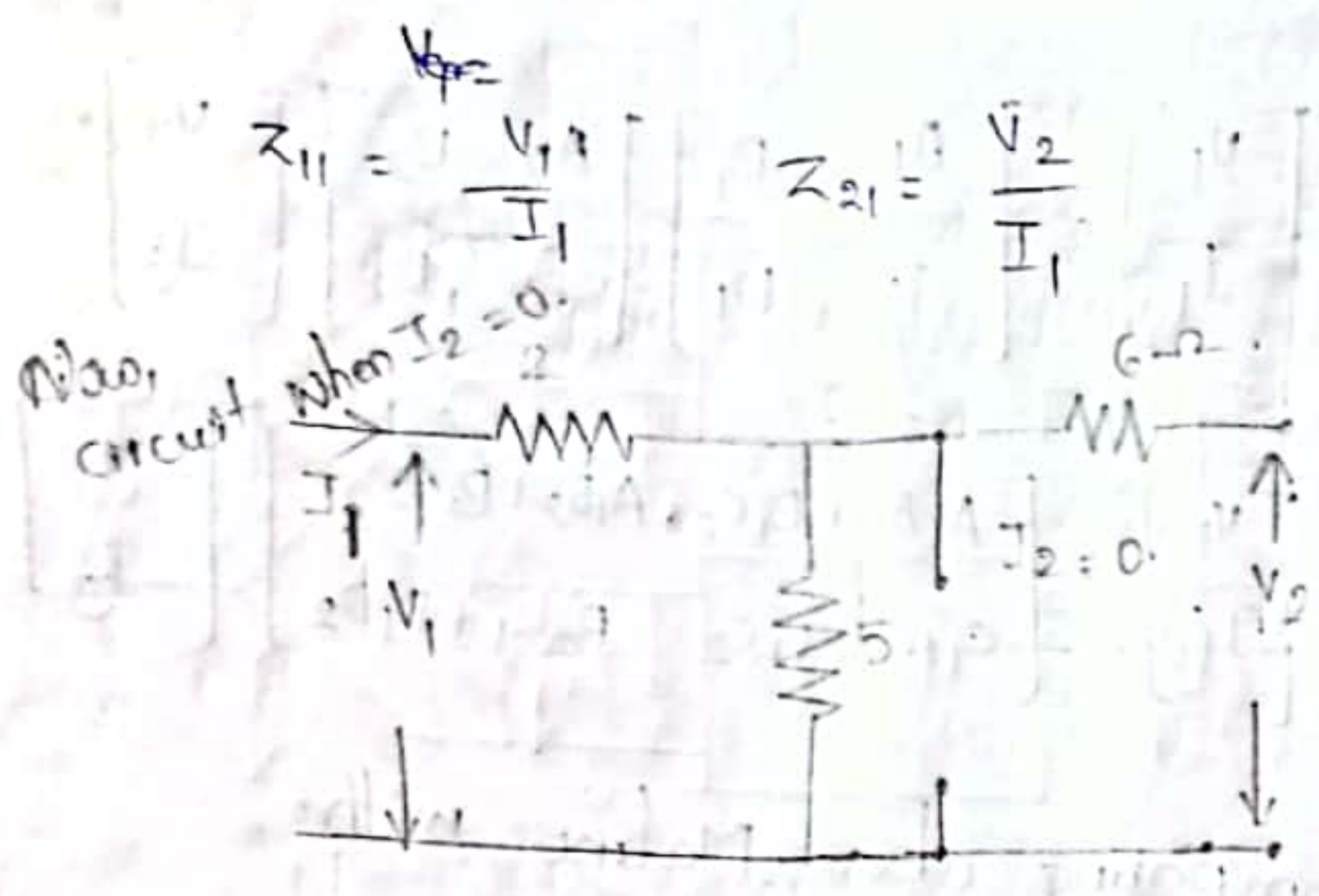
$$V_1 = Z_{11} I_1 \quad V_2 = Z_{21} I_1$$



from figure

$$V_1 = I_1 Z_{eq} = I_1 (7)$$

$$V_1 = 7 I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{7 I_1}{I_1} = (7 \Omega)$$

When

$$Z_{21} = \frac{V_2}{I_1}$$

V_2 is equal the voltage dropped across 5Ω

$$V_2 = 5 I_1$$


$$\frac{V_2}{I_1} = 5 \Omega$$

$$\therefore Z_{21} = 5 \Omega$$

When I_1 is made = 0

i.e. port 1 is open circuited.

circuit is modified as.

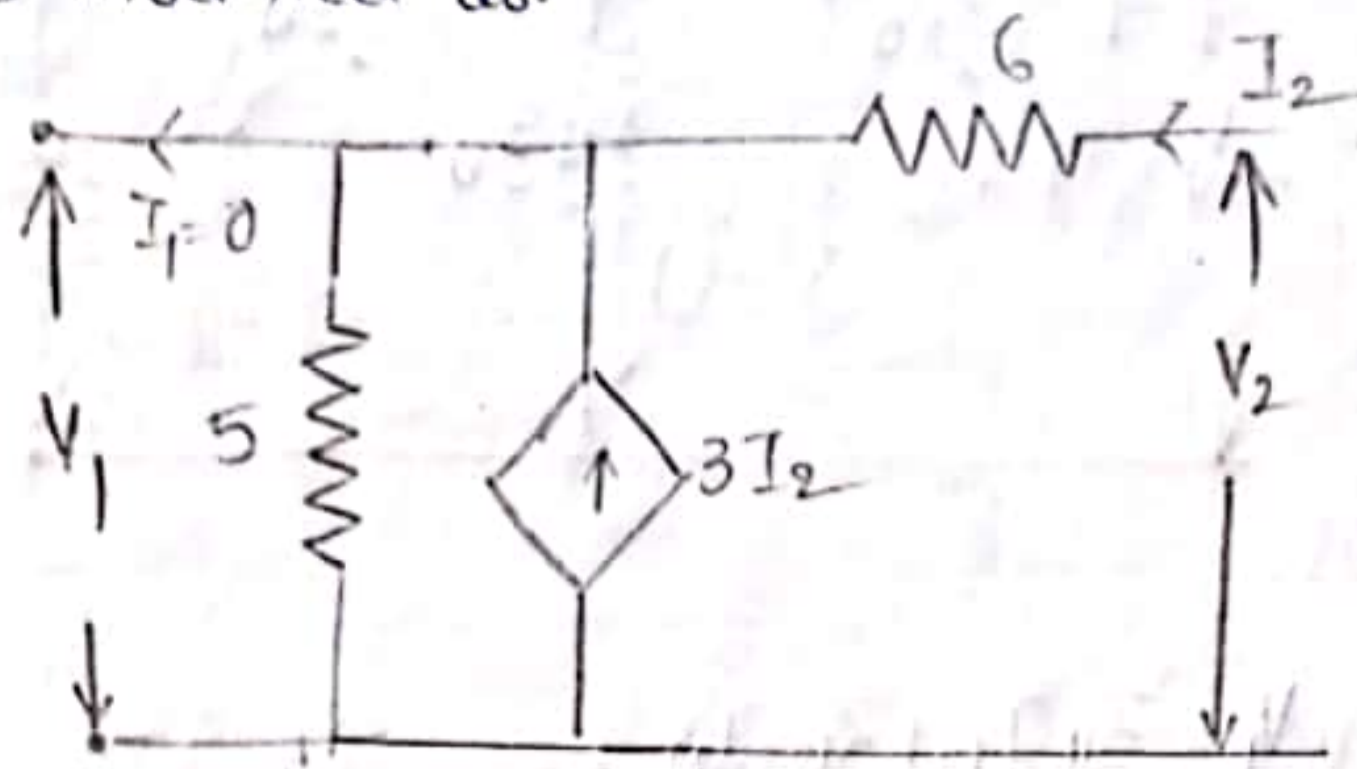

Now, $Z_{12} = \frac{V_1}{I_2}$, $Z_{22} = \frac{V_2}{I_2}$

When the voltage developed across 5- Ω is V_1 voltage.

Now,

$$V_1 = 5(3I_2 + I_2)$$

$$= 5(4I_2)$$

$$V_1 = 20I_2$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{20I_2}{I_2} = 20\ \Omega.$$

V_2 is the voltage drop across 6- Ω & $3I_2$ (or) 5- Ω resistor.


$$\therefore V_2 = 20I_2 + 6I_2.$$

$$V_2 = 26I_2$$

$$\therefore Z_{22} = \frac{V_2}{I_2} = \frac{26I_2}{I_2} = 26\ \Omega.$$

$$\therefore Z_{11} = 7\ \Omega, \quad Z_{12} = 20\ \Omega, \quad Z_{21} = 5\ \Omega, \quad Z_{22} = 26\ \Omega.$$

Find out Z -parameters:

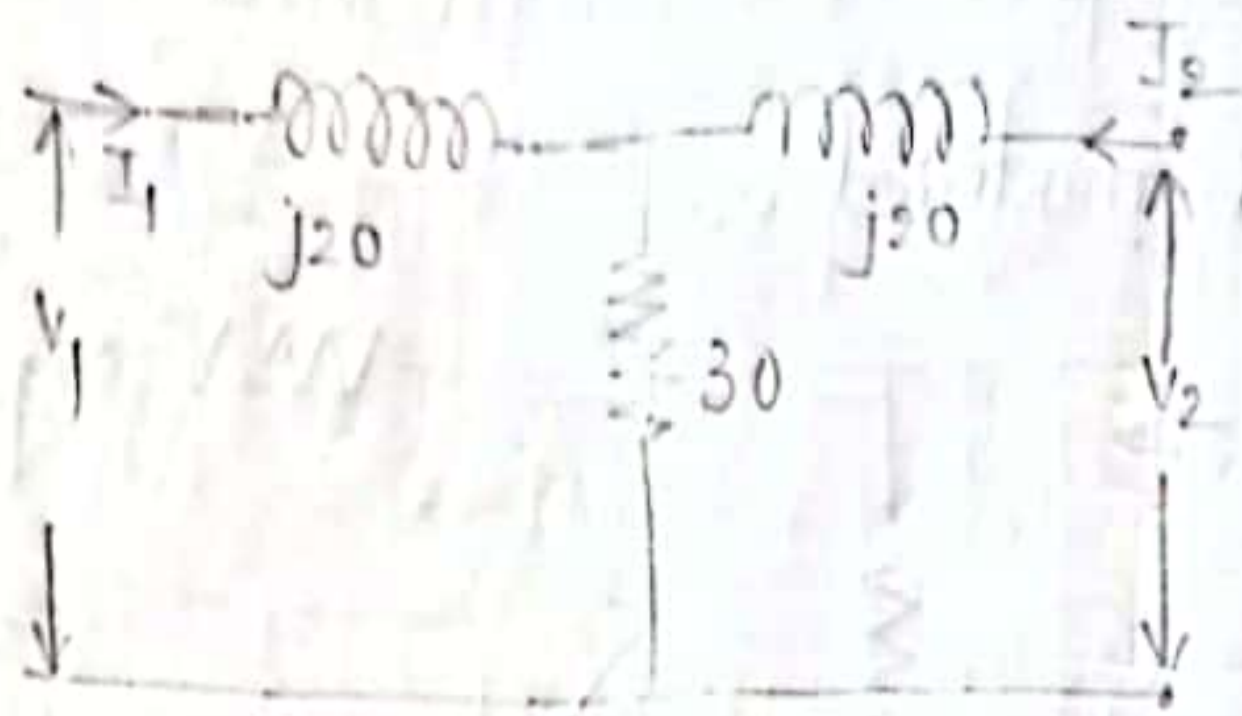


Ans

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

When port 2 is open-circuited

$$I_2 = 0$$

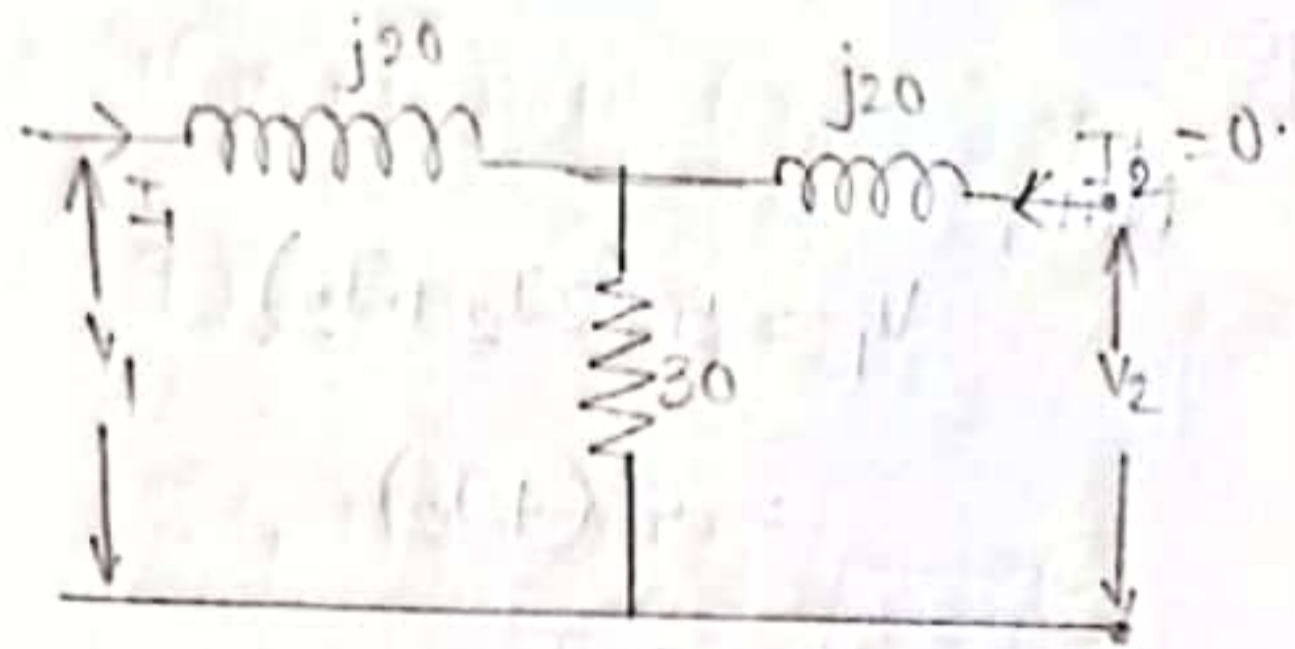

$$V_1 = Z_{11} I_1 \quad \& \quad V_2 = Z_{21} I_1$$

from figure

$$V_1 = j20 I_1 + 30 I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{(30 + j20) I_1}{I_1} = 30 + j20$$

V_2 is voltage drop across 30- Ω .

$$V_{30-\Omega} = 30 I_1$$


$$V_2 = 30 I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{30 I_1}{I_1}$$

$$= 30$$

When port 1 is closed.

$$I_1 = 0$$

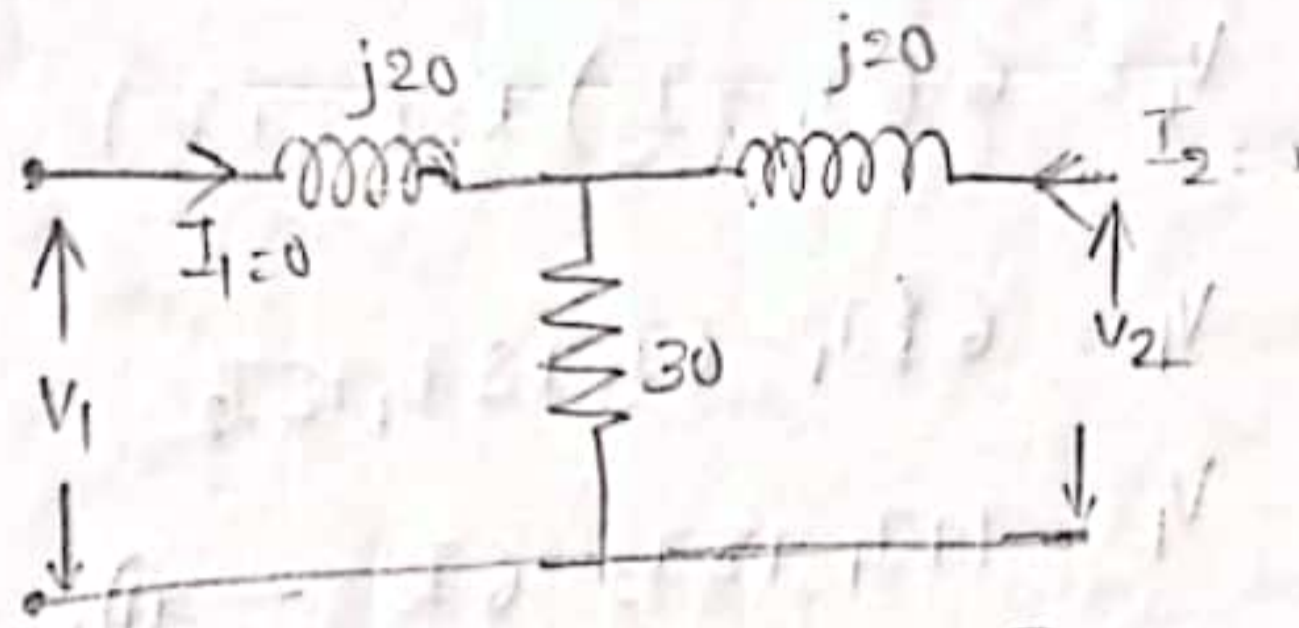

$$V_1 = Z_{12} I_2$$

$$V_2 = Z_{22} I_2$$

from figure.

$$V_2 = j20 I_2 + 30 I_2$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{(j20 + 30) I_2}{I_2}$$

$$Z_{22} = (30 + 20j) \Omega$$

V_1 is voltage drop across 30Ω .

$$V_1 = 30 I_2$$

$$Z_{21} = \frac{V_1}{I_2}$$

$$= \frac{30 I_2}{I_2}$$


$$= 30 \Omega$$

$$= 30 \Omega$$

Find out z-parameters.

Sol: $\frac{W.k.T}{V_1 = 38 z_{11} I_1 + z_{12} I_2 \rightarrow \textcircled{1}}$

$V_2 = z_{21} I_1 + z_{22} I_2$

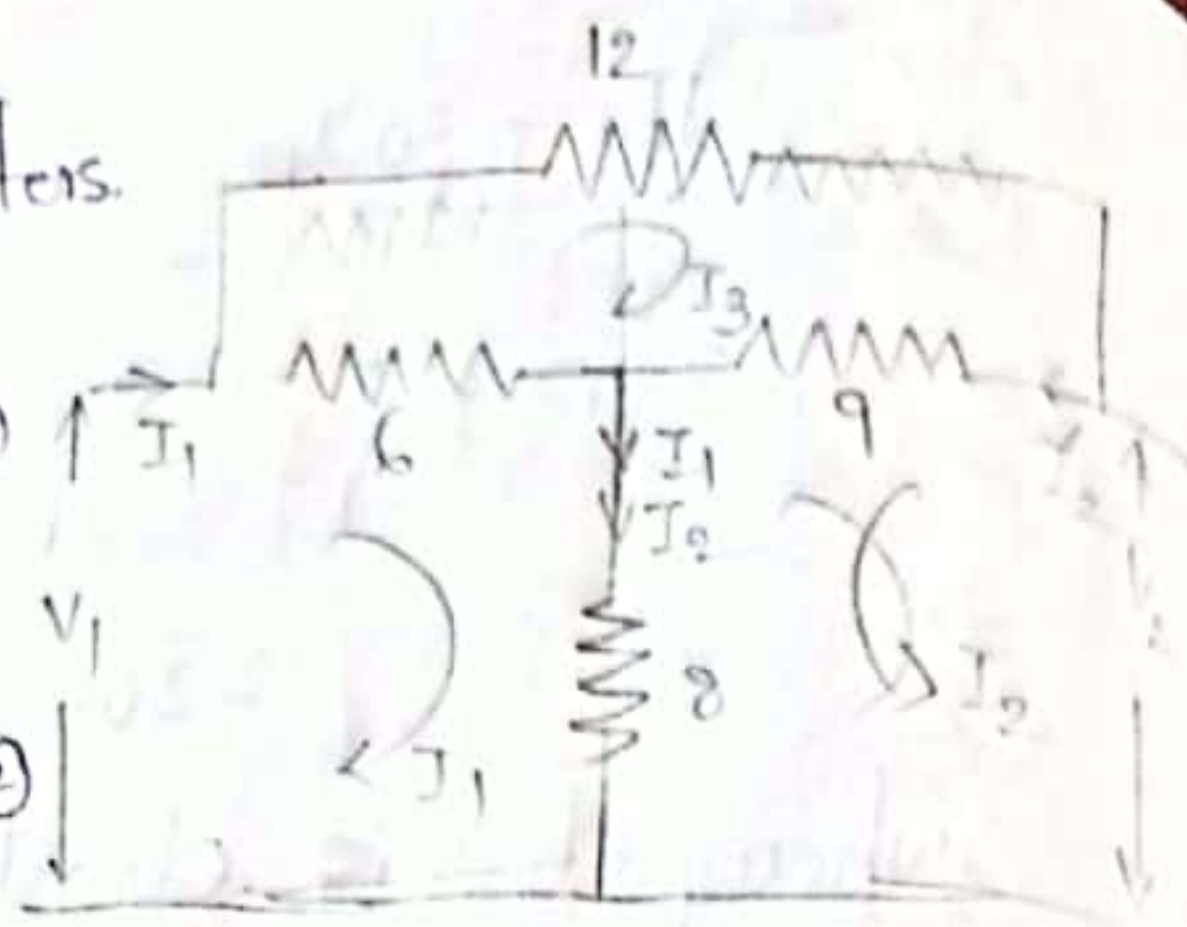

from KVL

$$V_1 = 6(I_1 - I_3) + 8(I_1 + I_2)$$

$$V_1 = 6I_1 - 6I_3 + 8I_1 + 8I_2$$

$$V_1 = 14I_1 + 8I_2 - 6I_3 \rightarrow \textcircled{1}$$

$$V_2 = 9(I_2 + I_3) + 8(I_1 + I_2)$$

$$= 9I_2 + 9I_3 + 8I_1 + 8I_2$$

$$V_2 = 8I_1 + 17I_2 + 9I_3 \rightarrow \textcircled{2}$$

$$-12I_3 - 9(I_3 + I_2) - 6(I_3 - I_1) = 0$$

$$-12I_3 - 9I_3 - 9I_2 - 6I_3 + 6I_1 = 0$$

$$-27I_3 - 9I_2 + 6I_1 = 0$$

$$6I_1 = 9I_2 + 27I_3$$

$$I_1 = \frac{3}{2}I_2 + \frac{9}{2}I_3$$

$$I_3 = -\frac{I_2}{3} + \frac{2I_1}{9}$$

Substitute I_3 in V_1

$$\begin{aligned}V_1 &= 14I_1 + 8I_2 - 6\left(-\frac{I_2}{3} + \frac{2I_1}{9}\right) \\&= 14I_1 + 8I_2 + 2I_2 - \frac{4I_1}{3} \\&= \frac{38I_1}{3} + 10I_2.\end{aligned}$$

Substitute I_3 in V_2

$$\begin{aligned}V_2 &= 8I_1 + 17I_2 + 9I_3 \\&= 8I_1 + 17I_2 + 9\left(\frac{2I_1}{9} - \frac{I_2}{3}\right) \\&= 8I_1 + 17I_2 + 2I_1 - 3I_2 \\&= 10I_1 + 14I_2.\end{aligned}$$

$$\therefore V_1 = \frac{38}{3}I_1 + 10I_2 \quad \text{--- (3)}$$

$$V_2 = 10I_1 + 14I_2. \quad \text{--- (4)}$$

Comparing with (1), (2) and (3) & (4)

we get

$$z_{11} = \frac{38}{3} ; z_{12} = 10$$

$$z_{21} = 10 ; z_{22} = 14.$$