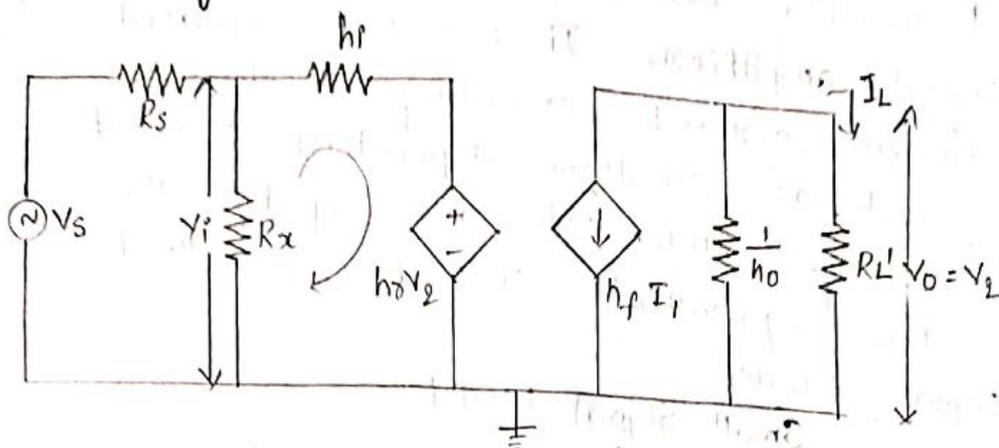


Multistage Amplifiers

Exact analysis of BJT with the h-parameter model.



Current Gain:-

$$A_I = \frac{I_2}{I_1} = \frac{I_L}{I_1}$$

Using current division

$$I_L = -h_f I_1 \times \frac{\frac{1}{h_o}}{\frac{1}{h_o} + R_L'} = \frac{-h_f I_1}{1 + R_L' h_o}$$

$$I_L = \frac{-h_f I_1}{1 + R_L' h_o}$$

$$A_I = \frac{I_L}{I_1} = \frac{-h_f I_1}{1 + R_L' h_o} \times \frac{1}{I_1} = \frac{-h_f}{1 + R_L' h_o}$$

$$A_I = \frac{-h_f}{1 + h_o R_L'}$$

Input Resistance (Ri) :-

$$R_i = \frac{V_1}{I_1}$$

Apply KVL at input node

$$\Rightarrow -V_1 + h_i I_1 + h_r V_2 = 0$$

$$-V_1 + h_i I_1 + h_r I_L R_L' = 0$$

$$-V_1 + h_i I_1 + h_r R_L' A_I I_1 = 0$$

$$-V_1 + I_1 (h_i + h_r R_L' A_I) = 0$$

$$\Rightarrow V_1 = I_1 (h_i + h_r R_L' A_I)$$

$$R_i = \frac{V_1}{I_1} = h_i + h_{re} R_L' A_V$$


Voltage gain (A_V):

$$A_V = \frac{V_2}{V_1} = \frac{V_0}{V_1} \cdot \frac{I_L R_L'}{V_1} = \frac{A_V I_1 R_L'}{V_1}$$

$$A_V = \frac{A_V R_L'}{R_i}$$

Output Resistance (R_o):

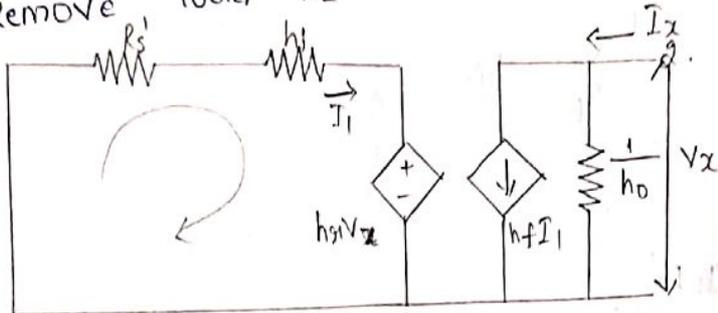- * voltage source is short circuited.
- * Remove load R_L .



Apply KVL at loop 1:

$$R_s' I_1 + h_i I_1 + h_{se} V_x = 0$$

$$I_1 (h_i + R_s') = -h_{se} V_x$$

$$\frac{I_1}{V_x} = \frac{-h_{se}}{h_i + R_s'} \quad \text{--- (1)}$$

Substitute eq (1) in eq (2)

$$\frac{I_x}{V_x} = h_f \left(\frac{-h_{se}}{h_i + R_s'} \right) + \frac{1}{h_o}$$


$$\frac{1}{R_o} = \frac{1}{h_o} - \frac{h_{se} h_f}{h_i + R_s'}$$

Apply KCL at node 2:

$$I_x = h_f I_1 + \frac{V_x}{h_o}$$

$$\frac{I_x}{V_x} = \frac{h_f I_1}{V_x} + \frac{1}{h_o} \quad \text{--- (2)}$$

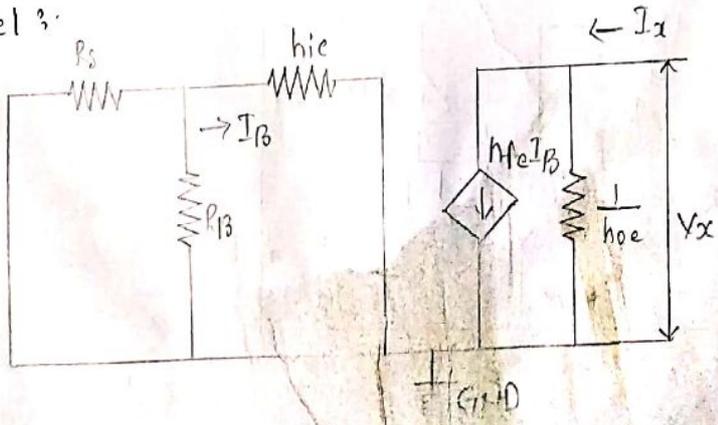Approximate analysis of BJT with the h-parameters model:



Current Gain :-

$$A_I = \frac{I_L}{I_B} = \frac{-h_{fe}}{1 + h_{oe}R_L'}$$

If $(h_{oe}R_L' \leq 0.1)$

$$A_I \approx \frac{-h_{fe}}{1}$$

$$A_I \approx -h_{fe}$$

Input Resistance :-

$$R_i = \frac{V_i}{I_B}$$

$$V_i = I_B h_{ie} \Rightarrow \frac{V_i}{I_B} = h_{ie}$$

$$R_i = h_{ie}$$

Voltage Gain :-

$$A_v = \frac{V_o}{V_i} = \frac{I_L R_L'}{I_B h_{ie}}$$

$$A_v = \frac{-h_{fe} R_L'}{h_{ie}}$$

Output Resistance :-

$$R_o = \frac{V_x}{I_x}$$


Apply KCL at node x:

$$I_x = h_{fe} I_B + \frac{V_x}{h_{oe}}$$

$$I_x = \frac{V_x}{h_{oe}}$$

$$R_o = \frac{V_x}{I_x} = h_{oe}$$

Common Collector Amplifier :-

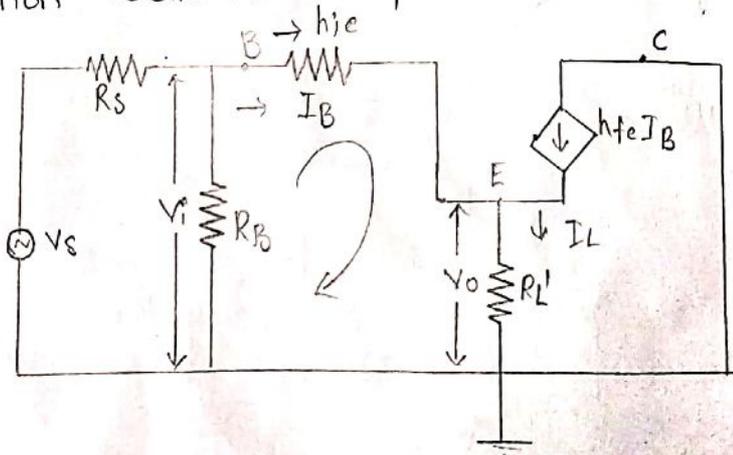

Current Gain :-

$$A_I = \frac{I_L}{I_b}$$

Apply KCL at node E :-

$$I_L = I_b + h_{fe} I_b = I_b (1 + h_{fe})$$

$$\frac{I_L}{I_b} = 1 + h_{fe}$$

$$A_I = 1 + h_{fe}$$

Input Resistance :-

$$R_i = \frac{V_i}{I_b}$$

Using KVL in input loop

$$\Rightarrow -V_i + I_b h_{ie} + I_L R_L' = 0$$

$$\Rightarrow -V_i + I_b h_{ie} + I_b (1 + h_{fe}) R_L' = 0$$

$$\Rightarrow V_i = I_b h_{ie} + I_b R_L' (1 + h_{fe})$$

$$V_i = I_b [h_{ie} + R_L' (1 + h_{fe})]$$

$$\frac{V_i}{I_b} = h_{ie} + R_L' (1 + h_{fe})$$

$$R_i = h_{ie} + (1 + h_{fe}) R_L'$$

Voltage Gain :-

$$A_v = \frac{V_o}{V_i} = \frac{I_L R_L'}{V_i}$$

$$= \frac{I_b (1 + h_{fe}) R_L'}{I_b [h_{ie} + R_L' (1 + h_{fe})]}$$

$$(1 + h_{fe}) R_L' \gg h_{ie}$$

$$= \frac{(1 + h_{fe}) R_L'}{R_L' (1 + h_{fe})}$$

$$A_v \approx 1$$

Output Resistance :-


$$R_o = \frac{V_x}{I_x}$$

Using KCL at E :-

$$I_x + I_b + h_{fe} I_b = 0$$

$$I_x = -I_b (1 + h_{fe}) \quad \text{--- } \textcircled{1}$$

Using KVL in input loop:

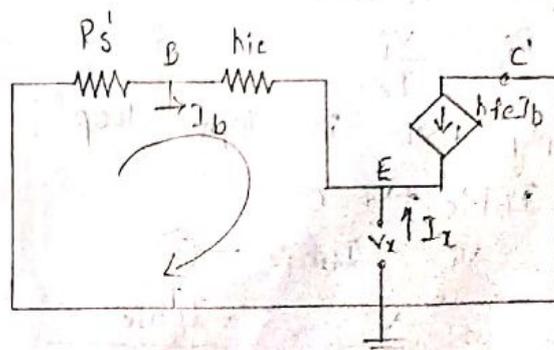


$$\Rightarrow I_b R_s' + I_b h_{ie} + V_x = 0$$

$$V_x = -I_b (R_s' + h_{ie}) \quad \text{--- (2)}$$

$$\frac{\text{(2)}}{\text{(1)}} \Rightarrow \frac{V_x}{I_x} = \frac{-I_b (R_s' + h_{ie})}{-I_b (1 + h_{fe})}$$

$$R_o = \frac{R_s' + h_{ie}}{1 + h_{fe}}$$

Common Base Amplifier :-

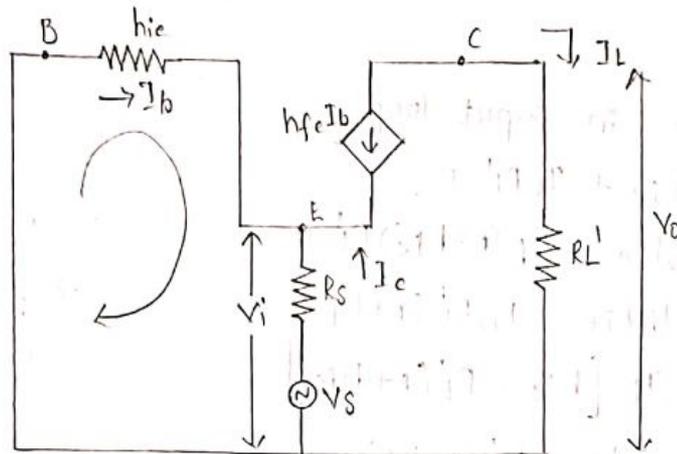

Current Gain :-

$$A_I = \frac{I_L}{I_e}$$

$$I_L = -h_{fe} I_b \quad \text{--- (1)}$$

Apply KCL at node E :-

$$I_b + I_e + h_{fe} I_b = 0$$

$$I_e = -(1 + h_{fe}) I_b \quad \text{--- (2)}$$

$$\frac{\text{(1)}}{\text{(2)}} \Rightarrow \frac{I_L}{I_e} = \frac{-h_{fe} I_b}{-(1 + h_{fe}) I_b} = \frac{h_{fe}}{1 + h_{fe}}$$

$$A_I \cong 1.$$

Input Resistance :-

$$R_i = \frac{V_i}{I_e}$$

Apply KVL in input loop.

$$I_b h_{ie} + V_i = 0$$

$$V_i = -I_b h_{ie} \quad \text{--- (3)}$$

$$\frac{\text{(3)}}{\text{(2)}} \Rightarrow \frac{V_i}{I_e} = \frac{-I_b h_{ie}}{-(1 + h_{fe}) I_b} = \frac{h_{ie}}{1 + h_{fe}}$$

$$R_i = \frac{h_{ie}}{1 + h_{fe}}$$

Voltage Gain:

$$A_v = \frac{V_o}{V_i}$$

$$V_o = I_L R_L' = -h_{fe} I_b R_L'$$

From eq (3) $\Rightarrow V_i = -I_b h_{ie}$

$$\frac{V_o}{V_i} = \frac{-h_{fe} I_b R_L'}{-I_b h_{ie}} = \frac{h_{fe} R_L'}{h_{ie}}$$

$$A_v = \frac{h_{fe} R_L'}{h_{ie}}$$

Output Resistance:

$$R_o = \frac{V_x}{I_x}$$


$$= \frac{V_x}{h_{fe} I_b}$$

$$\therefore I_b = 0$$


$$R_o = \infty$$

If h_{oe} is mentioned then R_o should be calculated

using $R_o = \frac{1+h_{fe}}{h_{oe}}$

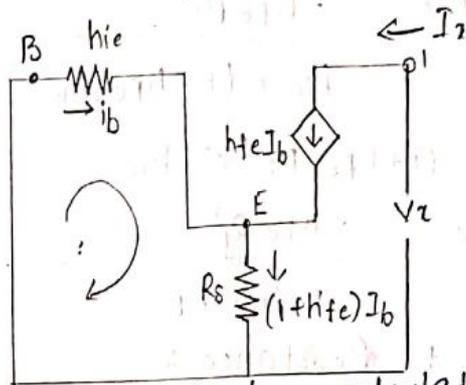

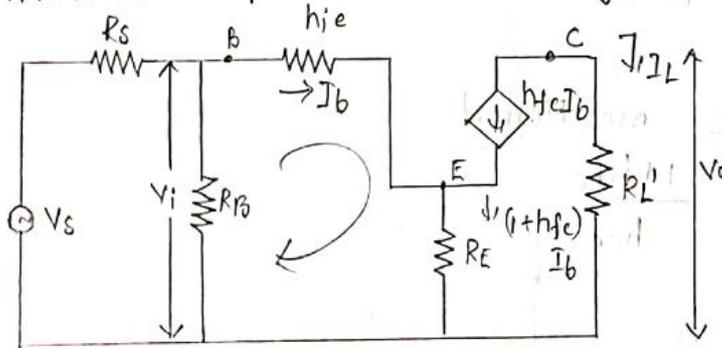Common Emitter Amplifier with unbypassed RE:



Current Gains:

$$A_I = \frac{I_L}{I_b}$$

$$\therefore I_L = -h_{fe} I_b$$

$$A_I = \frac{-h_{fe} I_b}{I_b}$$

$$A_I = -h_{fe}$$

Input Resistance:

$$R_i = \frac{V_i}{I_b}$$

Apply KVL in input loops

$$\Rightarrow -V_i + I_b h_{ie} + (1+h_{fe}) I_b R_E = 0$$

$$V_i = I_b [h_{ie} + (1+h_{fe}) R_E]$$

$$R_i = \frac{V_i}{I_b} = h_{ie} + (1+h_{fe}) R_E$$

Voltage Gain:

$$A_v = \frac{V_o}{V_i} = \frac{-h_{fe} I_b R_L'}{I_b [h_{ie} + (1+h_{fe}) R_E]}$$

$$A_v = \frac{-h_{fe} R_L'}{h_{ie} + (1+h_{fe}) R_E}$$

If $(1+h_{fe}) R_E \gg h_{ie}$

$$A_v \approx \frac{-h_{fe} R_L'}{(1+h_{fe}) R_E} \approx \frac{-R_L'}{R_E}$$

Output Resistance:


$$R_o = \frac{V_x}{I_x}$$




$$= \frac{V_x}{h_{fe} I_b}$$

$$R_o = \infty$$

If h_{oe} is mentioned

$$R_o \approx \frac{1+h_{fe}}{h_{oe}}$$

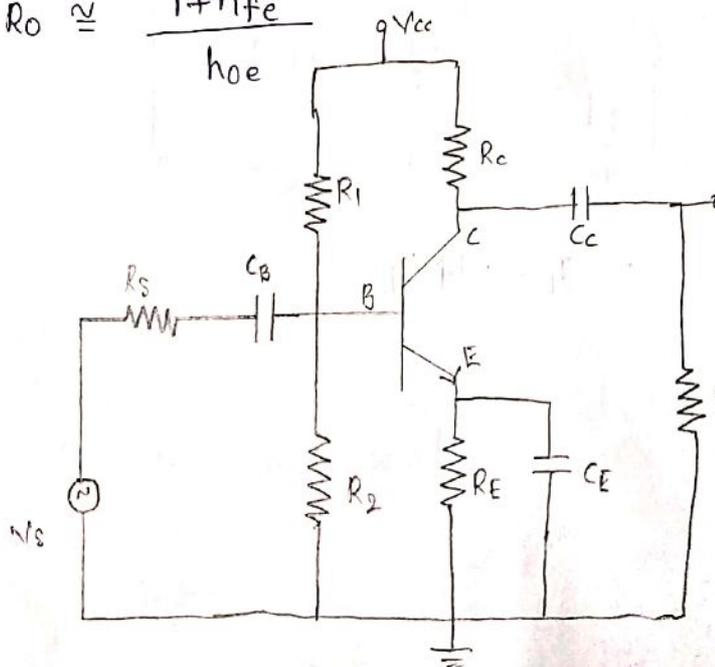


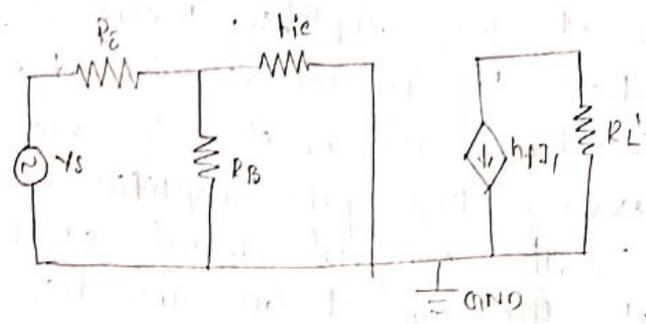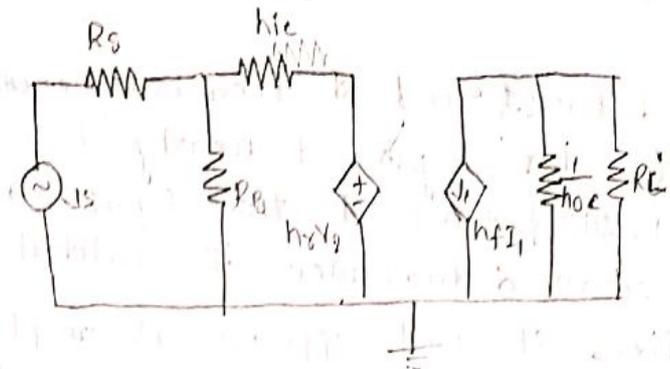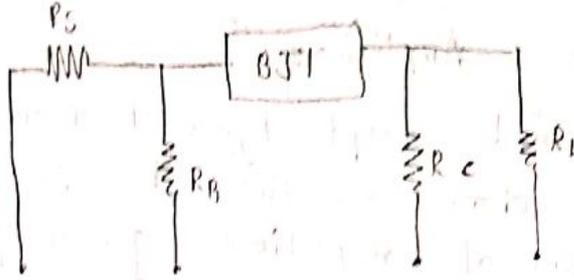

Unit - II Multistage Amplifiers

Introduction:-

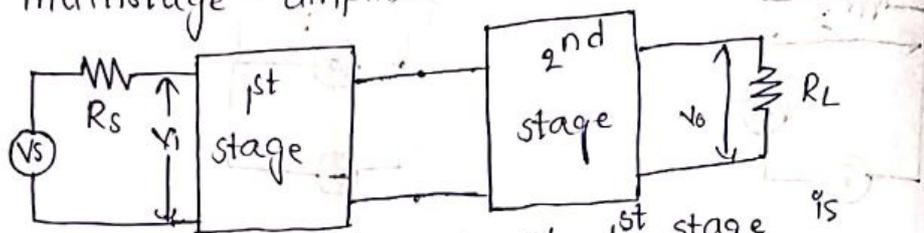Single stage amplifiers may provide smaller voltage and current gains and these are insufficient to drive high resistive loads. These by using more than one stage of amplification to achieve sufficient voltage and current gains. Such an amplifier is called a multistage amplifier.



In multistage amplifier, the o/p of 1st stage is connected as i/p to the 2nd stage as shown in above fig. Such a connection is commonly referred to as cascading.

In amplifiers, cascade is also used to achieve consistent input and output impedances for specific applications.

Depending upon the type of amplifier used in individual stages, multistage amplifiers can be classified into several types.

A multistage amplifier using two or more single stage CE amplifiers is called as cascaded amplifiers.

A multistage amplifier with common emitter as the 1st stage and common base as the second stage is called as cascode amplifier.


Methods of interstage coupling:-

When amplifiers are cascaded, it is necessary to use a coupling network between the output of one amplifier and the input of the following amplifier. This type of coupling is called interstage coupling.

These are 3 coupling schemes commonly used in multistage amplifiers


1. RC coupling
2. Transformer coupling
3. Direct coupling

RC Coupling :-

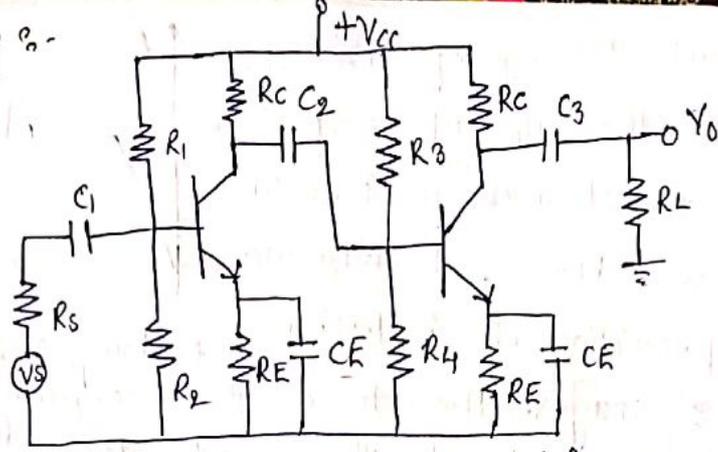

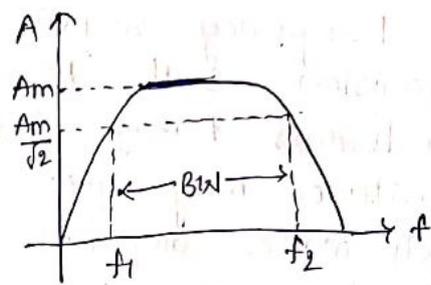a. RC coupled amplifier

In RC coupled amplifiers, the output of 1st stage is coupled to the i/p of the next stage through a coupling capacitor and resistive load.




frequency response

This coupling method does not affect the Q-point of the next stage. Since the coupling capacitor blocks the dc component of the 1st stage from reaching the base of the 2nd stage.


The RC MLW is block broad band in nature. Therefore, it gives wide band frequency response without peak at any frequency.

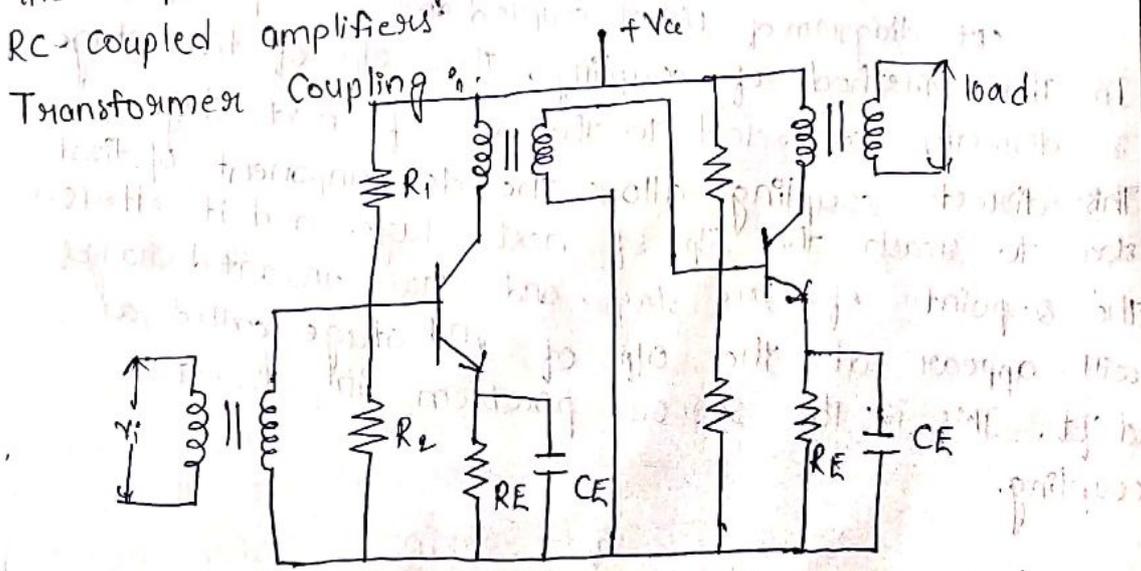However, its frequency response drops at very low frequencies due to coupling capacitors and also at high frequencies due to structural stray capacitance. The amplifiers using this scheme are called RC-coupled amplifiers.



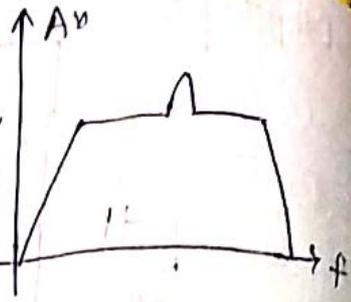a. CKT diagram of transformer coupled amplifiers



In this method, the o/p of first stage is couple to the i/p of next stage through a transformer as shown in fig (a). As we know, transformer



blocks dc, providing dc isolation b/w the 2 stages. Therefore, this coupling does not affect the Q-point of the next stage.


Frequency response of this coupling is poor in comparison with RC coupled amplifier. The transformer leakage inductance and interwinding capacitance may give resonance at certain frequency which makes amplifier to give very high gain at that frequency. By putting shunting capacitors across each winding of the transformer, we can get resonance at any desired frequency. Such amplifiers are called tuned voltage amplifiers. These are used in the radio and TV receivers.

Direct Coupling:

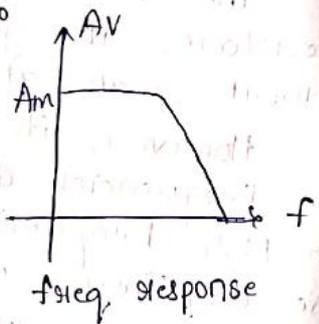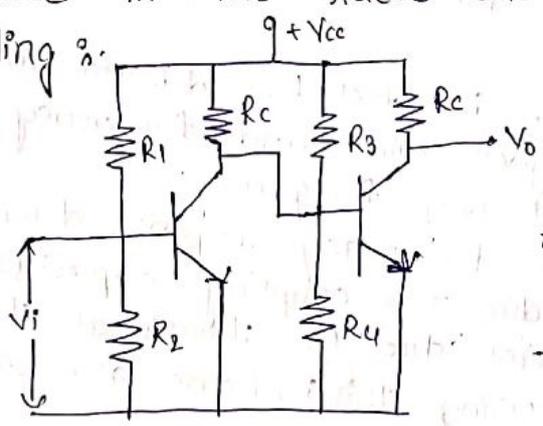


circuit diagram of Direct coupled amp.

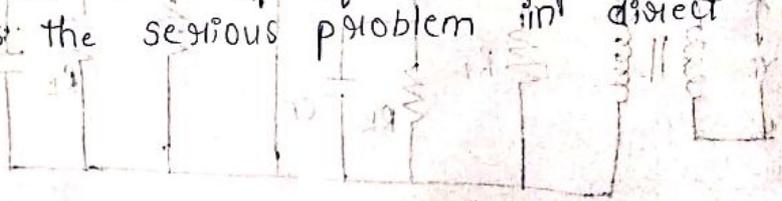In this method of coupling, the o/p of first stage is directly connected to the i/p of next stage. This direct coupling allows the dc component of first stage to reach the i/p of next stage and it affects the Q-point of 2nd stage and thus unwanted changes will appear at the o/p of 2nd stage called as drift. This is the serious problem in direct coupling.



Due to the absence of coupling capacitors, it has good frequency response at low frequencies. But at higher frequencies stray capacitances reduce the gain of the amplifier.

n-stage cascaded amplifier:

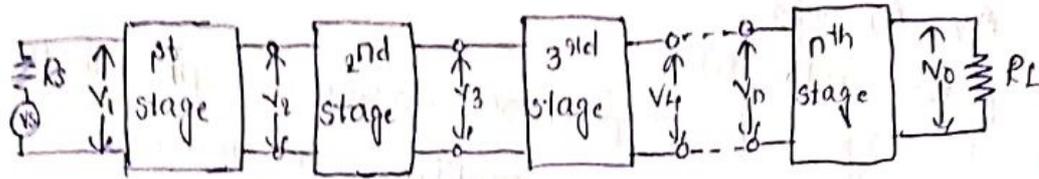

B.D of n-stage cascaded amplifier

The above fig. shows the block diagram of n-stage cascaded amplifiers.

There are n-no. of stages are cascaded, such that the o/p of each stage connected as i/p to the next stage.

Overall voltage gain:

The voltage gain of 1st stage amplifier is given by

$$A_{V1} = \frac{V_2}{V_1}$$

The voltage gain of 2nd stage amplifier is given by

$$A_{V2} = \frac{V_3}{V_2}$$

Similarly the voltage gain of nth stage amplifier is given by

$$A_{Vn} = \frac{V_n}{V_n}$$

The overall voltage gain of n-stage cascaded amplifier is given by

$$A_V = A_{V1} \cdot A_{V2} \cdot A_{V3} \cdot \dots \cdot A_{Vn} \quad \text{--- (1)}$$

$$A_V = \frac{V_2}{V_1} \cdot \frac{V_3}{V_2} \cdot \frac{V_4}{V_3} \cdot \dots \cdot \frac{V_n}{V_n} \quad \text{--- (2)}$$

From eq (1), we can say that the overall voltage gain is the product of voltage gains of individual stages.

Overall Current Gain:

Similar to the overall voltage gain, the overall current gain is given by

$$A_I = A_{I1} \cdot A_{I2} \cdot A_{I3} \cdot \dots \cdot A_{In} \quad \text{--- (3)}$$

It is the product of current gains of individual stages called overall current gain.

Overall Power gain:

Overall power gain is the product of overall voltage gain and overall current gain and it is given by

$$A_p = A_v \cdot A_i \quad \text{--- (3)}$$

Overall phase shift (θ):

The first stage of amplifier introduces phase shift of θ_1 , second stage of amplifier introduces phase shift of θ_2 . Similarly, the n th stage of amplifier introduces phase shift of θ_n .

The overall phase shift is the sum of phase shifts of individual stages.

$$\theta = \theta_1 + \theta_2 + \dots + \theta_n \quad \text{--- (4)}$$

From eq (4), we can say that, the total phase shift is the sum of phase shifts of individual stages.

1) A 3-stage amplifier has a 1st stage voltage gain of 30, 2nd stage of voltage gain of 200 and 3rd stage voltage gain of 400. Find the total voltage gain in decibals.

Given, $A_{v1} = 30$,

$$A_{v2} = 200$$

$$A_{v3} = 400$$

$$A_v = A_{v1} \cdot A_{v2} \cdot A_{v3} = 30 \times 200 \times 400$$

$$A_v = 2400000$$

$$\begin{aligned} \text{Total voltage gain in decibals} &= 20 \log_{10} A_v \\ &= 20 \log_{10} (2400000) \\ &= 127.6 \text{ dB} \end{aligned}$$

2) a) A multistage amplifier uses 5 stages, each of which has a power gain of 30. what is the total power gain of amplifier in decibals?

b) If the -ve fb of 20 dB is introduced, find the resultant power gain.

a) For a 5 stage of MSA,
 $A_p = 5 \times 30 = 150$

Total power gain in decibals = $20 \log A_p$
 $= 20 \log 150$
 $= 43.52 \text{ dB}$

b) total power gain $\rightarrow 20 \text{ dB}$

$$20 \log A_p = 20$$

$$\log A_p = 1$$


If 20 dB of -ve fb,

$$A_p(\text{dB}) = (43.52 - 20) \text{ dB} = 23.52 \text{ dB}$$

Configurations in multistage amplifiers:
 Based on using of configuration for individual stage, there are several types of multi stage amplifiers.

1. Two stage CE-CE cascaded amplifier
 2. CE-CB cascaded amplifier
 3. CC-CC darlington amplifier
 4. Boot strapped amplifier
- Two stage CE-CE cascaded amplifier is high i/p resistance & transistor amp. ckt.

Two stage CE-CE cascaded amplifier:

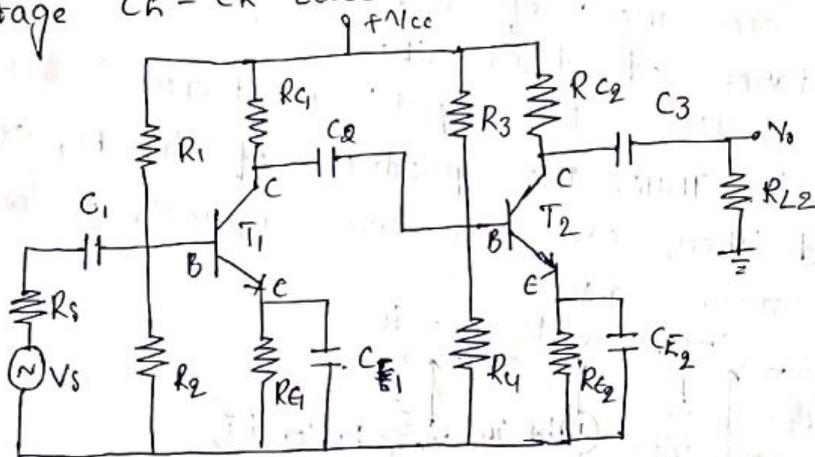


The above fig. shows the circuit diagram of 2-stage CE-CE cascaded amplifier. The transistor T_1 and its associated component constitutes one CE amplifier and transistor T_2 and its associated component constitutes another CE

amplifier. The main objective of cascaded amplifier is to raise the voltage gain of an amplifier.

Analysis of second stage :-

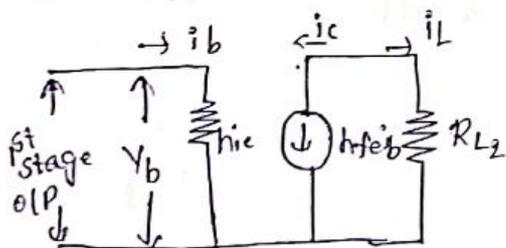To measure the characteristics of an amplifier circuit diagram is replaced by its equivalent circuit. Here we assume that $h_{oe} R_{L2} < 0.1$, then we can use approximate analysis for 2nd stage.



i) Current gain (A_{I2}) :-

$$A_{I2} = \frac{i_L}{i_b} = \frac{-i_c}{i_b} = \frac{-h_{fe} i_b}{i_b} = -h_{fe}$$

ii) input resistance (R_{I2}) :-


$$R_{I2} = \frac{V_b}{i_b} = \frac{h_{ie} i_b}{i_b} = h_{ie}$$

iii) Voltage gain (A_{V2}) :-

$$A_{V2} = \frac{A_{I2} R_{L2}}{R_{I2}} = \frac{-h_{fe} R_{L2}}{h_{ie}}$$

Analysis of first stage :-

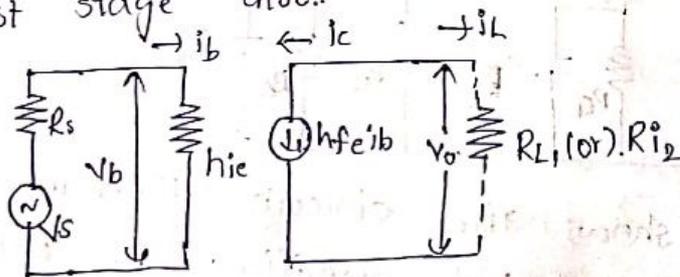The input resistance of second stage becomes the load resistance of first stage. For CE amplifier, the input resistance is in order of ohms (Ω). Thus, the product of $h_{oe} R_{L1} < 0.1$ is satisfied. Then, we can use approximate analysis for first stage also.



i) Current gain (A_{I1}) :-

$$A_{I1} = \frac{i_L}{i_b} = \frac{-i_c}{i_b} = \frac{-h_{fe} i_b}{i_b} = -h_{fe}$$

ii) input resistance (R_{I1}) :

$$R_{I1} = \frac{V_b}{i_b} = \frac{h_{ie} i_b}{i_b} = h_{ie}$$


iii) Voltage gain (A_{V1}) :

$$A_{V1} = \frac{A_{I1} R_L}{R_{I1}} = \frac{-h_{fe} R_L}{h_{ie}}$$

iv) Output resistances (R_{O1} & R_{O2}) :

$$R_{O1} = R_{O2} = \infty$$

CE-CB Cascoded amplifier :

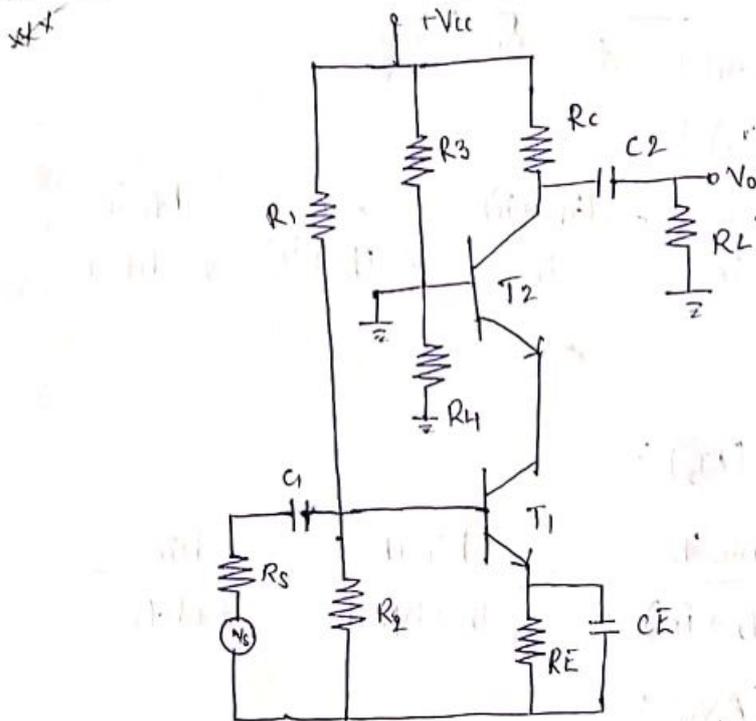

a) ckt diagram of cascoded amp.


Fig (a) shows the circuit diagram of CE-CB cascoded amplifier. It consists of CE amplifier followed by CB amplifier and they are direct coupled with each other.

The CB amplifier has two greater advantages over CE amplifier and they are largest bandwidth and high voltage gain, but it suffers with very smaller input impedance. This problem of CB amplifier is solved by connecting CE amplifier at the input side of CB amplifier. Therefore, CE-CB cascoded amplifier gives the added advantages of both CE and CB amplifiers i.e., highest input impedance of CE amplifier, and larger bandwidth and higher

Voltage gain of CB amplifier:

Analysis of Second Stage:

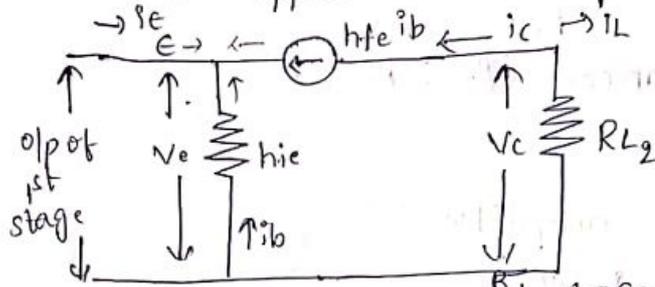For the analysis of second stage, we assume that the product of $h_{oe} R_L < 0.1$ condition is satisfied. Thus, we can use approximate analysis.



b) app. model of 2nd stage

i) Current gain (A_{I_2}):

$$A_{I_2} = \frac{i_L}{i_e} = \frac{-i_c}{i_e} = \frac{-(i_b + i_e)}{i_e} = \frac{-i_c}{i_b + i_c} = \frac{h_{fe} i_b}{i_b + h_{fe} i_b}$$

$$A_{I_2} = \frac{h_{fe}}{1 + h_{fe}}$$

ii) Input resistance (R_{I_2}):

$$R_{I_2} = \frac{V_e}{I_e} = \frac{h_{ie} i_b}{i_b + i_c} = \frac{h_{ie} i_b}{i_b + h_{fe} i_b} = \frac{h_{ie}}{1 + h_{fe}}$$

iii) Voltage gain (A_{V_2}):


$$A_{V_2} = \frac{A_{I_2} R_{L_2}}{R_{I_2}} = \frac{\left(\frac{h_{fe}}{1 + h_{fe}}\right) R_{L_2}}{\frac{h_{ie}}{1 + h_{fe}}} = \frac{h_{fe} R_{L_2}}{h_{ie}}$$

Analysis of first stage:

For the analysis of 1st stage, we assume that, the product of $h_{oe} R_L < 0.1$.

By the input impedance of CB amplifier, which is very small value become the load impedance of 1st stage, thus the product of $h_{oe} R_L < 0.1$ is satisfied.

Hence we can use approximate analysis.

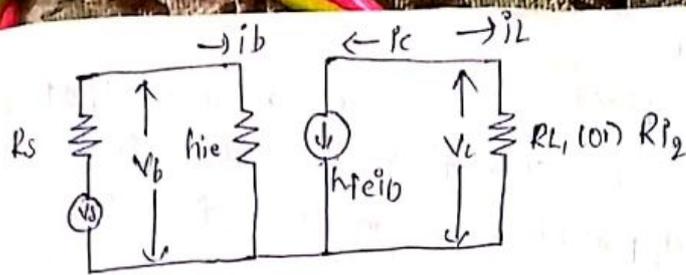

Current gain :-

$$A_{I1} = \frac{i_L}{i_b} = \frac{-h_{fe} i_b}{i_b} = -h_{fe}$$

$$R_{I1} = \frac{V_b}{i_b} = \frac{h_{ie} i_b}{i_b} = h_{ie}$$

$$A_v = \frac{V_c}{V_b} = \frac{-h_{fe} R_{L1}}{h_{ie}}$$

For both 1 & 2 stages.


$$R_{O1} = R_{O2} = \infty$$

Overall voltage gain $A_v = A_{v1} \cdot A_{v2}$

Overall current gain $A_I = A_{I1} \cdot A_{I2}$

Overall power gain $A_p = A_v \cdot A_I$

CC-CC Darlington Amplifier :-

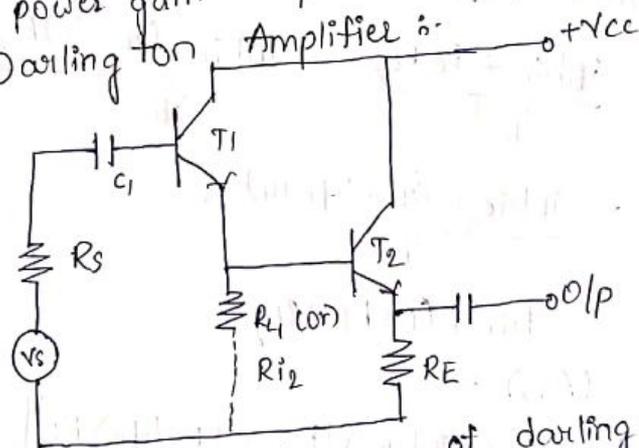


Fig(a) shows the ckt diagram of darlington amplifiers. The o/p of 1st stage is directly connected to the i/p of next stage.

For some application it is necessary to have an amplifier with high input impedance. Emitter followers may be used to have input resistance are about 500k Ω .

For achieving still higher i/p impedances, the Darlington connection is used. The Darlington connection has two transistors forming a composite pair. The darlington ckt consists of two cascaded CC- amplifiers as shown in Fig.

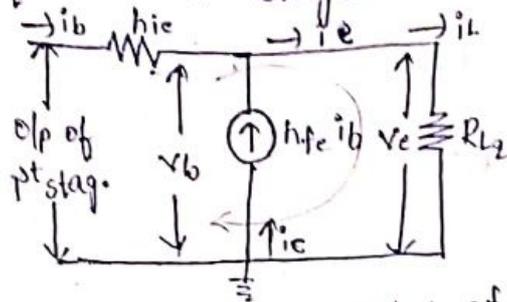Analysis of ~~first~~ ^{second} stage:
 For the analysis of ~~first~~ ^{second} stage, we assume that product of $h_{oe}R_L < 0.1$ condition is satisfied.
 Thus, we can use approximate analysis for the analysis of second stage.



a) approximate model of second stage.

i) Current gain (AI_2):

$$AI_2 = \frac{i_L}{i_b} = \frac{i_e}{i_b} = \frac{i_b + i_c}{i_b} = \frac{i_b + h_{fe}i_b}{i_b} = 1 + h_{fe}$$

ii) input resistance (RI_2):

$$RI_2 = \frac{V_b}{i_b} = \frac{i_b h_{ie} + i_e R_{L2}}{i_b} = \frac{i_b h_{ie} + (i_b + i_c) R_{L2}}{i_b}$$

$$= \frac{i_b h_{ie} + (i_b + h_{fe} i_b) R_{L2}}{i_b}$$

$$RI_2 = h_{ie} + (1 + h_{fe}) R_{L2}$$


iii) Voltage gain (AV_2):

$$AV_2 = \frac{AI_2 R_{L2}}{RI_2} = \frac{(1 + h_{fe}) [h_{ie} + (1 + h_{fe}) R_{L2}]}{h_{ie} + (1 + h_{fe}) R_{L2}}$$

$$= \frac{(1 + h_{fe}) R_{L2}}{h_{ie} + (1 + h_{fe}) R_{L2}}$$

Analysis of first stage:

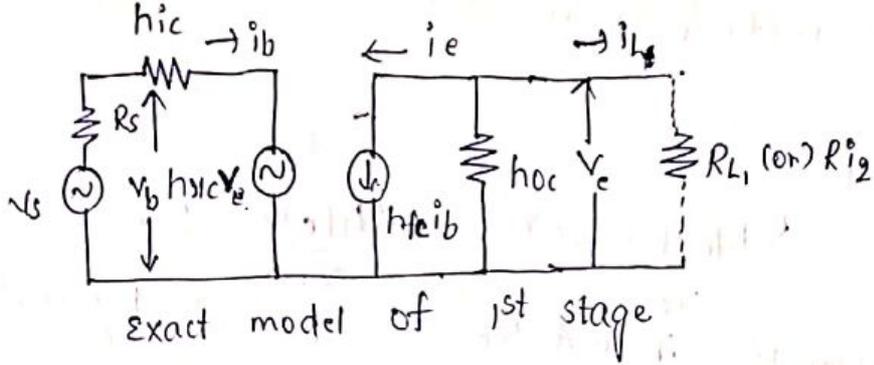For the analysis of first stage, $h_{oe}R_{L1} < 0.1$ condition is not satisfied, since the i/p resistance of second stage which is very large value becomes the load resistance of first stage. Hence we can use exact analysis for the analysis of first stage.



i) Current gain (A_{I_1}):

$$A_{I_1} = \frac{i_L}{i_b} = \frac{-i_e}{i_b} = -\frac{h_{fc}i_b}{i_b}$$

where $i_e = h_{fe}i_b + h_{oc}V_e$
 $= h_{fc}i_b + h_{oc}(i_L R_L)$

$$i_e = h_{fc}i_b + h_{oc}(-i_e R_L)$$

$$i_e + h_{oc}i_e R_L = h_{fc}i_b$$

$$i_e(1 + h_{oc}R_L) = h_{fc}i_b$$

$$\frac{i_e}{i_b} = \frac{h_{fc}}{1 + h_{oc}R_L}$$

$$A_{I_1} = \frac{-i_e}{i_b} = \frac{-h_{fc}}{1 + h_{oc}R_L} = \frac{1 + h_{fe}}{1 + h_{oc}R_L}$$

ii) Input resistance (R_{I_1}):

$$R_{I_1} = \frac{V_b}{i_b} = \frac{i_b h_{ie} + h_{ie} V_e}{i_b} = \frac{i_b h_{ie} + h_{ie} (i_L R_L)}{i_b}$$

$$= \frac{i_b h_{ie} + h_{ie} (-i_e R_L)}{i_b}$$

$$= h_{ie} - h_{ie} R_L \frac{i_e}{i_b}$$

$$R_{I_1} = h_{ie} + h_{ie} R_L A_{I_1} = h_{ie} + R_L A_{I_1}$$

iii) Voltage gain (A_{V_1}):

$$A_{V_1} = \frac{A_{I_1} R_L}{R_{I_1}} = \frac{V_e}{V_b} = \frac{i_L R_L}{V_b} = \frac{-i_e R_L}{V_b}$$

$$A_{V_1} = \frac{-i_e}{i_b} \cdot \frac{i_b}{V_b} \cdot R_L$$

$$A_{V_1} = \frac{A_{I_1} R_L}{R_{I_1}}$$

CC-CE

* $h_{ic} = h_{ie}$
 $h_{fc} = -(1 + h_{fe})$
 $h_{yc} = 1$
 $h_{oc} = h_{oe}$

iv) Output resistance (R_{o1}):

$$R_{o1} = \frac{1}{y_{o1}}$$

$$y_{o1} = \frac{i_e}{V_e} = \frac{h_{fc} i_b + h_{oc} V_e}{V_e} = \frac{h_{fc} i_b}{V_e} + h_{oc}$$

The relation b/w i_b and V_e is obtained by applying KVL to the i/p loop with $V_s = 0$.

$$(h_{ic} + R_s) i_b + h_{sc} V_e = 0$$

$$(h_{ic} + R_s) i_b = -h_{sc} V_e$$

$$\frac{i_b}{V_e} = \frac{-h_{sc}}{h_{ic} + R_s}$$

$$y_{o1} = h_{fc} \left(\frac{-h_{sc}}{h_{ic} + R_s} \right) + h_{oc}$$

$$y_{o1} = h_{oc} - \frac{h_{fc} h_{sc}}{h_{ic} + R_s}$$

$$R_{o1} = \frac{1}{y_{o1}} = \frac{1}{h_{oc} - \frac{h_{fc} h_{sc}}{h_{ic} + R_s}}$$

$$R_{o1} = \frac{1}{h_{oc} + \frac{(h_{fc} + 1)}{h_{ic} + R_s}}$$


As $\frac{h_{fc} + 1}{h_{ic} + R_s} \ll h_{oc}$, h_{oc} is neglected, then

$$y_{o1} = \frac{1 + h_{fc}}{h_{ic} + R_s}$$

$$R_{o1} = \frac{h_{ic} + R_s}{1 + h_{fc}}$$

Similarly, $R_{o2} = \frac{R_s + h_{ic}}{1 + h_{fc}}$

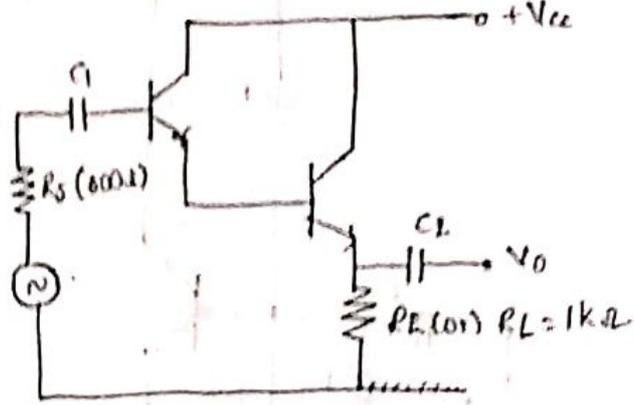For the ckt shown, calculate i/p resistance, current gain, voltage gain and o/p resistance. For both the stages given $h_{ie} = 1.1k\Omega$, $h_{fe} = 50$, $h_{oe} = 25 \times 10^{-6}$, $h_{oe} = 25 \mu A/V$



For second stage:

$$A_{I2} = 1 + h_{fe} = 1 + 50 = 51$$

$$R_{I2} = h_{ie} + (1 + h_{fe})R_L = 1.1 \times 10^3 + (51) \times 10^3 = 52.1k\Omega$$

$$A_{V2} = \frac{51 \times 10^3}{52.1 \times 10^3} = 0.978$$

For first stage:

$$A_{I1} = \frac{1 + h_{fe}}{1 + h_{oe}R_L} = \frac{1 + 50}{1 + (25 \times 10^{-6}) \times 10^3 \times 52.1} = \frac{51}{1 + (25 \times 10^{-3})} \quad R_{L1} = R_{I2}$$

$$A_{I1} = 49.7 \quad 22.14$$

$$R_{I1} = h_{ie} + R_{L1} A_{I1} = 1.1 \times 10^3 + 10^3 (49.7) \times 52.1$$

$$R_{I1} = 50.8k\Omega \quad 1.15M\Omega$$

$$A_{V1} = \frac{22.14}{49.7 \times 10^3} = 0.978$$


$$R_{O1} = A_{V1} \cdot \frac{A_{I1} R_{L1}}{R_{I1}} = \frac{22.14 \times 52.1 \times 10^3}{1.15 \times 10^6} = 1.0030$$

$$R_{O1} = \frac{h_{ie} + R_s}{1 + h_{fe}} = \frac{1.1 \times 10^3 + 600}{1 + 50} = 33.33\Omega$$

$$(R_{O1} = R_{S2})$$

$$R_{O2} = \frac{R_{S2} + h_{ie}}{1 + h_{fe}} = \frac{1.1 \times 10^3 + 33.33}{51} = 22.22\Omega$$

Boot - Strapped Emitter Follower :-

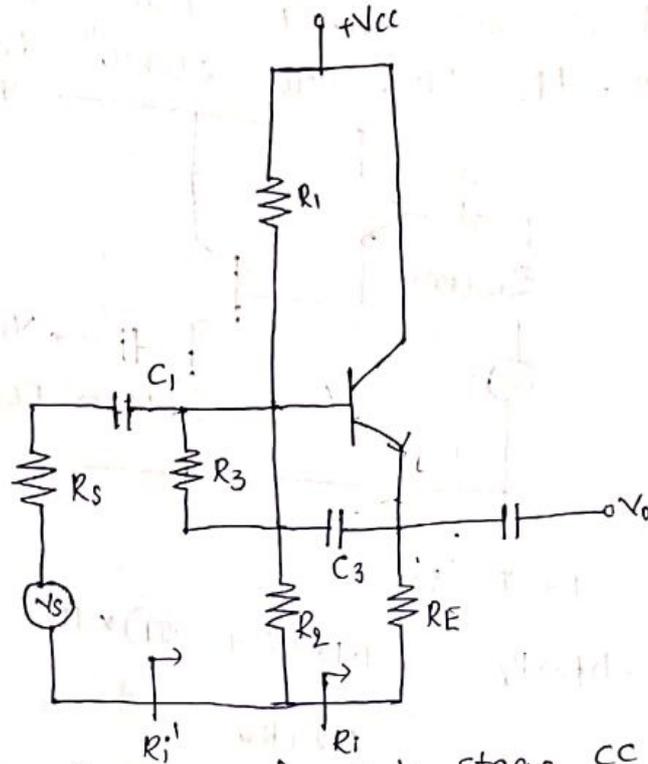

→ The main feature of single stage CC amplifier and two stage CC amplifier is their high i/p resistance. But this high i/p resistance is decreased by the presence of biasing resistors. To overcome this decrease in i/p resistance due to biasing resistors, the single stage emitter-follower circuit is modified by the addition of a resistor R_3 b/w the emitter terminal and the base junction. The bottom of R_3 is connected to the emitter terminal through a capacitor C_3 and the top of R_3 is connected to the base-junction.

→ This modified ckt is called boot strapped emitter follower.

→ Even for low frequency of the i/p signal the capacitor C_3 acts as a short ckt. Thus the resistors R_1 & R_2 pulled to the o/p side. Then the effect of R_1 & R_2 not considered on i/p side.

Using Miller's Theorem, the effective resistance due to R_3 on i/p side is given by

$$R_{eff} = \frac{R_3}{1 - A_v}$$

For an emitter follower (cc amp) voltage gain $A_v \approx 1$, then R_{eff} becomes extremely large.

For example with $A_v = 0.995$, $R_3 = 100k\Omega$ then

$$R_{eff} = \frac{100k\Omega}{1 - 0.995}$$

$$R_{eff} = 20M\Omega$$

If $R_1 = 500k\Omega$, then $R_i' = R_1 \parallel R_{eff}$

$$= 500k\Omega \parallel 20M\Omega$$

$$R_i' = 487.8k\Omega$$

Hence the high i/p resistance is maintained by the addition of resistor R_3 .

Analysis:

$$i) R_i' = \frac{V_b}{i_b}$$

$$= \frac{h_{ie} i_b + i_e R_L}{i_b}$$

$$= \frac{h_{ie} i_b + i_c R_L + i_b R_L}{i_b}$$

$$= \frac{h_{ie} i_b + (i_b + h_{fe} i_b) R_L}{i_b}$$


$$R_i' = h_{ie} + R_L + h_{fe} R_L$$

$$R_i' = R_1 \parallel R_{eff}, \text{ where } R_{eff} = \frac{R_3}{1 - A_v}$$

$$A_I = 1 + h_{fe}$$

$$A_v = \frac{A_I R_L}{R_L}$$

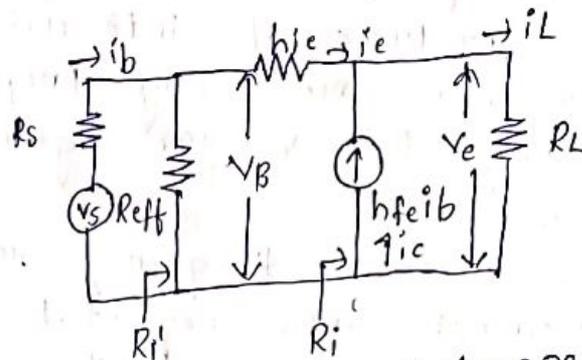
$$R_o = \frac{R_s + h_{ie}}{1 + h_{fe}}$$



app. model of bootstrapped emitter follower

Frequency Response of an amplifier:
It is the plot of voltage gain of an amplifier against the frequency of the i/p signal. In general the entire frequency range can be divided into 3 parts.

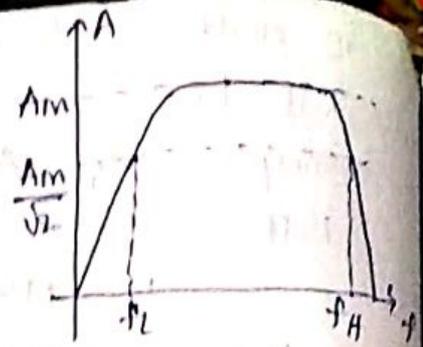- i) Low freq. region
- ii) Mid " "
- iii) High " "



Mid Frequency Region:

In mid frequency range the voltage gain is practically constant i.e., it is not effected by the capacitances of the amplifier ckt.

→ The reactance of the coupling capacitors is very small so that they are not effecting the voltage gain in mid frequency range.


The reactance of internal capacitances of the transistors are very large and they are not effecting the voltage gain in mid frequency range.

Thus in mid frequency range all the capacitive reactances are neglected and the gain is maximum and constant

Low frequency Region:

In low frequency region, the amplifier ckt behaves like the simple high pass filter and it is shown in fig (b).

From the ckt diagram shown in fig (b).

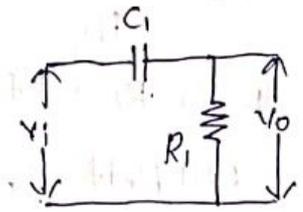

$$V_o = \frac{V_i \times R_1}{R_1 + \frac{1}{j\omega C_1}}$$

$$A_L = \frac{V_o}{V_i} = \frac{R_1}{R_1 + \frac{1}{j\omega C_1}}$$

Both NR & D.R is divided with R1.

$$A_L = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{\omega R_1 C_1}}$$

$$= \frac{1}{1 - j \left[\frac{1}{2\pi f R_1 C_1} \right]}$$

let $2\pi R_1 C_1 = \frac{1}{f_L}$

$$A_L = \frac{1}{1 - j\left(\frac{f}{f_L}\right)}$$

$$|A_L| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}}$$

at $f = f_L$


$$|A_L| = \frac{1}{\sqrt{2}}$$

Therefore the frequency at which the gain is $\frac{1}{\sqrt{2}}$ times the its midband value is called the lowest cut off frequency. This drop corresponds to a dB reduction of 3 dB and hence it is also called as lowest 3 dB frequency.

High frequency Region:

In high frequency region the amplifier behaves like low pass filter and it is shown in fig (c).

From the ckt diagram shown in fig (c).

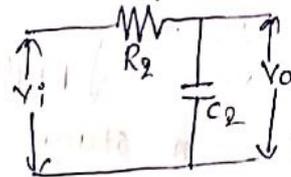

$$V_o = \frac{V_i \left(\frac{1}{j\omega C_2} \right)}{R_2 + \frac{1}{j\omega C_2}}$$

$$A_H = \frac{V_o}{V_i} = \frac{1/j\omega C_2}{R_2 + \frac{1}{j\omega C_2}}$$

$$= \frac{1/j\omega C_2}{\frac{R_2 j\omega C_2 + 1}{j\omega C_2}} = \frac{1}{1 + R_2 j\omega C_2}$$

let $2\pi R_2 C_2 = \frac{1}{f_H}$

$$A_H = \frac{1}{1 + j\left(\frac{f}{f_H}\right)}$$

$$|A_H| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

At $f = f_H$, $|A_H| = \frac{1}{\sqrt{2}}$

At which the gain of an amplifier is $\frac{1}{\sqrt{2}}$ times of its mid band value is called highest cut off frequency. This drop corresponds to a dB reduction of 3dB and hence it is also called as highest 3dB frequency.


Effect of cascading on

WKT,

The gain of an amplifier at low frequencies is given by

$$A_L = \frac{1}{\sqrt{1 + (f_L/f)^2}} \quad (\text{Single stage})$$

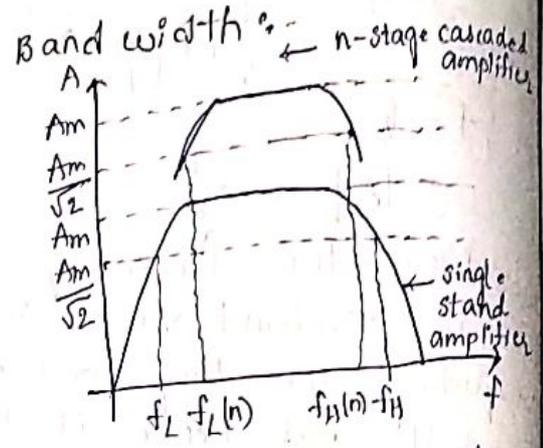The lowest 3dB frequency at $f = f_L$, the gain becomes $\frac{1}{\sqrt{2}}$.



frequency response of single staged n-stage cascaded amplifier.

|||, for n-stage cascaded amplifier the lowest 3dB frequency is given by

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (f_L/f_L(n))^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{(1)^n}{\left[\sqrt{1 + (f_L/f_L(n))^2} \right]^n}$$

$$\left[\sqrt{1 + (f_L/f_L(n))^2} \right]^n = \sqrt{2}$$

$$\left[1 + (f_L/f_L(n))^2 \right]^n = 2$$

$$1 + (f_L/f_L(n))^2 = 2^{1/n}$$

$$(f_L/f_L(n))^2 = 2^{1/n} - 1$$

$$f_L/f_L(n) = \sqrt{2^{1/n} - 1}$$

$f_L(n) > f_L$

$$f_L(n) = \frac{f_L}{\sqrt{2^{1/n} - 1}} \quad \text{--- (1)}$$

WKT, The gain of single stage amplifiers at high frequencies is given by

$$A_H = \frac{1}{\sqrt{1 + (f/f_H)^2}}$$

The higher 3 dB frequency at $f = f_H$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (f_H/f_H)^2}}$$

IIIrd, for n-stage cascaded amplifiers the higher 3 dB frequency is given by

$$\frac{1}{\sqrt{2}} = \left[\frac{1}{1 + \left(\frac{f_H(n)}{f_H}\right)^2} \right]^n$$

[Equating D.R & S.O.B.S]

$$2 = \left[1 + \left(\frac{f_H(n)}{f_H}\right)^2 \right]^n$$

$$1 + \left(\frac{f_H(n)}{f_H}\right)^2 = 2^{1/n}$$

$$\left(\frac{f_H(n)}{f_H}\right)^2 = 2^{1/n} - 1$$

$$f_H(n) = f_H \sqrt{2^{1/n} - 1} \quad \text{--- (2)}$$

From eq (1) & (2) we conclude that as $f_H(n)$ is greater than f_L and $f_H(n) < f_H$, the band width of n-stage cascaded amplifiers decreases over the band width of single stage amplifier.

Differential Amplifier :

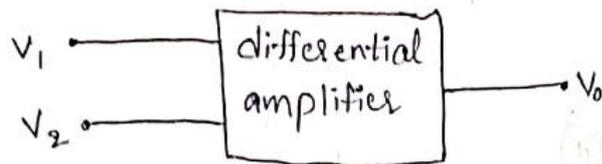


fig: Block diagram representation of differential amplifiers.

The differential amplifier (or) difference amplifier amplifies the difference b/w two i/p signals. For an ideal differential amplifier we can write that

$$V_o \propto V_1 - V_2$$

$$V_o = A_d (V_1 - V_2)$$

where A_d = constant proportionality (or) differential mode gain.

with this gain differential amplifier amplifies the difference of two i/p's

$$V_o = V_d A_d \quad \text{--- (1)}$$

But in practical cases the o/p voltage is also proportional to the average (or) common level of two inputs.

i.e., $V_o \propto \frac{V_1 + V_2}{2}$

$$V_o = A_c \left(\frac{V_1 + V_2}{2} \right)$$

$$V_o = A_c V_c \quad \text{--- (2)}$$

where A_c = constant of proportionality (or) common mode gain.

Therefore, the total o/p voltage

$$V_o = A_d V_d + A_c V_c \quad \text{--- (3)}$$

In the design of differential amplifiers one goal is to minimize the effect of common mode signal.

These are used in microphone pre-amplifiers, audio pre-amplifiers, radio & T.V signal recovery, digital to analog converters and so on.

Common Mode Rejection Ratio (CMRR)
 It is the ability of differential amplifiers to reject the common mode signal and it is expressed in the ratio and it is defined as the ratio of differential mode gain to the common mode gain.

In ideal cases $A_d = \infty$ & $A_c = 0$

$$P = \frac{A_d}{A_c}$$

$$P = \infty$$

The o/p voltage in terms of CMRR is
 WKT, the o/p voltage of differential amplifier.

$$V_o = A_d V_d + A_c V_c$$

$$= A_d V_d \left(1 + \frac{A_c V_c}{A_d V_d} \right)$$


$$V_o = A_d V_d \left(1 + \frac{1}{P} \frac{V_c}{V_d} \right)$$

The o/p voltage in terms of CMRR.
 In ideal condition CMRR is infinity then the o/p is proportional to difference of two i/p's only. In practical cases CMRR is very large and it greatly rejects the common mode signals i.e. the o/p voltage is mostly proportional to the difference sq. l.

The differential amplifier used in BJT :-
 Operating mode of differential amplifier :-
 Based on polarities of two inputs of differential amplifier, there are two modes of operations.

1. differential mode of operation.
2. Common mode of operation

Differential Mode of operation :-

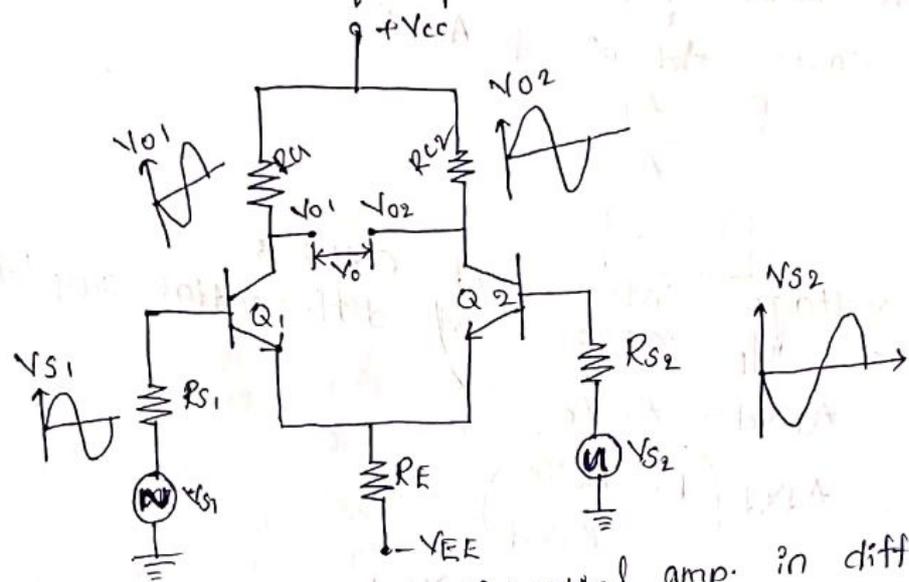

a) ckt diagram of differential amp. in differential mode
 → When a differential amplifier as shown in fig (a), has two inputs are equal in magnitude with opposite phase, the mode of operation is called differential mode. Thus the amplified outputs at collector of transistor Q_1 and collector of transistor Q_2 are equal in magnitude with opposite phase.

→ The total o/p voltage is the difference of two individual o/p's.


i.e., $V_0 = V_{01} - V_{02}$

For ex :- $V_{01} = 10V ; V_{02} = -10V$

$V_0 = 10 - (-10) = 20V$

Thus, the total o/p voltage = 20V
 From the above value, we conclude that in differential mode of operation the total o/p voltage is twice that of the individual o/p's.

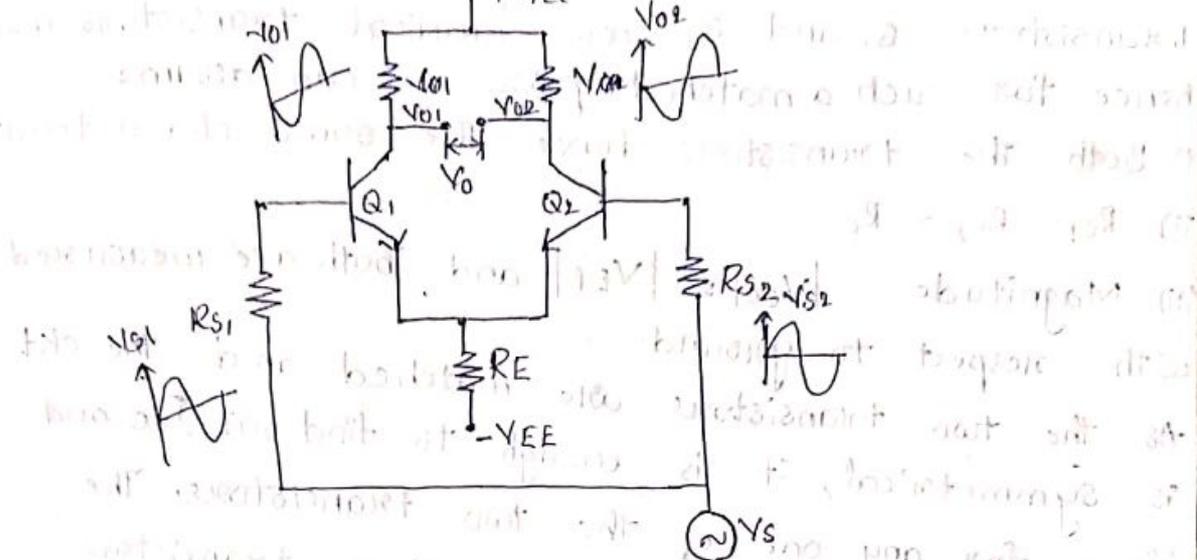Common Mode of operation in differential amp.



b) ckt diagram of common mode in differential amp. → when a differential amplifier as shown in fig (b), with same input for the transistors Q_1 and Q_2 , the mode of operation is called common mode. Thus two amplified opps at collector of transistor Q_1 and collector of transistor Q_2 are equal in magnitude and phase.

→ Hence, the total output voltage is equal to difference of two individual outputs and it is equal to zero.

The dc analysis of differential amplifier :- The dc analysis means to obtain the operating point values. I_{CQ} & V_{CEQ} . The supply voltages are dc, while the input voltages/signals are AC. So, dc equivalent circuit can be obtained by reducing the ac input signals to zero. The dc equivalent ckt is obtained as shown in below figure.

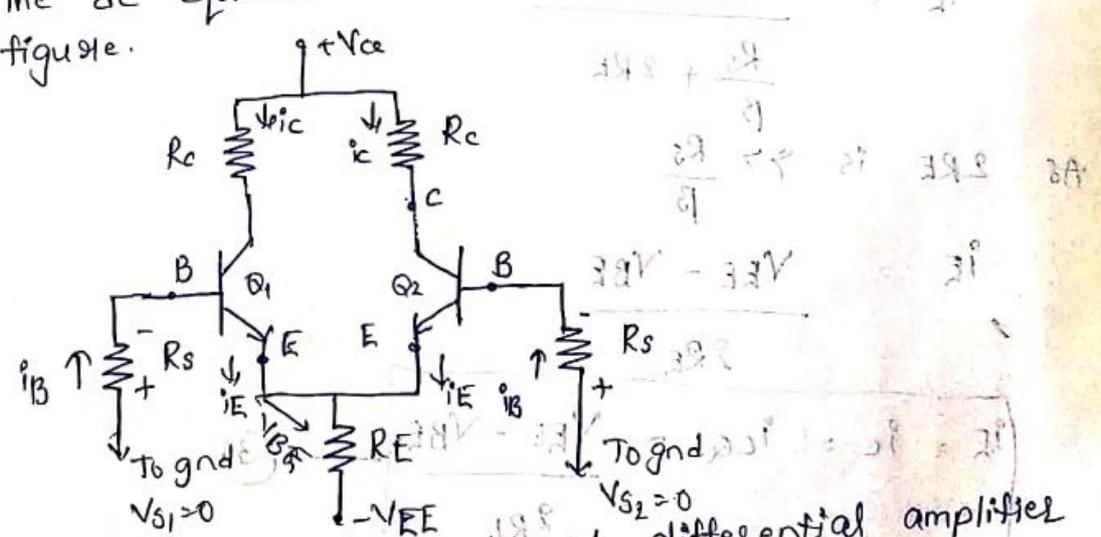


Fig: dc equivalent ckt of differential amplifier

From the above figure, assuming $R_{S1} = R_{S2} = R_S$, the transistors Q_1 and Q_2 are identical transistors and hence for such a matched pair we can assume

i) Both the transistors have the same characteristics

ii) $R_{C1} = R_{C2} = R_C$

iii) Magnitude $|V_{CC}| = |V_{EE}|$ and both are measured with respect to ground.

As the two transistors are matched and the ckt is symmetrical, it is enough to find out I_{CQ} and V_{CEQ} for any one of the two transistors. The same is applicable for the other transistor.

Applying KVL to base emitter loop of transistor Q_1 ,

$$I_B R_S + V_{BE} + 2I_E R_E - V_{EE} = 0 \quad \text{--- (1)}$$

We know that $I_C = \beta I_B \quad \therefore I_C \ll I_E$

$$I_B = \frac{I_E}{\beta} \quad \text{--- (2)}$$

Substitute eq (2) in eq (1)

$$\left(\frac{I_E}{\beta}\right) R_S + V_{BE} + 2I_E R_E - V_{EE} = 0$$

$$I_E \left[\frac{R_S}{\beta} + \frac{V_{BE}}{I_E} + 2R_E - \frac{V_{EE}}{I_E} \right] = 0$$


$$I_E \left[\frac{R_S}{\beta} + 2R_E \right] + V_{BE} - V_{EE} = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{\frac{R_S}{\beta} + 2R_E}$$

As $2R_E$ is $\gg \frac{R_S}{\beta}$

$$I_E = \frac{V_{EE} - V_{BE}}{2R_E}$$
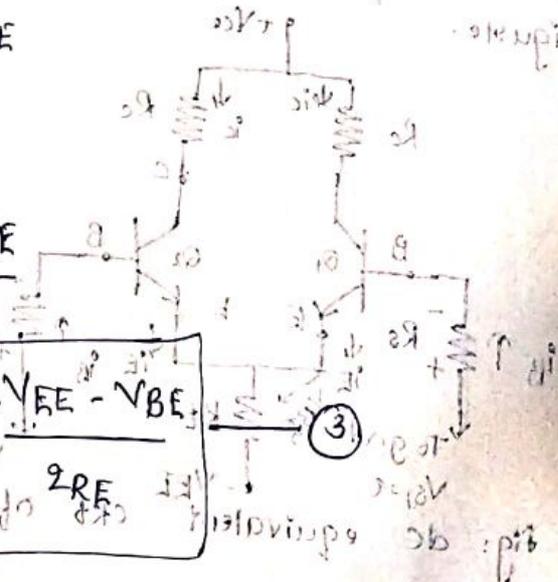
$$I_E = I_C = I_{CQ} = \frac{V_{EE} - V_{BE}}{2R_E} \quad \text{--- (3)}$$



From the collector to emitter loop,

$$V_{CE} = V_C - V_E \quad \text{--- (4)}$$

$$V_C = V_{CC} - I_C R_C \quad \text{--- (5)}$$

The voltage at emitter terminal by neglecting the voltage drop across resistor R_S is given by:

$$V_E = -V_{BE} \quad \text{--- (6)}$$

Sub. eq 6, 5 in (4)

$$V_{CE} = V_{CC} - I_C R_C + V_{BE} = V_{CEQ} \quad \text{--- (7)}$$

Now the Q point coordinates are $Q (V_{CEQ}, I_{CQ})$

$$Q \left(V_{CC} - I_C R_C + V_{BE}, \frac{V_{EE} - V_{BE}}{2R_E} \right)$$

