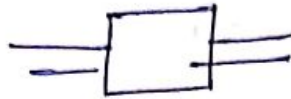



4. Two-port networks

port is having one receiving end and one sending end.

two port means two sending ends and two receiving ends.



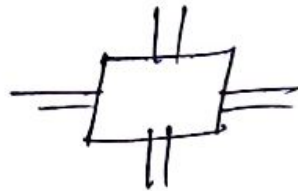suppose we taken n port network has ' n ' no. of output ports and ' n ' no. of input port.




two port network parameters are classified into

1. z -parameters / open circuit parameters.
2. y -parameters / short circuit parameters
3. ABCD-parameters / transmission parameters
4. H -parameters
5. Inverse ABCD-parameters
6. Inverse H -parameters / g -parameters.

i) 2-parameters:-

$$(V_1, V_2) = f(I_1, I_2)$$

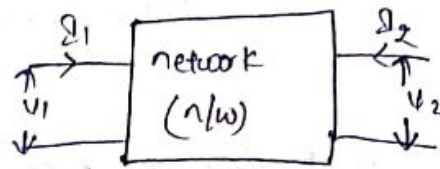

$$V_1 = z_{11}I_1 + z_{12}I_2 \rightarrow (1)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \rightarrow (2)$$

If $I_2 = 0$ i.e., port-2 is open circuit

from eqn (1) & (2)

$$V_1 = z_{11}I_1 + z_{12}(0)$$

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

and $V_2 = z_{21}I_1 + z_{22}(0)$

$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

If $I_1 = 0$ i.e., port -1 acts as open circuit

from eqn (1) & (2)

$$V_1 = z_{11}(0) + z_{12}I_2$$


$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

and $V_2 = z_{21}(0) + z_{22}I_2$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

Equivalent circuit :-

from equation (1) & (2)

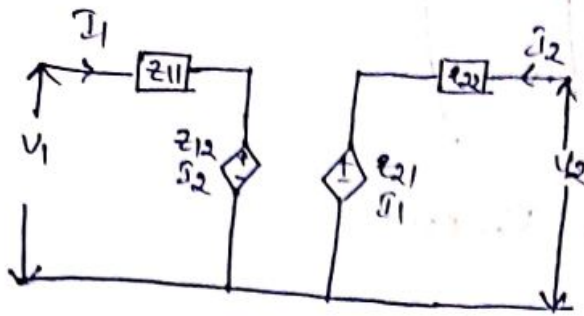

Z_{11} = driving point impedance at port-1

Z_{12} = forward impedance

Z_{21} = reverse impedance


Z_{22} = driving point impedance at port-2

Y-parameters :-

$$(I_1, I_2) = f(V_1, V_2)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (1)$$

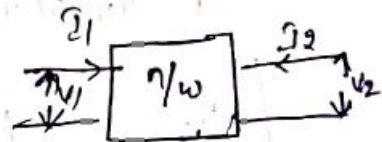
$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (2)$$



in matrix-form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

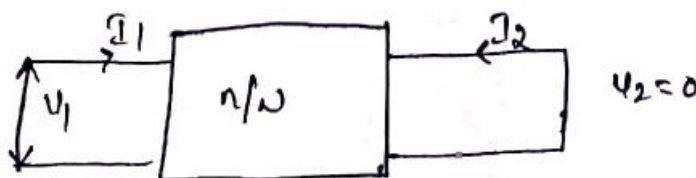If $V_2 = 0$ i.e., port-2 is short circuit



from eqn(1) & (2)

$$I_1 = Y_{11} U_1 + Y_{12} U_2$$

$$Y_{11} = \frac{I_1}{U_1} \Big|_{U_2=0}$$

and $I_2 = Y_{21} U_1 + Y_{22} U_2$

$$Y_{21} = \frac{I_2}{U_1} \Big|_{U_2=0}$$

if $U_2=0$; the port-2 is short circuit.



from eqn(1) & (2)

$$I_1 = Y_{11} U_1 + Y_{12} U_2$$


$$Y_{12} = \frac{I_1}{U_2} \Big|_{U_1=0}$$

and $I_2 = Y_{21} U_1 + Y_{22} U_2$

$$Y_{22} = \frac{I_2}{U_2} \Big|_{U_1=0}$$

Equivalent circuit:

from eqn (1) & (2)

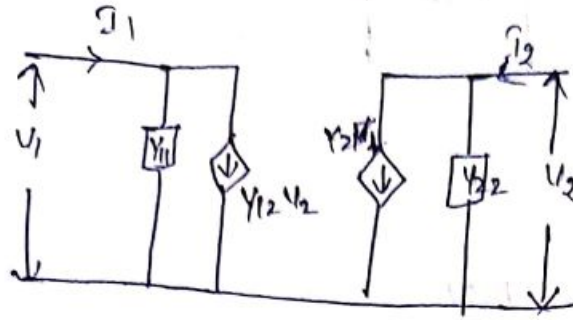

Y_{11} = driving point admittance at port-1

Y_{12} = forward admittance

Y_{21} = Reverse admittance


Y_{22} = driving point admittance at port-2

ABCD-parameters:-

$$(V_1, I_1) = f(V_2, -I_2)$$

$$V_1 = AV_2 - BI_2 \rightarrow (1)$$


$$I_1 = CV_2 - DI_2 \rightarrow (2)$$

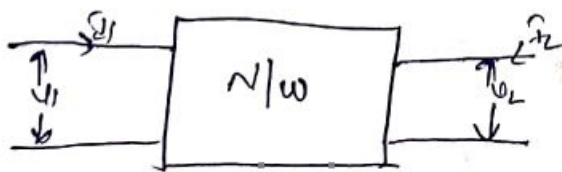

in matrix form

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

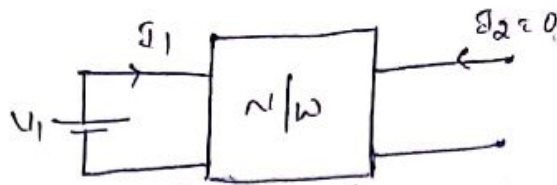If $I_2 = 0$; i.e., port-2 as open circuit



from eqn (1) & (2)


$$V_1 = A V_2 - B I_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2 = 0}$$

and $I_1 = C V_2 - D I_2$

$$C = \frac{I_1}{V_2} \Big|_{I_2 = 0}$$

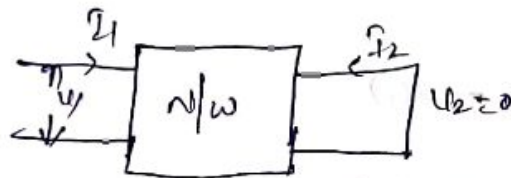If $V_2 = 0$; i.e., port-2 as short-circuited.



from eqn (1) & (2)

$$V_1 = A V_2 - B I_2$$

$$B = -\frac{V_1}{I_2} \Big|_{V_2 = 0}$$

and $I_1 = C V_2 - D I_2$

$$D = -\frac{I_1}{I_2} \Big|_{V_2 = 0}$$

Equivalent circuit:

h-parameters:-

A \Rightarrow reverse voltage gain

D \Rightarrow reverse current gain

B \Rightarrow forward impedance

C \Rightarrow forward admittance

h-parameters:-

$$(V_1, I_2) = f(I_1, V_2)$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (2)$$



In matrix form

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

If $V_2 = 0$; i.e., the port-2 was short-circuit



from eqn (1) & (2)

$$V_1 = h_{11} I_1 + h_{12}(0)$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

and

$$I_2 = h_{21} I_1 + h_{22}(V_2)$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

If $I_2=0$, the port-2 acts as open circuit



$$V_1 = h_{11}(I_1) + h_{12}(V_2)$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

and

$$I_2 = h_{21}(I_1) + h_{22}(V_2)$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$h_{11} \Rightarrow$ forward impedance

$h_{12} \Rightarrow$ forward voltage gain

$h_{21} \Rightarrow$ Reverse current gain.

$h_{22} \Rightarrow$ backward impedance.

Relations:-

* z-parameters in terms of Y-parameters :-

$$Z = \frac{1}{Y} = [Y]^{-1}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{Y_{11}Y_{22} - Y_{12}Y_{21}} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & \frac{-Y_{12}}{\Delta Y} \\ \frac{-Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}, \quad \Delta Y = \frac{1}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$

$$z_{11} = \frac{Y_{22}}{\Delta Y}$$

$$z_{12} = \frac{-Y_{12}}{\Delta Y}$$

$$z_{21} = \frac{-Y_{21}}{\Delta Y}$$

$$z_{22} = \frac{Y_{11}}{\Delta Y}$$

2-parameters in terms of ABCD-Parameters

we know that 2-parameters equations

$$V_1 = z_{11}I_1 + z_{12}I_2 \rightarrow (1)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \rightarrow (2)$$

and ABCD-parameters

$$V_1 = AV_2 - BI_2 \rightarrow (3)$$

$$I_1 = CI_2 - DI_2 \rightarrow (4)$$

$$(4) \Rightarrow CI_2 = I_1 + DI_2$$

$$V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \rightarrow (5)$$

substitute (5) in (3)

$$V_1 = A \left[\frac{1}{C}I_1 + \frac{D}{C}I_2 \right] - BI_2$$

$$= \frac{A}{C}I_1 - \left[\frac{BC + AD}{C} \right] I_2 \rightarrow (6)$$

Comparing (1) & (6) Equations

$$z_{11} = A/C, \quad z_{12} = \left[\frac{-BC + AD}{C} \right]$$

Comparing (2) & (5) Equations

$$z_{21} = \frac{1}{C}, \quad z_{22} = +D/C$$

* z-parameters in terms of h-parameters:

we know that z-parameters equations

$$V_1 = z_{11} I_1 + z_{12} I_2 \rightarrow (1)$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \rightarrow (2)$$

and h-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (3)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (4)$$

Eqn (4) \Rightarrow $h_{22} V_2 = I_2 - h_{21} I_1$

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \rightarrow (5)$$

(3) \Rightarrow $V_1 = h_{11} I_1 + h_{12} \left[\frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1 \right]$

$$V_1 = \frac{h_{11} h_{22} - h_{21} h_{12}}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2 \rightarrow (6)$$

Comparing (1) & (6) equations

$$z_{11} = \frac{h_{11} h_{22} - h_{21} h_{12}}{h_{22}} ; z_{12} = \frac{h_{12}}{h_{22}}$$

Comparing (2) & (5) equations

$$z_{22} = \frac{1}{h_{22}} ; z_{21} = \frac{-h_{21}}{h_{22}}$$

* 4-parameters in terms of 2-parameters:-

4 parameters equations are

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (1)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (2)$$

$$Y = \frac{I}{V} = [Y]^{-1}$$

$$= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \frac{+1}{z_{11}z_{22} - z_{12}z_{21}} \begin{bmatrix} +z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{z_{22}}{\Delta z} & \frac{-z_{12}}{\Delta z} \\ \frac{-z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{bmatrix}$$

$$Y_{11} = \frac{z_{22}}{\Delta z}$$

$$Y_{12} = \frac{-z_{12}}{\Delta z}$$

$$Y_{21} = \frac{-z_{21}}{\Delta z}$$

$$Y_{22} = \frac{z_{11}}{\Delta z}$$

* Y -parameters in terms of ABCD-parameters.

Y -parameter $I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (1)$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (2)$$

ABCD-parameter equations:-

$$V_1 = AV_2 - BI_2 \rightarrow (3)$$

$$I_1 = CV_2 - DI_2 \rightarrow (4)$$

$$(3) \Rightarrow BI_2 = AV_2 - V_1$$

$$I_2 = \frac{A}{B} V_2 - \frac{1}{B} V_1 \rightarrow (5)$$

Substitute (5) in (4)

$$I_1 = CV_2 - D \left[\frac{A}{B} V_2 - \frac{1}{B} V_1 \right]$$

$$I_1 = \left[\frac{BC-AD}{B} \right] V_2 + \frac{D}{B} V_1 \rightarrow (6)$$

Compare (1) & (6) equations

$$Y_{11} = \frac{D}{B} \quad ; \quad Y_{12} = \frac{BC-AD}{B}$$

compare (2) & (5) equations

$$Y_{21} = -\frac{1}{B} \quad ; \quad Y_{22} = \frac{A}{B}$$

"Y-parameters in terms of h-parameters

Y-Parameters Equations are

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (1)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (2)$$

h-parameters Equations are

$$V_1 = h_{11} I_1 + h_{12} I_2 \rightarrow (3)$$

$$I_2 = h_{21} I_1 + h_{22} I_2 \rightarrow (4)$$

$$(3) \Rightarrow h_{11} I_1 = V_1 - h_{12} I_2$$

$$I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} I_2 \rightarrow (5)$$

$$(4) \Rightarrow I_2 = h_{21} \left[\frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} I_2 \right] + h_{22} I_2$$

$$= \frac{h_{21}}{h_{11}} V_1 + \frac{h_{11} h_{22} - h_{21} h_{12}}{h_{11}} I_2 \rightarrow (6)$$

compare (1) & (5) equations

$$Y_{11} = \frac{1}{h_{11}} ; Y_{12} = -\frac{h_{12}}{h_{11}}$$

compare (2) & (6) equations

$$Y_{21} = \frac{h_{21}}{h_{11}} ; Y_{22} = \frac{h_{11} h_{22} - h_{21} h_{12}}{h_{11}}$$

10. ABCD-parameters in terms of z-parameters

ABCD-parameters Equations are:

$$V_1 = A V_2 - B I_2 \rightarrow (1)$$

$$I_1 = C V_2 - D I_2 \rightarrow (2)$$

z-parameters equations are

$$V_1 = z_{11} I_1 + z_{12} I_2 \rightarrow (3)$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \rightarrow (4)$$

$$(4) \Rightarrow z_{21} I_1 = V_2 - z_{22} I_2$$

$$I_1 = \frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \rightarrow (5)$$

$$(3) \Rightarrow V_1 = z_{11} \left[\frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \right] + z_{12} I_2$$

$$V_1 = \frac{z_{11}}{z_{21}} V_2 + \frac{z_{12} z_{21} - z_{11} z_{22}}{z_{21}} I_2 \rightarrow (6)$$

compare (1) & (6) equations

$$A = \frac{z_{11}}{z_{21}} ; B = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{21}}$$

compare (2) & (5) equations

$$C = \frac{z_{12}}{z_{21}} ; D = \frac{z_{22}}{z_{21}}$$

ABCD parameters in terms of Y-parameters:-

ABCD parameters Equations:

$$V_1 = A V_2 - B I_2 \rightarrow (1)$$

$$I_1 = C V_2 - D I_2 \rightarrow (2)$$

Y-parameters Equations:-

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (3)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (4)$$

$$(4) \Rightarrow Y_{21} V_1 = I_2 - Y_{22} V_2$$

$$V_1 = \frac{1}{Y_{21}} I_2 - \frac{Y_{22}}{Y_{21}} V_2 \rightarrow (5)$$

$$(3) \Rightarrow Y_{11} \left[\frac{1}{Y_{21}} I_2 - \frac{Y_{22}}{Y_{21}} V_2 \right] + Y_{12} V_2$$

$$I_1 = \frac{Y_{11}}{Y_{21}} I_2 + \frac{Y_{12} Y_{21} - Y_{11} Y_{22}}{Y_{21}} V_2 \rightarrow (6)$$

Compare (1) & (5) equations

$$A = \frac{1}{Y_{21}} \quad ; \quad B = \frac{Y_{22}}{Y_{21}}$$

Compare (2) & (6) equations

$$C = \frac{Y_{12} Y_{21} - Y_{11} Y_{22}}{Y_{21}} \quad ; \quad D = \frac{Y_{11}}{Y_{21}}$$

* ABCD parameters in terms of h parameters? -

ABCD parameters Equations:-

$$V_1 = A V_2 - B I_2 \rightarrow (1)$$

$$I_1 = C V_2 - D I_2 \rightarrow (2)$$

h parameters Equations

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (3)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (4)$$

$$(4) \Rightarrow h_{21} I_1 = I_2 - h_{22} V_2$$

$$I_1 = \frac{1}{h_{21}} I_2 + \frac{h_{22}}{h_{21}} V_2 \rightarrow (5)$$

$$(5) \Rightarrow V_1 = h_{11} \left[\frac{1}{h_{21}} I_2 + \frac{h_{22}}{h_{21}} V_2 \right] - h_{12} V_2$$

$$V_1 = \frac{h_{11}}{h_{21}} I_2 + \left[\frac{h_{11} h_{22} + h_{12} h_{21}}{h_{21}} \right] V_2 \rightarrow (6)$$

compare (1) & (6) equations

$$A = \left[\frac{h_{11} h_{22} + h_{12} h_{21}}{h_{21}} \right] ; B = \frac{h_{12}}{h_{21}}$$

compare (2) & (5) equations

$$C = \frac{-h_{22}}{h_{21}} ; D = \frac{1}{h_{21}}$$

* h-parameters in terms of z-parameters

h-parameter Equations are:

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (2)$$

z-parameters Equations:

$$V_1 = z_{11} I_1 + z_{12} I_2 \rightarrow (3)$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \rightarrow (4)$$

$$(4) \Rightarrow z_{22} I_2 = V_2 - z_{21} I_1$$

$$I_2 = \frac{1}{z_{22}} V_2 - \frac{z_{21}}{z_{22}} I_1 \rightarrow (5)$$

$$(3) \Rightarrow V_1 = z_{11} I_1 + z_{12} \left[\frac{1}{z_{22}} V_2 - \frac{z_{21}}{z_{22}} I_1 \right]$$

$$V_1 = \frac{z_{12}}{z_{22}} V_2 + \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{22}} I_1 \rightarrow (6)$$

comparing (1) & (6) equations

$$h_{11} = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{22}} ; h_{12} = \frac{z_{12}}{z_{22}}$$

comparing (2) & (5) equations:

$$h_{21} = \frac{-z_{21}}{z_{22}} ; h_{22} = \frac{1}{z_{22}}$$

h-parameters in terms of y-parameters:

h-parameter equations are:

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow (2)$$

y-parameter Equations:

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow (3)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow (4)$$

$$(3) \Rightarrow Y_{11} V_1 = I_1 - Y_{12} V_2$$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \rightarrow (5)$$

$$(4) \Rightarrow I_2 = Y_{21} \left[\frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2 \rightarrow (6)$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 + \frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{11}} V_2 \rightarrow (6)$$

Compare (1) & (5) equations

$$h_{11} = \frac{1}{Y_{11}}, \quad h_{12} = \frac{-Y_{12}}{Y_{11}}$$

Compare (2) & (6) equations

$$h_{21} = \frac{Y_{21}}{Y_{11}}, \quad h_{22} = \frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{11}}$$

h-parameters in terms of ABCD parameters

h-parameters equations are:

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow (1)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow (2)$$

ABCD-parameters equations are:

$$V_1 = AV_2 - BI_2 \rightarrow (3)$$

$$I_1 = CI_2 - DI_2 \rightarrow (4)$$

$$(4) \Rightarrow DI_2 = CI_2 - I_1$$

$$I_2 = \frac{C}{D} V_2 - \frac{1}{D} I_1 \rightarrow (5)$$

$$(3) \Rightarrow V_1 = AV_2 - B \left[\frac{C}{D} V_2 - \frac{1}{D} I_1 \right]$$

$$V_1 = \frac{AD-BC}{D} V_2 + \frac{B}{D} I_1 \rightarrow (6)$$


compare (1) & (6) equations

$$h_{11} = \frac{B}{D}; \quad h_{12} = \frac{AD-BC}{D}$$

compare (2) & (5) equations


$$h_{21} = \frac{1}{D}; \quad h_{22} = \frac{C}{D}$$

find z-parameters

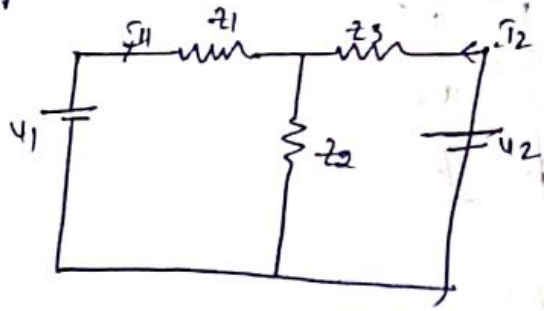

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{I_1 \times z_{eq}}{I_1}$$

$$= z_{eq} = z_1 + z_2$$

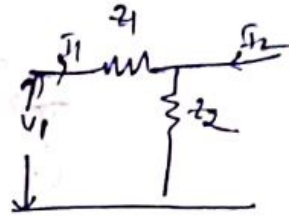


$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{I_1 \times z_2}{I_1} = z_2$$

when $I_1=0$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$


$$= \frac{I_2 \times z_{eq}}{I_2} = z_{eq}$$

$$= z_2 + z_3$$

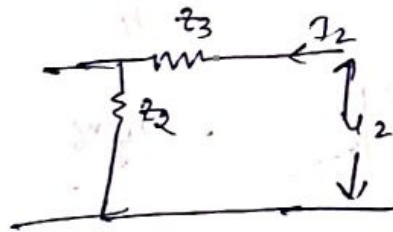


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$
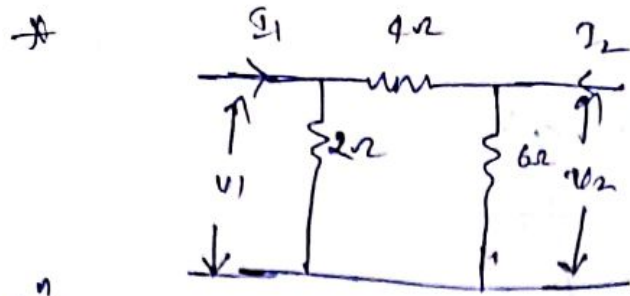
$$= \frac{I_2 \times z_{22}}{I_2} = z_{22}$$



$I_2 = 0$ port-2 \Rightarrow open

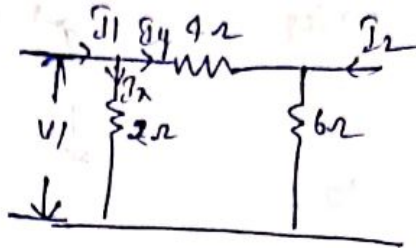

$$R_{eq} = (6+4) \parallel 2$$

$$= 10 \parallel 2 = 1.66 \Omega$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{I_1 \times R_{eq}}{I_1} = 1.66 \Omega$$


$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{I_1 \times 6}{I_1}$$

$$= I_1 \times \frac{2}{2+4+6} \times 6 = 1 \Omega$$

$I_1 = 0$ port-1 \Rightarrow open

$$Z_{22} = (2+4) \parallel 6$$

$$= 6 \parallel 6 = 3 \Omega$$

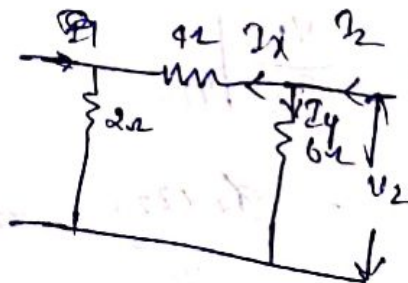

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{I_2 \times Z_{eq}}{I_2}$$


$$= 3 \Omega$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$= \frac{8 \times 2}{8} = 2$$

$$\frac{8 \times \frac{6}{2+4+6} \times 2}{8}$$

$$= 1 \Omega$$

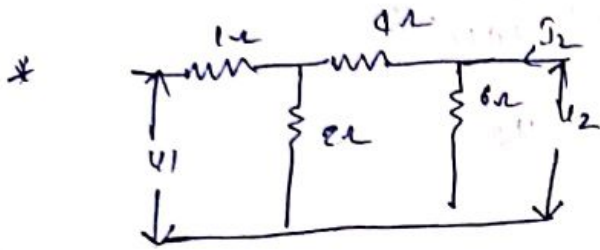


$I_2=0$ port-2 \Rightarrow open

$$R_{eq} = ((6+4) \parallel 2) + 1$$

$$= (10 \parallel 2) + 1$$

$$= 1.66 + 1$$

$$= 2.66 \Omega$$

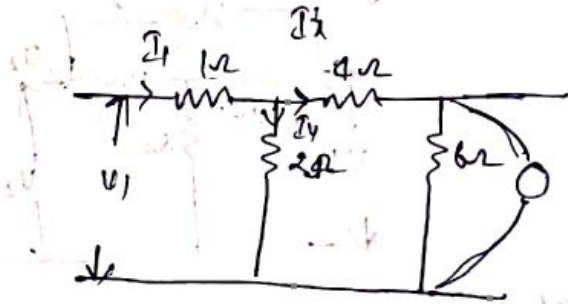

$$Z_{11} = \frac{V_1}{I_1} = \frac{I_1 \times R_{eq}}{I_1} = 2.66 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{8 \times 6}{8} = \frac{I_1 \cdot 2}{2+4+6} \cdot 6$$

$$= 1 \Omega$$


$I_{20} \Rightarrow$ port (1) \Rightarrow open

$$R_{eq} = (2+4) \parallel 6$$

$$= 3\Omega$$

$$I_{22} = \frac{V_2}{R_2} = \frac{I_1 \times R_{eq}}{R_2} = 3\Omega$$

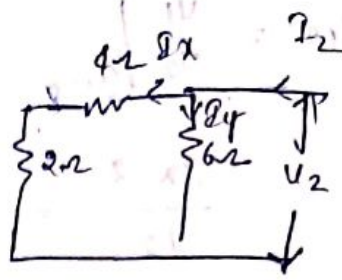
$$I_{12} = \frac{-V_1}{R_2} = \frac{I_1 \cdot 2}{R_2} = \frac{I_1 \cdot \frac{6}{2+4+6} \cdot 2}{R_2} = 1\Omega$$



* obtain short-circuit parameters




port-2 is short

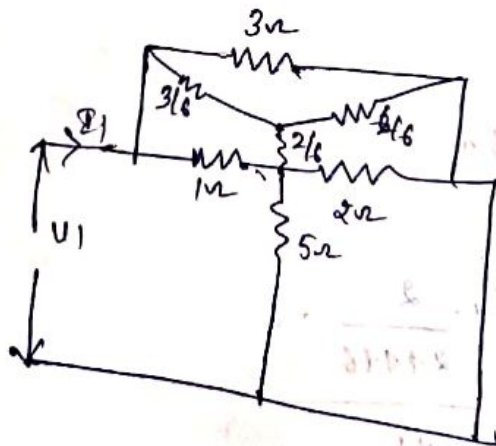

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{I_1}{R_{eq}} \Big|_{V_2=0}$$

$$Y_{11} = \frac{1}{R_{eq}}$$

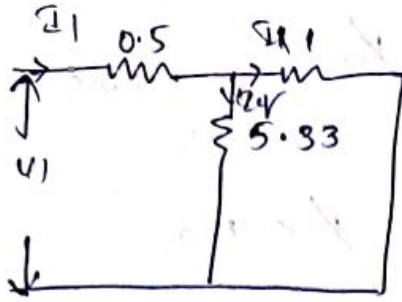

$$R_{eq} = 1.342 \Omega$$


$$Y_{11} = \frac{1}{1.342} = 0.745 \text{ S}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{I_2}{V_1} \cdot \frac{I_2}{I_1}$$

$$= \frac{\cancel{I_2} \times 5.33}{\cancel{I_1} \times 1.342} = -\frac{5.33}{1.342} \text{ S}$$

$$= -\frac{5.33}{1.342} = -0.692 \text{ S}$$

Port-1 is short:

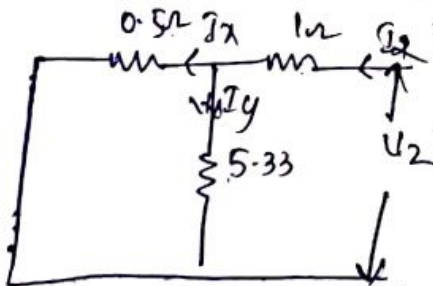

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{I_2 / R_{eq}}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{1}{R_{eq}} = \frac{1}{(0.5 + 5.33) \Omega}$$

$$= \frac{1}{5.83} = 0.689 \text{ S}$$

$$V_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$= \frac{I_1 \cdot 0.005}{V_2} = \frac{I_1 \cdot 5 \cdot 10^{-3}}{V_2} \times 1000$$

$$\frac{I_1 \cdot 5 \cdot 10^{-3}}{5.33 + 0.5}$$


$$= \frac{0.457}{1.45}$$

$$= 0.315 \text{ V}$$


$$\left[\begin{array}{l} \frac{35}{6}, \frac{16}{3} \\ \frac{16}{3}, \frac{19}{3} \end{array} \right]^{-1}$$

$$0.85$$


*

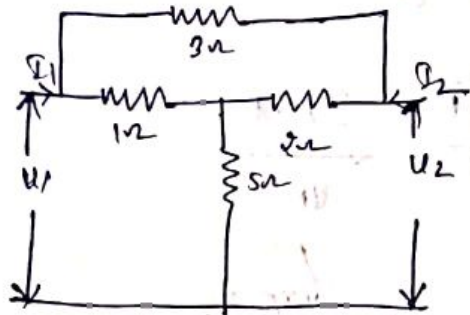

find z-parameters

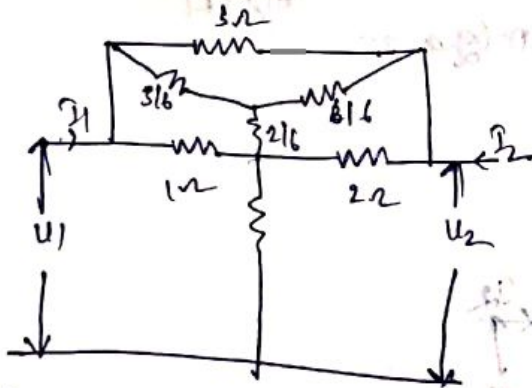

port-2 is open $I_2 = 0$

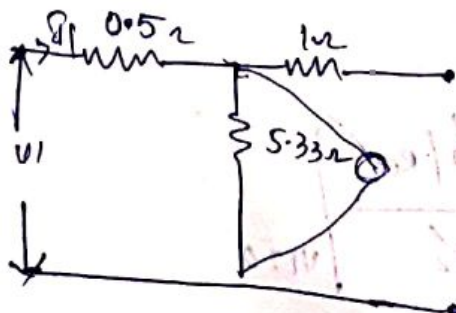

$$R_{eq} = 0.5 + 5.33$$

$$= 5.83$$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{I_1 \cdot R_{eq}}{I_1} = 5.83 \Omega$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{I_2 \cdot 5.33}{I_1}$$

$$= \frac{I_1 \cdot 5.33}{I_1} = 5.33 \Omega$$

port - 1 is open $I_1=0$


$$Z_{22} = \frac{V_2}{I_2}$$

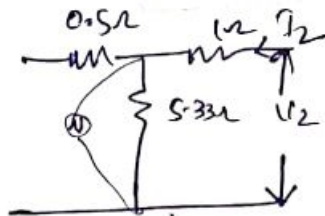


$$Z_{22} = \frac{V_2}{I_2} = R_{eq} = 0.5 + 5.33 = 6.33$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{I_2 \cdot R_{eq}}{I_2} = 6.33 \Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{I_2 \cdot 5.33}{I_2} = 5.33 \Omega$$

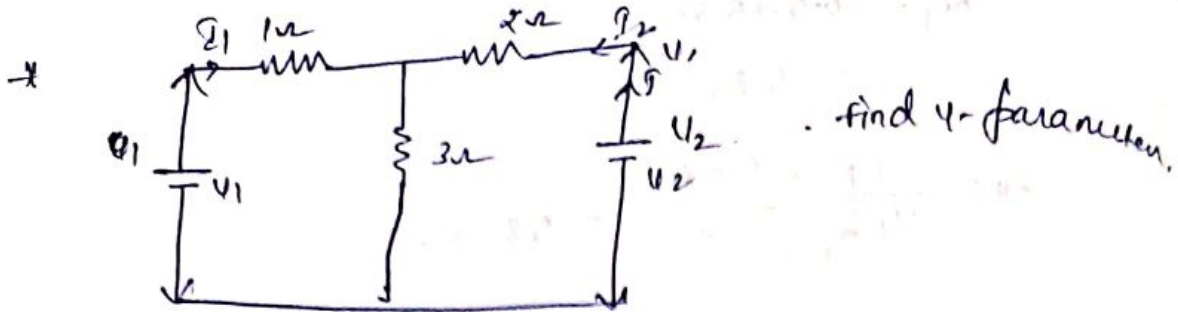

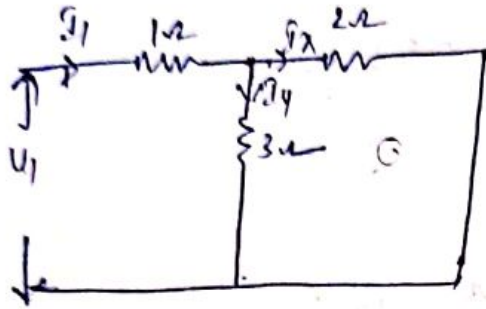solⁿ.
 $V_2 = 0$; port-2 is shortcircuited



$$R_{eq} = (2 \parallel 3) + 1$$

$$= \frac{2 \times 3}{2+3} + 1 = \frac{6}{5} + 1$$

$$= 11/5$$


$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{V_1 / R_{eq}}{V_1} = \frac{1}{R_{eq}}$$

$$= 1/5 \Omega$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{I_2 \cdot 2}{V_1} = \frac{I_1 \cdot \frac{3}{3+2} \cdot 2}{V_1} = \frac{I_1 / R_{eq}}{V_1} \cdot 2 \cdot \frac{3}{5}$$

$$= \frac{2}{5} \cdot R_{eq}$$
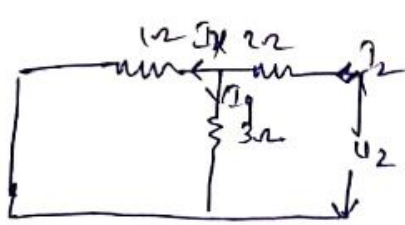
$$= \frac{2}{5} \times \frac{11}{5} = \frac{22}{25} \Omega^{-1}$$




port-1 is short-circuited
 $V_2 = 0$

$$R_{eq} = (1 \parallel 3) + 2 = \frac{3}{4} + 2 = 2 \frac{1}{4} \Omega$$

$$I_{sc} = \frac{1}{R_{eq}} = \frac{4}{11} A$$



$$V_{oc} = \frac{I_{sc} \cdot R_{eq}}{R_{eq}} = \frac{2 \cdot 3}{1+3} = \frac{12}{4} = 3V$$

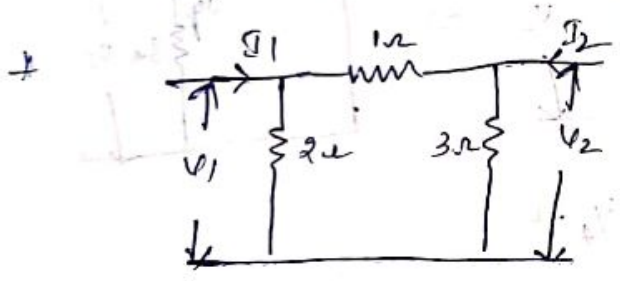[-ve due to opposite direction of current]



find Y-parameters

sol. when $V_2 = 0$; port-2 is short ckt

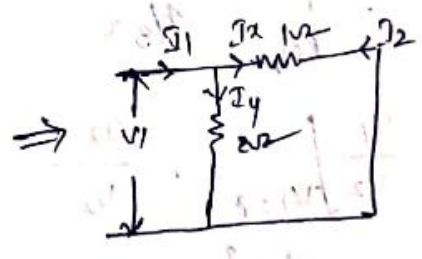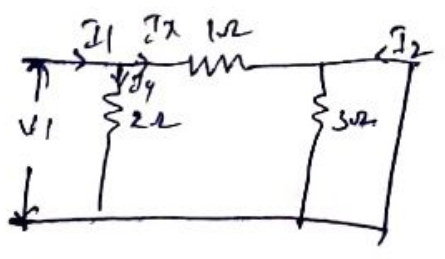

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$R_{eq} = 1 \parallel 2$$


$$= \frac{1 \times 2}{1+2} = \frac{2}{3}$$

$$Y_{11} = \frac{1}{R_{eq}} = \frac{1}{2/3} = 3/2 \text{ V}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{I_2=0} = -\frac{I_1}{V_1}$$

$$= \frac{I_1 \cdot \frac{2}{1+2}}{I_1 \cdot R_{eq}} = \frac{2/3}{2/3} = -1 \text{ V}$$

when $V_1=0$ port -1 is short circuited

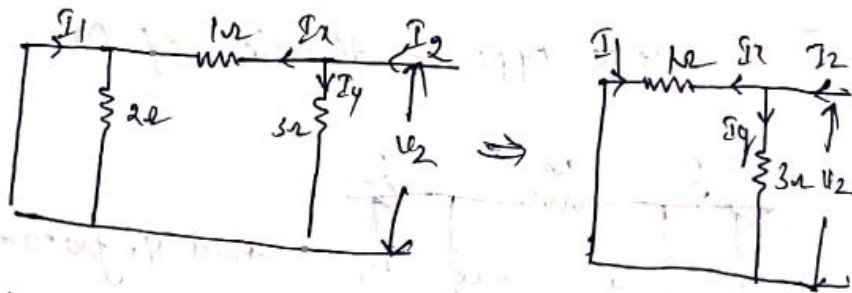


$$R_{eq} = 1 \parallel 3 = \frac{1 \times 3}{1+3} = 3/4$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{I_2}{R_{eq}}$$

$$= \frac{1}{R_{eq}} = 4/3 \text{ V}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{I_1}{V_2}$$

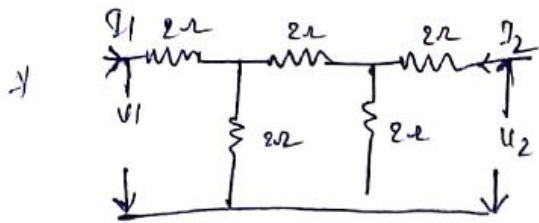
$$= \frac{I_1 \cdot \frac{3}{1+3}}{I_1 \cdot R_{eq}} = \frac{3/4}{3/4} = -1 \text{ V}$$



find Z, Y parameters.

Z parameters

If $I_2 = 0$; port 2 is open circuited

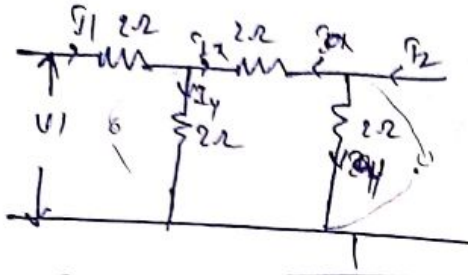

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{V_1 / R_{eq}}{I_1} = \frac{1}{R_{eq}} = R_{eq}$$

$$R_{eq} = ((2+2) \parallel 2) + 2$$


$$= 10/3$$

$$Z_{11} = 10/3 \Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{-I_1 \cdot 2}{I_1}$$

$$= -I_1 \cdot \frac{2}{2+2+2} \cdot 2 = \frac{-4}{6} = -2/3 \Omega$$

If $I_1 = 0$; port 1 is open circuit

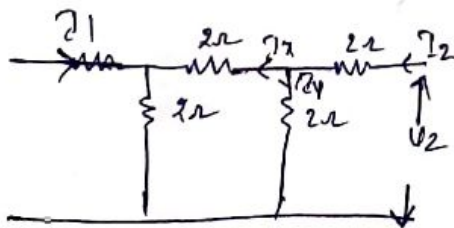

$$Req = ((2+2) \parallel 2) + 2$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 2eV$$

$$= 10/3 \Omega$$


$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{-I_2 \cdot 2}{I_2}$$

$$= -\frac{2}{2+2+2} \cdot 2$$

$$\frac{-4}{6}$$

$$= -4/6 = -2/3 \Omega$$

Y-parameters

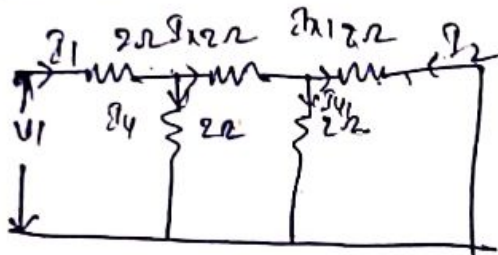

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Req \quad Y_{11} = \frac{1}{Req}$$

$$Req = ((2 \parallel 2) \parallel 2) + 2$$

$$= \frac{2 \cdot 2 \cdot 2}{3+2} + 2 = \frac{8}{5} + 2$$

$$= 16/5$$

$$Y_{11} = \frac{5}{16}$$

$$I_2 = \frac{I_1 \cdot 2}{2+2+2}$$


$$= \frac{2I_1}{6} = \frac{I_1}{3}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{I_2}{V_1}$$

$$= \frac{-\frac{I_1 \cdot 2}{3 \cdot 2+2}}{\frac{I_1 \cdot R_{eq}}{16/5}} = \frac{-\frac{2}{12}}{16/5}$$

$$= -\frac{2}{12} \times \frac{5}{16} = -\frac{5}{96} \text{ } \checkmark$$

$V_1=0$

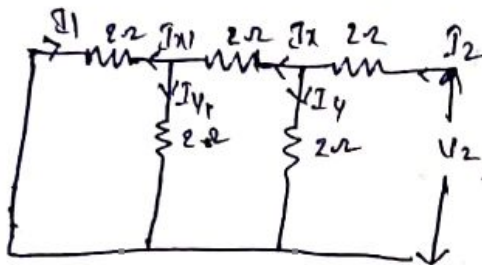

$$R_{eq} = [(2 \parallel 2) + 2] \parallel 2 + 2$$

$$= 16/5 \Omega$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{I_2}{V_2} \Big|_{R_{eq}}$$


$$= \frac{1}{R_{eq}} = 5/16$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-I_2}{V_2} \Big|_{V_1=0}$$

$$I_2 = \frac{I_2 \cdot 2}{2+2+2} = \frac{I_2}{3}$$

$$Y_{12} = -\frac{\frac{I_2}{3} \cdot 2}{\frac{I_2 \cdot R_{eq}}{16/5}} = \frac{-\frac{2}{12}}{16/5} = -\frac{5}{96} \text{ } \checkmark$$

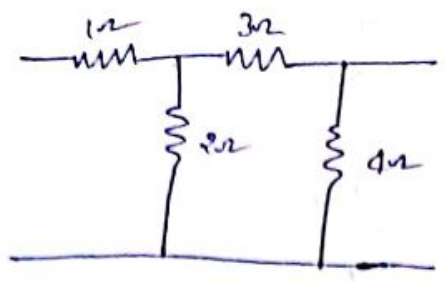
* find ABCD-parameters for the given network:



$$V_1 = AV_2 - BV_2$$

$$I_1 = CV_2 - DI_2$$

If $I_2 = 0$, the port -2 is open ckt

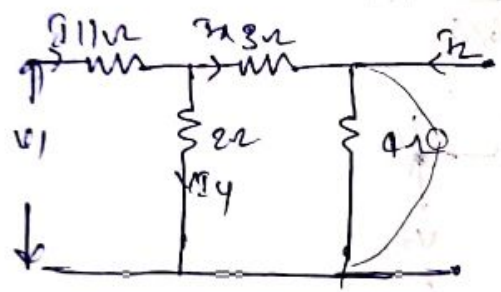

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{I_1 \cdot R_{eq}}{I_1 \cdot 4\Omega}$$

$$R_{eq} = \frac{7 \times 2}{7+2} \parallel (3+4) \parallel 2 + 1$$

$$= \frac{7 \times 2}{7+2} + 1 = \frac{14}{9} + 1$$

$$= \frac{23}{9}$$


$$I_1 \times \frac{I_1 \cdot 2}{2+3+4} = \frac{2I_1}{9}$$

$$A = \frac{I_1 \cdot \frac{23}{9}}{\frac{2I_1}{9} \cdot 4} = \frac{23}{8}$$

$$C = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{I_1}{I_2 \cdot 4}$$

$$= \frac{2/1}{\frac{I_1 \cdot 2}{2+3+4}} = \frac{9}{8} \Omega$$

If $V_2 = 0$ the port-2 is short circuit

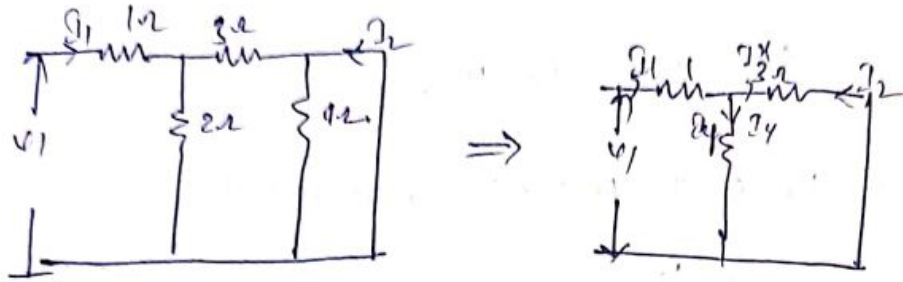

$$B = \frac{-V_1}{I_2} \Big|_{V_2=0}$$

$$= \frac{-I_1 \cdot R_{eq}}{I_2} = \frac{+I_1 \cdot R_{eq}}{+I_4}$$

$$= \frac{+I_1 \cdot R_{eq}}{I_4}$$

$$R_{eq} = (3 \parallel 2) + 1 = \frac{3 \times 2}{3+2} + 1$$

$$= \frac{6}{5} + 1 = \frac{11}{5}$$


$$I_4 = \frac{I_1 \cdot 2}{3+2} = \frac{2I_1}{5}$$

$$B = \frac{I_1 \cdot 11/5}{2I_1/5} = 11/2 \Omega$$

$$D = \frac{-I_1/I_2}{+I_4} = \frac{-I_1}{+I_4} = \frac{I_1}{2I_1/5}$$

$$= 5/2 \Omega$$


v H-parameters for this circuit

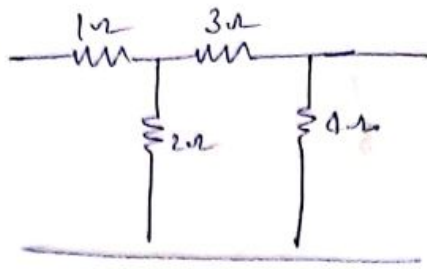

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

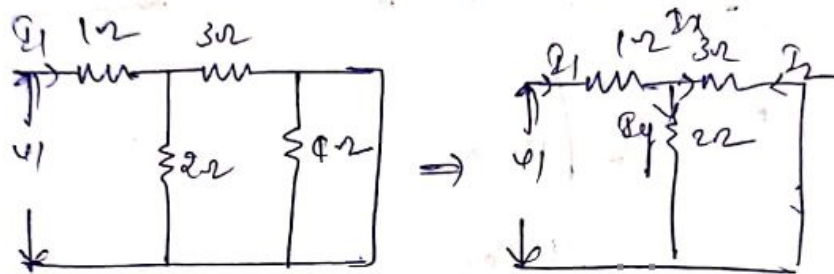when $V_2 = 0$ the port -2 is short-circuited



$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = \frac{I_1 \cdot R_{eq}}{I_1}$$


$$R_{eq} = 2(3 \parallel 2) + 1 = \frac{6}{5} + 1 = \frac{11}{5}$$

$$h_{11} = R_{eq} = \frac{11}{5} \Omega$$

$$h_{21} = \frac{I_2}{I_1} = \frac{-I_1}{I_1}$$

$$= \frac{-I_1 \cdot \frac{2}{2+3}}{I_1} = -\frac{2}{5}$$

when \$I_2 = 0\$ port 1 is open ckt

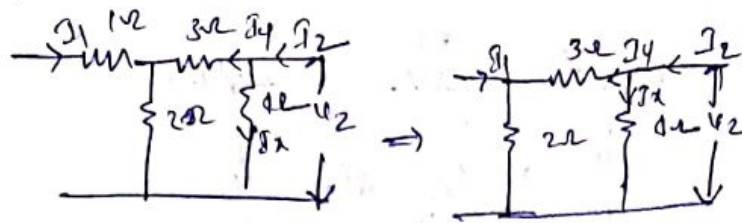

$$h_{22} = \frac{U_2}{I_2} = \frac{3 \times 4}{2 + 3 + 4} = \frac{12}{9} = \frac{4}{3}$$

$$R_{eq} = (2+3) \parallel 4$$

$$= 5 \parallel 4 = \frac{5 \times 4}{5+4} = \frac{20}{9} \Omega$$




$$I_4 = \frac{I_2 \cdot 4}{2+3+4} = \frac{4I_2}{9}$$

$$h_{12} = \frac{U_1}{I_2} = \frac{3 \times 4}{2+3+4} = \frac{12}{9} = \frac{4}{3}$$

$$h_{22} = \frac{I_2}{U_2} = \frac{I_2}{I_2 \cdot R_{eq}}$$

$$= \frac{1}{R_{eq}} = \frac{1}{20/9} = \frac{9}{20} \Omega^{-1}$$

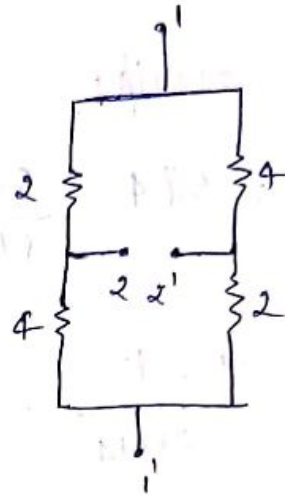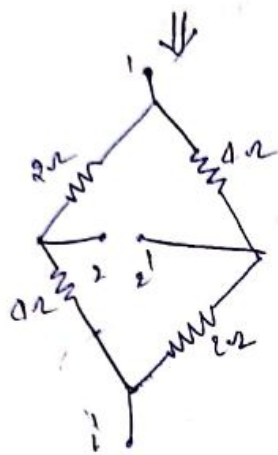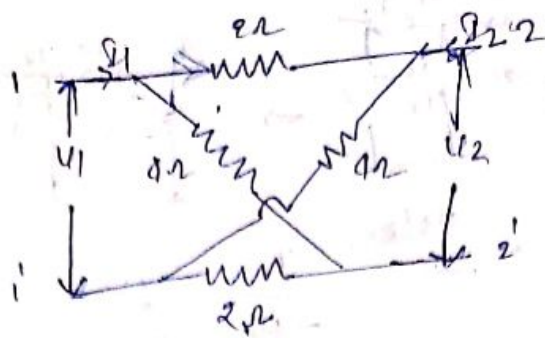→ find $z, Y, ABCD, b$ -parameters for given circuit.



z-parameters:-

when $I_2 = 0$ port-2 open ckt

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2 = 0}$$

$$= \frac{I_1 \cdot R_{eq}}{I_1} = R_{eq}$$

$$R_{eq} = (2+4) \parallel (2+4)$$

$$= 6 \parallel 6 = 3\Omega$$


$$z_{11} = 3\Omega$$

$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2 = 0}$$

V_2 = V_{drop} at 2Ω + V_{drop} at 4Ω

$$= 2 \cdot \frac{I_1}{2} + 4 \cdot \frac{I_1}{2} = 3I_1$$


$$z_{21} = \frac{3I_1}{I_1} = 3\Omega$$

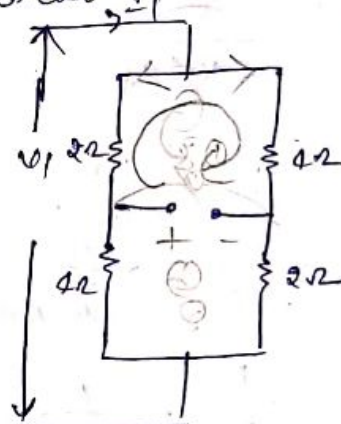

when $I_2 = 0$ port-1 is open circuit.


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{V_2 \cdot R_{eq}}{I_2}$$

$$= R_{eq}$$

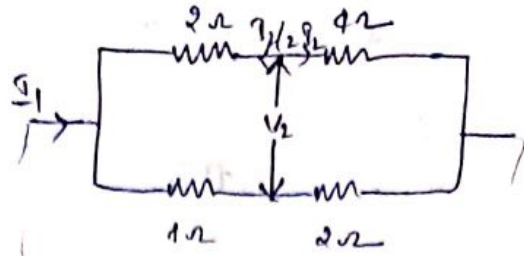

$$R_{eq} = (2+4) \parallel (2+4)$$

$$= 3 \Omega$$

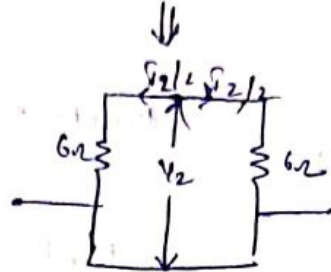

$$Z_{22} = 3 \Omega$$



$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{6 \cdot \frac{I_2}{2}}{I_2}$$

$$= 3 \Omega$$

$$\frac{0 \cdot I_2}{2} - \frac{2 \cdot I_2}{2} = -I_2$$


Y-parameters:-

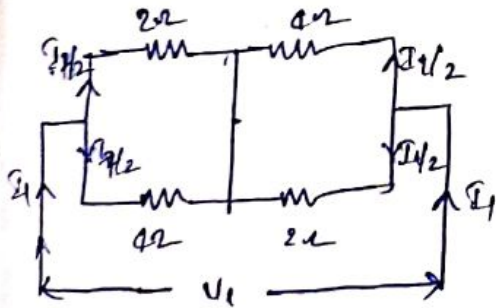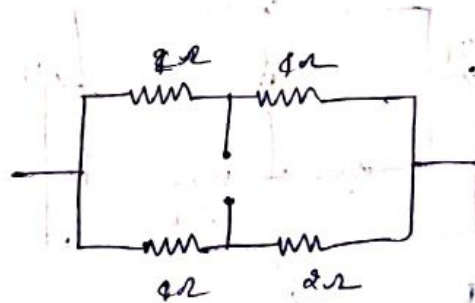when $I_2 = 0$, the port-2 is short circuited



$$Y_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} = \frac{V_1 / R_{eq}}{V_1}$$

$$= \frac{1}{R_{eq}} \text{ u}$$

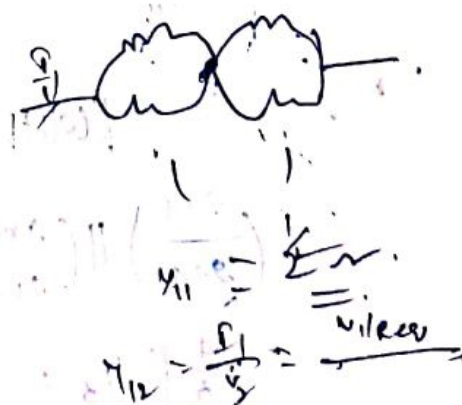

$$R_{eq} = (2 \parallel 4) \parallel (2 \parallel 4)$$

$$= \frac{2 \times 4}{2+4} \parallel \frac{2 \times 4}{2+4} = \frac{4}{3} \parallel \frac{4}{3}$$

$$= \frac{4/3 \times 4/3}{\frac{4}{3} + \frac{4}{3}} = \frac{16/9}{2/3}$$

$$= \frac{16}{9} \times \frac{3}{2} = 8/3 \Omega$$


$$Y_{11} = \frac{1}{R_{eq}} = \frac{1}{8/3} = \frac{3}{8} \text{ S}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{\text{Current through } 2\Omega + \text{Current through } 4\Omega}{V_1}$$

$$= \frac{I_1/2 + I_1/2}{I_1 \cdot R_{eq}} = \frac{I_1}{R_{eq} \cdot I_1}$$

$$= \frac{1}{R_{eq}} = \frac{3}{8} \text{ S} = -1/3 \text{ S}$$

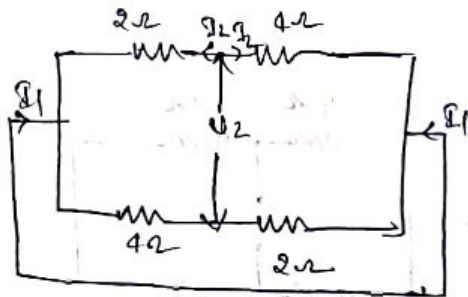when $V_1 = 0$, the port-1 is short-circuited.



$$Y_{22} = \frac{I_2}{V_2} = \frac{1}{I_2 \cdot R_{eq}} = \frac{1}{R_{eq}}$$

$$R_{eq} = (2 \parallel 4) \parallel (2 \parallel 4)$$

$$= \left(\frac{2 \times 4}{2+4} \right) \parallel \left(\frac{2 \times 4}{2+4} \right)$$

$$= \frac{4}{3} \parallel \frac{4}{3} = \frac{\frac{4}{3} \times \frac{4}{3}}{\frac{4}{3} + \frac{4}{3}} = \frac{16/9}{2/3}$$

$$= \frac{16}{9} \times \frac{3}{2} = 8/3$$

$$V_{22} = \frac{1}{8/3} = 3/8 \text{ V}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = 0$$

= current through 2Ω + current through 4Ω



$$= \frac{V_2}{2\Omega + 4\Omega} = \frac{V_2}{6\Omega}$$

$$= \frac{1}{6\Omega} = 1/6 \text{ S}$$

ABCD-parameters :-

when $I_2 = 0$

part-2 open circuited

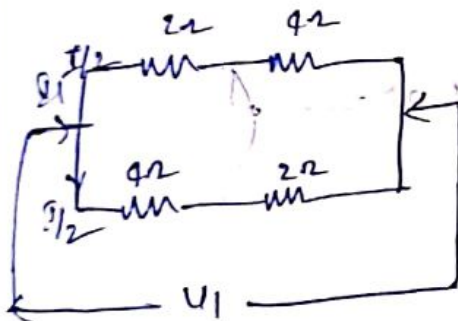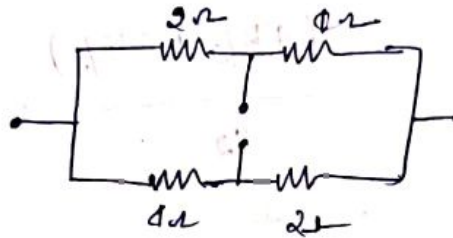

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2} = \frac{I_1 \cdot R_{eq}}{V_2}$$

(v drop at 4Ω + v drop at 2Ω)

$$R_{eq} = (2+4) \parallel (4+2)$$


$$= 6 \parallel 6 = 3\Omega$$

$$V_2 = 2I_1/2 + 4I_1/2 = 3I_1$$

$$A = \frac{I_1 \cdot 3\Omega}{3I_1} = 1$$

$$C_2 \frac{I_1}{V_2} = \frac{I_1}{\Delta I_1} = \frac{1}{\Delta}$$

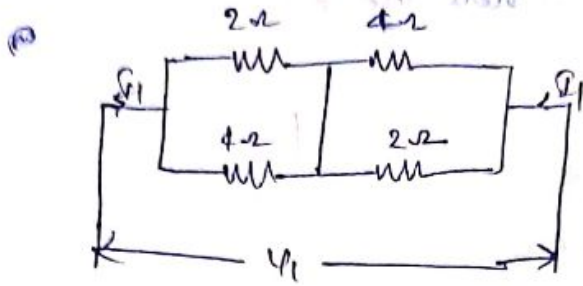when $V_2 = 0$ - the port 2 is short-circuited




$$B = \frac{-V_1}{I_2} = - \frac{(V_{drop\ at\ 4\ \Omega} + V_{drop\ at\ 2\ \Omega})}{I_2}$$

$$= - \frac{(4I_2/2 + 2I_2/2)}{I_2} = \frac{-3I_2}{I_2} = -3$$

$$D_2 \frac{I_2}{I_1} = \frac{-I_1}{I_2} = \frac{-I_1}{\frac{I_1 + I_1}{2}} = -1$$

current at 4Ω + current at 2Ω


H-parameters:-

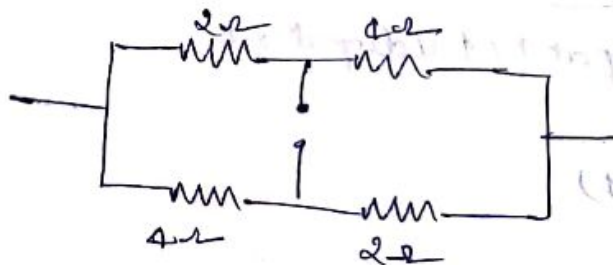

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

when V_2 port 2 is short circuited

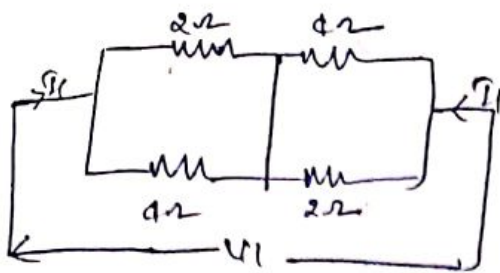

$$h_{11} = \frac{V_1}{I_1}$$

$$= \frac{I_1 \cdot R_{eq}}{I_1} = R_{eq}$$

$$R_{eq} = (2 \parallel 4) \parallel (2 \parallel 4)$$


$$= 8/3$$

$h_{11} = 8/3 \Omega$

$$h_{21} = \frac{I_2}{I_1} = \frac{\text{current through } 2\Omega + \text{current through } 4\Omega}{I_1}$$

$$= \frac{I_1(2/2 + 4/2)}{I_1} = \frac{I_1(1 + 2)}{I_1} = \frac{3I_1}{I_1} = 3$$

when I_2 port 2 is open circuit

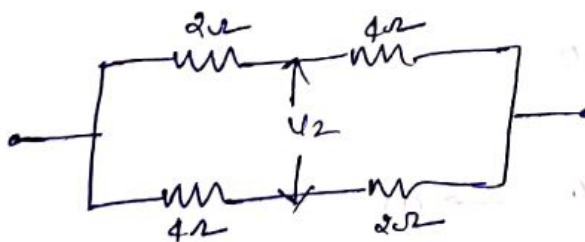

$$h_{22} = \frac{I_2}{V_2} = \frac{I_2}{I_2 \cdot R_{eq}} = \frac{1}{R_{eq}}$$


$$R_{eq} = (2+4) \parallel (2+4) = 6 \parallel 6$$

$$= 3 \Omega$$


$h_{22} = \frac{1}{3} \text{ V}$

$$h_{22} = \frac{I_2}{V_1} = \frac{I_2}{I_2/2 + I_2/2} = \frac{I_2}{I_2} = 1$$

* find z & y - parameters

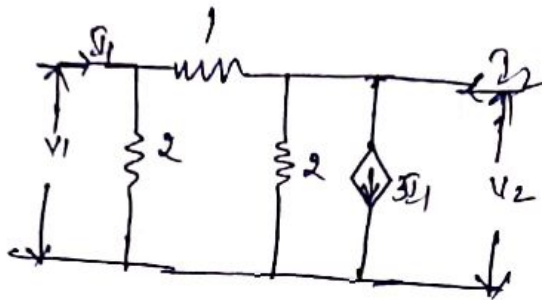

when $I_2 = 0$, port-2 open

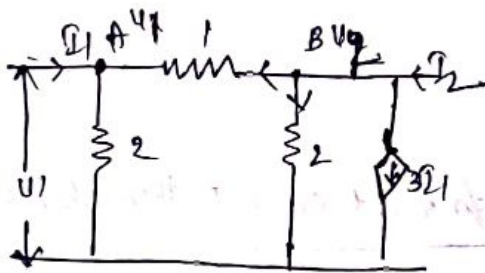

Current from high potential to low potential

Apply KCL at node B

$$I_2 = 3I_1 + \frac{V_2}{2} + \frac{V_2 - V_1}{1}$$

$$3I_1 + \frac{V_2}{2} + V_2 - V_1 = 0$$

$$3I_1 + \frac{3V_2}{2} - V_1 = 0 \rightarrow (1)$$

Apply KCL at node A

$$I_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{1} \rightarrow (2)$$

substitute (2) into

$$3 \left[\frac{3V_1}{2} - V_2 \right] + \frac{3V_2}{2} - 4V_1 = 0$$

$$\frac{9V_1}{2} - 3V_2 + \frac{3V_2}{2} - 4V_1 = 0$$

$$\frac{7V_1}{2} - \frac{5V_2}{2} = 0$$

$$3V_1 + \frac{3}{2} \left[\frac{3V_1}{2} - V_1 \right] - 4V_1 = 0$$

$$3V_1 + \frac{9}{4}V_1 - \frac{3}{2}V_1 - 4V_1 = 0$$

$$\frac{3}{2}V_1 + \frac{5}{4}V_1 = 0$$

$$\frac{3}{2}V_1 = -\frac{5}{4}V_1$$

$$\frac{3}{2} \left| \frac{V_1}{2} = \frac{V_1}{2} \right|$$

$$\frac{3}{2} \times \frac{2V_1}{2} = -\frac{6}{5}$$

2212

$$\frac{V_2}{V_1} \Big|_{2220}$$

$$\boxed{211 = -6/5}$$



$$V_1 = \left[\frac{3V_1 + 3V_2}{2} \right] + \left[\frac{3V_1 + 3V_2}{2} \right] - 4V_2$$

$$= \frac{3V_1}{2} + \frac{3V_2}{4} + \frac{3V_1}{2} + \frac{3V_2}{2} - 4V_2$$

$$V_1 = \frac{3V_1}{2} + \frac{5V_2}{4}$$

$$-\frac{7V_1}{2} = \frac{5V_2}{4} \Rightarrow \frac{V_2}{V_1} = \frac{-7 \times 2}{5} = -\frac{14}{5}$$

when $S_1=0$; port -1 is open circuit

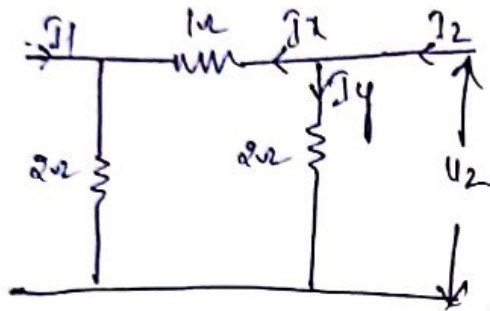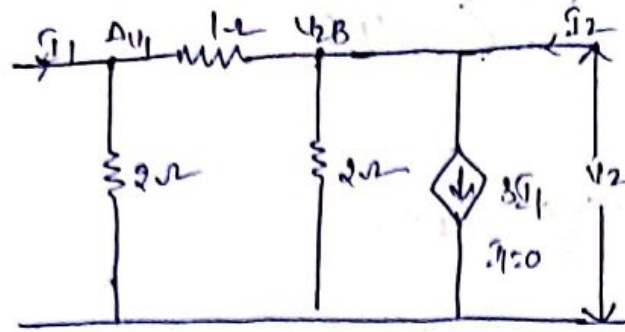

$$Z_{12} = \frac{V_2}{I_2} = \frac{R_{eq} \cdot I_2}{I_2}$$

$$R_{eq} = (1+2) \parallel 2 = \frac{3 \times 2}{3+2} = \frac{6}{5}$$


$$Z_{12} = \frac{6}{5} \Omega$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{I_1 \cdot 2}{I_2} = \frac{\cancel{I_2} \cdot \frac{2}{1+2+2} \cdot 2}{\cancel{I_2}}$$


$$Z_{12} = \frac{4}{5} \Omega$$

Y-parameters

when $V_2 = 0$; port-2 is short-circuit

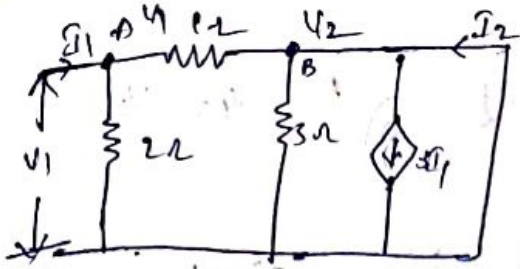

apply \Downarrow

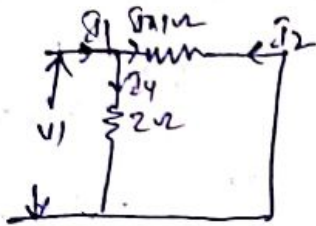


$$Y_{11} = \frac{I_1}{V_1} = \frac{Y_{11} R_{eq}}{V_1} = \frac{1}{R_{eq}}$$

$$R_{eq} = 1 \parallel 2 = \frac{2}{3}$$


$$V_1 = 3/2 V$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{-I_1}{2 \cdot 3/2} = -\frac{1}{2} = -\frac{I_1}{R_{eq}} = \frac{-I_1 \cdot \frac{2}{V_1}}{2 \cdot 1/1.5} = -1$$

when $V_1 = 0$; port-1 is short-circuit

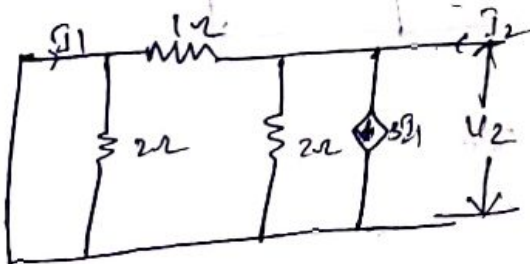

\Downarrow

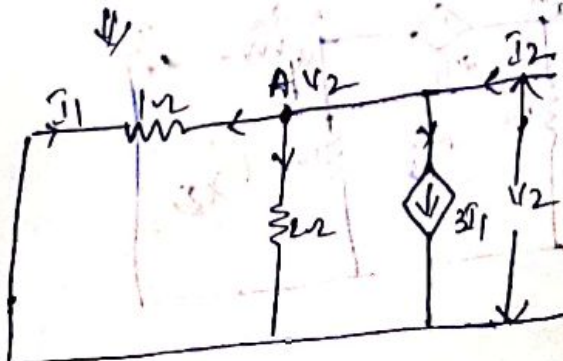

Apply KCL at node A:

$$\frac{V_2}{1} + \frac{V_2}{2} + 3I_1 = I_2$$

But $I_1 = -\frac{V_2}{1}$

~~$$\frac{3V_2}{2} = I_2 - 3I_1 \Rightarrow$$~~

~~$$\frac{3V_2}{2} = I_2 - 3(-\frac{V_2}{1})$$~~

$$\frac{V_2}{1} + \frac{V_2}{2} - 3V_2 = I_2$$

$$\frac{3V_2}{2} - 3V_2 = I_2$$

~~$$Y_{22} = \frac{I_1}{V_2} = \frac{I_2}{V_2} = \frac{-V_2}{V_2} = -1 \Omega$$~~


$$-3V_2 = I_2$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{I_2}{V_2} = -3/2 \Omega$$

* find y-parameters then find h-parameters.



when $V_2 = 0$; port 2 is short ckt

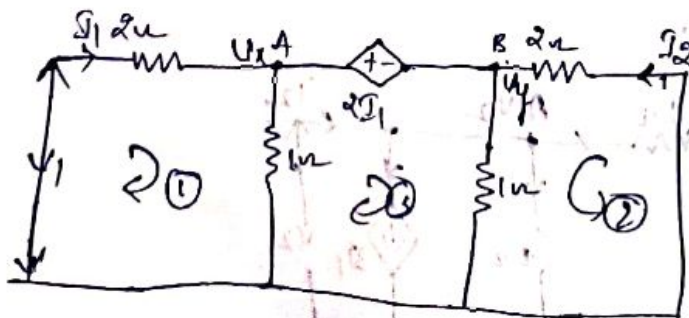

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Apply KCL for the loops

$$\text{loop 1} - 3I_1 - I_3 = 41 \rightarrow (1)$$

$$\text{loop 2} - 3I_2 + I_3 = 0 \rightarrow (2)$$

$$I_3 = -3I_2$$

$$\text{loop 3} - 2I_3 + I_2 - I_1 = -2I_1 \rightarrow (3)$$

$$(1) \Rightarrow 3I_1 - (-3I_2) = 41$$

$$\boxed{3I_1 + 3I_2 = 41} \rightarrow (4)$$

$$(3) \Rightarrow 2(-3I_2) + I_2 - I_1 + 2I_1 = 0$$

$$-6I_2 + I_2 + I_1 = 0$$

$$\boxed{I_1 - 5I_2 = 0} \rightarrow (5)$$

using (4) & (5) eqns

$$41 = \frac{I_1}{5}$$

$$I_1 = 5I_2$$

$$I_2 = I_1/5$$

$$3I_1 + 3[I_1/5] = 41$$

$$\frac{18I_1}{5} = 41$$

$$I_1 = \frac{41}{18} = \frac{5}{18}$$


$$V_{21} = \frac{I_2}{41} \quad \text{using (4) \& (5) equations}$$

$$: \frac{I_2}{361} (18I_2 + 3I_2) = 41$$

$$18I_2 = 41$$

$$V_{21} = \frac{I_2}{41} = \frac{1}{18} \text{ V}$$

when $V_1 = 0$; port-(1) is short ckt

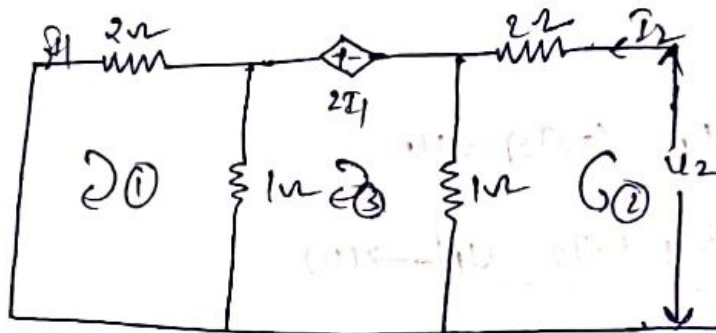

Apply KVL for loops

$$\text{Loop-1} \Rightarrow 3I_1 - I_3 = 0$$

$$I_3 = 3I_1 \rightarrow (1)$$

$$\text{Loop-2} \Rightarrow 3I_2 - I_3 = V_2$$

$$3I_2 - 3I_1 = V_2 \rightarrow (2)$$

$$\text{Loop-3} \Rightarrow 2I_3 + I_2 - I_1 = -2I_1$$

$$2(3I_1) + I_2 - I_1 = -2I_1$$

$$5I_1 + I_2 = 0 \rightarrow (3)$$

$$V_{22} = \frac{I_2}{V_2}$$

from eqn (2) & (3)

$$3I_2 - 3\left[-\frac{I_2}{5}\right] = V_2$$

$$3I_2 + \frac{3I_2}{5} = V_2$$

$$\frac{18I_2}{5} = V_2$$

$$V_{22} = \frac{I_2}{V_2} = \frac{5}{18} \Omega$$

$V_{12} =$ from eqn (2) & (3)

$$= \frac{I_1}{V_2}$$

$$3(-5I_1) - 3I_1 = V_2$$

$$-18I_1 = V_2$$

$$\boxed{V_{12} = \frac{I_1}{V_2} = -\frac{1}{18} \Omega}$$

$$h_{11} = \frac{1}{Y_{11}} = \frac{18}{5} \Omega \quad h_{21} = \frac{V_{21}}{Y_{11}} = \frac{1/18}{5/18} = \frac{1}{5}$$

$$h_{12} = \frac{-Y_{12}}{Y_{11}} = \frac{-(-1/18)}{5/18} = \frac{1/18}{5/18} = \frac{1}{5}$$

$$h_{22} = \frac{Y_{11}V_{22} - V_{21}Y_{12}}{Y_{11}} = \frac{\frac{5}{18} \cdot \frac{5}{18} - \frac{1}{18} \cdot \frac{1}{18}}{5/18} = \frac{\frac{25}{324} - \frac{1}{324}}{5/18} = \frac{\frac{24}{324}}{5/18} = \frac{4}{18} / \frac{5}{18} = \frac{4}{5} \Omega$$