

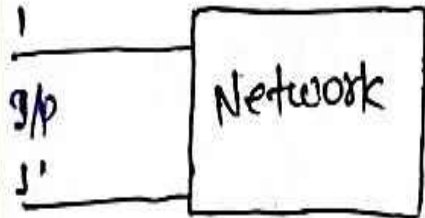


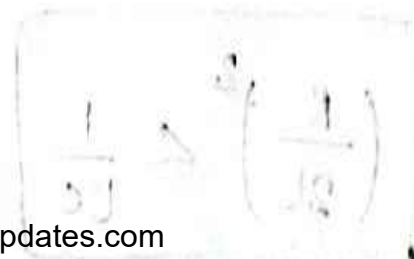* One port Network :- A port is defined as any pair of terminals into which energy is drawn or which energy is supplied.



A network having only one pair of terminals (11') is known as one port network.

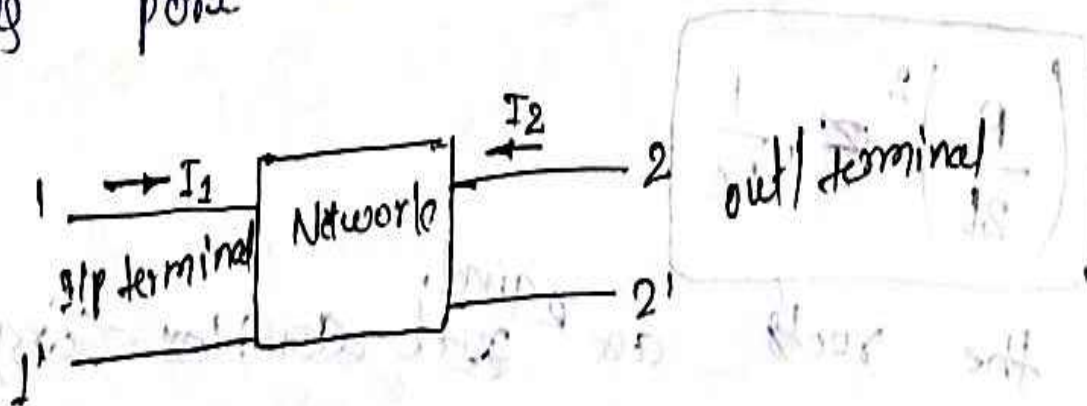* Two port Network! A Network which has two pairs of terminals one is input terminal and second one is output terminals the two terminals port are (11'), (22')




Active Networks :- If two ports have Sources in their branches is known as Active ports.

Passive ports :- If the two ports do not contain any Sources in their branches is known as passive ports.

* To describe two port Network there are Six parameters.

- (i) Open circuit impedance parameters (or) Z parameters
- (ii) Short circuit admittance " (or) Y " "
- (iii) Transmission " (or) ABCD " "
- (iv) Inverse Transmission " (or) A'B'C'D' " "
- (v) Hybrid Parameters (or) h Parameters
- (vi) Inverse hybrid " " (or) g " "

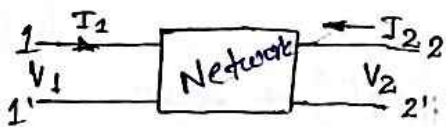(i) Open circuit impedance parameters (or) Z parameters.



The general eqn for Z parameters is given by

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (i)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (ii)}$$

Where

$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$ are the network functions and also called as impedance parameters

To calculate this parameter two variables are defined by equating to zero.

Let $I_2 = 0$ in eqn (i) then

$$V_1 = Z_{11}I_1$$

$$Z_{11} = \frac{V_1}{I_1} \quad \left(\text{Where } I_2 = 0 \right)$$

Where Z_{11} is driving point impedance at port 1 by open circuiting second port it is called as open circuit input impedance.

iii)

Put

$$I_2 = 0 \text{ in (ii)}$$

then

$$Z_{21} = \frac{V_2}{I_1} \text{ (where } I_2 = 0 \text{) (open circuit forward transfer impedance)}$$

This Z_{21} is called as open circuit forward transfer impedance.

By open circuiting input port (ii) that is $I_1 = 0$ in (i)

$$V_1 = Z_{12} I_2$$

$$Z_{12} = \frac{V_1}{I_2} \text{ (where } I_1 = 0 \text{)}$$

Where

Z_{12} is known as open circuit reverse transfer impedance.


By substituting $I_1 = 0$ in eqn (iii)

$$V_2 = Z_{22} I_2$$

$$Z_{22} = \frac{V_2}{I_2} \text{ (where } I_1 = 0 \text{)}$$

Where Z_{22} is known as open circuit output impedance.

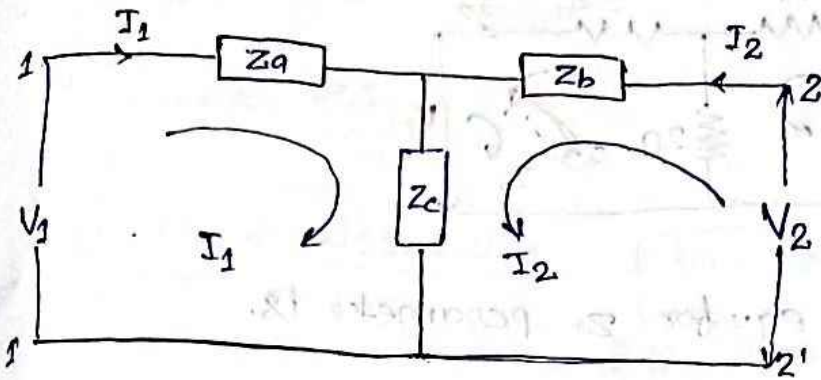* For the given network determine Z parameters :-



The generalised eqn for Z parameters is,

$$Z_{11}I_1 + Z_{12}I_2 = V_1$$

$$Z_{21}I_1 + Z_{22}I_2 = V_2$$

By applying taking loop eqn.

gn loop (i)

$$I_1 Z_a + (I_1 + I_2) Z_c = V_1$$

$$V_1 = I_1(Z_a + Z_c) + I_2 Z_c \quad \text{--- (i)}$$

gn loop (ii) nd.

$$Z_b I_2 + (I_2 + I_1) Z_c = V_2$$


$$(Z_b + Z_c) I_2 + (Z_c) I_1 = V_2 \quad \text{--- (ii)}$$

By comparing (i) & (ii) from generalised eqn of Z-parameters,

$$Z_{11} = (Z_a + Z_c), \quad Z_{12} = Z_c$$

$$Z_{21} = Z_c, \quad Z_{22} = Z_b + Z_c$$

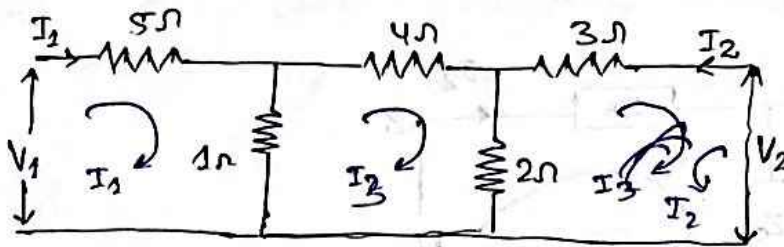Determine z-parameters for given problem.



The generalise equ for z-parameter is.

$$Z_{11}I_1 + Z_{12}I_2 = V_1$$

$$Z_{21}I_1 + Z_{22}I_2 = V_2$$

loop equ

$$V_1 = 5I_1 + 1(I_1 - I_3)$$

$$V_1 = 6I_1 - I_3 \quad \text{--- (i)}$$

$$I_3 = 6I_1 - V_1$$

$$V_2 = 3I_2 + 2I_2 + 2I_3$$

$$V_2 = 5I_2 + 2I_3 \quad \text{--- (ii)}$$

$$V_2 = 5I_2 + 2(6I_1 - V_1)$$

$$4I_3 + 2I_3 + 2I_2 + I_3 - I_1 = 0$$

$$7I_3 - I_1 + 2I_2 + 7I_3 = 0$$

$$I_3 = \frac{I_1 - 2I_2}{2} \quad \text{--- (iii)}$$

Sub (iii) in (i) & (iii),

$$V_1 = 6I_1 - \frac{I_1 + 2I_2}{7}$$

$$V_1 = \frac{42I_1 - I_1 + 2I_2}{7}$$

$$V_1 = \frac{41I_1 + 2I_2}{7}$$

$$V_1 = 5.85I_1 + 0.285I_2$$

Sub (iii) in (ii)

By comparing generalised eqn of Z-parameters

$$\begin{matrix} Z_{11} = 5.85 \\ Z_{12} = 0.285 \end{matrix}$$

$$V_2 = 5I_2 + 2 \left(\frac{I_1 - 2I_2}{7} \right)$$

$$V_2 = \frac{35I_2 + 2I_1 - 4I_2}{7}$$


$$V_2 = \frac{31I_2 + 2I_1}{7}$$

$$V_2 = 4.42I_2 + 0.285I_1$$

By comparing generalised eqn of Z-parameters

$$Z_{21} = 0.285, Z_{22} = 4.42$$

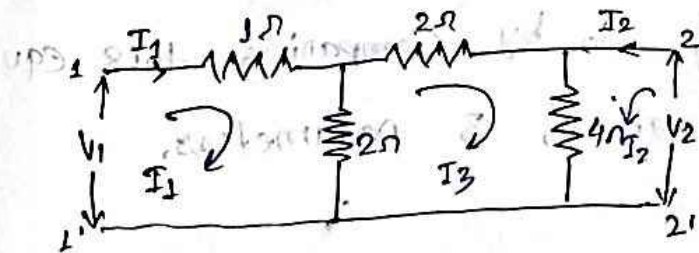* Determine Z-parameters for given problem.



The generalised eqn for Z-parameters

$$Z_{11}I_1 + Z_{12}I_2 = V_1$$

$$Z_{21}I_1 + Z_{22}I_2 = V_2$$

Applying KVL for loop (i)

$$1I_1 + 2(I_1 - I_3) = V_1$$

$$\boxed{3I_1 - 2I_3 = V_1} \quad \text{--- (i)}$$

Applying KVL for loop (ii)

$$\boxed{4I_2 + 4I_3 = V_2} \quad \text{--- (ii)}$$

Applying KVL for loop (iii)

$$2(I_3 - I_1) + 2I_3 + 4I_3 + 4I_2 = 0$$

$$-2I_1 + 8I_3 + 4I_2 = 0$$

$$\boxed{I_3 = \frac{-4I_2 + 2I_1}{8}} \quad \text{--- (iii)}$$

Sub (iii) in (i) & (ii)

Sub (iii) in (i)

$$3I_1 - 2\left(\frac{-4I_2 + 2I_1}{8}\right) = V_1$$

$$\frac{12I_1 + 4I_2 - 2I_1}{4} = V_1$$

$$\frac{10I_1 + 4I_2}{4} = V_1$$

$\boxed{2.5I_1 + I_2 = V_1}$ So by comparing this eqn with generalise eqn of 3 parameters.

$$\boxed{\begin{matrix} Z_{11} = 2.5 \\ Z_{12} = 1 \end{matrix}}$$

sub (iii) in (ii),

$$4I_2 + 4 \left[\frac{-4I_2 + 2I_1}{8} \right] = V_2$$

$$4I_2 - 2I_2 + I_1 = V_2$$


$$2I_2 + I_1 = V_2$$

$$I_1 + 2I_2 = V_2$$

By Comparing this equ with generalise equ of Z parameters,

$$Z_{21} = 1, \quad Z_{22} = 2$$

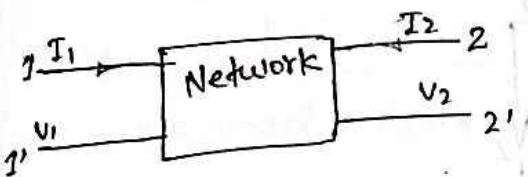Short Circuit Admittance (or) Y Parameters :-
 Y-Parameter



Here, \$V_1, V_2\$ - independent Variable.
 \$I_1, I_2\$ - dependent Variable.

The generalised equations are.

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (i)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (ii)}$$

Short circuiting the o/p port
 put \$V_2 = 0\$ in equ (i)

then $I_1 = Y_{11}V_1$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

\$Y_{21}\$ - input transfer admittance

put \$V_2\$ in equ (ii) Y_{11} - short circuit I/P admittance.

\$V_2 = 0\$ in equ (ii)

$$I_2 = Y_{21}V_1$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

Put $V_1 = 0$ in eqn (i) Short circuiting the I^r shorted port.

$$I_1 = Y_{12} V_2$$

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1 = 0}$$

$Y_{12} \rightarrow$ output transfer admittance


Put $V_1 = 0$ in eqn (ii)

$$I_2 = Y_{22} V_2$$

$$Y_{22} = \frac{I_2}{V_2} \bigg|_{V_1 = 0}$$

$Y_{22} \rightarrow$ Short circuit output admittance.

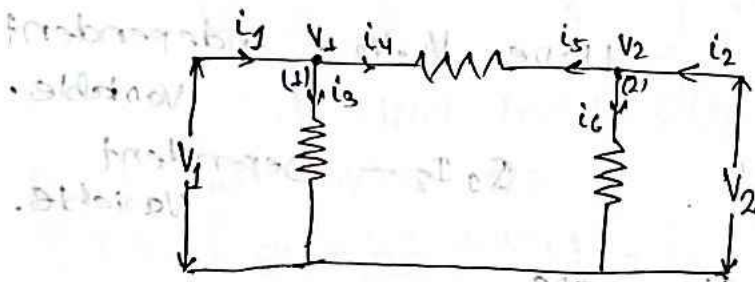* Determine Y-Parameters for the CRT shown in fig.



Assuming at from node (1) i_3 & i_4

& at node (2) i_5 & i_6 .

At node 1, applying KCL

$$i_1 = i_3 + i_4$$

$$i_1 = i_3 + i_4$$

$$i_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{2}$$

$$i_1 = V_1 - \frac{V_2}{2} \quad \text{--- (1)}$$

At node 2, applying KCL

$$i_2 = i_5 + i_6$$

$$i_2 = \frac{V_2 - V_1}{2} + \frac{V_2}{6}$$

$$i_2 = -\frac{V_1}{2} + \frac{V_2}{3} \quad \text{--- (2)}$$

The generalised eqn of Y-parameters are.

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$


$$Y_{11} = 12S, \quad Y_{12} = -0.52S$$

$$Y_{21} = -0.52S, \quad Y_{22} = 12S$$

Here $Y_{11} = Y_{22}$ this condition is called as Condition for Symmetric.

If $Y_{12} = Y_{21}$ then this is called as Condition for reciprocity.

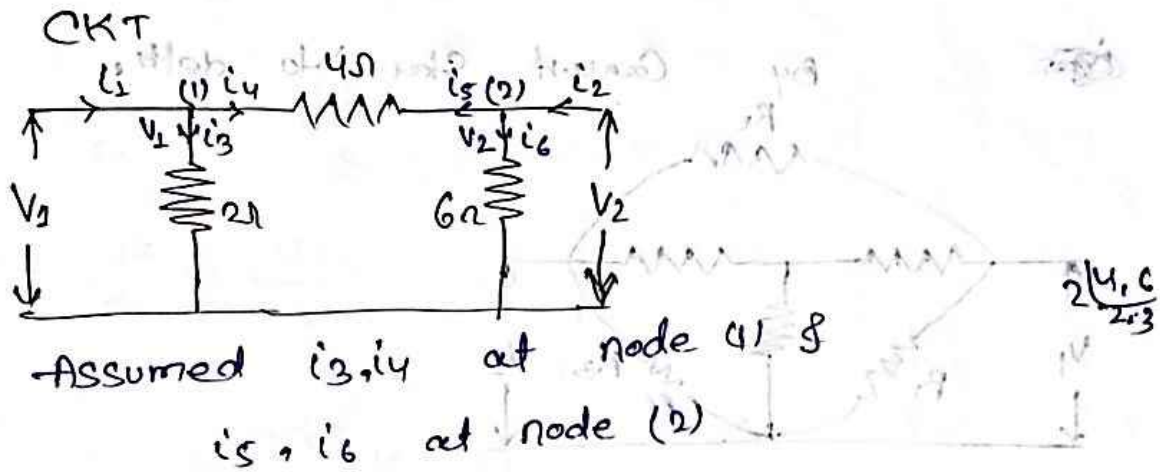* Determine the Y-parameters for the given



At node (1) applying KCL,

$$i_1 = i_3 + i_4$$

$$i_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{4} \quad \text{--- (1)}$$

$$i_1 = \frac{2V_1 + V_1 - V_2}{4}$$

$$i_1 = \frac{3V_1 - V_2}{4}$$

At node (2) by applying KCL

$$i_2 = i_5 + i_6$$

$$i_2 = \frac{V_2 - V_1}{4} + \frac{V_2}{6}$$

$$i_2 = \frac{3V_2 - 3V_1 + 2V_2}{12}$$

$$i_2 = \frac{5V_2 - 3V_1}{12}$$

$$i_2 = \frac{5V_2}{12} - \frac{V_1}{4}$$

$$i_2 = -\frac{V_1}{4} + \frac{5V_2}{12}$$

The generalised eqn for Y -parameters is


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = 0.75 \text{ S}, Y_{12} = 0.25 \text{ S}$$


$$Y_{21} = -0.25 \text{ S}, Y_{22} = 0.4167 \text{ S}$$

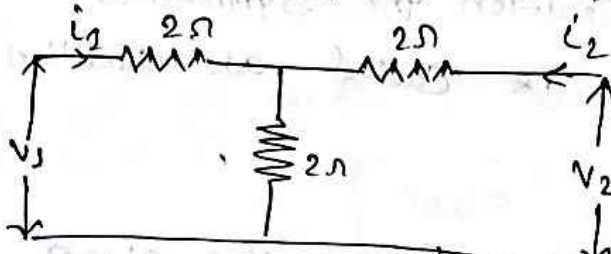Determine Y -parameters for the given CKT.




~~Applying KCL at node (1)~~

~~By~~ Convert Star into delta.

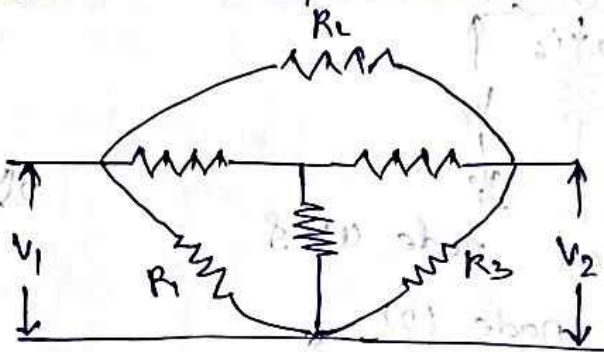

$$R_1 = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
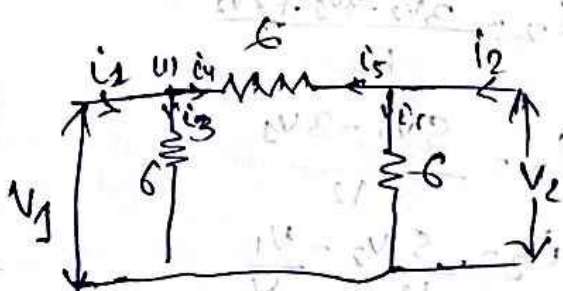
$$R_1 = \frac{2 \times 2 + 2 \times 2 + 2 \times 2}{2} = 6 \Omega$$



Applying KCL at Node (1).

$$i_1 = \frac{V_1}{6} + \frac{V_1 - V_2}{6}$$

$$i_1 = \frac{V_1}{3} - \frac{V_2}{6} \quad \text{--- (1)}$$

$$i_2 = -\frac{V_1}{6} + \frac{V_2}{3}$$


$$i_2 = \frac{2V_2 - V_1}{6}$$

$$Y_{11} = 0.33 \text{ S}$$

$$Y_{21} = -0.16 \text{ S}$$

$$Y_{12} = -0.16 \text{ S}$$

$$Y_{22} = 0.33 \text{ S}$$

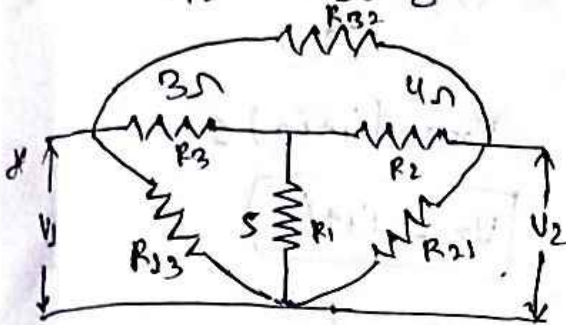


$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{5 \times 4 + 4 \times 3 + 3 \times 5}{4}$$

$$R_{23} = \frac{20 + 12 + 15}{4} = \frac{47}{4}$$

$$R_{21} = \frac{47}{3} = \frac{47}{3}$$

$$R_{32} = \frac{47}{5} = \frac{47}{5}$$

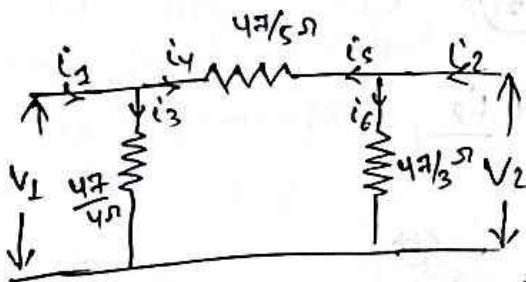

Applying KCL at node (1) Applying KCL at node (2)

$$i_1 = \frac{4V_1}{47} - \frac{5(V_1 - V_2)}{47}$$

$$i_2 = \frac{3V_2}{47} + \frac{(V_2 - V_1)5}{47}$$

$$i_2 = \frac{3V_2 + 5V_2 - 5V_1}{47}$$

$$i_1 = \frac{4V_1 + 5V_1 - 5V_2}{47}$$

$$i_2 = \frac{8V_2 - 5V_1}{47}$$

$$i_1 = \frac{9V_1}{47} - \frac{5V_2}{47}$$


$$i_2 = \frac{-5V_1 + 8V_2}{47}$$

Generate eqn for Y-parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \Rightarrow Y_{11} = \frac{9}{47} = 0.1915, Y_{12} = -0.106$$

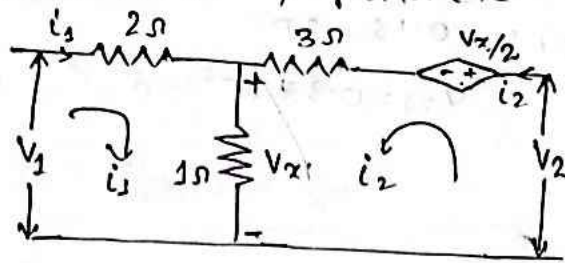* Determine Y parameters for the given CKT.



$V_x =$ Voltage drop across 1Ω

$$V_x = (i_1 + i_2) \cdot 1$$

$$V_x = i_1 + i_2$$

~~$V_x =$ Voltage drop~~

At loop (i) By applying KVL,

$$2i_1 + 1(i_1 + i_2) = V_1$$

$$3i_1 + i_2 = V_1 \quad \text{--- (i)}$$

At loop (ii) By applying KVL

$$3i_2 + 1(i_1 + i_2) + \frac{V_x}{2} = V_2$$

$$V_x = i_1 + i_2 \quad ; \quad 3i_2 + i_1 + i_2 + \frac{i_1 + i_2}{2} = V_2$$

$$V_2 = i_1 + 4i_2 + \frac{V_x}{2} \quad \text{--- (ii)}$$

$$V_2 = i_1 + 4i_2 + \frac{i_1}{2} + \frac{i_2}{2}$$

$$V_2 = \frac{3}{2}i_1 + \frac{9}{2}i_2 \quad \text{--- (iii)}$$

By (i) & (iii) $\frac{3}{2}$ multiply in (i)

~~$$V_2 = i_1 + 4i_2 + \frac{i_1 + i_2}{2} = V_2 \quad \times \frac{3}{2}$$~~

$$\frac{9}{2}i_1 + \frac{9}{2}i_2 = \frac{3}{2}V_1$$

$$\frac{9}{2}i_1 + \frac{9}{2}i_2 = V_2$$

$$\frac{3}{2}i_2 - \frac{7}{2}i_2 = \frac{3}{2}V_1 - V_2$$

$$-2i_2 = \frac{3}{2}V_1 - V_2$$


$$i_2 = -\frac{3}{4}V_1 + \frac{1}{2}V_2$$

ABCD (or) ^{Transmission} parameters.

Let us consider a network consisting of input variables at port 1 1' and output variables V_2 & I_2 at port 2 2'. The port 1 1' is called as sending end port and the port 2 2' is called as receiving end port.

The ABCD parameters provide a direct relationship between input & output.

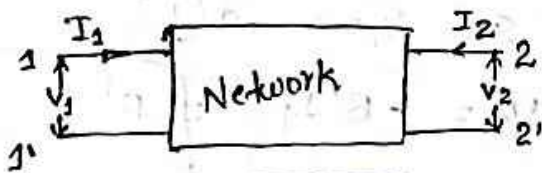The generalised equations for ABCD parameter is given by.



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Procedure:- By making the port 2 2' open that is $I_2 = 0$.

$$V_1 = AV_2 - BI_2 \quad \text{--- (i)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (ii)}$$

By open circuit at port 2 2', Then equ. (i) becomes

$$V_1 = AV_2 - B(0) \quad ; \quad V_1 = AV_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

Substitute $I_2 = 0$ in equ. (ii)

$$I_1 = CV_2 - D(0)$$

$$I_1 = CV_2$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

By short circuiting the port 2' that is $V_2 = 0$ in eqn (1)

$$V_1 = A(0) - B(I_2) =$$

$$B = \frac{-V_1}{I_2} \Big|_{V_2=0}$$


then ~~in eqn~~

By sub the $V_2 = 0$ in eqn (1)

$$I_1 = 0 - D'I_2$$

$$D' = \frac{-I_1}{I_2} \Big|_{V_2=0}$$

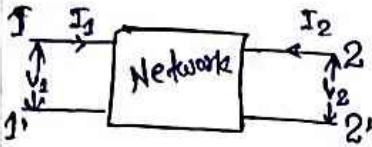* Inverse transmission parameters
(or) A'B'C'D' parameters.



Let us consider a network consisting of input variable at port 1' and output variable 2'. The port 1' is called as sending end port and the port 2' is called as receiving end port.

The A'B'C'D' parameters provided a direct relationship btw i/p & o/p

The generalised eqn for A'B'C'D' parameter is given by,

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$

Procedure:- By making the port 1' open that is $I_1 = 0$

Then eqn (1) becomes;

$$V_2 = A'V_1 - B'(0)$$

$$A' = \frac{V_2}{V_1} \Big|_{I_1=0}$$

By short CKT at port 1'

then $V_1 = 0$

Sub $V_1 = 0$ in (1)

$$V_2 = -B'I_1$$

$$B' = \frac{-V_2}{I_1} \Big|_{V_1=0}$$

Sub $I_2 = 0$ in (2)

$$I_2 = C'V_1 - D'I_1$$


$V_1 = 0$ in (2)

$$I_2 = -D'I_1$$

$$D' = \frac{-I_2}{I_1} \Big|_{V_1=0}$$

$$C' = \frac{I_2}{V_1} \Big|_{I_1=0}$$

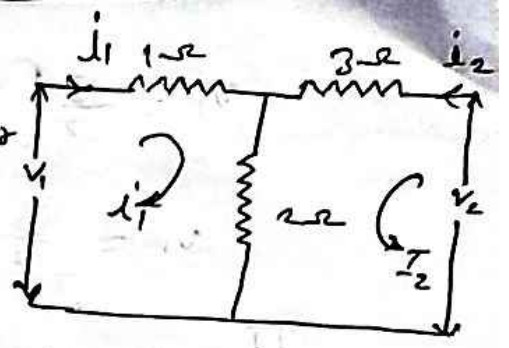Q. determine transmission parameter for the given circuit



By applying KVL for the loop ①

$$1i_1 + 2(i_1 + i_2) = V_1$$

$$3i_1 + 2i_2 = V_1 \quad \text{--- ①}$$

By applying KVL for the loop

$$3i_2 + 2(i_1 + i_2) = V_2$$

$$2i_1 + 5i_2 = V_2 \quad \text{--- ②}$$

The generalised equation for ABCD are

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

From eqn ①,

$$3i_1 + 2i_2 = V_1$$

$$3i_1 = V_1 - 2i_2$$

$$i_1 = \frac{V_1 - 2i_2}{3}$$

value of i_1 put in eqn ②



$$2\left(\frac{V_1 - 2i_2}{3}\right) + 5i_2 = V_2$$

$$\frac{2V_1}{3} - \frac{4i_2}{3} + 5i_2 = V_2$$

$$\frac{4i_2 + 15i_2}{3} = V_2 - \frac{2V_1}{3}$$

$$19i_2 = 3V_2 - 2V_1$$

$$V_1 = \frac{3}{2} \left[V_2 + - \frac{11}{3} I_2 \right]$$

$$V_1 = \frac{3}{2} V_2 - \frac{11}{2} I_2$$

The generalised eqn with comparing

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{3}{2}, B = \frac{11}{2}$$

$$3I_1 + 2I_2 = \frac{3}{2}V_2 - \frac{11}{2}I_2$$

$$3I_1 = \frac{3}{2}V_2 - \frac{11}{2}I_2 - 2I_2$$

$$3I_1 = \frac{3}{2}V_2 - \left[\frac{15}{2}I_2 \right]$$


$$I_1 = \frac{1}{2}V_2 - \frac{5}{2}I_2$$

The gene by comparing eqn with generalised eqn

$$I_1 = CV_2 - DI_2$$

$$C = \frac{1}{2}, D = -\frac{5}{2}$$

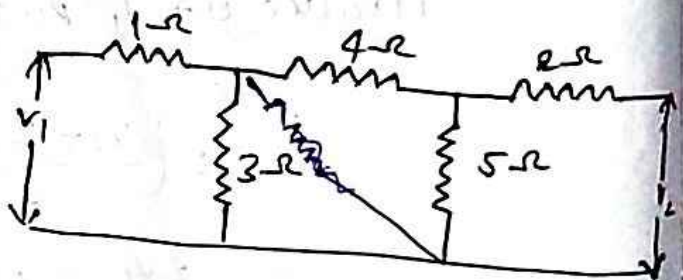Q. For the given circuit calculate ABCD parameters




convert the star connected system

$$R_a = \frac{3 \times 4}{3+4+5} = 1 \Omega$$

$$R_b = \frac{4 \times 5}{3+4+5} = 1.6 \Omega$$
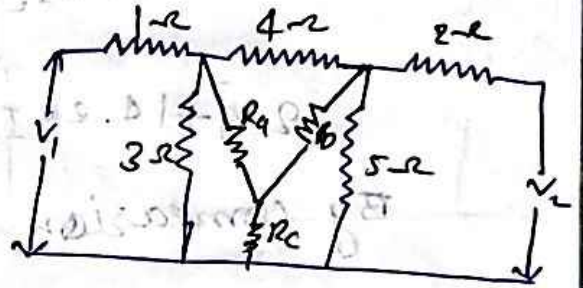
$$R_c = \frac{5 \times 3}{3+4+5} = 1.25 \Omega$$



By applying KVL

$$V_1 = 2I_1 + 1.25(I_1 + I_2)$$

$$V_1 = 3.25I_1 + 1.25I_2 \quad \text{--- (1)}$$

By applying KVL

$$V_2 = 3.6I_2 + 1.25(I_1 + I_2) =$$

$$V_2 = 4.85I_2 + 1.25I_1 \quad \text{--- (2)}$$

From eqn (1),

$$3.25I_1 + 1.25I_2 = V_1$$

$$3.25I_1 = V_1 - 1.25I_2$$


$$I_1 = \frac{V_1 - 1.25I_2}{3.25}$$

From eqn (2)

$$1.25 \left(\frac{V_1 - 1.25I_2}{3.25} \right) + 4.85I_2 = V_2$$

$$\frac{1.25V_1 - 1.56I_2}{3.25} + 4.85I_2 = V_2$$

$$1.25V_1 - 1.56I_2 + 15.76 = 3.25V_2$$

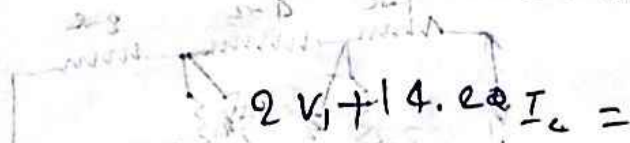

$$2V_1 + 14.2I_2 =$$

By comparison, the generalised eqn


$$A = 2, \quad B = -14.2$$

From

$$V_1 = 2.6V_2 - 11.3I_2$$

$$3.6I_2 + 1.25(I_1 + I_2)V_2 = V_1$$

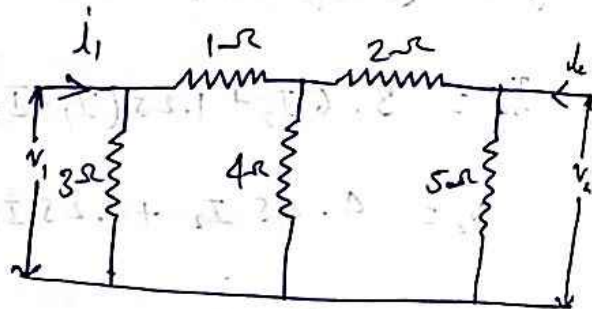8. Determine the
- (i) Z parameters
 - (ii) Y parameters
 - (iii) ABCD parameters



Determine the Z parameters following the given circuit

$$R_{a2} = \frac{1 \times 3 + 1 \times 4 + 4 \times 3}{3 + 4}$$


$$= \frac{7 + 3 + 4}{2.3}$$

$$R_b = 1 \times 3 +$$

$$R_a = \frac{1 \times 3}{1 + 3 + 4} = \frac{3}{8} = 0.375 \Omega$$

$$b = \frac{1 \times 4}{1 + 3 + 4} = \frac{4}{8} = 0.5 \Omega$$
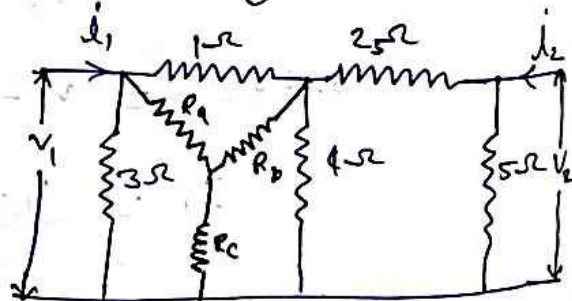
$$c = \frac{4 \times 3}{1 + 3 + 4} = \frac{12}{8} = \frac{3}{2} = 1.5 \Omega$$







$$R_1 = \frac{1.5 \times 2.5}{1.5 + 2.5 + 5} = 0.416 \Omega$$

$$R_2 = \frac{2.5 \times 5}{1.5 + 2.5 + 5} = 1.389 \Omega$$

$$R_3 = \frac{5 \times 1.5}{1.5 + 2.5 + 5} = 0.83 \Omega$$

=

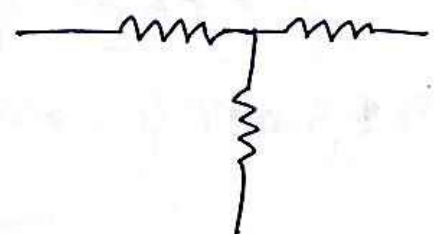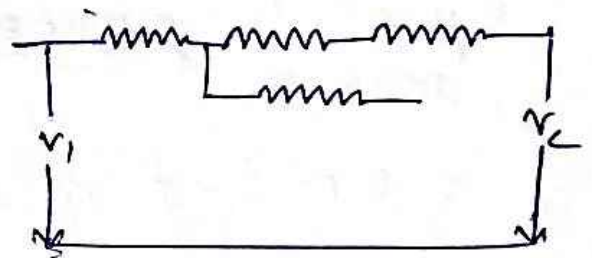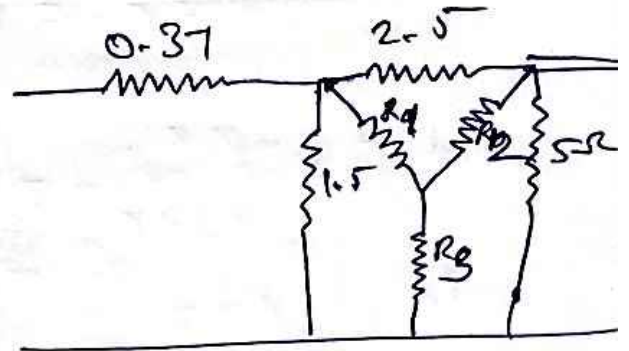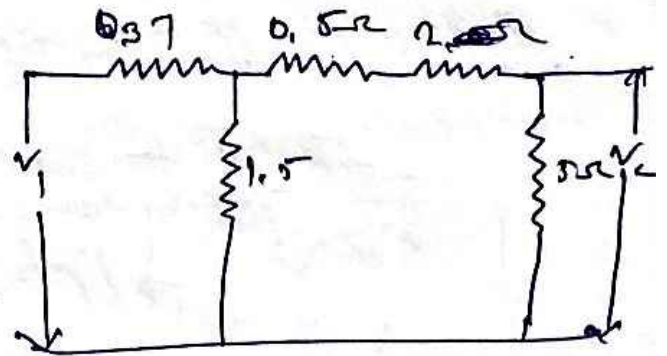

Determine inverse ABCD parameters for the given network.

By applying KVL for loop ①

$$i_1 + 1(i_1 + i_2) = V_1$$

$$2i_1 + i_2 = V_1 \quad \text{--- (1)}$$

By applying KVL for loop ②

$$i_2 + (i_2 + i_1) = V_2$$

$$i_1 + 2i_2 = V_2 \quad \text{--- (2)}$$

from eqn (1)

$$i_2 = V_1 - 2i_1 \quad \text{--- (3)}$$

Comparing eqn with generalised eqn then

$$\boxed{C' = 1, \text{ and } D' = 2}$$

from eqn

By substituting eqn (3) in eqn (2)

$$i_1 + 2(V_1 - 2i_1) = V_2$$

$$i_1 + 2V_1 - 4i_1 = V_2$$


$$2V_1 - 3i_1 = V_2$$

$$\boxed{A' = 2, \text{ and } B' = 1}$$

$$A' = 2 \text{ } \Omega, \text{ and } B' = 1 \text{ } \Omega$$

$$C' = 1 \text{ } \Omega, \text{ and } D' = 2$$

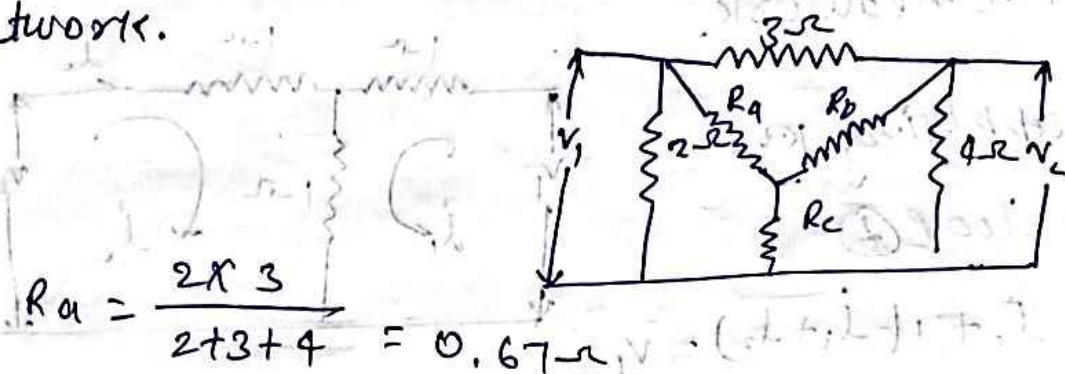Q. Calculate A' B' C' D' parameters for the given network.




$$R_a = \frac{2 \times 3}{2+3+4} = 0.67 \Omega$$

$$R_b = \frac{3 \times 4}{2+3+4} = 0.85 \Omega$$

$$R_c = \frac{4 \times 2}{2+3+4} = 0.57 \Omega$$

By applying KVL for loop ①,

$$0.67 I_1 + 0.889 (I_1 + I_2) = V_1$$

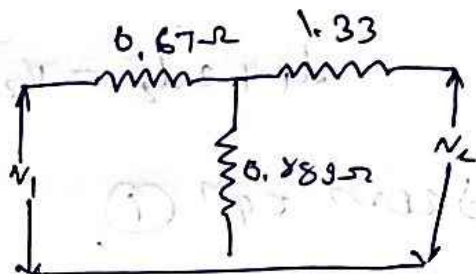

$$1.559 I_1 + 0.889 I_2 = V_1 \quad \text{--- (1)}$$

By applying KVL for loop ②,

$$1.33 I_2 + 0.889 (I_2 + I_1) = V_2$$

$$0.889 I_1 + 2.219 I_2 = V_2 \quad \text{--- (2)}$$

from eqn ①,

$$0.889 I_2 = V_1 - 1.559 I_1$$

$$I_2 = \frac{V_1 - 1.559 I_1}{0.889} \quad \text{--- (3)}$$

Comparing eqn with generalised b/w 2 parameters.

substituting eqn (3) in eqn (2)

$$0.889 I_1 + 2.219 \left(\frac{V_1 - 0.559 I_1}{0.889} \right)$$

$$= 0.889 I_1 + \frac{2.219}{0.889} V_1 - \frac{2.219 \times 0.559 I_1}{0.889}$$


$$= 2.49 V_1 - 0.506 I_1$$

Comparing

$$= A^{-1} = 2.49 \Omega, \quad B = 0.506 \Omega$$



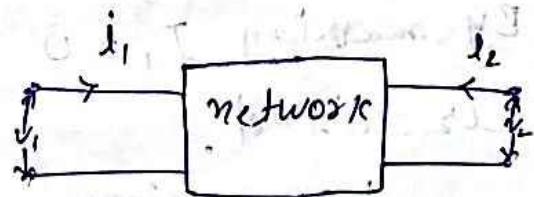Let us consider a network with two port terminal (1), (2-2'). The (1-1') port terminal the V_1, I_1 and (2-2') port terminal are V_2, I_2 . In Hybrid parameter the voltage at (1-1') and current at (2-2') are dependent variable. Then the standard eqn. of H-parameters are given by.



$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$h_{11}, h_{12}, h_{21}, h_{22}$ are called Hybrid parameters

In matrix form

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Procedure :-

by making $V_2 = 0$ i.e. eq (2) port is short circuited.

$$V_1 = h_{11} I_1$$

$$h_{11} = \frac{V_1}{I_1} / V_2 = 0$$

h_{11} is called as short circuit input impedance.

By substituting $V_2 = 0$ in eq (2)

$$I_2 = h_{21} I_1$$

$$h_{21} = \frac{I_2}{I_1} / V_2 = 0$$

h_{21} is called as short circuit forward current gain.

By making $I_1 = 0$ i.e. (1-1) port is open circuited.

by making $I_1 = 0$ i.e. eq (1)

$$V_1 = h_{12} V_2$$

$$h_{12} = \frac{V_1}{V_2} / I_1 = 0$$

h_{12} is called as open circuit reverse voltage gain.

By substituting $I_1 = 0$ in eqn (1)


then,

$$h_{12} I_2 = h_{22} V_2$$

$$h_{22} = \frac{I_2}{V_2} \quad / I_1 = 0$$

h_{22} is called as open circuit output admittance.

* INVERSE-PARAMETER OR g parameters

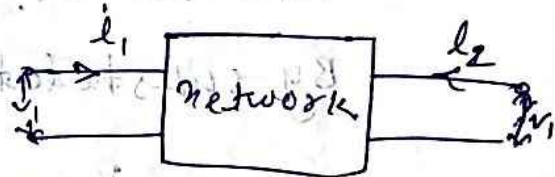

Let us consider a two port network with input terminal I_1, V_1 at (1-1') and output terminals V_2, I_2 at (2-2') to calculate g parameters for the given network.

Then current at (1-1') and voltage at (2-2') are dependent variable then the standard eqn (1) + g parameter are given by

$$I_1 = g_{11} V_1 + g_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = g_{21} V_1 + g_{22} I_2 \quad \text{--- (2)}$$

where,

$g_{11}, g_{12}, g_{21}, g_{22}$ are called inverse hybrid parameters.

In matrix form:-

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

* Produce the

By making $I_2 = 0$ at (2-2') is open circuited. port

$$I_1 = g_{11} V_1$$

$$g_{11} = \frac{I_1}{V_1} / I_2 = 0$$

g_{11} is called open circuit input admittance.

By substituting $I_2 = 0$ in eqn (2)

$$V_2 = g_{21} V_1$$

$$g_{21} = \frac{V_2}{V_1} / I_2 = 0$$

g_{21} is called as open circuit gain.

By making $V_1 = 0$ i.e. port (1-1') is short circuited.

the substituting $V_1 = 0$


$$I_1 = g_{22} I_2$$

$$g_{22} = \frac{I_1}{I_2} / V_1 = 0$$

g_{12} is called short circuit-revers current gain.



By substituting $v_1 = 0$ in eqn (2)

$$V_2 = g_{22} V_2$$

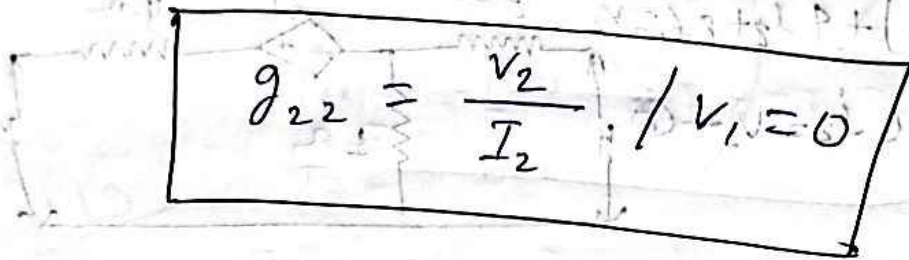


g_{22} is called short circuit output admittance.

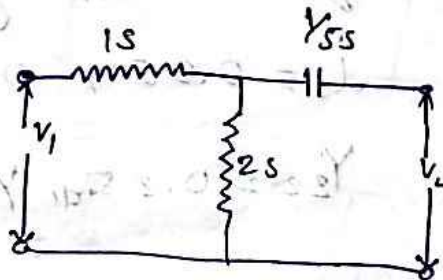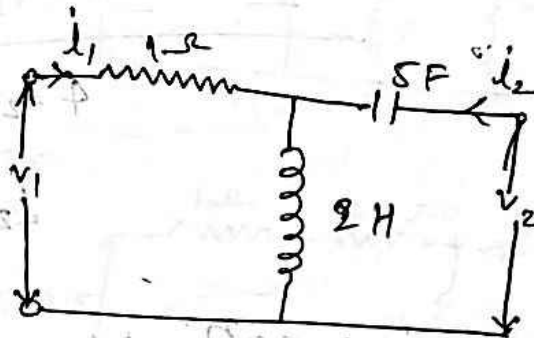* Calculate Z parameters for the given networks.



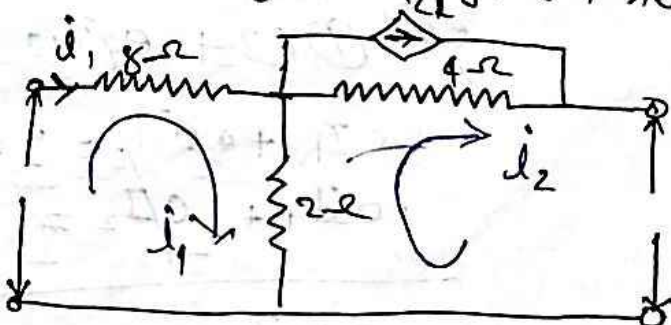Obtain Y-parameters for the given network



By applying KVL for loop (1)


$$8i_1 + 2(i_1 + i_2) = V_1$$

$$10i_1 + 2i_2 = V_1 \quad \text{--- (1)}$$

By applying KVL for loop (2)

$$2(i_1 + i_2) + 4i_2 + 8i_1 = V_2$$
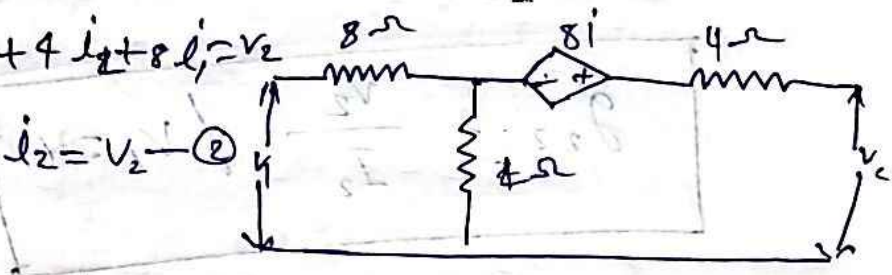
$$10i_1 + 6i_2 = V_2 \quad \text{--- (2)}$$



Eqn (1) + Eqn (2)

$$10i_1 + 2i_2 = V_1$$

$$10i_1 + 6i_2 = V_2$$

$$4i_2 = V_1 - V_2$$

$$i_2 = 0.25V_1 - 0.25V_2$$

Comparing eqn with generalised between

$$i_2 = 0.25V_1 - 0.25V_2$$

$$Y_{22} = 0.25 \text{ S}, \quad Y_{21} = 0.25 \text{ S}$$

Again,

Eqn (1) x 3 + Eqn (2)

$$30i_1 + 6i_2 = 3V_1$$

$$10i_1 + i_2 = V_2$$

$$20i_1 = 3V_1 - V_2$$

$$i_1 = \frac{3V_1 - V_2}{20}$$

$$I_1 = \frac{3}{20} V_1 - \frac{1}{20} V_2$$

$$= 0.15V, -0.05$$

comparision eqn with generalised &

eqn

$$Y_{11} = 0.15V$$

$$Y_{12} = -0.05V$$


$$Y_{21} = 0.05V$$

$$Y_{22} = 0.25V$$

18/09/19


Q. Determine h-parameter for the given circuit
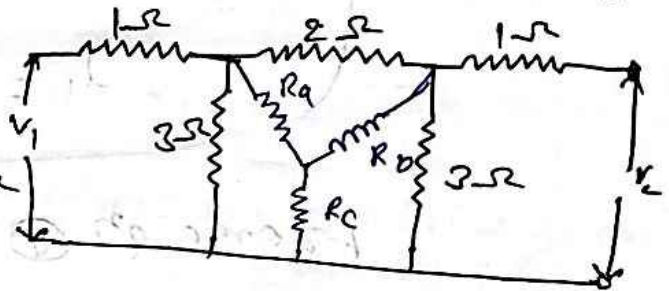
$$R_a = \frac{2 \times 3}{2 + 3 + 3} = 0.75 \Omega$$



$$R_b = \frac{2 \times 3}{2 + 3 + 3} = 0.75 \Omega$$

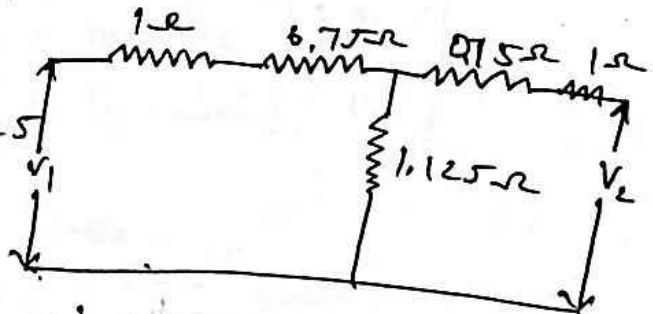
$$R_c = \frac{3 \times 3}{2 + 3 + 3} = 1.125 \Omega$$



Apply KVL loop ①

$$1.75 I_1 + 1.125 (I_1 + I_2) = V_1$$

$$2.875 I_1 + 1.125 I_2 = V_1$$

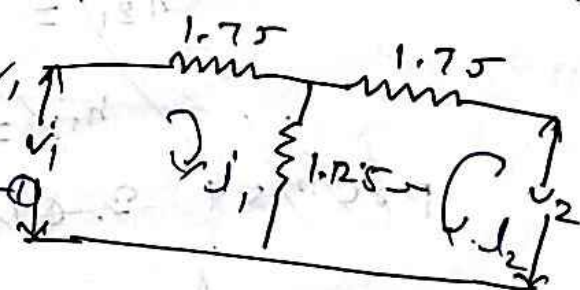

By apply KVL loop ②

$$1.75 I_2 + 1.125 (I_2 + I_1) = V_2$$

$$1.125 I_1 + 2.875 I_2 = V_2 \quad \text{--- (2)}$$

The generalised eqn b/w h-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_1 = h_{21} + h_{22} V_2$$

Comparing eqn with standard equation

from eqn (7),

$$2.875 I_1 + 1.75 I_2 = V_1$$

$$I_1 = \frac{V_1 - 1.75 I_2}{2.875 I_1 + 1.75 I_2}$$

$$I_1 = 0.347 V_1 - 0.608 I_2$$

From eqn (8)

$$1.125 I_1 + 2.875 I_2 = V_2$$

$$2.875 I_2 = V_2 - 1.125 I_1$$

$$I_2 = 0.391 V_2 - 0.391 I_1$$

$$h_{21} = 0.347, \quad h_{22} = 0.391$$

$$h_{11} = 2.875, \quad h_{12} = 1.125$$

$$I_2 = 0.391 I_1 + 0.347 V_2$$

$$h_{21} = 0.391, \quad h_{22} = 0.347$$

$$h_{11} = 2.875$$

* Relation between Z-parameters and Y-parameters

Let us consider the standard eqⁿ of Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

Let us consider the standard equation of Y-parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

The Y-parameters in matrix form is given by,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

By using Cramer's rule

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}} = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y} \quad \text{--- (3)}$$

$$V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}} = \frac{Y_{21} I_2 - Y_{21} I_1}{\Delta Y}$$

By comparing eq (3) & (4) with (1) & (2)

$$z_{11} = \frac{Y_{22}}{\Delta Y}, \quad z_{12} = -\frac{Y_{12}}{\Delta Y}$$

$$z_{21} = -\frac{Y_{21}}{\Delta Y}, \quad z_{22} = \frac{Y_{11}}{\Delta Y}$$

Q. For a given Yz -matrix $Y_{11} = 3 \Omega$, $Y_{12} = 1 \Omega$, $Y_{21} = 2 \Omega$, $Y_{22} = 1 \Omega$. Find the admittance matrix (1) & find the product of ΔY and ΔZ .

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 2 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

By using cramer's rule:

$$V_1 = \frac{\begin{vmatrix} I_1 & 1 \\ I_2 & 1 \end{vmatrix}}{\begin{vmatrix} 3 & 1 \\ 2 & 1 \end{vmatrix}}$$

$$I_1 - I_2 = \Delta Y = 1$$

$$V_1 = I_1 - I_2$$

$$V_2 = \frac{\begin{vmatrix} 3 & I_1 \\ 2 & I_2 \end{vmatrix}}{\begin{vmatrix} 3 & 1 \\ 2 & 1 \end{vmatrix}}$$

$$V_2 = \frac{3I_2 - 2I_1}{\Delta Y} = \Delta Y = 1$$

* Expression of Y parameter in terms of Z parameters

Let us consider the standard equation Z -parameters

$$I_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$I_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

Let us consider the standard equation of Y parameter

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

Then the Z -parameter in form is given by,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

By applying Cramer's rule :-

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}} = \frac{Z_{22} V_1 - Z_{12} V_2}{\Delta Z}$$

$$= \frac{Z_{22}}{\Delta Z} V_1 - \frac{Z_{12}}{\Delta Z} V_2 \quad \text{--- (3)}$$

$$I_2 = \frac{\begin{vmatrix} Z_{11} & I_1 \\ Z_{21} & I_2 \end{vmatrix}}{\begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}} = \frac{Z_{11} V_2 + Z_{21} V_1}{\Delta Z}$$

$$= \frac{Z_{11}}{\Delta Z} V_2 - \frac{Z_{21}}{\Delta Z} V_1 \quad \text{--- (4)}$$

By comparing eqn (3) & (4) with (1) & (2)
then,

$$Y_{11} = \frac{Z_{22}}{\Delta Z} \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z} \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

Q. The z-parameter of two port network

$Z_{11} = 5 \Omega$, $Z_{12} = 4 \Omega$, $Z_{22} = 10 \Omega$, $Z_{21} = 5 \Omega$
calculate y-parameter,

$$Y_{11} = \frac{10}{30} = \frac{1}{3} = 0.33$$

$$Y_{12} = -\frac{4}{30} = -0.133$$

$$Y_{21} = \frac{5}{30} = \frac{1}{6} = 0.167$$

$$Y_{22} = \frac{5}{30} = 0.167$$

Q. A two port network is described by
 ~~$V_1 = I_1 + 2I_2$~~ $V_1 = I_1 + 2I_2$, $V_2 = 2I_1 + 3I_2$
determine the admittance matrix

Given that,

$$V_1 = I_1 + 2I_2 \quad \text{--- (1)}$$

$$V_2 = 2I_1 + 3I_2$$

$$Z_{11} = 1 \quad Z_{12} = 2$$

$$Z_{21} = 2 \quad Z_{22} = 3$$

$$Y_{11} = \frac{3}{-1} = -3$$

$$Y_{12} = -\frac{2}{1} = -2$$

$$Y_{21} = -\frac{2}{1} = -2$$

$$Y_{22} = -\frac{1}{1} = -1$$

$$\begin{bmatrix} 1 & 2 \\ 2 & 3 \end{bmatrix}$$

$$= -1$$

* Interconnection of two port network



(i) Cascaded connection of two port network

(ii) Series

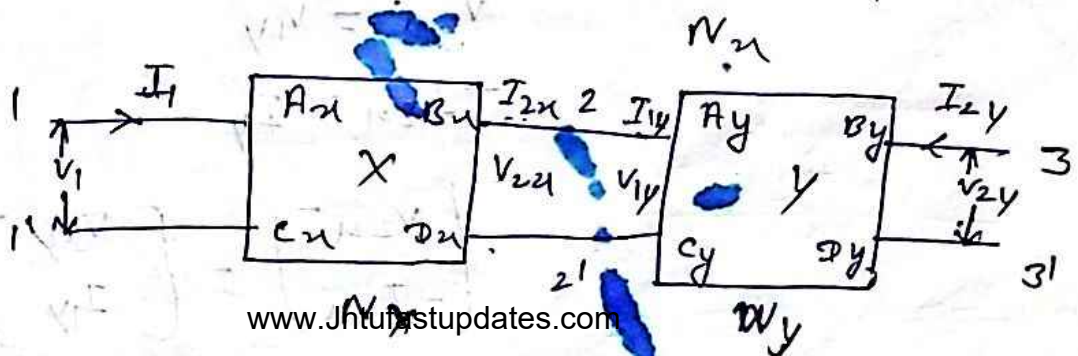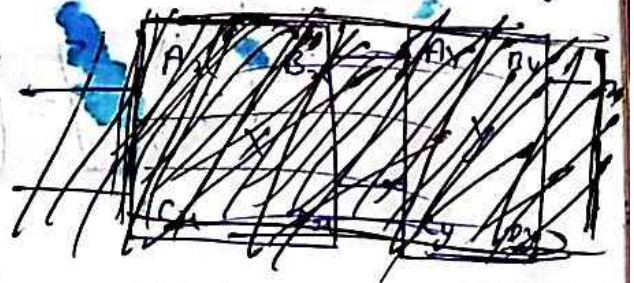(iii) Parallel

* ~~Casces~~ ^{cascad} connection of two port network :-

Let us consider two port network N_x and N_y which are connected in cascaded connection with port voltage and current



Then the standard equation for the ~~Nu network~~ is given by,

$$V_1 = A_u V_2 - B_u I_2$$

$$I_1 = C_u V_2 - D_u I_2$$

Then the ABCD parameters in matrix form is given by,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_u & B_u \\ C_u & D_u \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \text{--- (1)}$$

The standard equation of ABCD parameters for Ny network is given by,

$$V_1 = A_y V_2 - B_y I_2$$

$$I_1 = C_y V_2 - D_y I_2$$

Then the ABCD parameter in matrix form is given by,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \text{--- (2)}$$

$$V_2 = V_1$$

$$-I_2 = I_1$$


$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_u & B_u \\ C_u & D_u \end{bmatrix} \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} \begin{bmatrix} V_{2y} \\ -I_{2y} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{2y} \\ -I_{2y} \end{bmatrix}$$

19/09/19

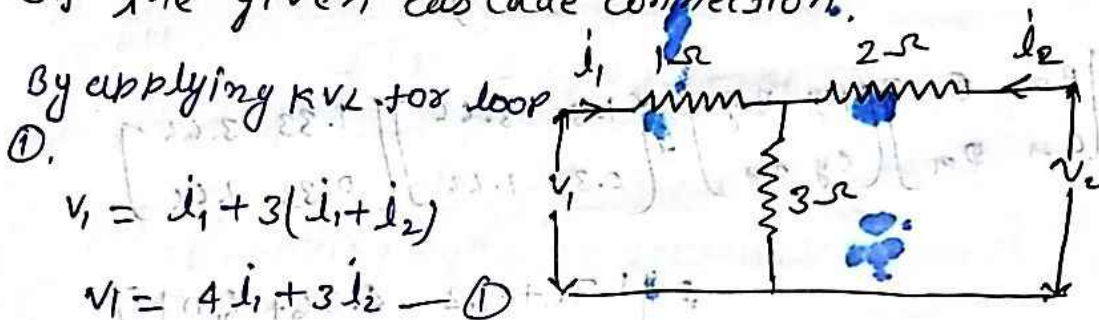Q. Two identical network shown in fig. are connected in cascade connection calculate the ABCD parameters of the given cascade connection.



$$V_1 = i_1 + 3(i_1 + i_2)$$

$$V_1 = 4i_1 + 3i_2 \quad \text{--- ①}$$

for loop ②,

$$V_2 = 2i_2 + 3(i_2 + i_1)$$

$$V_2 = 3i_1 + 5i_2 \quad \text{--- ②}$$

from eqn ②,

$$3i_1 + 5i_2 = V_2$$

$$3i_1 = V_2 - 5i_2$$

$$i_1 = \frac{1}{3}V_2 - \frac{5}{3}i_2 \quad \text{--- ③}$$

comparing with generalised eqn ③ then,

$$C_2 = 0.33, \quad D = 1.66$$

from eqn ①,

$$4i_1 + 3i_2 = V_1$$

$$4 \left(\frac{1}{3}V_2 - \frac{5}{3}i_2 \right) + 3i_2 = V_1$$

Substituting eqn (3) in eqn (1),

$$4 \left(\frac{1}{3} V_2 - \frac{5}{3} I_2 \right) + 3 I_2 = V_1$$

$$1.33 V_2 - 6.66 I_2 + 3 I_2 = V_1$$

$$1.33 V_2 - 3.66 I_2 = V_1$$

Comparing with generalised standard eqn

$$A = 1.33, B = 3.66$$

In matrix form


$$\begin{bmatrix} A_{21} & B_{21} \\ C_{21} & D_{21} \end{bmatrix} = \begin{bmatrix} 1.33 & 3.66 \\ 0.33 & 1.66 \end{bmatrix}$$

$$\begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} = \begin{bmatrix} 1.33 & 3.66 \\ 0.33 & 1.66 \end{bmatrix} \begin{bmatrix} 1.33 & 3.66 \\ 0.33 & 1.66 \end{bmatrix}$$

$$= \begin{bmatrix} 1.76 + 1.2 & 4.86 + 6.07 \\ 0.43 + 0.54 & 1.2 + 2.75 \end{bmatrix}$$

$$= \begin{bmatrix} 2.95 & 10.93 \\ 0.97 & 3.95 \end{bmatrix}$$

Q. Two network X and Y are connected in cascade connection then calculate ABCD parameters of cascade connection when X and Y are cascade

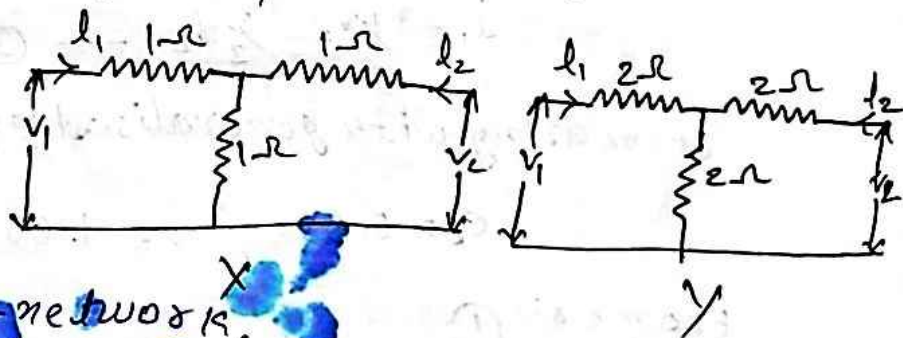

consider X-network,

By applying KVL for loop (1),

$$I_1 + (I_1 + I_2) = V_1$$

$$2I_1 + I_2 = V_1 \quad \text{--- (1)}$$

From loop ②,

$$l_2 + (l_2 + l_1) = V_2$$

$$l_1 + 2l_2 = V_2 \quad \text{--- ②}$$

From eqn ①,

$$l_1 + 2l_2 = V_2 \quad \text{--- ③}$$

$$l_1 = V_2 - 2l_2$$

Comparing eqn. with generalised standard eqn

$$e = 1, \quad D = 2$$

Substituting eqn ③ in eqn ①,

$$2(V_2 - 2l_2) + l_2 = V_1$$

$$2V_2 - 3l_2 = V_1$$

Comparing eqn with generalised standard eqn

$$A = 2, \quad B = 3$$

In matrix form

$$\begin{bmatrix} A_{11} & B_{11} \\ C_{11} & D_{11} \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$$

Again ~~too~~

consider a y-network.

By applying KVL for loop ①,

$$2l_1 + 2(l_1 + l_2) = V_1$$

$$4l_1 + 2l_2 = V_1$$

for loop ②,

$$2l_2 + 2(l_2 + l_1) = V_2$$

$$2l_1 + 4l_2 = V_2$$

$$2l_1 = V_2 - 4l_2$$

$$I_1 = \frac{1}{2} V_2 - 2 I_2 \quad \text{--- (3)}$$

comparing eqn with generalised standard eqn

$C = 0.5$, $D = 2$
 substituting eqn (3) in eqn (1),

$$4 \left(\frac{1}{2} V_2 - 2 I_2 \right) + 2 I_2 = V_1$$

$$2 V_2 - 6 I_2 = V_1$$

comparing eqn with generalised standard eqn

$$A = 2, \quad B = 6$$

In matrix form,

$$\begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} = \begin{bmatrix} 2 & 6 \\ 0.5 & 2 \end{bmatrix}$$

The network interconnection,

$$\begin{bmatrix} A_u & B_u \\ C_u & D_u \end{bmatrix} \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} = \begin{bmatrix} 2 & 6 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} 2 & 6 \\ 0.5 & 2 \end{bmatrix}$$

$$= \begin{bmatrix} 4 + 1.5 & 12 + 6 \\ 2 + 1 & 6 + 4 \end{bmatrix}$$

$$= \begin{bmatrix} 5.5 & 18 \\ 3 & 10 \end{bmatrix}$$


* series connection of two port network :-

The transmission parameters are used to calculate the parameters of cascade connection in the similar way the z-parameters can be used to derived the parameters of series

connected two port network and Y -parameters can be used to derived the parameters of parallel connected two port network.

Let us consider X -networks then the standard eqn of Z -parameters for X -network is given by
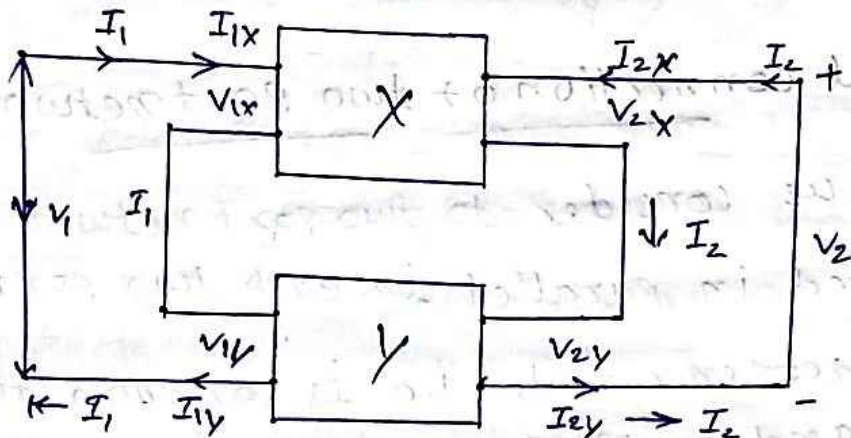
$$V_{1X} = Z_{11X} I_{1X} + Z_{12X} I_{2X}$$



$$V_{2X} = Z_{21X} I_{1X} + Z_{22X} I_{2X}$$

Let us consider Y -networks then the standard eqn of Z -parameters for Y -network

$$V_{1Y} = Z_{11Y} I_{1Y} + Z_{12Y} I_{2Y}$$

$$V_{2Y} = Z_{21Y} I_{1Y} + Z_{22Y} I_{2Y}$$

Then the inter connection of

$$\left\{ \begin{array}{l} I_{1X} = I_{1Y} = I_1 \quad V_1 = V_{1X} + V_{1Y} \\ I_{2X} = I_{2Y} = I_2 \quad V_2 = V_{2X} + V_{2Y} \end{array} \right.$$

$$V_1 = Z_{11X} I_1 + Z_{12X} I_2 + Z_{11Y} I_1 + Z_{12Y} I_2$$

$$V_1 = (Z_{11X} + Z_{11Y}) I_1 + (Z_{12X} + Z_{12Y}) I_2$$

$$V_2 = Z_{21X} I_1 + Z_{22X} I_2 + Z_{21Y} I_1 + Z_{22Y} I_2$$

$$V_2 = (Z_{21X} + Z_{21Y}) I_1 + (Z_{22X} + Z_{22Y}) I_2$$

By comparing the above eqn with standard eqn

i.e

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = (Z_{11x} + Z_{11y})$$

$$Z_{12} = (Z_{12x} + Z_{21y})$$

$$Z_{21} = (Z_{21x} + Z_{21y})$$

$$Z_{22} = (Z_{22x} + Z_{22y})$$


* Parallel connection of two port network:-

Let us consider two port networks connected in parallel in each two port in has a reference node, i.e. is common to input and output port. and if the two port are connected show that they have common reference node then, the parallel connection of two port networks can be derived by using Y -parameters. then the Y -parameters of x -network are given by

$$\left. \begin{aligned} I_{1x} &= Y_{11x} V_{1x} + Y_{12x} V_{2x} \\ I_{2x} &= Y_{21x} V_{1x} + Y_{22x} V_{2x} \end{aligned} \right\} \text{--- (1)}$$

Then the standard eqn of Y -parameters for Y -network are given by,
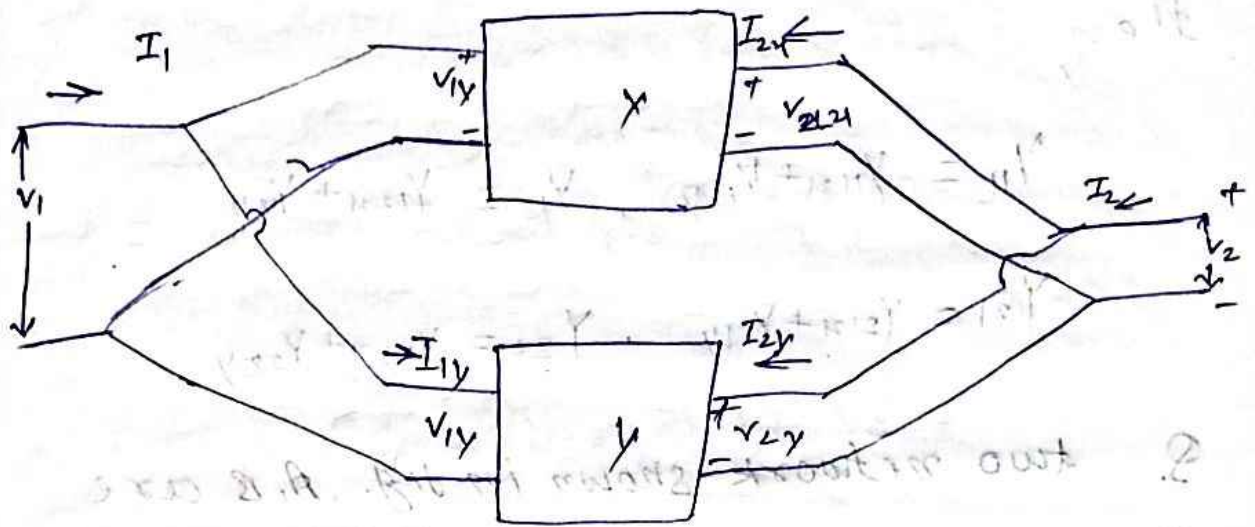
$$\left. \begin{aligned} I_{1y} &= Y_{11y} V_{1y} + Y_{12y} V_{2y} \\ I_{2y} &= Y_{21y} V_{1y} + Y_{22y} V_{2y} \end{aligned} \right\} \text{--- (2)}$$



From the interconnection of the two port network



$$\left. \begin{aligned} v_1 &= v_{1x} = v_{1y} \\ v_2 &= v_{2x} = v_{2y} \end{aligned} \right\} \text{--- (3)}$$

$$\left. \begin{aligned} I_1 &= I_{1x} + I_{1y} \\ I_2 &= I_{2x} + I_{2y} \end{aligned} \right\} \text{--- (4)}$$

By substituting eqn (3) & (4) in eqn (1) & (2)

$$\begin{aligned} I_1 &= I_{1x} + I_{1y} \\ &= Y_{11x} v_1 + Y_{12x} v_2 + Y_{11y} v_1 + Y_{12y} v_2 \end{aligned}$$

$$I_1 = (Y_{11x} + Y_{11y}) v_1 + (Y_{12x} + Y_{12y}) v_2 \text{--- (5)}$$

$$\begin{aligned} I_2 &= I_{2x} + I_{2y} \\ &= Y_{21x} v_1 + Y_{22x} v_2 + Y_{21y} v_1 + Y_{22y} v_2 \end{aligned}$$

$$I_2 = (Y_{21x} + Y_{21y}) v_1 + (Y_{22x} + Y_{22y}) v_2 \text{--- (6)}$$

The stand eqn of Y parameters are given by

$$\left. \begin{aligned} I_1 &= Y_{11} v_1 + Y_{12} v_2 \\ I_2 &= Y_{21} v_1 + Y_{22} v_2 \end{aligned} \right\} \text{--- (7)}$$


By comparing equations (5), (6) with (7)

then,

$$Y_{11} = Y_{11u} + Y_{11y}, \quad Y_{12} = Y_{12u} + Y_{12y}$$

$$Y_{21} = Y_{21u} + Y_{21y}, \quad Y_{22} = Y_{22u} + Y_{22y}$$

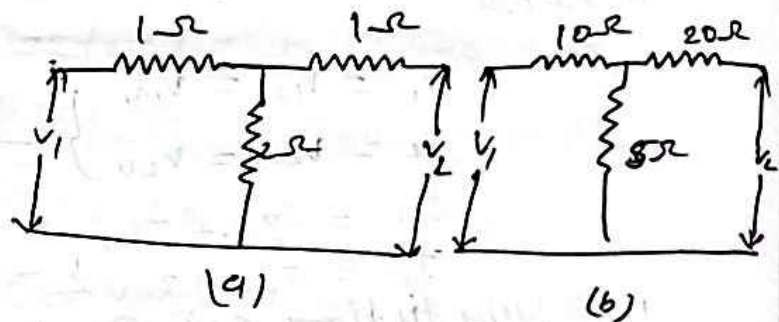Q. two network shown in fig. A, B are connected series obtained the z-parameters of the combination.



consider (a) network.

By applying KVL for loop (1),

$$i_1 + 2(i_1 + i_2) = V_1$$

$$3i_1 + 2i_2 = V_1 \quad \text{--- (1)}$$

from loop (2),

$$i_2 + 2(i_1 + i_2) = V_2$$

$$2i_1 + 3i_2 = V_2 \quad \text{--- (2)}$$

from eqn (2)

$$z_{11} = 3, \quad z_{12} = 2$$

$$z_{21} = 2, \quad z_{22} = 3$$

consider (b) network of 2 parameters,
KVL loop ①

$$10i_1 + 5(i_1 + i_2) = V_1$$

$$15i_1 + 5i_2 = V_1 \quad \text{--- ①}$$

loop ②,

$$20i_2 + 5(i_2 + i_1) = V_2$$

$$5i_1 + 20i_2 = V_2$$

comparing with eqⁿ standard eqⁿ.

$$Z_{11} = 15, \quad Z_{12} = 5,$$

$$Z_{21} = 5, \quad Z_{22} = 25$$

in series ^{in series} connection of network.


$$Z_{11} = 3 + 15 = 18$$

$$Z_{12} = 2 + 5 = 7$$

$$Z_{21} = 2 + 5 = 7$$

$$Z_{22} = 3 + 25 = 28$$

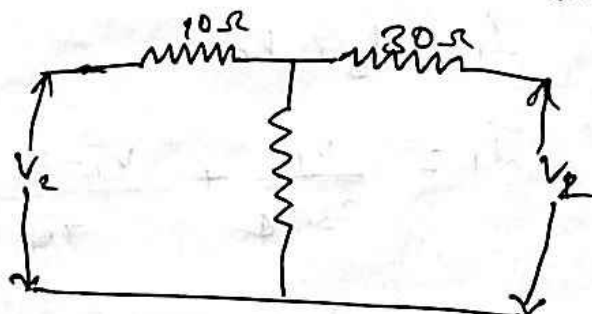Q. Two identical succession of the network shown in fig. are connected in parallel calculate the parameters of the final combination



By applying KVL for loop ①

$$10i_1 + 20(i_1 + i_2) = V_1$$

$$20i_1 + 10i_2 = V_1 \quad \text{--- ①}$$

loop ②

$$30i_2 + 10(i_2 + i_1) = V_2$$

$$10i_1 + 40i_2 = V_2 \quad \text{--- ②}$$

$$R_a = \frac{10 \times 30 + 30 \times 10 + 10 \times 10}{10 + 10 + 30}$$



$$= 23.33$$

$$R_b = \frac{10 \times 30 + 30 \times 10 + 10 \times 10}{10}$$

$$= 70$$

$$R_c = \frac{10 \times 30 + 30 \times 10 + 10 \times 10}{10}$$

$$= 70$$

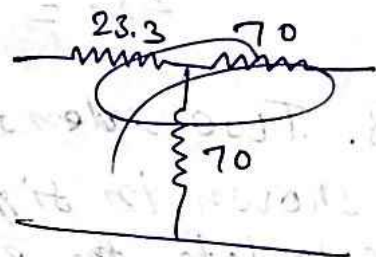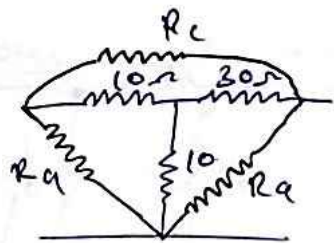


Applying KVL for loop ①

$$i_1 = i_3 + i_4$$

$$i_1 = \frac{V_1}{23.34} + \frac{V_1 - V_2}{70}$$
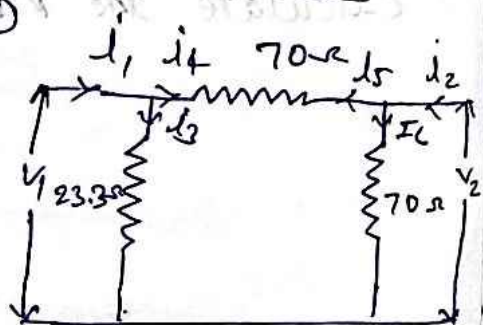
$$= \frac{(V_1)70 + 23.34V_1 - 23.34V_2}{23.34 \times 70}$$



$$i_1 = \frac{46.66V_1 - 23.34V_2}{1633.8}$$

$$i_1 = 0.0285V_1 - 0.014V_2$$

By applying KCL at node ②

$$i_2 = i_5 + i_6$$

$$i_2 = \frac{V_2}{70} + \frac{V_1 - V_2}{23.33}$$

$$i_2 = \frac{23.34V_2 + 70V_1 - 70V_2}{1633.8}$$

$$= \frac{70V_1 - 46.66V_2}{1633.8}$$

$$= 0.0428V_1 - 0.0285V_2$$

$$Y_{11} = 0.0285 + 0.0285 = 0.057$$

$$Y_{12} = -0.0285$$

24/09/19 $Y_{21} = 0.0856$

* Poles and zeros of network function :-

The network function $N(s)$ is given by.

$$N(s) = \frac{P(s)}{Q(s)} = \frac{a_0 s^m + a_1 s^{m-1} + a_2 s^{m-2} + \dots + a_{m-1} s + a_m}{b_0 s^m + b_1 s^{m-1} + b_2 s^{m-2} + \dots + b_{m-1} s + b_m}$$

where, $a_0, a_1, a_2, a_3, \dots, a_n$ are the coefficients of polynomial of $P(s)$.

$b_0, b_1, b_2, b_3, \dots, b_m$ are the coefficients of polynomial of $Q(s)$.

The given numerator and denominator polynomials is factorised, then,

$$N(s) = \frac{a(s-z_0)(s-z_1)(s-z_2) \dots}{b(s-p_1)(s-p_2)(s-p_3) \dots}$$

here, z_1, z_2, z_3 are known as zero (0) and p_1, p_2, p_3 are known as poles of the network function.


The zeros of the network function are determined zero (0)

The poles of the function are determined by (x)

EX.
$$N(s) = \frac{(s+1)(s+3)}{(s+2)(s+3+j4)(s+3-j4)}$$


-1, -3 are zero's of $N(s)$

then, -2, -3, -j4, -3+j4 are the poles

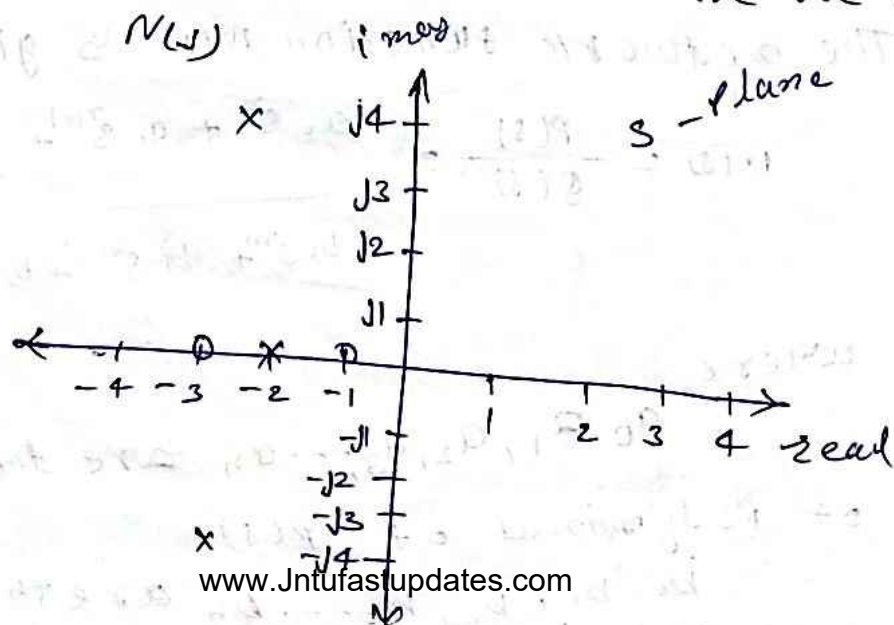


Draw the pole zero diagram for the given network. $V(s)$
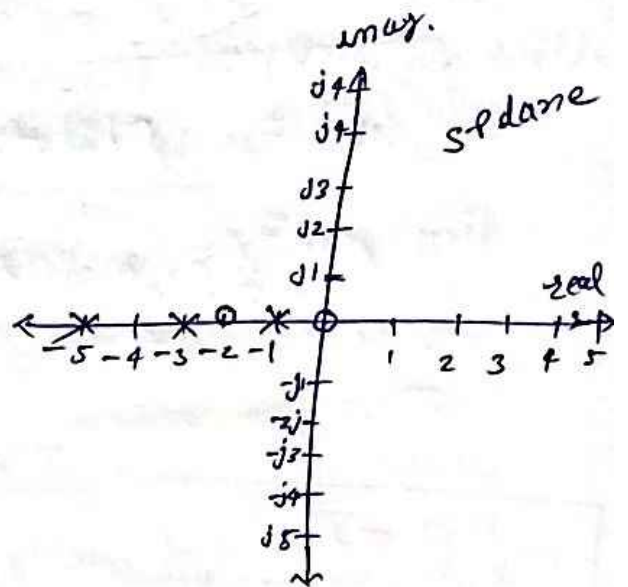
$$V(s) = \frac{s(s+2)}{(s+1)(s+3)(s+5)}$$



For the given network function draw the poles zero's diagram.

$$I(s) = \frac{5s}{(s+1)(s^2+4s+5)}$$

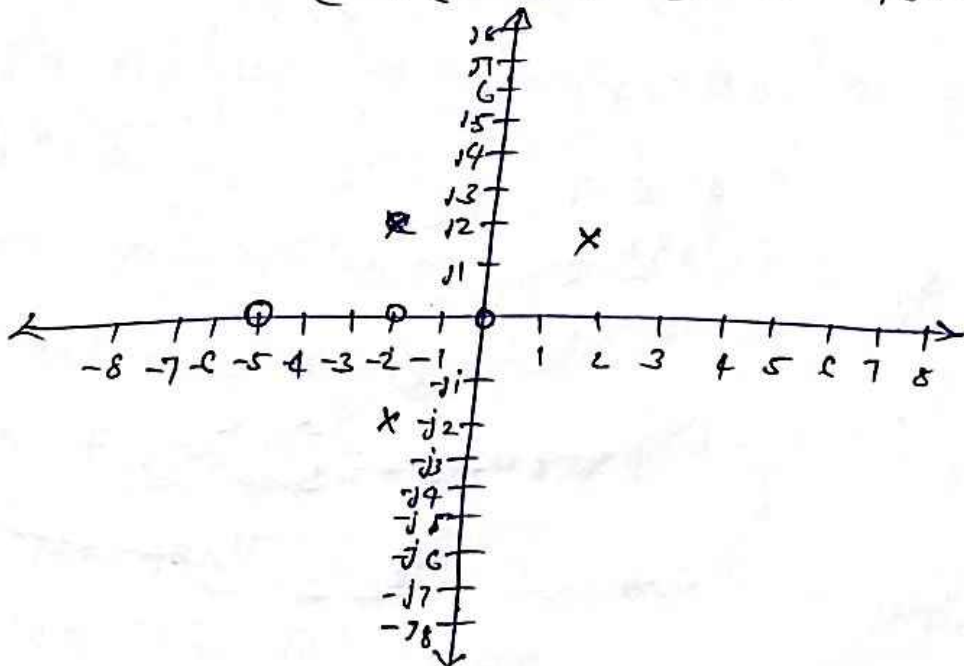

$$= \frac{-4 \pm \sqrt{(4)^2 - 4 \cdot 1 \cdot 5}}{2 \cdot 1} = \frac{4 \pm j4}{2}$$