

Concept of power Electronics:-

- \* power Electronics is a combination of power Engineering and Electronic Engineering & Control Engineering,
- \* power Engineering is mainly concerned with generation, transmission, distribution & utilization of Electric Energy at high efficiency.
- \* Electronic Engineering is mainly concerned production, transmission & reception of data & signals of very low power level, of the order of a few Watts (or) milliwatts.
- \* The main concept of power Electronics is the Bulk amount of power can be converted & controlling by low ~~with~~ Electronic devices.

EX:- A Semi Conductor power switches such as thyristor, GTOs etc., work on the principle of Electronics (movement of holes & electrons), but have the name power attached to them only as a description of their power Ratings.

Applications of power Electronics:-

- \* The area of Modern power electronics began with invention of SCR by Bell Laboratories in

1956. power Electronics System today incorporate power  
Semi Conductors as well as micro Electronic integrated ckt's

→ Conventional power Controllers, based on thyristors, mercury  
-vne rectifiers, magnetic amplifiers, rheostatic Controllers  
have been replaced by power Electronic Controllers using  
Semi Conductor devices in almost all applications.

1. AeroSpace:- Space Shuttle, power Supplies, Satellite power  
Supplies.

### \* Advantages :-

1. High Efficiency due to low loss.
2. High reliability
3. Long life & less maintenance due to absence of any  
moving parts.
4. Small size and less weight result in less launch space  
& therefore lower installation cost.

### \* Dis Advantages :-

1. power Electronic Controllers have low overload Capacity
2. Regulation of power is difficult.
3. Ac to D.C and Ac to A.C Converters operate  
at a low i/p power factor under certain operating  
Conditions
4. power - Electronic Circuits have a tendency to generate  
harmonics in the supply systems as well as in  
load circuit.

# Types of power Converters:-

1. Diode Rectifiers
2. A.C to D.C Converters
3. D.C to D.C Converters
4. D.C to A.C Converter
5. A.C to A.C Converters
6. Static Switches.

## \* Power Semi Conductors Diode - free electrons

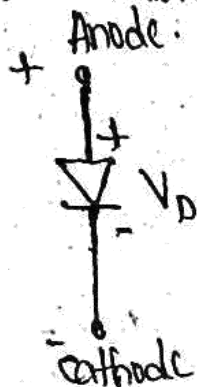


fig:- Symbol

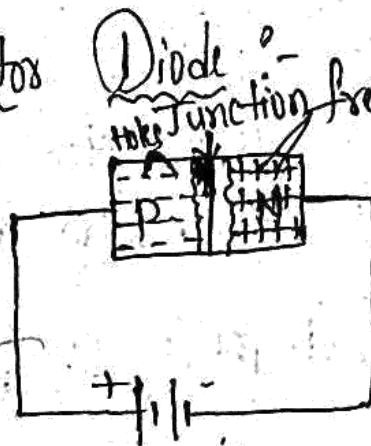


fig: Diode Construction

- Diode is a unidirectional & uncontrolled device.
- Diode is a semiconductor device with two terminals that conducts current in one direction only known as unidirectional.
- A p-n junction is the simplest form of semiconductor diode which in ideal condition behaves as a short circuit when it is forward biased and an open circuit when it is reverse biased.

## Working:-


- A diode working principle depends on the interaction



of n-type and p-type Semiconductor has plenty of free electrons and a very few number of holes. In other words we can say that the concentration of free electrons is high and that of holes is very low in an n-type Semiconductor. free electrons in the n-type Semi Cond. are referred as majority charge carriers, and holes in the n-type Semiconductor are referred as minority charge carriers.

→ A p-type Semiconductor has a high concentration of holes and low concentration of free electrons.

### \* V-I Characteristics of Diode :-

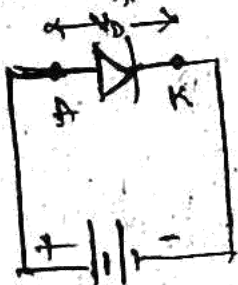

→ When anode is +ve wrt Cathode diode is said to be forward biased. With the increase of source voltage " $V_s$ " from zero value. initially diode current is zero, from,  $V_s = 0$  to "cut-in voltage", the forward diode current is very small. Cut in voltage is also known as threshold voltage (or) turn-on voltage.

→ Cut in-voltage <sup>around</sup> "0.7 V"


→ When diode conducts, there is a forward voltage drop of order of "0.8 to 1V"

→ The diode is reverse biased. On this condition, a small reverse current called leakage current.





of the order of mA (or) mA purpose. The leakage current is almost independent of magnitude of reverse voltage until this voltage reaches break down voltage.

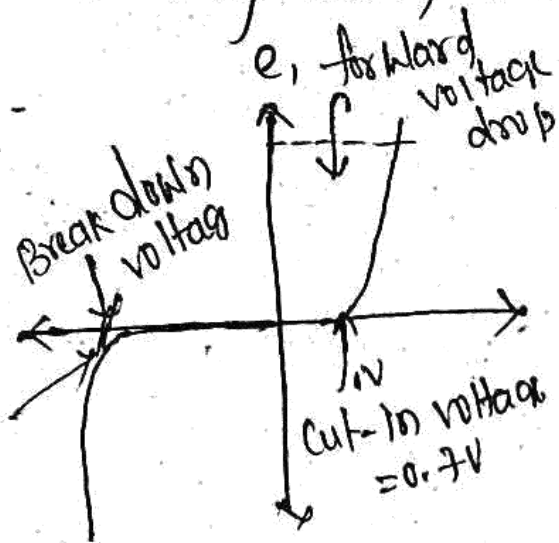
→ A large Reverse break down voltage associated with high reverse current, leads to excessive power loss that may destroy the diode.



### \* Diode As a Rectifier :-

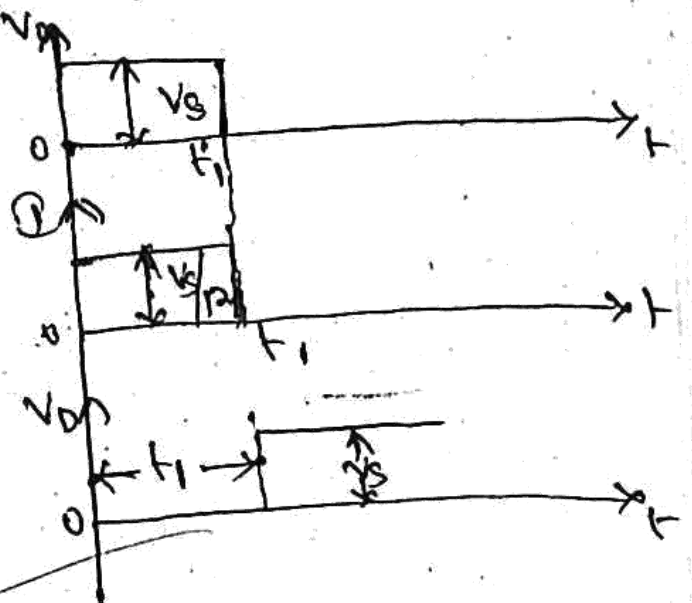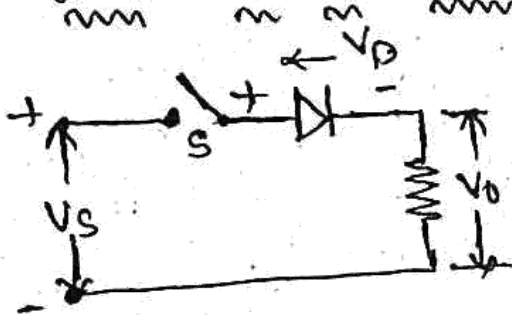

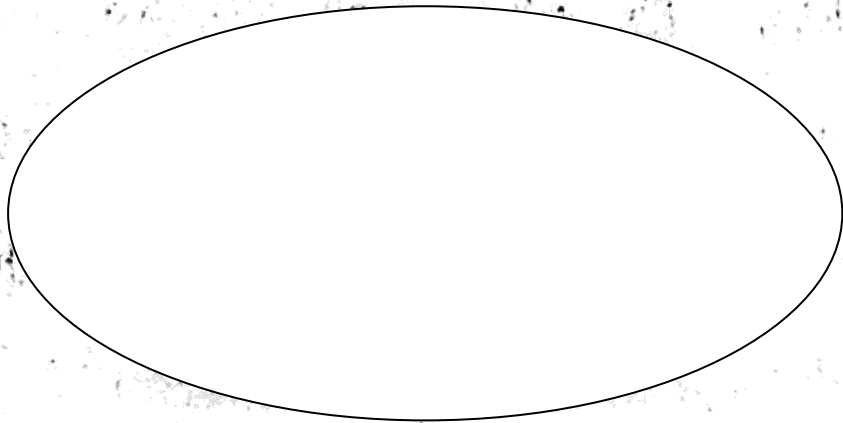→ On the other hand, when switch 'S' is closed, the current rises instantaneously to  $V_s/R$  as shown in fig (b). Hence  $V_s$  is the DC source voltage.



04/07/19

### Applications of P.E :-

1. Aero Space :- (Air Craft power supplies)
2. ~~Satellite~~ power supply. Commercial purposes (TV, Refrigerators, etc.)  
It has more advantages that why we use power electronics in Commercial purpose.
3. Residential purposes (Omn Box)  $\downarrow$  All Electronic devices.
4. Industrial purposes (fan, heaters etc.) All industrial devices.
5. Tele-Communication (Battery, UPS power supply)
6. Traction purpose (Rail) <sup>charging</sup>
7. Utility purpose (HVDC)

# Power Conversions:-

(i) A.c to D.c Conversions:- (Phase Controlled Converter)

- 90% of applications is used variable speed <sup>D.C.</sup>
  - But ~~key~~ <sup>bridge</sup> a fixed D.C. is conn to double <sup>bridge</sup> rectifier. We have variable speed <sup>(ω)</sup> voltage.
- That's why we used phase controlled converters.

(ii) D.c to D.c Conversions:- (D.C Choppers).

→ It converts fixed D.C. to variable D.C.

(iii) D.c to A.c Conversions:- (Inverter):-

fixed voltage   
 ↓   
 variable voltage   
 (ω)   
 variable frequency.

(iv) A.c to A.c Conversions:- (A.c Regulators)

fixed voltage   
 ↓   
 variable voltage   
 (ω)   
 variable frequency.

- We need only "variable voltage" to fixed voltage is called A.c Regulator (or) A.c voltage controller.
- We need only variable frequency to fixed frequency is called Cyclo Converter.

\* Thyristor is always similar to p-n Junction



## Thyristor:-

→ By using device we can convert and control.


In older days THYRatron is used to convert and control.

→ Thyristor characteristics is similar to THYRatron tube.

**THYRISTOR.**

→ Thyristor construction is similar to transistor.

## Thyristor Construction:-

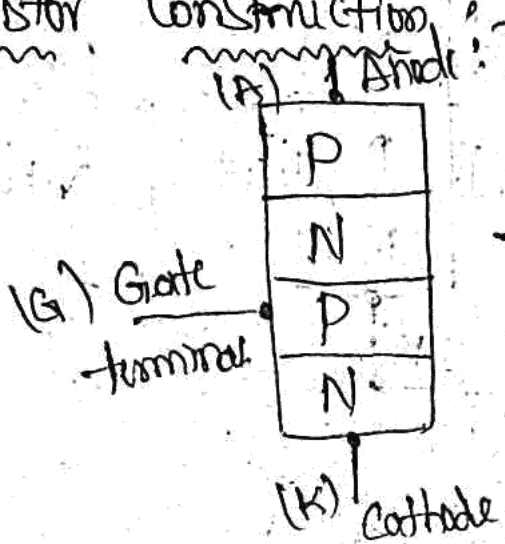

→ It has 4-layers.

PN-PN layers.


→ It has 3-junctions.

→ 3-terminals.

→ The terminal P layer connected is anode.

→ The terminal N layer connected is cathode.

→ Symbol of Thyristor

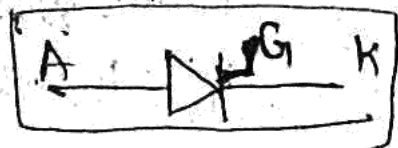

→ unidirectional device just like diode.

→ Thyristor is a control device (difference of Thyristor & diode is)

we can control current.


→ It always obtained controlled o/p.

→ Single chip available Rating is '10KV'.

→ Single chip can handle 40 MW or less  $I = 4KA$

- $J_1$  is formed outer 'p' layer inner 'N' layer
- $J_2$  is formed inner 'p' & 'N' layers
- $J_3$  is formed inner 'p' & outer 'N' layers

\* Characteristics of Thyristor:-

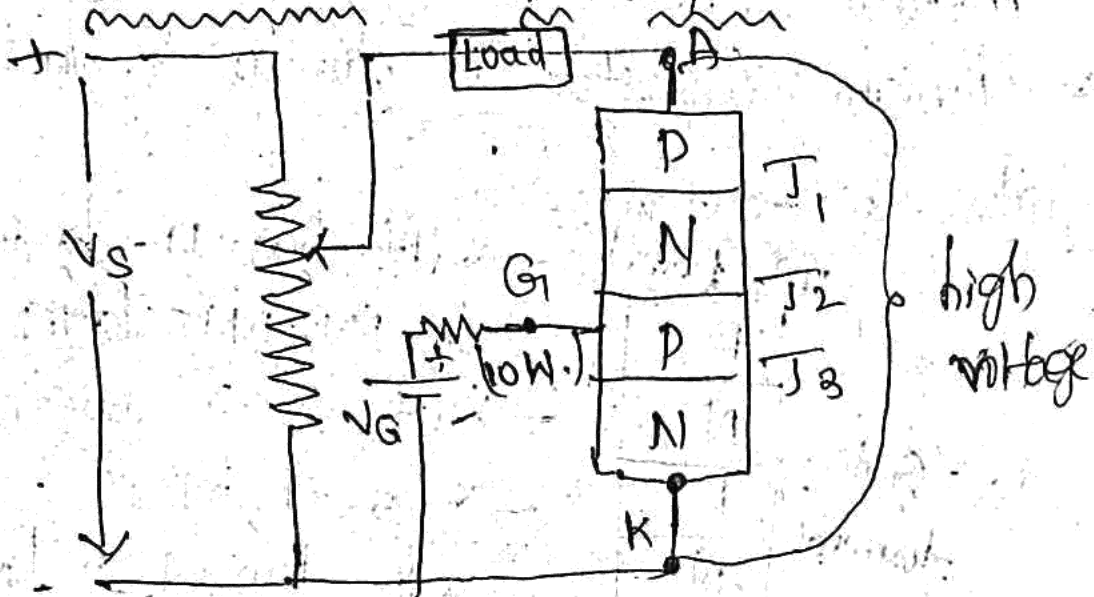


- Diode is Classified into
  - (i) forward bias Mode
  - (ii) Reverse Bias Mode.

→ There are three types of modes of

OFF state	1. Reverse Biasing Mode	→		(open)
	2. Forward Blocking mode	→		(open)
	3. Forward Conduction Mode	→		(close)
ON state				


# 1. Reverse Blocking Mode (RBM) :-

Symbol :-

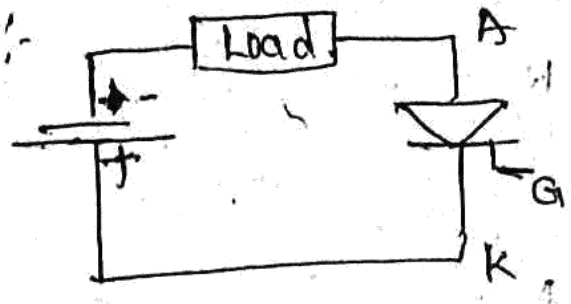

\* <sup>Here</sup> voltage is Reversed.  
 \* Reverse voltage is applied across the thyristor.

Structure :-

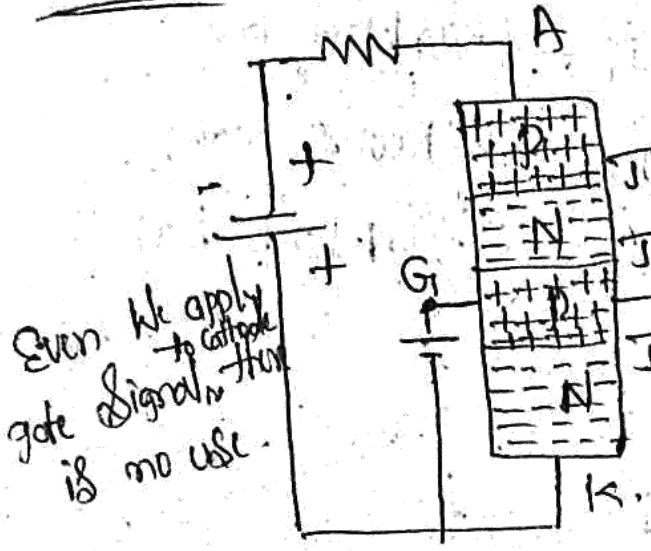


Even we apply gate signal, there is no use.

(Depreciation layer ↑, Resistance ↑)  
 Current = 0  
 Reverse bias  
 Forward bias (Repel Each other and goes to Junction)  
 Reverse bias  
 (Resistance ↓, Current ↑)

→ Here, two Reverse bias, the device is not at all comes to conduction

## Static V-I Characteristics :-

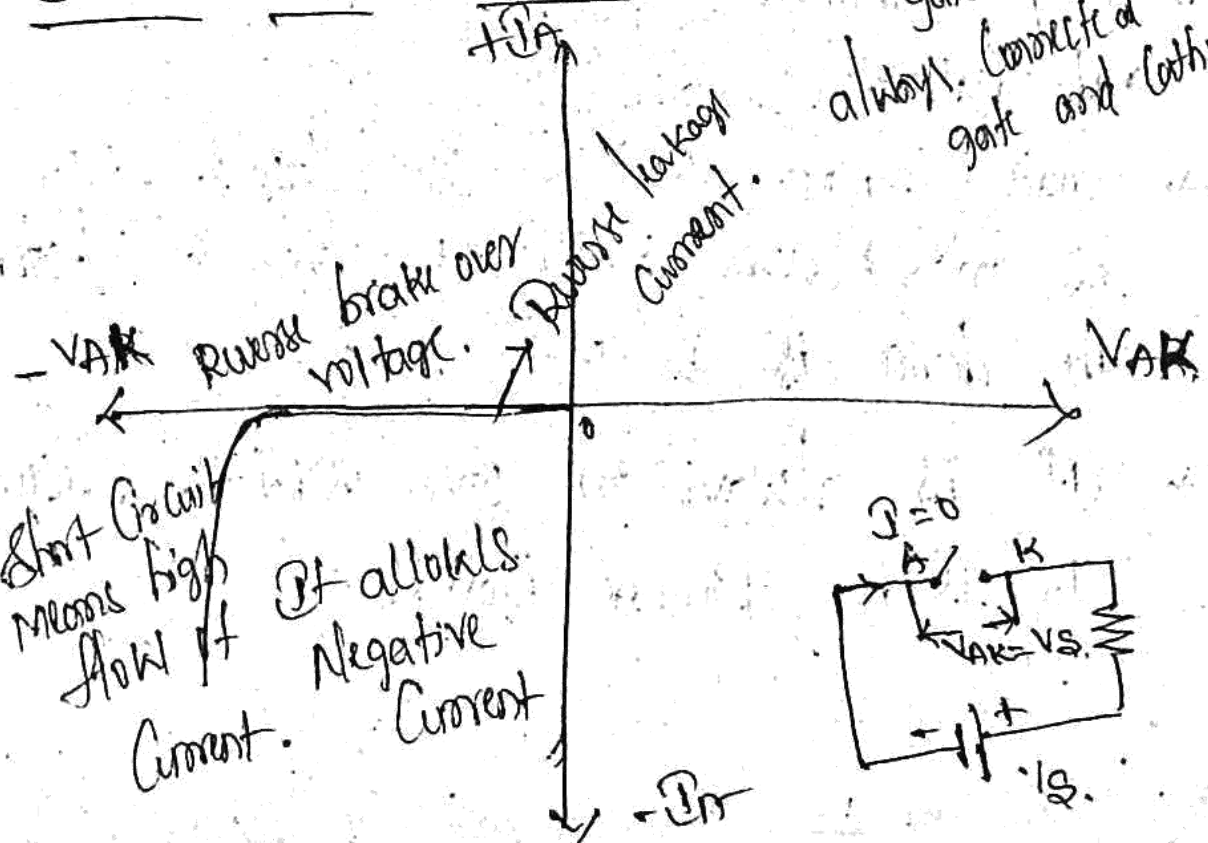


gate terminal is always connected to gate and cathode.




## 2. Forward Blocking Mode :- 05/07/19

Symbol

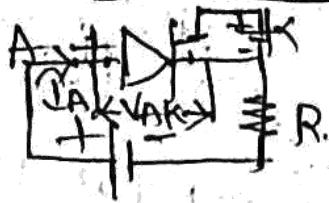


Structure :-

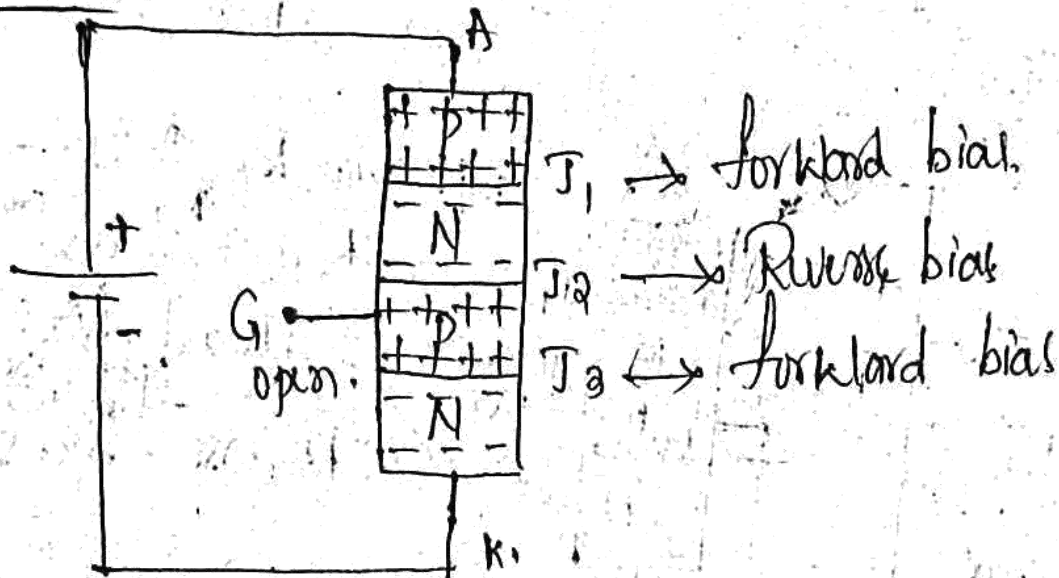

- $T_1$  is located at Centre
- $T_2$  is not allow the flow of electrons
- $T_2$  is block to flow of electrons
- only forward voltage is applied to anode and Cathode.
- Gate signal is in open state,  $T_2$  is in Reverse bias, no flow of electrons the device is in off state.
- It is always in open switch, because  $T_2$  is in Reverse bias.

# V-I Characteristics :-

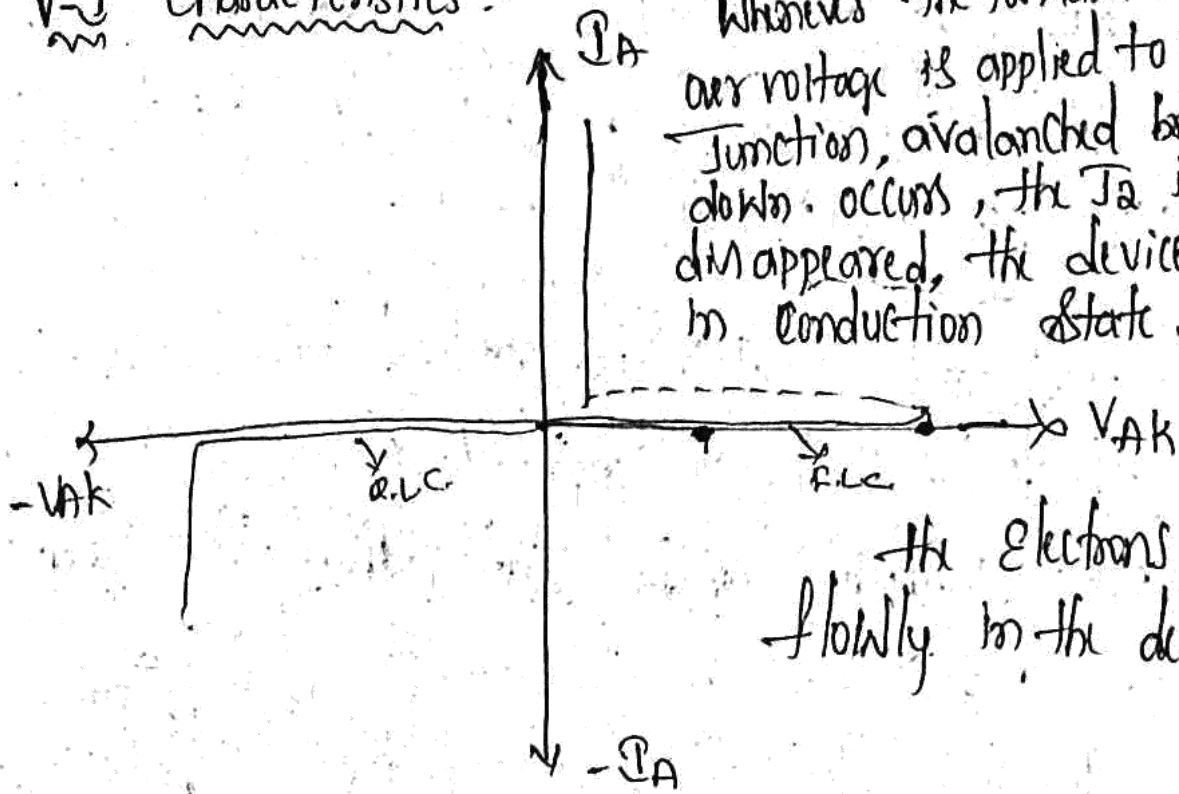


Whenever the forward break over voltage is applied to  $J_1$  junction, avalanche break down occurs, the  $J_2$  is disappeared, the device is in conduction state.

the electrons free flow in the device.

## 3. Forward Conduction Mode :-

### Structure :-

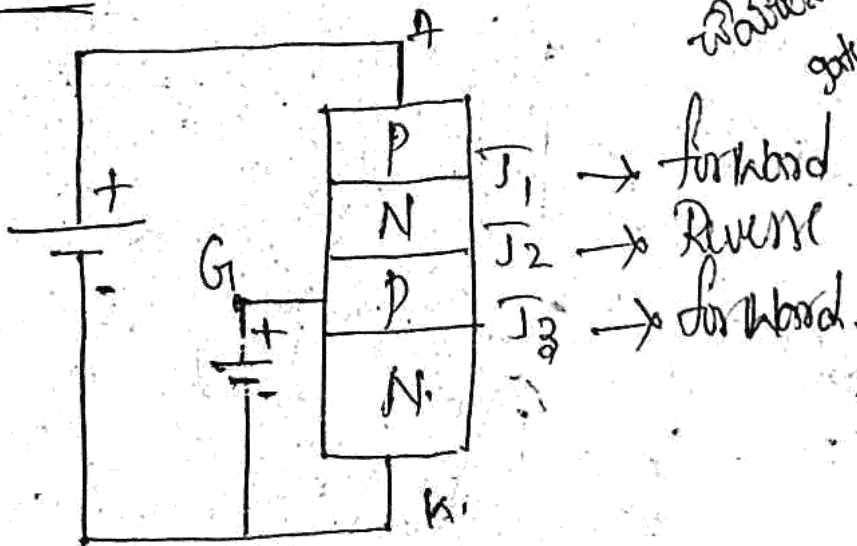

as time period  $\omega t$  on  $\omega t = \pi$  gate signal apply  $\omega t = 2\pi$ .


→ Whenever the gate device is in 'on' state, the gate signal is applied.

→ Whenever Gate is applied, the external charges is injected to the inner 'p' layer for the Reverse bias changed to forward bias.

→ So, the  $J_1, J_2, J_3$  are three are, in forward bias, so the electrons flows freely in the device.

→ forward voltage is applied to anode to Cathode at the same time Gate is applied b/w Cathode and Gate then the Conduction occurs.

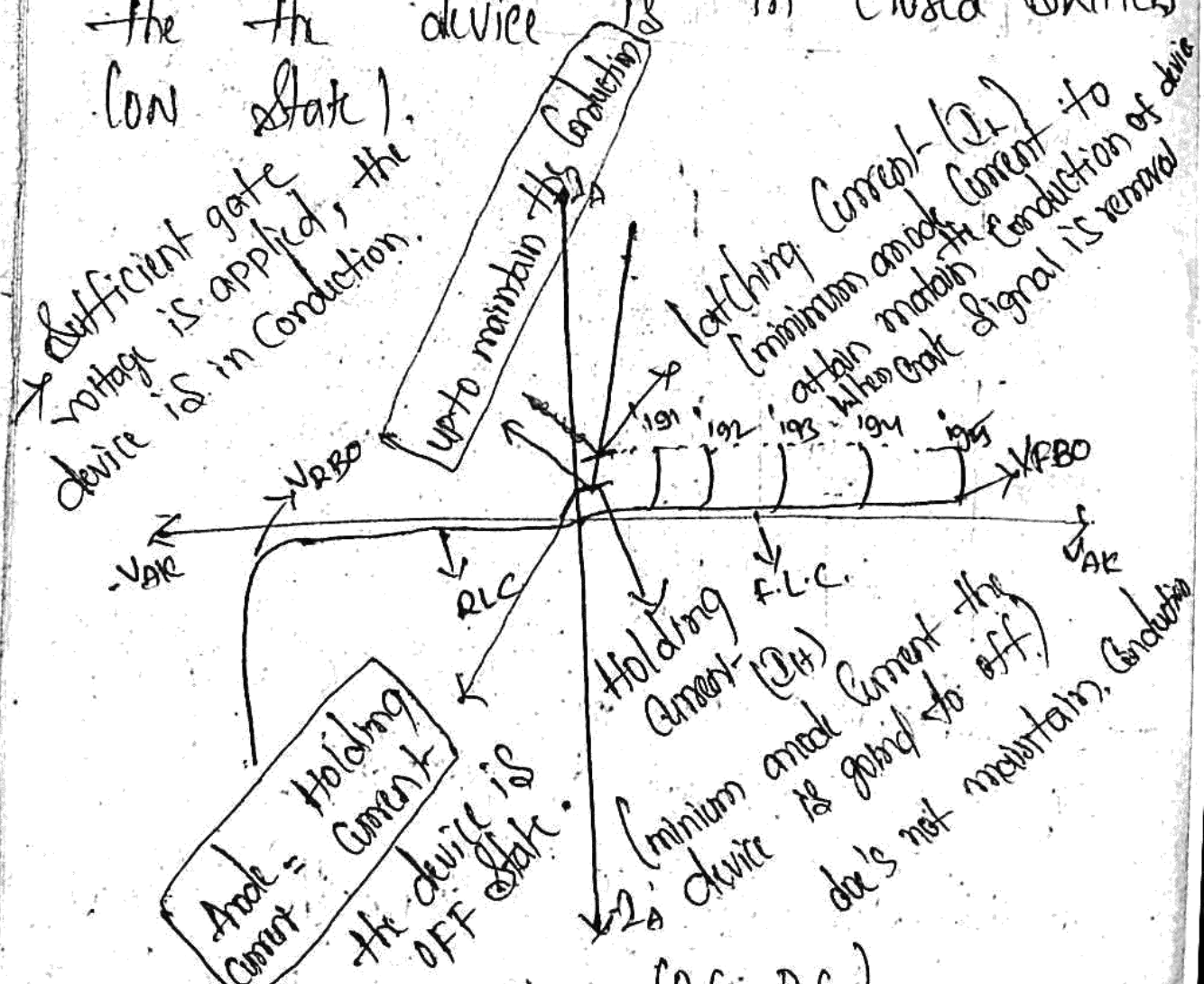→ Whenever the conduction occurs, the electrons flows freely from the anode to Cathode, then the device is in closed switch (low state).




→ Gate signal is applied to (A.C; D.C) Continuous signal, Digital Signal



→ Whenever the gate signal is removed, Current flows continuously  
 → Latching Current is 2 to 3 times of holding current  
 $I_L > I_H$  → the device is in on state.

\* Turn-on and Turn-off Methods of SCR:-

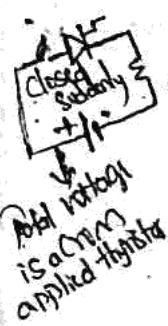(i) Turn-on :- Converts to F.  
 → The device is F.B.M to Conduction state.  
 OFF → ON.




1. Forward voltage turn on method (Not efficient)
2.  $\frac{dv}{dt}$  triggering (Not efficient Junction Capacitance more)
3. Gate triggering → Most Efficient and Economical.
4. Thermal triggering (Temperature (Not efficient))
5. Light triggering (Not efficient)

→ When the electrons move slowly to p to n junction, the device is in conduction, but temperature is high, so device is collapsed.

(i) Forward voltage triggering :- 8/07/19

→ Forward voltage Applied across device.

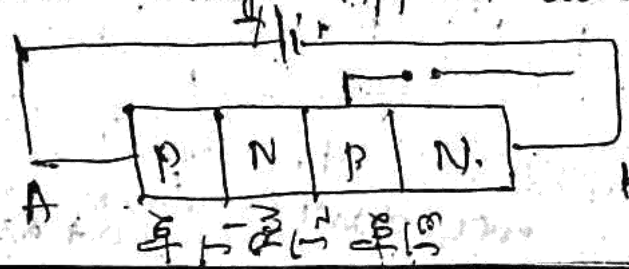


Forward voltage increased up to break over voltage (Rated Voltage)

then the Junction  $J_2$  is disappressed and electrons flow from 'A to K'. The device may come in Conduction (Rated voltages are required).

2.  $\frac{dv}{dt}$

Triggering :-

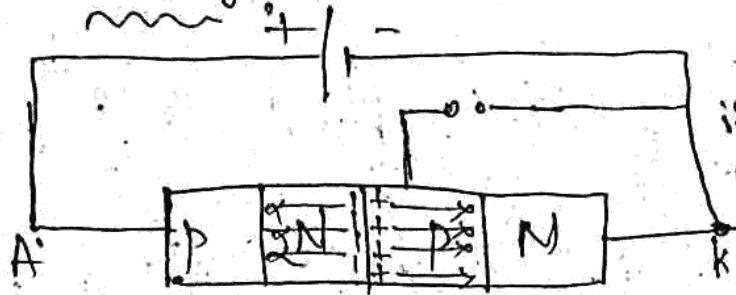

Whenever the voltage is applied, the Junction Capacitance varies. Current increases.

→ The rate of change of voltage

$$i_c = C_j \frac{dv}{dt}$$


→ Whenever the device is in conduction,  $i_c$  value increases.

$$\frac{dQ}{dt} = \frac{d(C \cdot V)}{dt} \quad Q = CV$$

$$\frac{dQ}{dt} = C_j \frac{dV}{dt} + V \frac{dC_j}{dt}$$

→ voltage increases. Conduction current increases.

3. Gate triggering :-

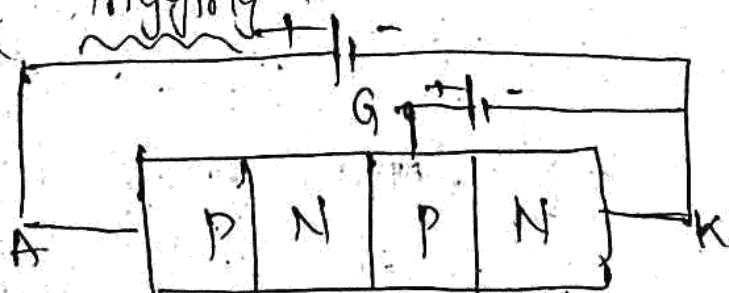

Main purpose is to turn on device once device is fully on. No need to gate signal. No change in conduction.

→ The forward voltage is applied Anode to Cathode.

→ The forward Gate voltage is applied to Gate and Cathode.

→ Whenever the Gate signal is applied, the external charges is applied to "J<sub>2</sub>" junction. The J<sub>2</sub> junction changes from Reverse bias to forward bias.

#### 4. Thermal Triggering :- (Temperature)

→ These are Electronic devices.


→ These devices are sensitive at small.

temperature.

→ The junction current are present in a long period then the temperature increases, ~~but~~ the junction break, automatically the device comes to stall.

#### 5. Light Triggering :-

only high light intensity

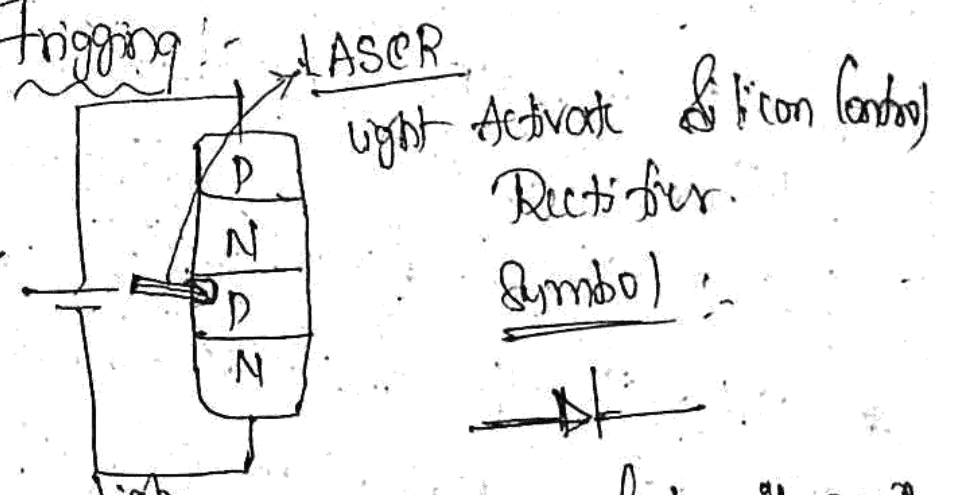

Whenever the high light intensity fall in "LASER" the External Energy Applied to Junction, then Junction comes to conduction (forward conduction).




Turn-off: Turn-off process of SCR is called Commutation  
 → The device is comes from f.c.M to f.B.M  
 ON → OFF State.

\* Two types of Methods :-


- (i) line Commutation for Natural Commutation
  - (ii) forced Commutation. (When applied to d.c. and <sup>mostly</sup> ~~some times~~ <sup>When applied to A.C. supply</sup> ~~A.C. supply~~)
- By using these two methods, to turn-off the devices.

Suppose,

(i)

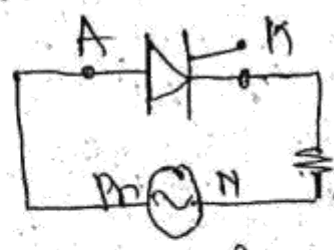

$0 < \pi \rightarrow$  forward voltage

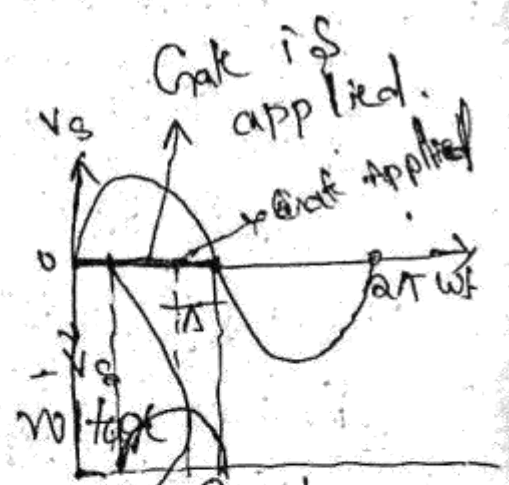

\* At this instant forward gate signal is applied the device is 'ON' state. (Closed Switch)


$V_0 = V_s$ , Closed Switch.

→ At ' $\pi$ ' -  $2\pi$ , Reverse.


Whenever the anode voltage is <sup>at ' $\pi$ '</sup> '0', forward bias is '0', so the device gets Reverse

\* Naturally the device is turn off due to line voltage that type is called line Commutation (line voltage is zero).

## 2. forced Commutation :- c)

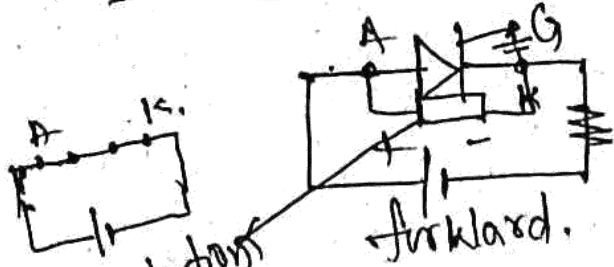

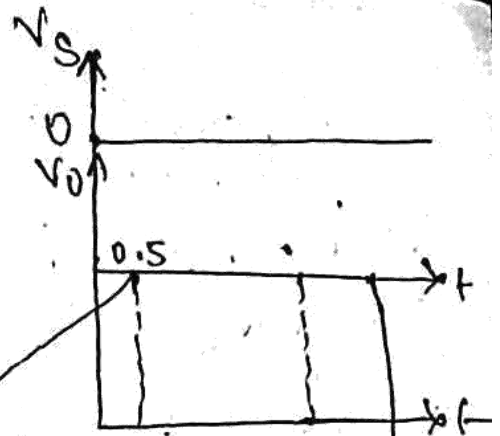Commutation circuit -  
(Requirement to turn off) Gate signal is applied



→  $V_0 = V_s$  the device is on.

This is constant forward voltage, ~~Whenever~~ whenever the Reverse bias, so we apply commutation circuit b/w 'A and K'.

→ Commutating elements is "L and C".


→ Impedance is low <sup>(Commutation CRT)</sup> compared to the closed circuit.

→ So, the current is diverted to "L" and "C". the resistance is reduced.

→ Whenever Anode current <sup>(below)</sup> less than holding current, the Junction "J<sub>2</sub>" gets reversed so the device is <sup>comes to</sup> OFF-state.

11/07/19 Time taken to Block the Current That type is Turn-off.  
 (ii) Turn-off time Characteristics:- (F.C.M - F.B.M) ON - OFF  
 → 1 k to times.

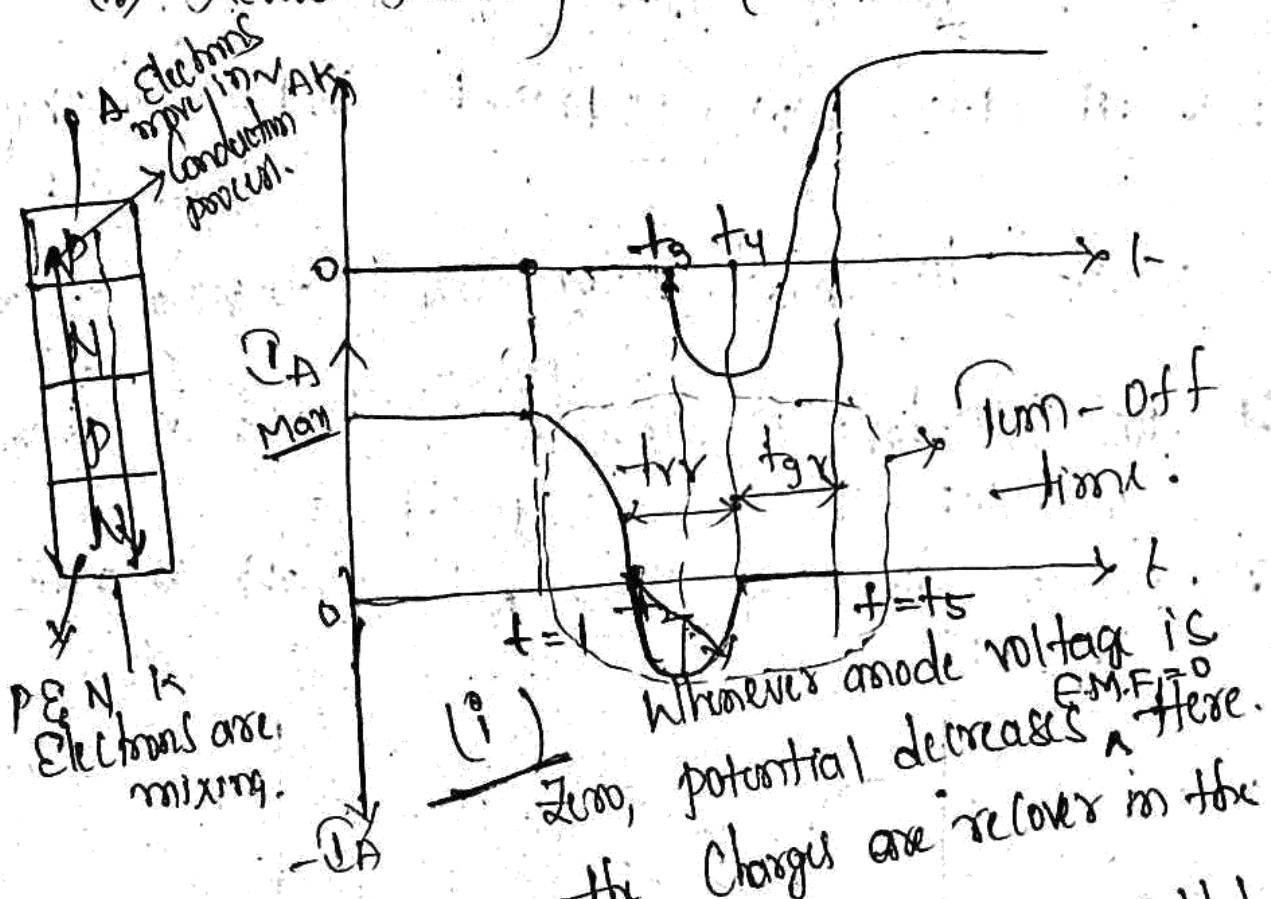- (ii) Gate Recovery time ( $t_{gr}$ ):
- (i) Reverse Recovery time ( $t_{rr}$ ):



(i) Whenever anode voltage is zero, potential decreases here. The charges are recover in the devices.  
 → the device is not suddenly off

→ These electrons are move in reverse direction when the  $V_a$  (for some period.)  
 → But some moments the electrons are slowly decreases and reaches to its original state.

(ii) Gate recovery time:  
 → But when the gate is applied to the device. some charges inject to the device.

So, those electrons are <sup>recovery</sup> in the the device (for time period).

→ This condition, the device is in Blocking State.


→ It is in  $\mu\text{sec}$  (or)  $\text{m-sec}$

→ It lies b/w  $50 \mu\text{s}$  to  $100 \mu\text{s}$  (Converter Grade SCR).

→ It lies b/w  $0$  to  $50 \mu\text{s}$  (Inverter Grade SCR)

\* Turn of time is more <sup>period</sup> is known as Converter Grade SCR.

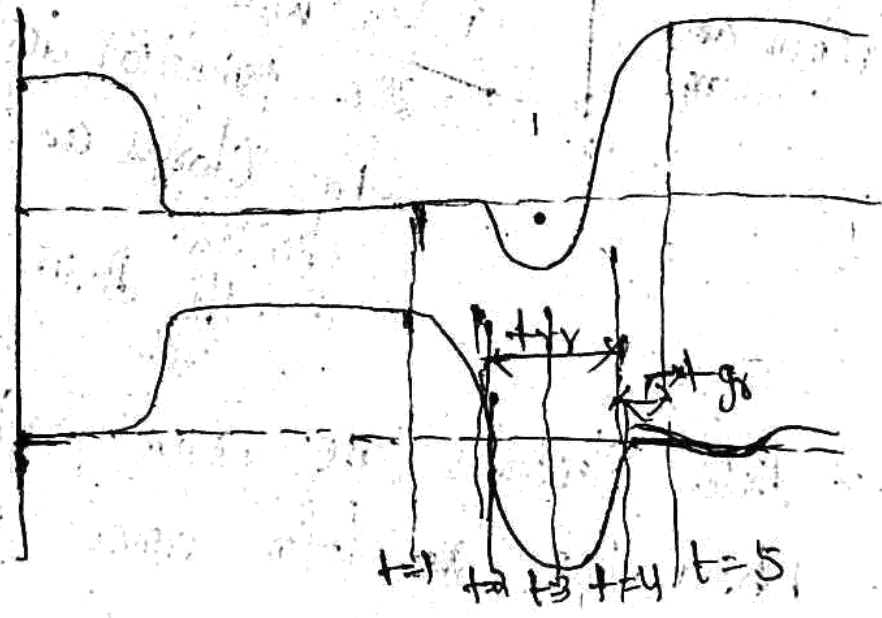\* Turn of time is small <sup>period</sup> is known as inverter Grade SCR.




## \* Protection of SCR:-

1. Voltage protection.
2. Current protection
3. Power protection →
4. Temp protection → Temperature increases, the junction breaks in the device.
5. Gate protection → So, we can control the device.

### 1. Voltage protection :- $(\frac{dv}{dt})$

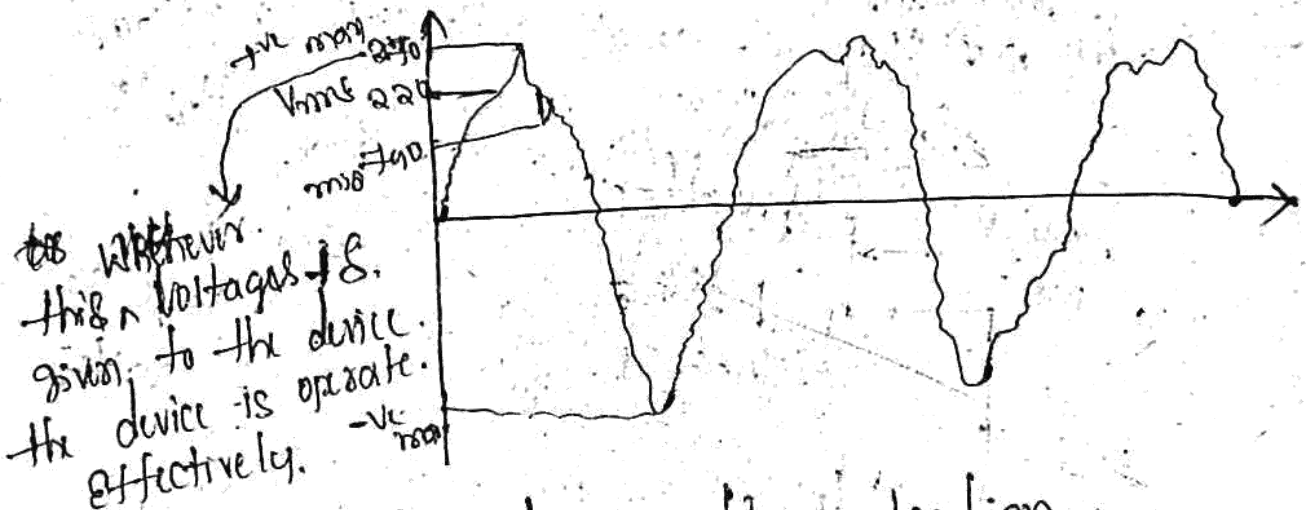- (i) Internal voltage. - the rating devices.
- (ii) External voltage



### (2) Current protection :- $\frac{di}{dt}$ protection.


- (i) Internal Current
- (ii) External Current
- (iii) False Current.

→ In desired SCR's whenever the sudden currents comes, the electrons moves slowly, and spread smoothly.

→ Whenever the sudden currents comes to the devices the device is damaged.



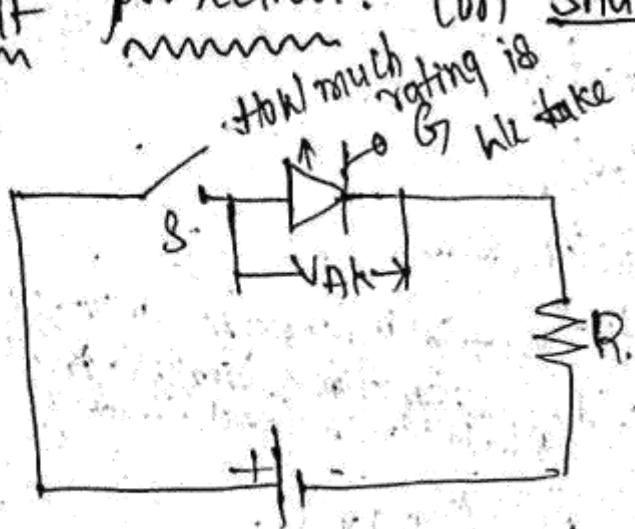
1.  $\frac{dv}{dt}$  protection? - (or) Snubber Circuit -



the voltage fluctuations due to fall so, we protect the drive

→ When the switch is closed, the initial voltage is ~~zero~~ <sup>supplied</sup>, the voltage is b/w  $V_{AK}$  because Gate 'G' is blocking state.

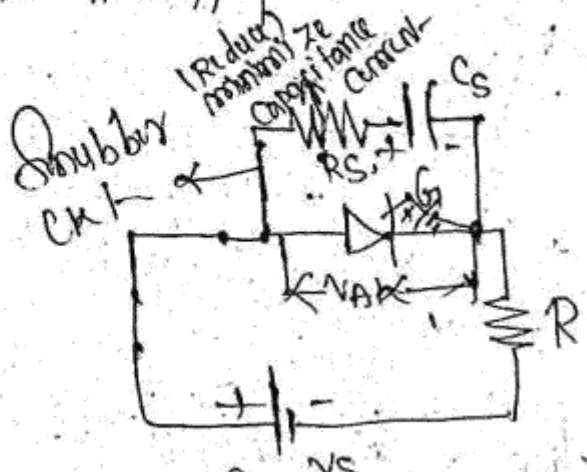→ The supply a small voltages (linear voltages)



Capacitor allows rate of change of voltage

→ In this case, the sudden voltage is supplied to the circuit, the voltage is supplied to the capacitor.


→ The capacitor does not allow sudden current.

→ It allows smooth circuit.

→ For some period the voltage across capacitor is fully charged with  $V_s$ .

$$V_s = C_s$$

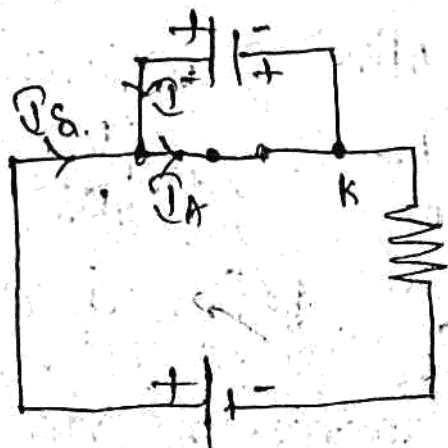→ Whenever the gate signal is applied, the device is in conduction.



$$I_A = I_G + I_C$$

→ For some time the fully charged capacitor is discharging, so capacitor current is '0'.

→ It acts as open ckt.

→ No " $R_g$ ", the SCR is controlled by  $I_G + I_C$ .

- No controlling  $I_G + I_C$ , the device will fail.

→ Snubber circuit is protected the

SCR to  $\frac{dv}{dt}$ .

17/07/19

4 4 4

1. A thyristor operating to a peak supply voltage 400V has been following specifications, repetitive  $I_p = 200$  A,  $\frac{dI}{dt} = 50$  A/ $\mu$ s,  $\left(\frac{dV}{dt}\right)_{max} = 200$  V/ $\mu$ s and  $\left(\frac{dV}{dt}\right)_{min}$ . Design a suitable snubber ckt. The minimum value of load resistances  $10 \Omega$ .

Sol :- Given data,

$$V_s = 400 \text{ V}$$


$$I_p = 200 \text{ A}$$

$$\left(\frac{dI}{dt}\right)_{max} = 50 \text{ A}/\mu\text{s}$$

$$\left(\frac{dV}{dt}\right)_{max} = 200 \text{ V}/\mu\text{s}$$

Safety factor of 2, for  $I_p$ ,  $\left(\frac{dI}{dt}\right)_{max}$ ,  $\left(\frac{dV}{dt}\right)_{max}$

$$R_L = 10 \Omega$$

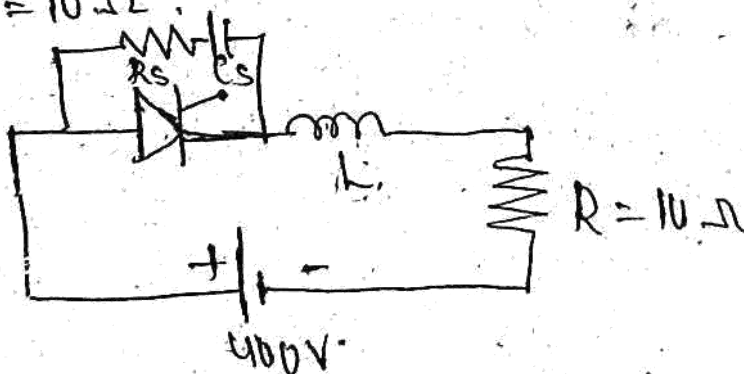

$$I_p = \frac{200}{2} = 100 \text{ A}, \quad \left(\frac{dI}{dt}\right)_{max} = \frac{50}{2} = 25 \text{ A}/\mu\text{s}$$

$$\left(\frac{dV}{dt}\right)_{max} = \frac{200}{2} = 100 \text{ V}/\mu\text{s}$$

$$L = \frac{V_s}{\left(\frac{dI}{dt}\right)_{\max}} = \frac{400}{25 \times 10^6} = 16 \text{ mH}$$

$$R_s = \frac{L}{V_s} \left(\frac{dV}{dt}\right)_{\max} = \frac{16 \times 10^{-3}}{400} \times \frac{1000}{10^{-6}} = 4 \Omega$$

When thyristor is turned on current through the thyristor

$$I_A = I_s + I_c = \frac{400}{10} + \frac{400}{4} = 140 \text{ A}$$

→ The peak current to a SCR is more than the permissible peak current of 100 A. The magnitude of  $R_s$  must be increased taking  $8 \Omega$  ( $R_{s0}$ )

Now the peak current SCR is

$$I_A = \frac{400}{10} + \frac{400}{8} = 90 \text{ A}$$

the resistance is negligible.

$$C_s = \left(\frac{2\tau}{R_s}\right) \cdot L \quad (\tau = 0.65 \mu\text{s})$$

$$= \left(\frac{2 \times 0.65}{8}\right) \times 16 \times 10^{-6}$$

$$C_s = 0.4 \text{ MF}$$

→ The value  $C_s$  is also reduced. The Energy stored  $C_s$  is small the SCR doesn't discharge from SCR when it is a turn on.

→ At instant of switch is closed transistor is open circuited and current through  $C_s$  is given by.

$$C_s \frac{dv}{dt} = \frac{V_s}{R_s + R_L}$$

$$0.3 \times 10^{-6} \frac{dv}{dt} = \frac{400}{8 + 10}$$

$$\frac{dv}{dt} = \frac{400}{18 \times 0.50 \times 10^{-6}} = 74.07 \text{ V}/\mu\text{s}$$

Since design value of  $\frac{dv}{dt}$  is less than the specified maximum of  $100 \mu\text{s}$ . Then the value of  $C_s$  chosen as correct.

$$L = 10 \mu\text{H}, R_s = 8 \Omega, C_s = 0.3 \mu\text{F}$$

\* firing or triggering CKK :-


Means controlling (turn voltage)

→ F.B.M to F.C.M.

OF → ON State.



Block diagram :-

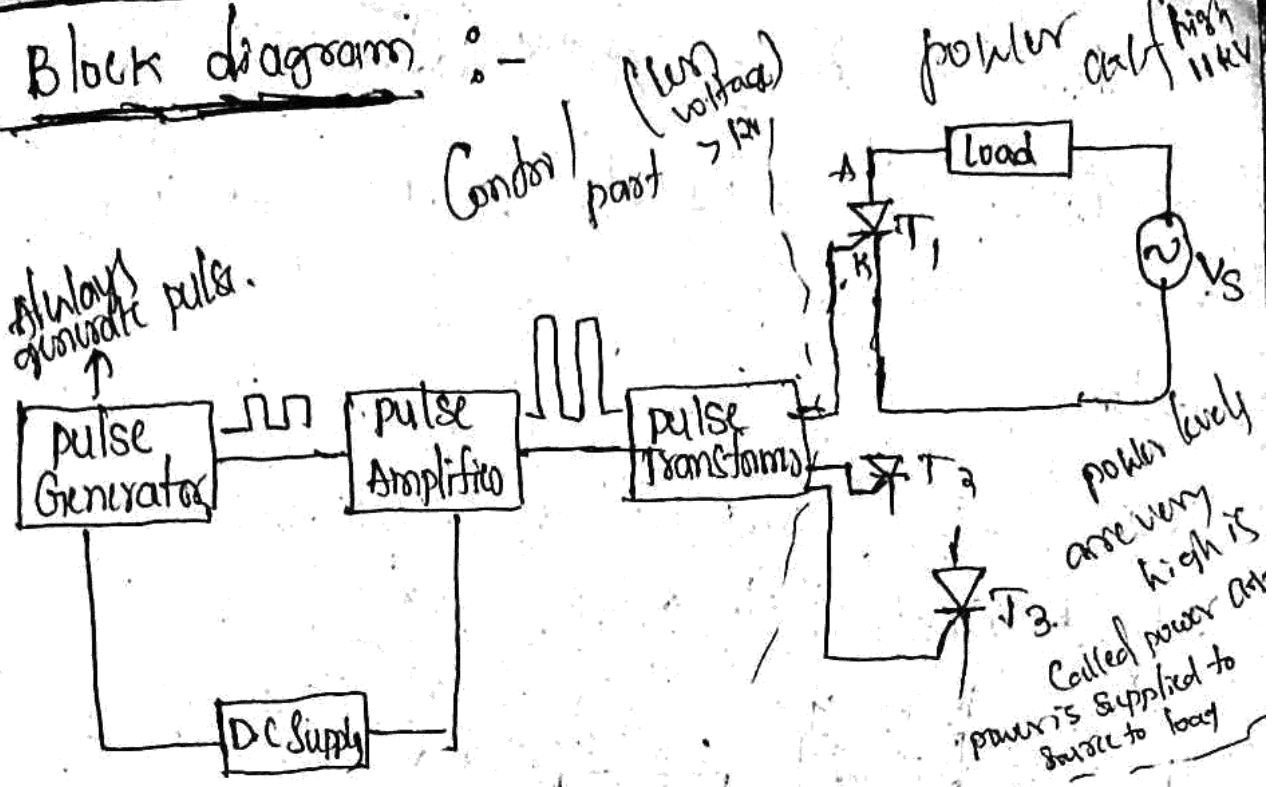

→ Generated pulses cannot turn on SCR  
 i.e., cannot provide sufficient Gate currents  
 (100 currents)

→ To avoid the problem, we go pulse  
 Amplifier

It means the magnitude increases.  
 Pulse Generator Amplifier does not repeat  
 the problem.

→ It gives greater currents.

→ pulse transformer blocks

- (i) transform pulses
- (ii) isolation process.

→ So, there is no isolation in the system  
 any problem arise in the system, then



The total system is damaged.

→ there is a isolation, the gate is on, the current flows through system.

18/04/02


These are classified into three types:

1. Resistance triggering.

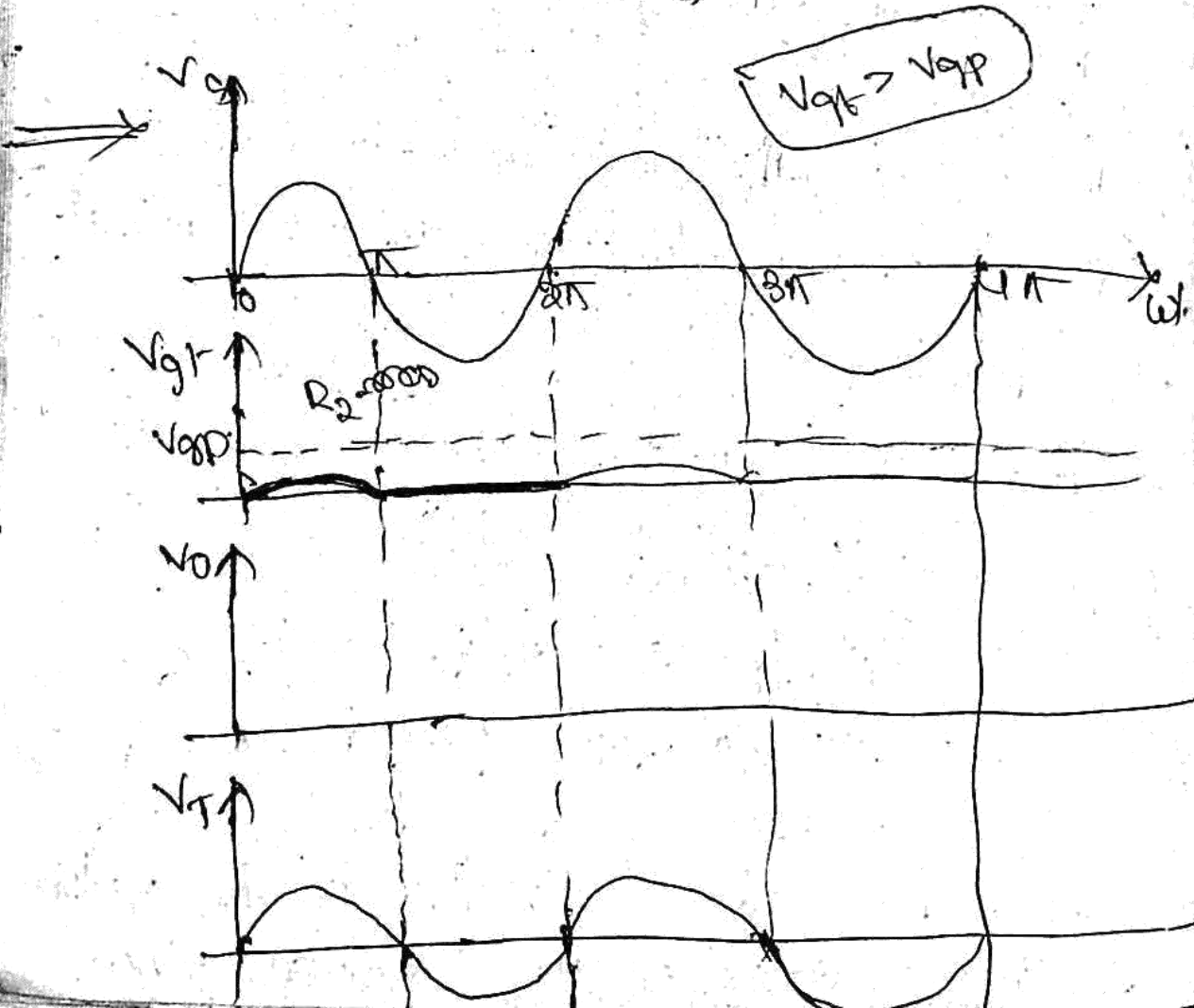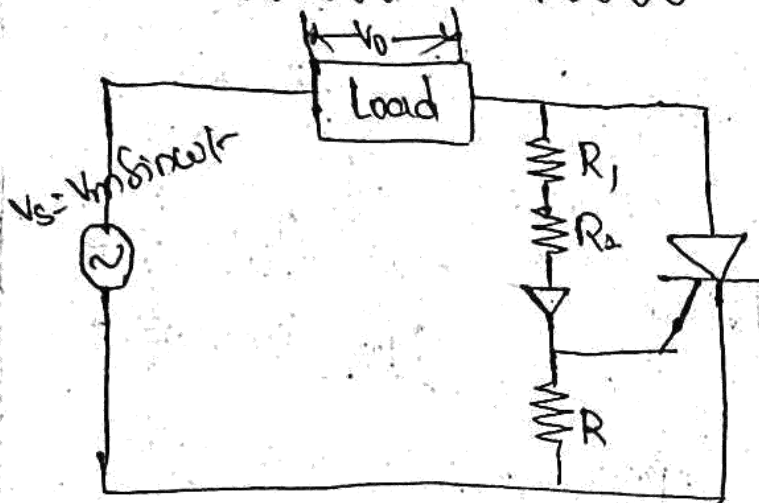

$R_2$  is min:-



$V_{gt} < V_{gp}$

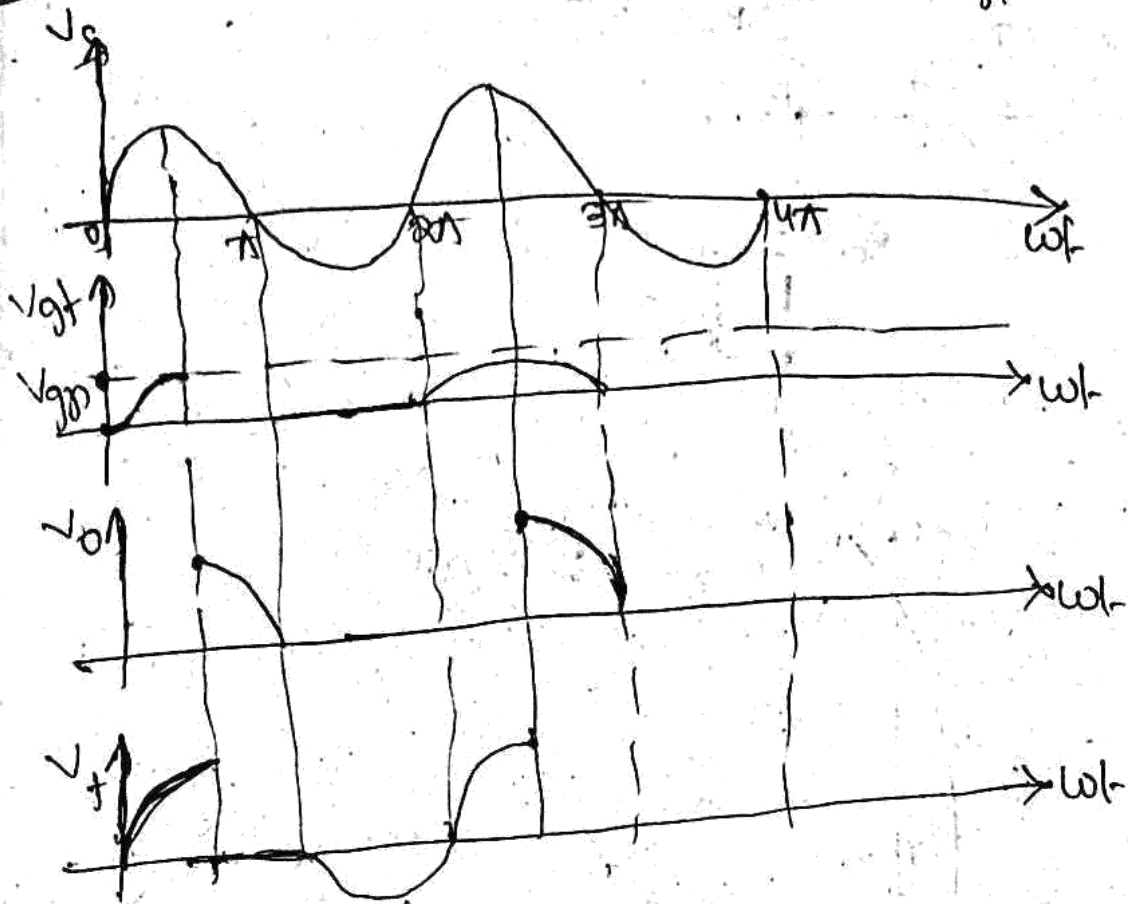


→ Main drawback is,

The Control voltage is possible is  $0-90^\circ$   
 $90^\circ-180^\circ$  this is not possible to Control


3. U.J.T Triggering:-

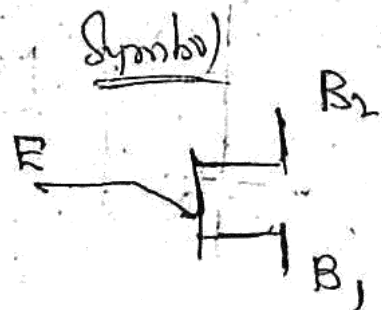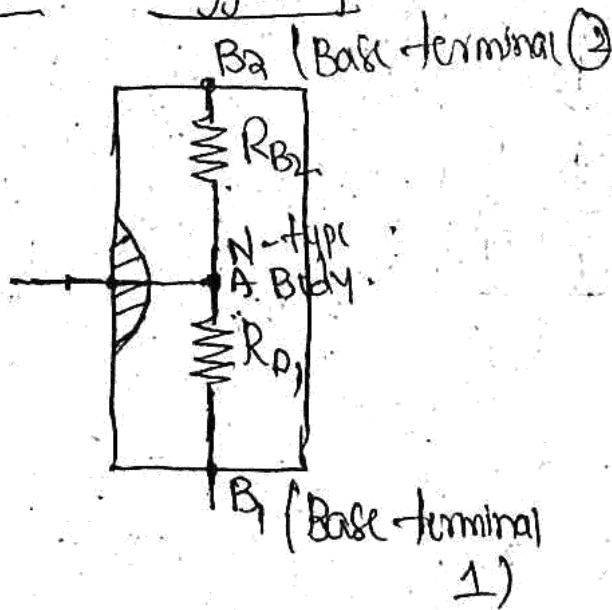

19/07/2019

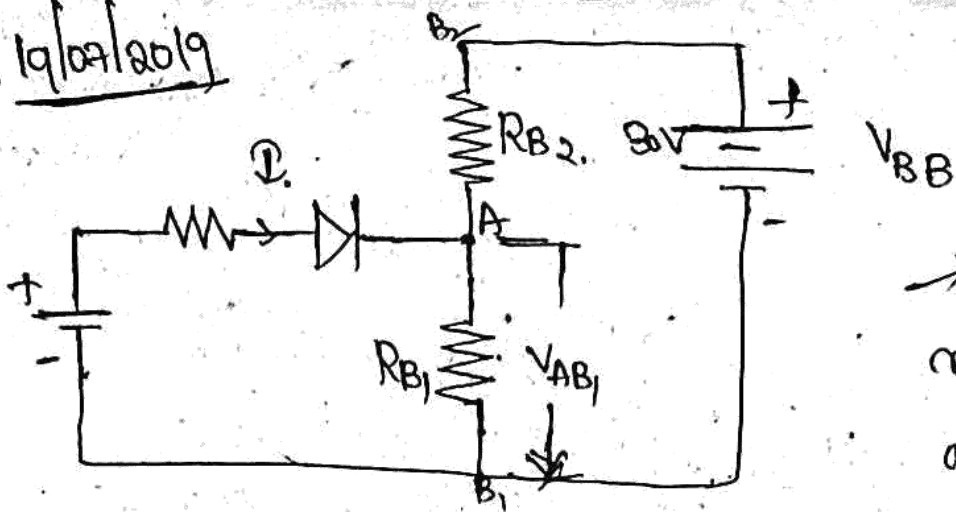


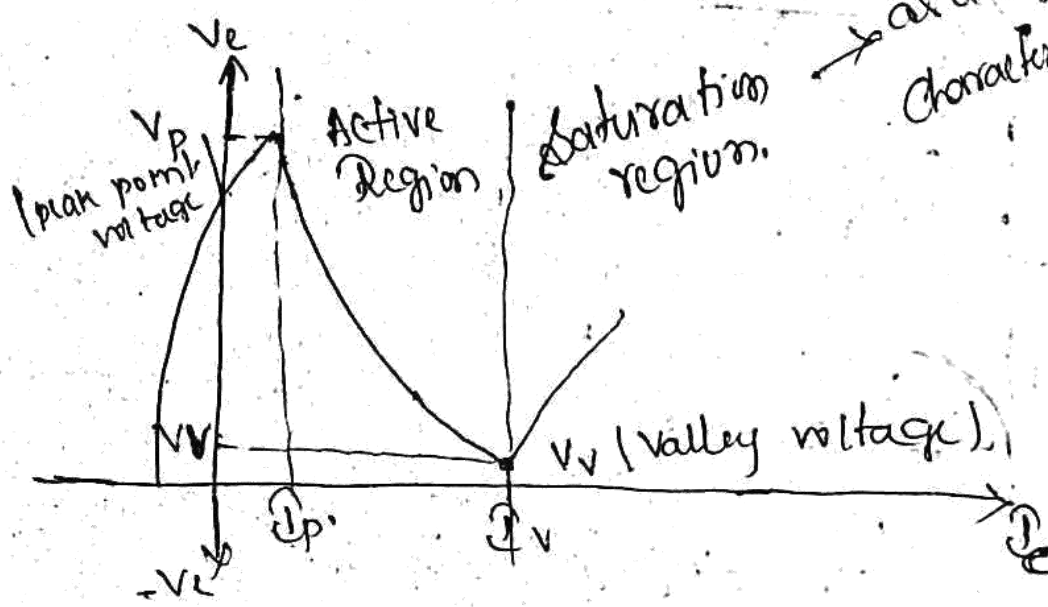→ UJT is mainly used as oscillators  
→ as a negative characteristic



\* UJT Oscillating Circuits :-

Sensitive device

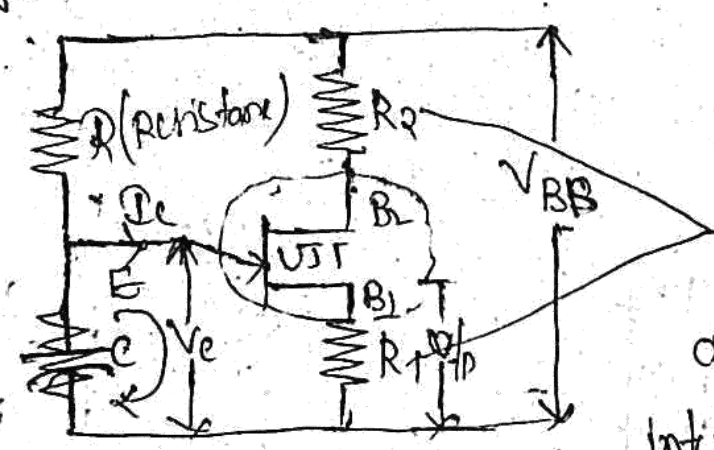

External resistance always less than the internal resistance of UJT.


→ When  $V_{BB}$  is applied to the  $R_1$  &  $R_2$ , the UJT gets off, due to Reverse bias.

→ Current through UJT is "0". It is off state.

→ When voltage is applied to the Resistor and Capacitance, Capacitance gets Charged.

→ Capacitance <sup>voltage</sup> = Emitter voltage,  $V_p$ .

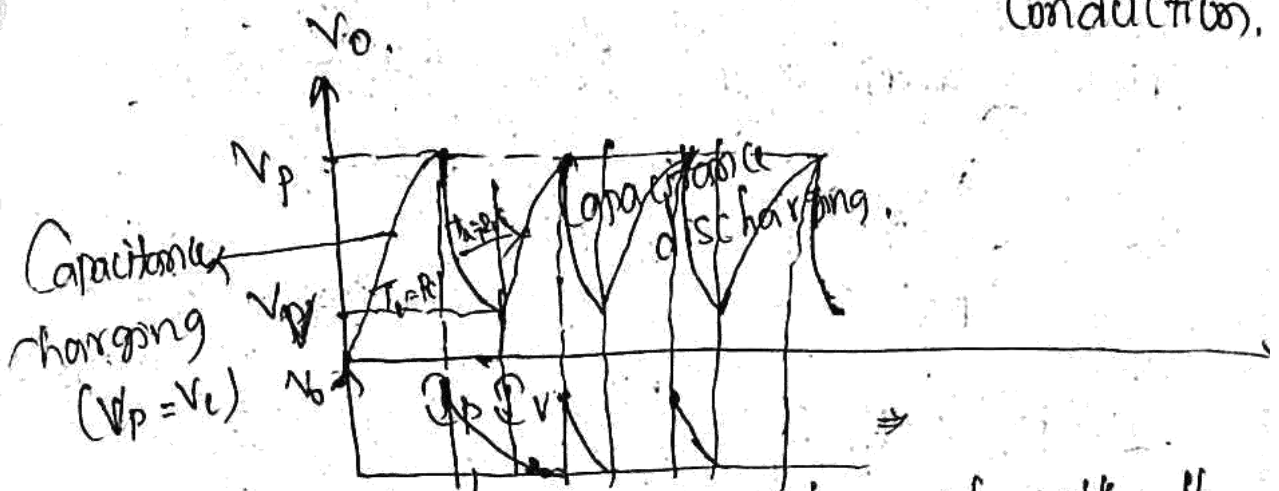→ When  $V_e = V_c = V_{BB} (1 - e^{-t/RC})$ .  
The diode is act as closed switch → gets start Conduction.



→ Again due to injection of volt the diode is in saturation and again the path gets off.

→ and Again Capacitance gets Charging.

Charging and discharging by changing the resistance values

$$V_p = \eta V_{BB} + V_p$$

$$= V_{BB} (1 - e^{-T/RC}) + V_b$$

$$V_b = V_b, \quad \eta = (1 - e^{-T/RC})$$

$$T = 1/f = RC \ln \left( \frac{1}{1-\eta} \right)$$



$$\alpha = \omega T = \omega RC \ln \left( \frac{1}{1-n} \right)$$

→  $R_2$  is used to control the temperature in device.

$$R_2 = \frac{10^4}{\eta V_{BB}}$$

→  $R_1$  is measure on triggering pulse.  
(How much time, How much time period).

$$\frac{V_{BB} \cdot R_1}{R_{BB} + R_1 + R_2} \left( \frac{5V}{V_{gt}} \right) \text{ SCR triggering voltage.}$$

$$R_{BB} = R_{B1} + R_{B2}$$

→ "R" is we can obtain peak point voltage peak point current by setting "R" maximum value.

i.e.,  $V_p$  and  $I_p$

when voltage across "C" reaches " $V_p$ ".

the voltage across "R" is  $V_{BB} - V_p$ .

and corresponding  $R_{max} = \frac{V_{BB} - V_p}{I_p}$


$$V_p = V_{BB} \eta + V_D$$

→ minimum value of "R" governed by valley point values  $V_v$  and  $I_v$  is given


by,

$$R_{min} = \frac{V_{BA} - V_v}{I_v}$$

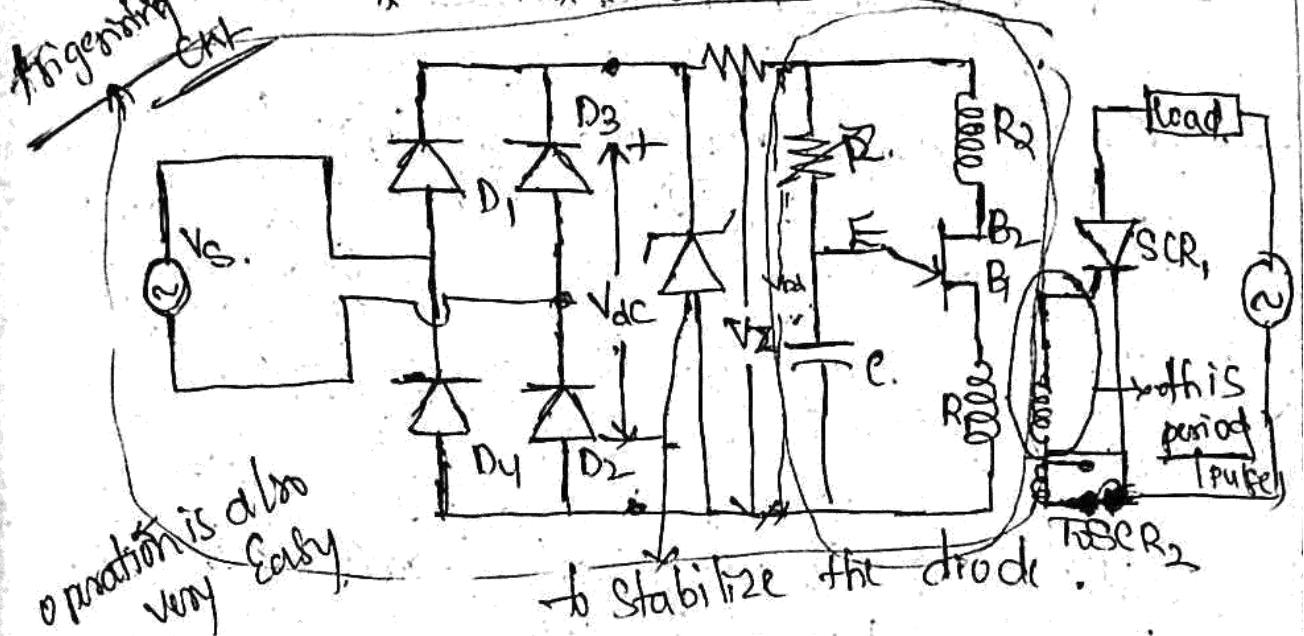
\* Synchronize UJT triggering (or) Ramp triggering \*



→ To Control load by using SCR

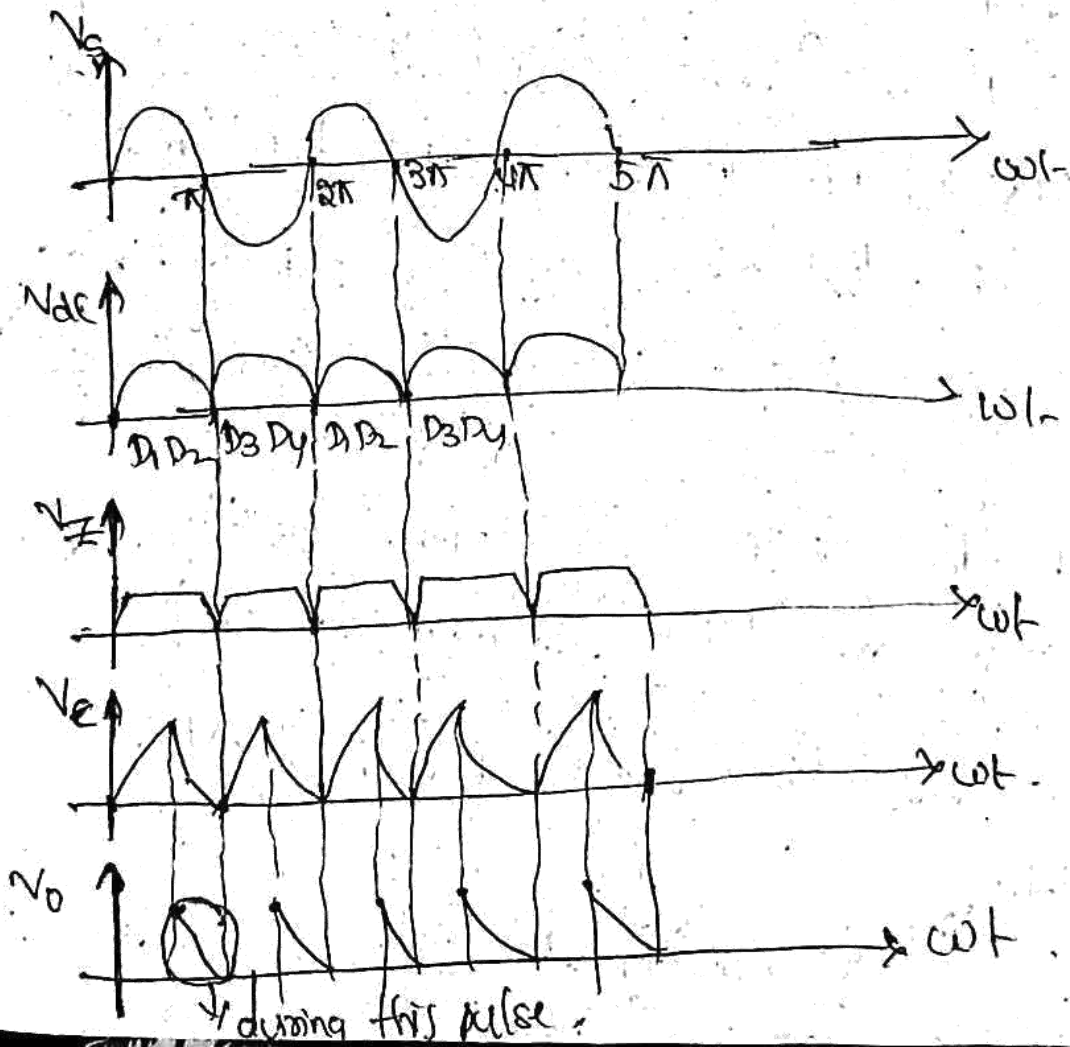

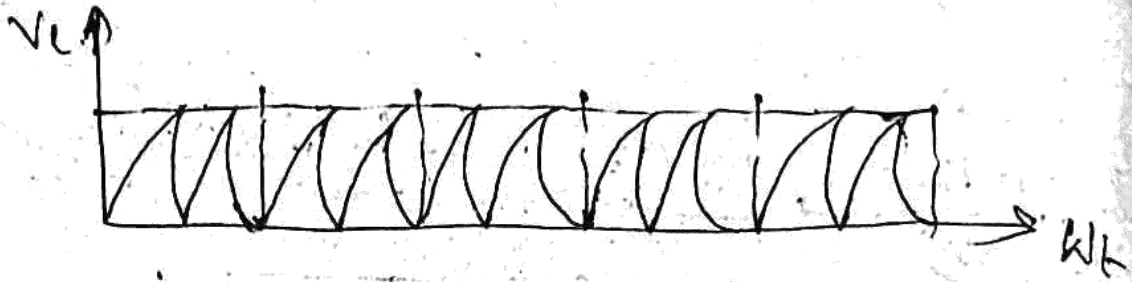→ By Changing "R" and "C", we can generate more pulses.




→ The o/p are generated during this period only (pulse)

20/09/19

\* BJT :-

→ Due to majority charge carriers, the current flow both currents

→ B.J.T is a bi direction device. 

→ It is a Current Control device.

→ ~~When~~ i/p impedance is low " $k\Omega$ "

→ Due to low i/p impedance, switching losses are more. (during the process on & off).

→ once the device comes to conduction, the conduction are low (Steady State)

→ The device can operate either Switch (or) Amplifier.   
 To Amplify the signal.


→ At small increase in Junction temperature the device fails that is called by second break over voltage.

→ This are avoided by MOSFET.

\* MOSFET :- (Metal oxide Semiconductor field Effect transistor)

→ The device is operated by field Effect Technology.


Symbol :-

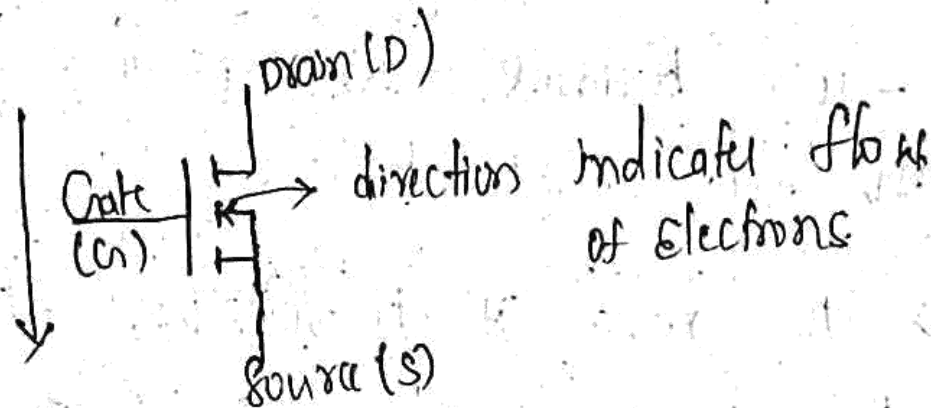

→ uni directional device. (drain to source)

→ It is a voltage Control device. \*\*\*\*

Construction :-

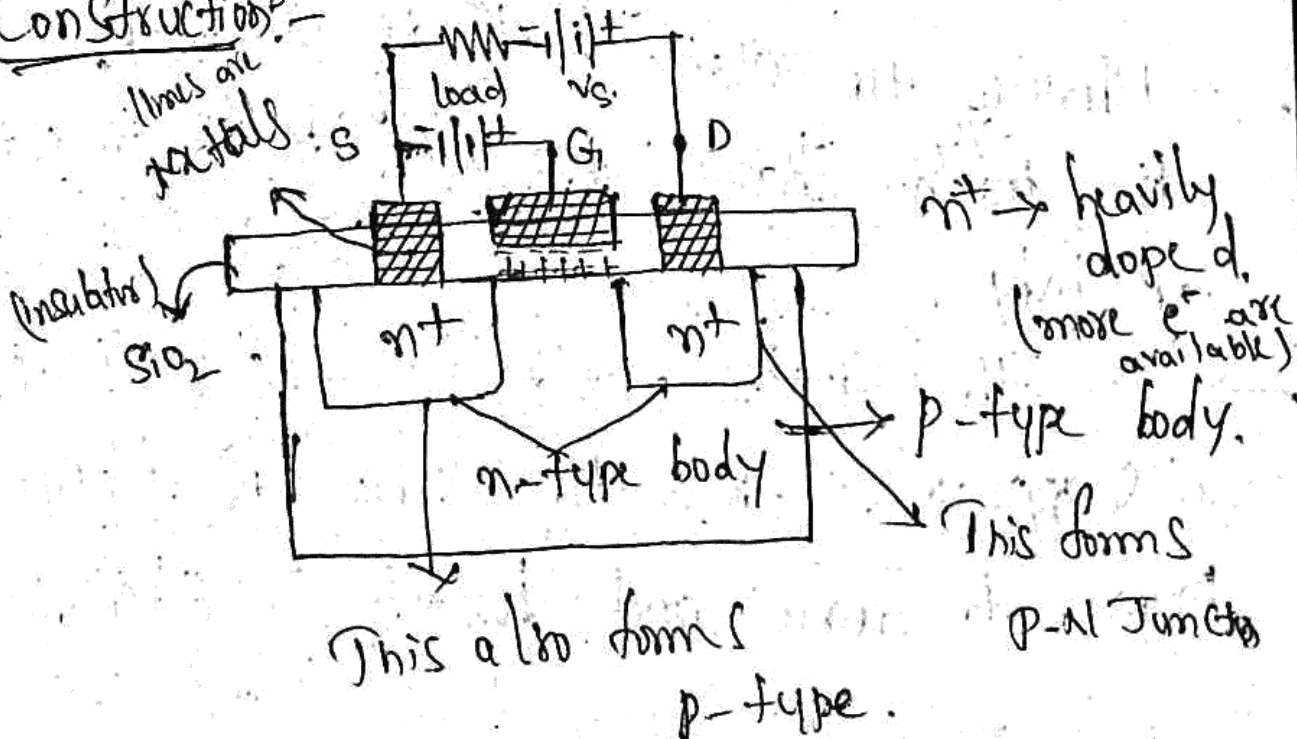

→ This metals are connected to  $SiO_2$  and  $n^+$  layer material

→ The Drain also connected to  $SiO_2$  and  $n^+$  layer materials.

→ Gate is not directly connect to  $SiO_2$  layer.

→ Whenever apply "S" and "D" the Junction becomes Reverse bias, there is no flow of electrons.

→ To make it to turn on, the Gate terminal is applied to Gate and Source terminal.

→ Whenever Gate voltage is applied, some electric field exists in the  $SiO_2$ .

→ Whenever the electric field is existed, the <sup>-ve</sup> positive charge produces <sup>+</sup> inside in p-type body.

→ By the electric field the Reverse bias disappears, then the current is flowing from Drain to Source and inside the electrons.



→ Then the device comes to conduction.  
It acts as ~~off~~ <sup>ON</sup> state, (closed switch).

→ Gate is  $\uparrow$ , Electric field  $\uparrow$ , flow of electrons  $\uparrow$ .

→ When ever Gate is removed, Electric field disappear, there is no flow of electrons, then it not comes to conduction.

→ i/p impedencies are very high (MΩ)

→ Switching losses are low.

→ Conducting loss are more in MOSFET.

→ Generally low rating voltages, @ We.   
circuit design some changes in MOSFET.

→ It can be classified into three types:

(i) p-FET


(ii) n-FET

(iii) D MOSFET.

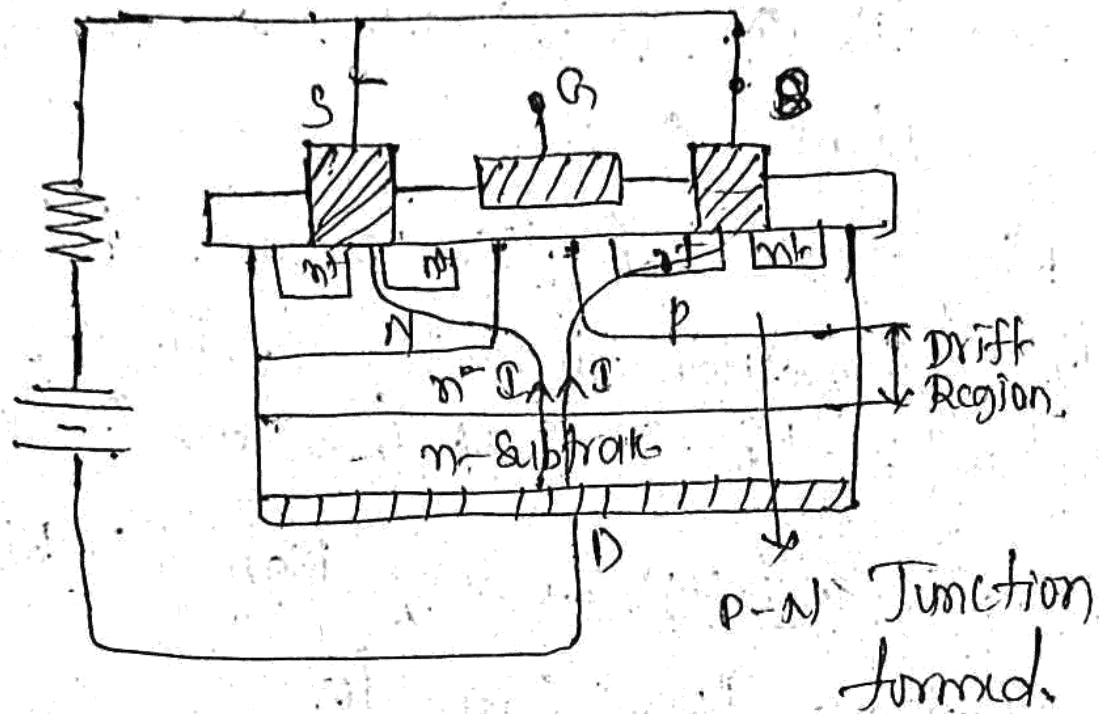(i) D. MOSFET:-

By considering we can increasing power Rating.

⇒ Drift region ↑ blocking voltage capability of device increases.



→ The junction gets Reverse bias, the device is in off state.

→ We can operate the device upto "2000V" and "150A".




→ used for low & medium power application.

→ To make conduction, the gate voltage is applied b/w gate and source terminal.


\* Characteristics :-

→ It always shows b/w v & I.

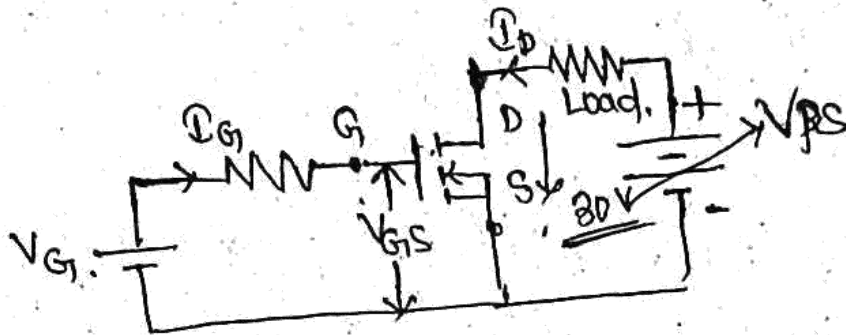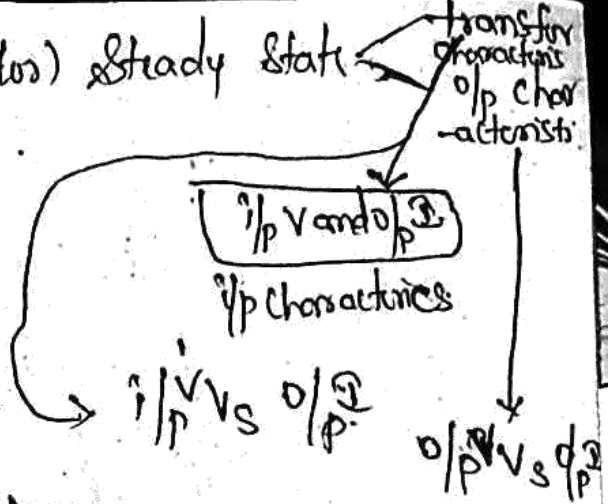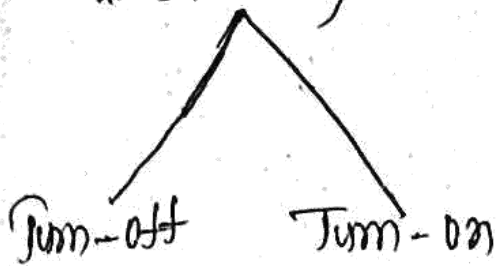1. Static Characteristics. (a) Steady State
2. Switching Characteristics.



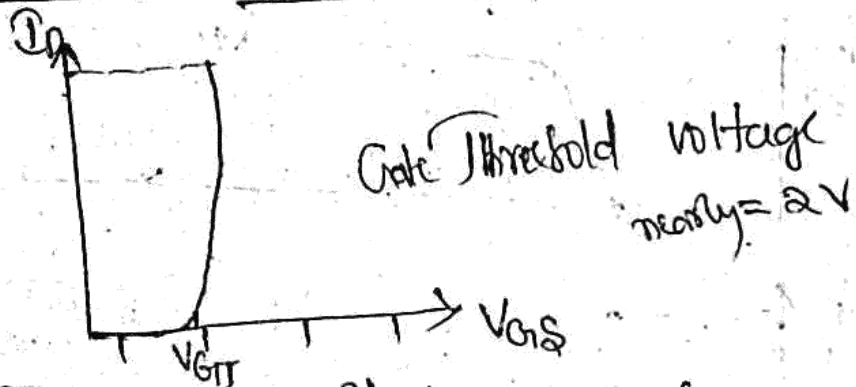
\* Transfer Charac : ( $V_{GS}$  vs  $I_D$ )



- Gate Current is slowly increasing.
- whenever sufficient voltage is applied
- once the device is on the current flows drain to source

O/p Characteristics :  $I_D$  vs  $V_{GS}$  vs  $V_{DS}$

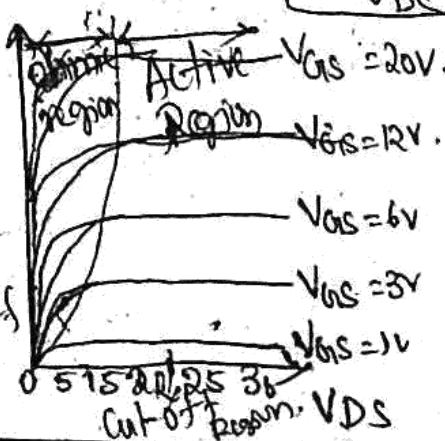Let have applied only 'n' base. '2V' is the value device is not on that is cut-off region.



ohmic  
Active  
cut-off

The voltage is kept constant ( $V_{GS}$ ) 'n'  
→  $V_{GS}$  is increase from slowly.


→ Gate voltage maintain "3V",  $V_{DS}$  increases from 0 to "30V". It Com turn on device.

→  $V_{DS}$  value decrease. increases from 0 to "30V". Gate voltage maintain "6V".

→ Ohmic Region acts as Switch in MOSFET.

→ Active Region Act as Amplifier.

\* Switching Characteristics :-

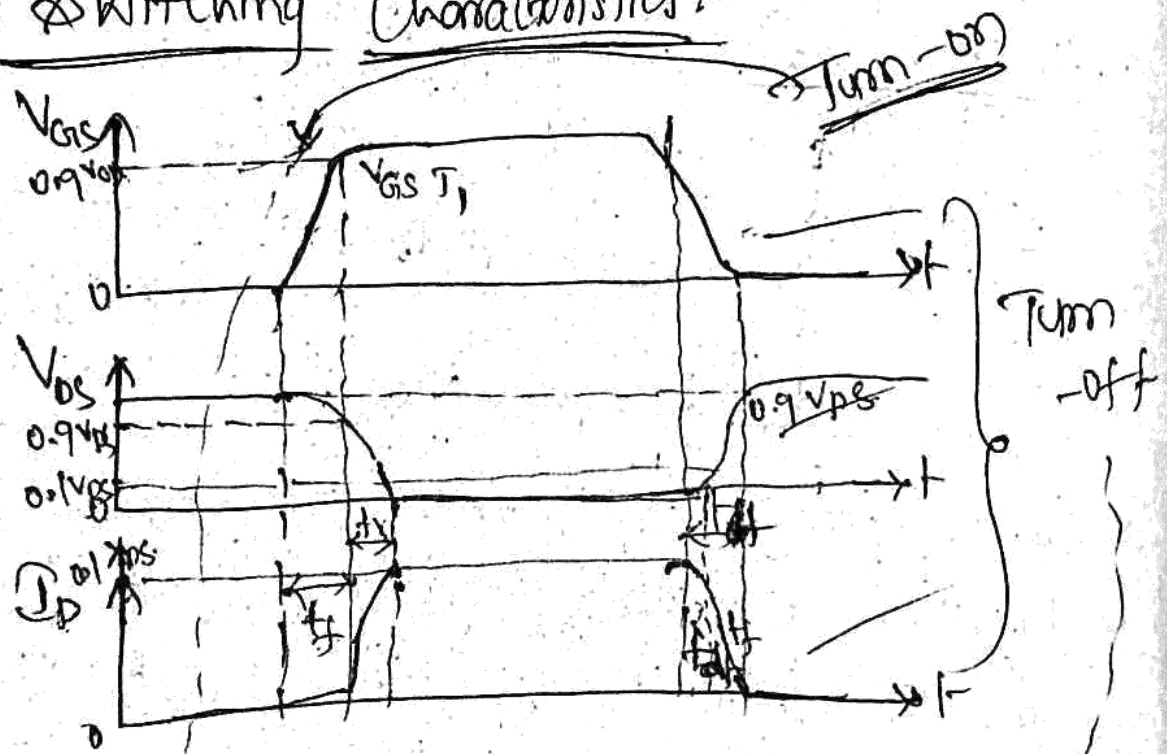

⇒  $t_{off} = t_d + t_f$

⇒  $t_{on} = t_d + t_r$

23/07/19



# \* IGBT :- Insulated Gate Bipolar Transistor :-

BJT

MOSFET

1. Switching losses are more
2. Conduction losses are low

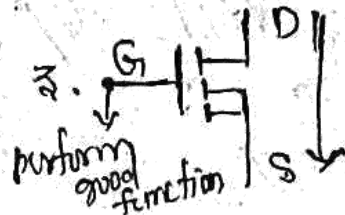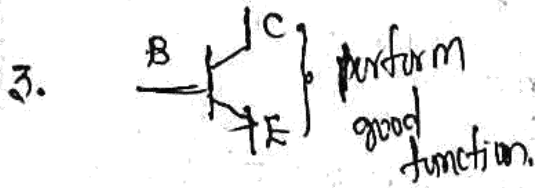1. Switching losses are low
2. Conduction losses are high



4. It is a bi-directional device

4. uni-directional device,

5. Second break down characteristics

5. No-break down characteristics

6. -ve temperature Co-efficient


6. +ve temperature Co-efficient (parallel operation is very easy)

7. Current Control device.

7. Voltage Control device.

→ By designing IGBT. These two advantages are taken is given by.

Symbol

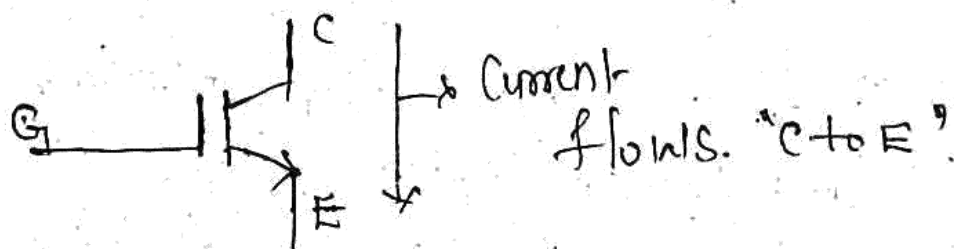


→ It is also voltage Control device.

→ It is also uni-direction device.



→ IGBT has less conduction & less switching losses.

### Structure of IGBT:-

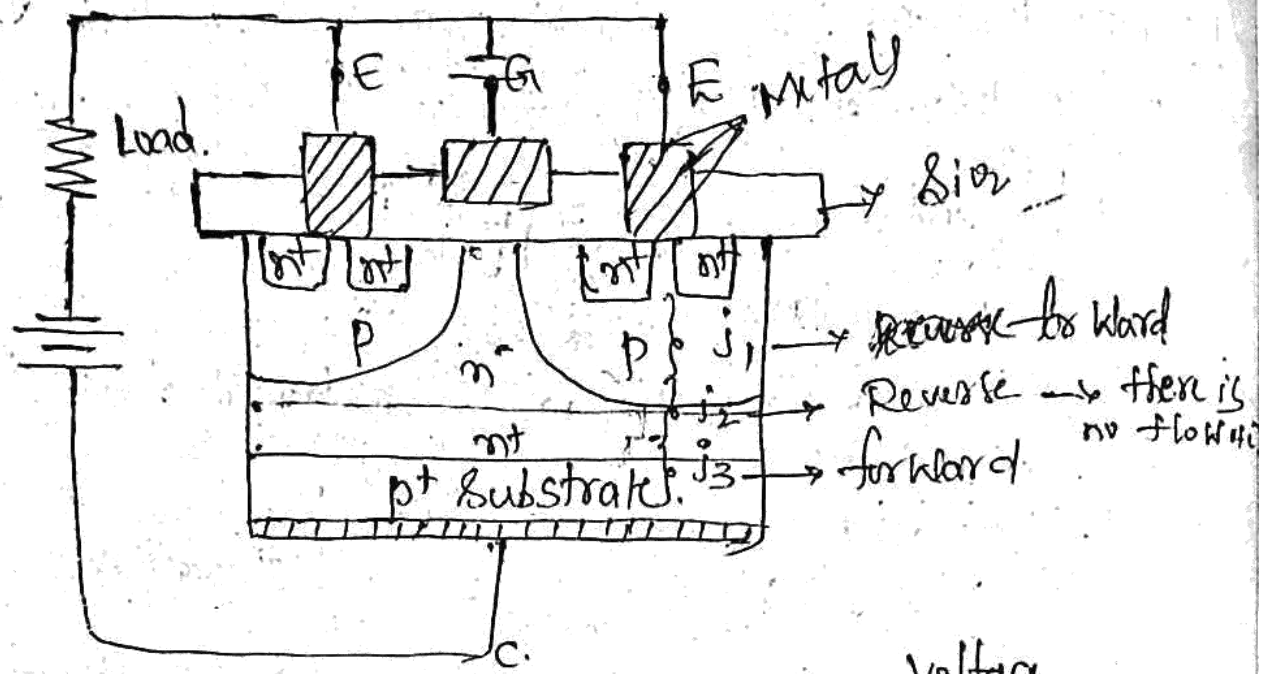


→ We must apply Gate <sup>voltage</sup> current b/w Gate and Emitter then Electric field exists. (Acts as closed state).


→ This device is also operate on field effect technology.

### Characteristics:-

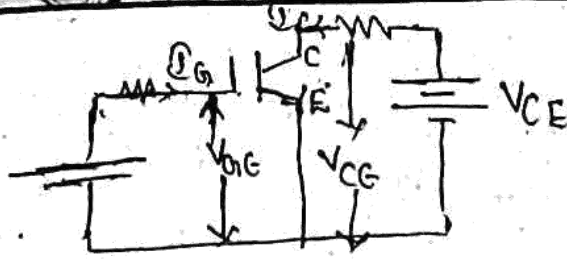1. Static characteristics { Transfer chara  
o/p chara
2. Switching characteristics { Turn-off char  
Turn-on char




Transfer Chara :-

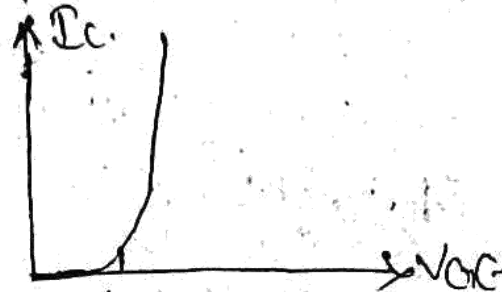


$V_{GET} \rightarrow$  Threshold gate voltage = 2V

of Characteristics :-

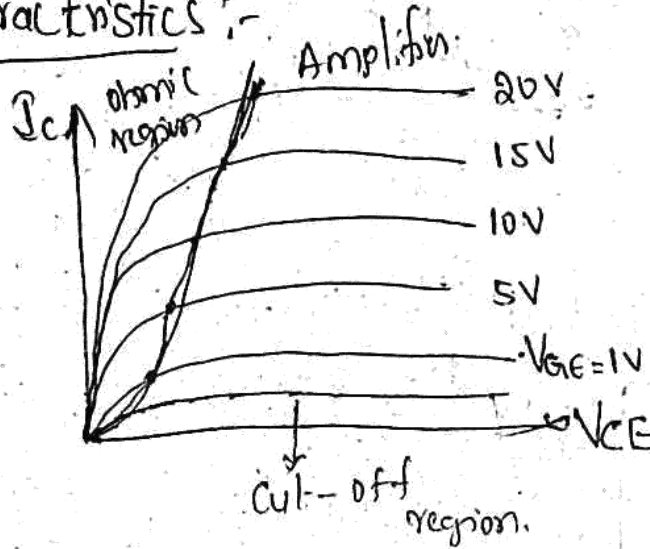

Switching Characteristics :-

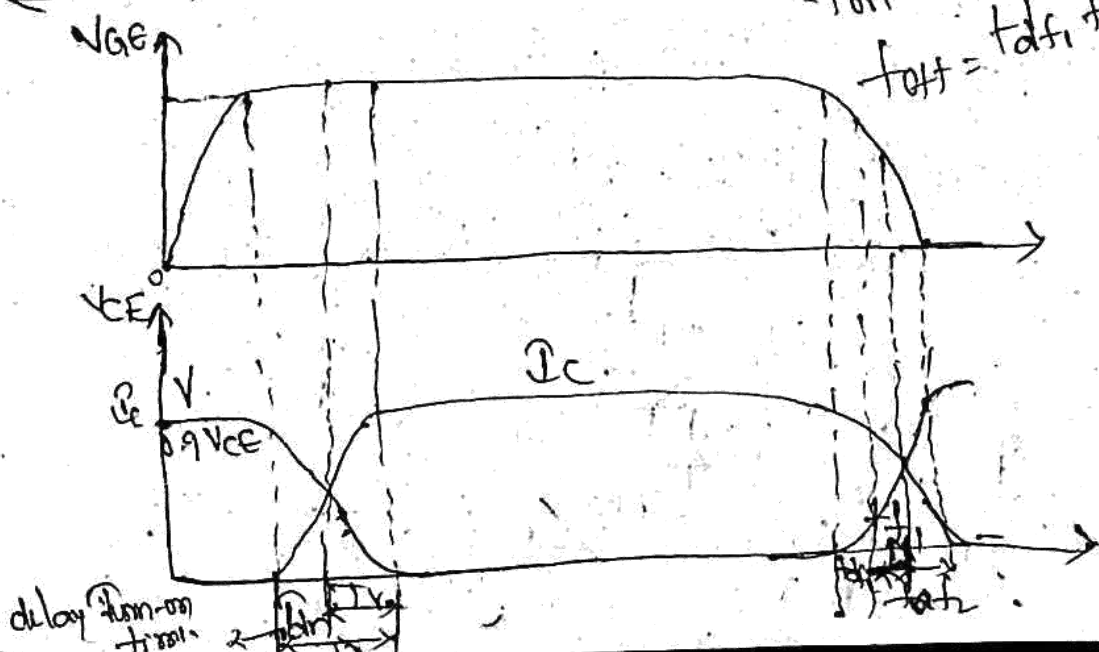

$$t_{on} = t_{d1} + t_{r1}$$

$$t_{off} = t_{f1} + t_{s1}$$

delay time  $t_{d1}$

# Applications :-

1. Inverter Application.
2. Speed Control of A.C Motors.
3. Air Craft power supply Applications.
4. Induction Transducers Applications



25/07/19

## \* Thyristor family devices :-

Inductor act as  
Conductor at high  
voltage

### 1. SCR :-



$V = 10KV$   
 $A = 5KA$

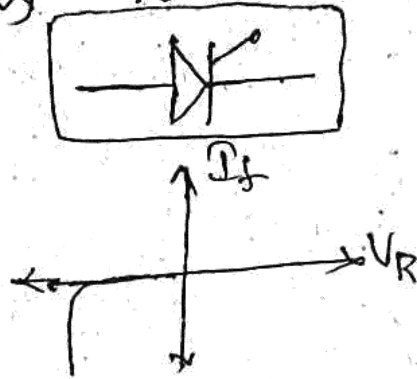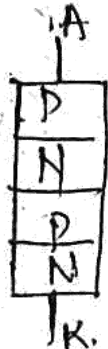
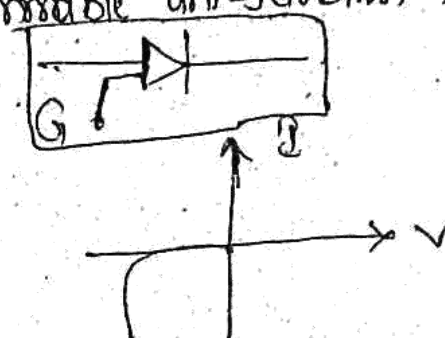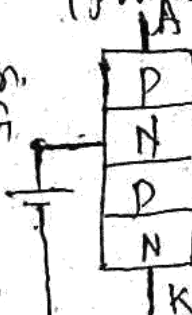
### 2. PUT :-

(programmable uni-junction transistor)

voltage more than  
7V the  
device comes  
into conduction.





Voltage is 200V  
Current is 4A


### Applications:-

→ Timing, logic, Cook Circuits.

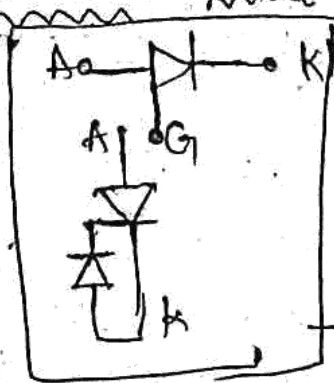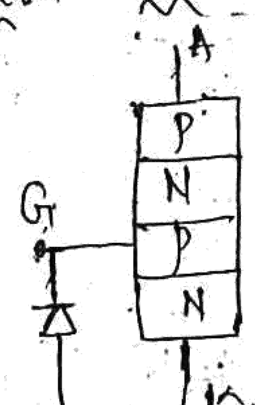
### 3. Silicon uni-directional Switch (SUS) :-



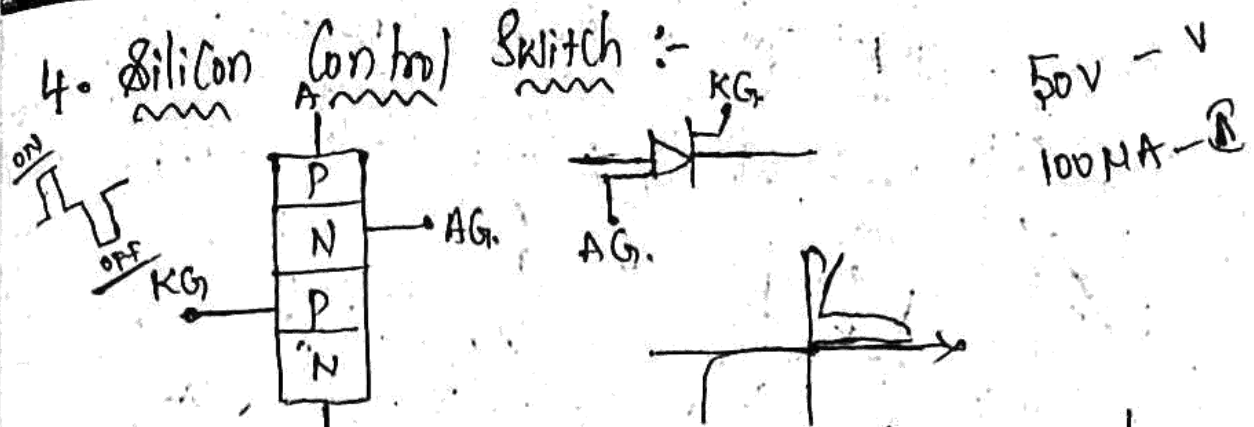
$V \rightarrow 20V$   
 $I \rightarrow 0.5A$



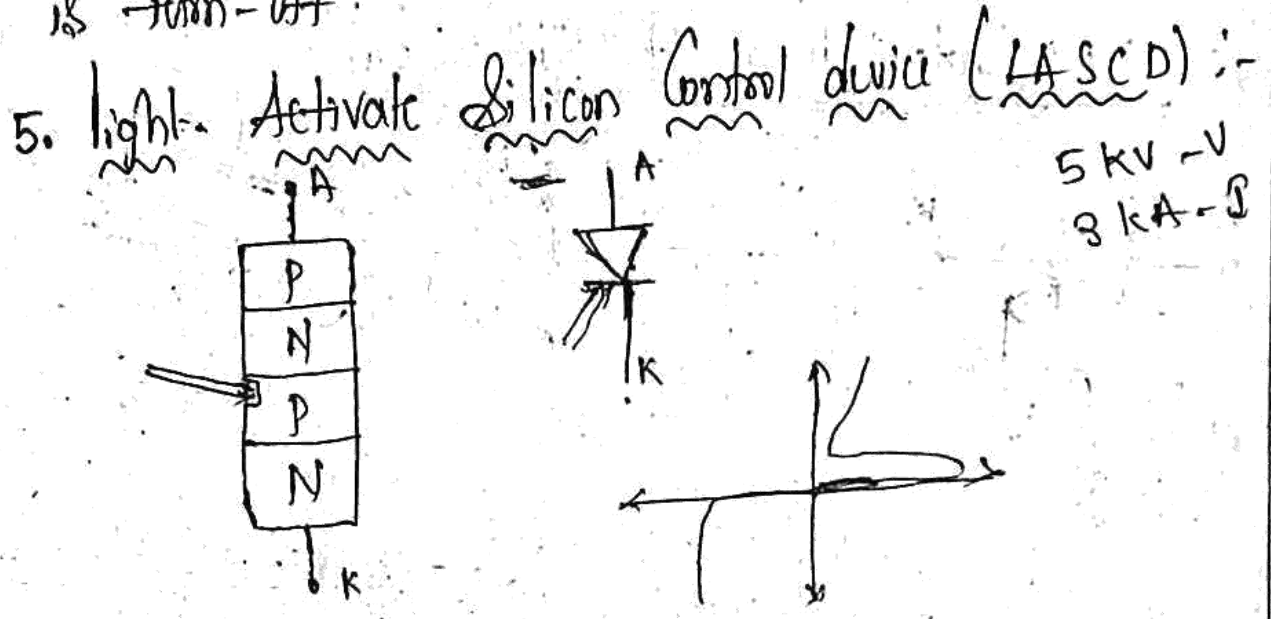Whenever +ve Gate voltage is applied the device is turn on, then -ve Gate voltage is applied the device is turn-off.



5. Direction A.c device :- (DIAC) :-

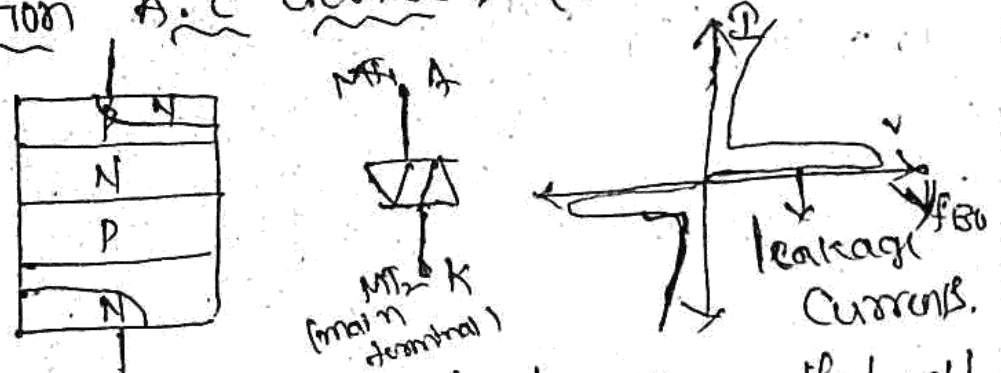


This device is turn on at fixed voltage, that volt - age is forward Break over voltage. the device is comes to conduction.


→ It is an uncontrol device.

→ We can't control the power and voltage

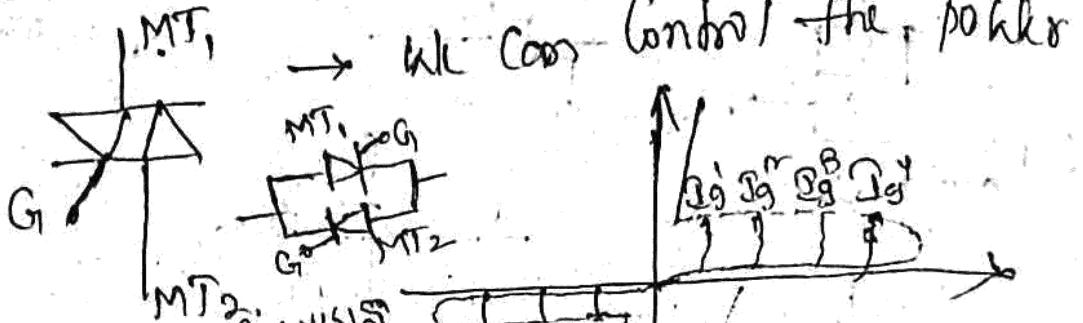
7. TRAC :- (Tri direction A.C thyristor) :-



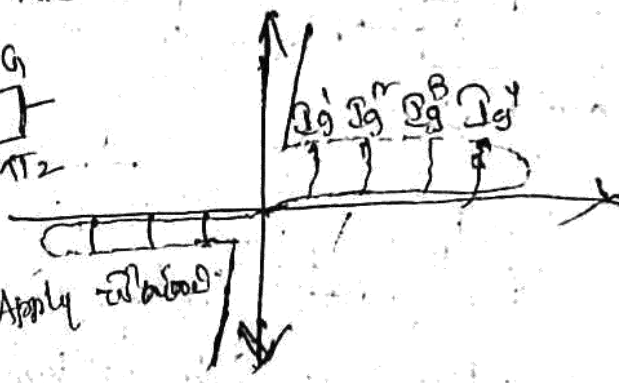
ଅବସ୍ଥା ON ବୋଲିବା ପାଇଁ  
 ଶୁଣାଣି Standard peak voltage Apply କରାଯାଏ।



8. GTO (Gate Turn-off Thyristor) :-

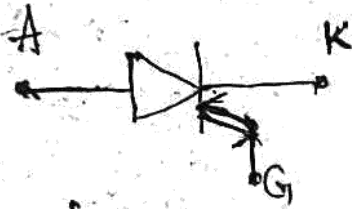

Self  
Commutating  
device.

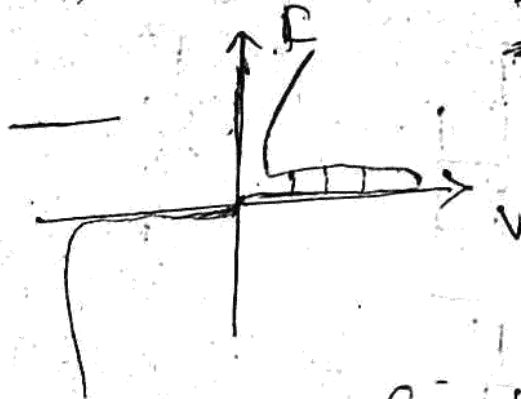

V - 6 kV  
I - 4 kA

→  $\frac{1}{3}$  rd of Reverse Gate Current is Required  
 to turn-off the device. (6A)