

13/09/19

D.C - D.C Converters

UNIT-IV

interval  $0 < t < t_1 (-RT)$


at the end of this mode the load current becomes.

$$i_1(t_0 = t_1 = LT) = I_2$$

mode II  $t_1 < t < t_2$

With initial current  $i_2(t=0) = I_2$



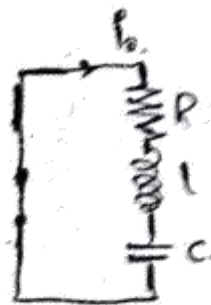
$$i_2(t) = I_2 \cdot e^{-t/RC} - R/R (1 - e^{-tR/C})$$



[Chopper is not regulated  
o/p voltage]

16/09/19

Set up Chopper:-

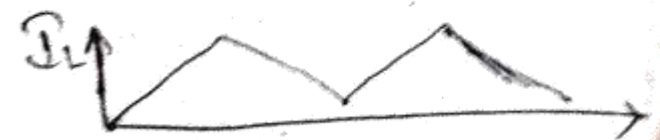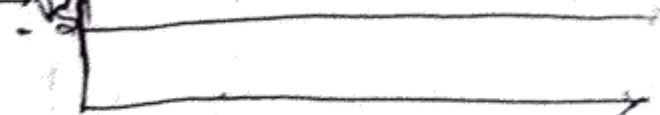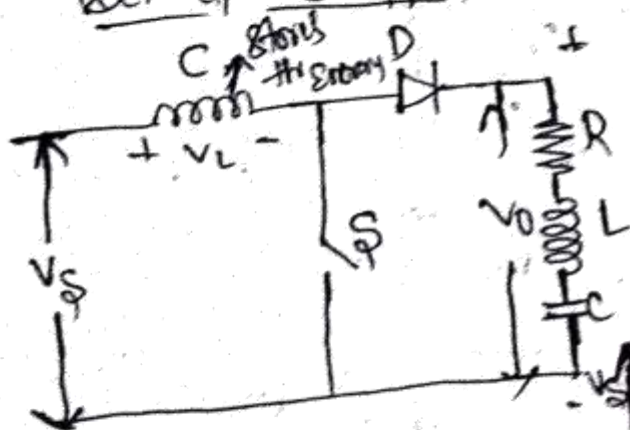

Energy Stored in inductor during on time



$$E_L = \frac{(\Delta I)^2}{2} \cdot t_1$$

$$E_L = (\text{Average voltage across inductor}) \cdot (\text{Average current})$$

$$E_L = V_s \left( \frac{I_1 + I_2}{2} \right) t_1$$

$$E_L = (V_s - V_o) \left( \frac{I_2 + I_1}{2} \right) t_2$$

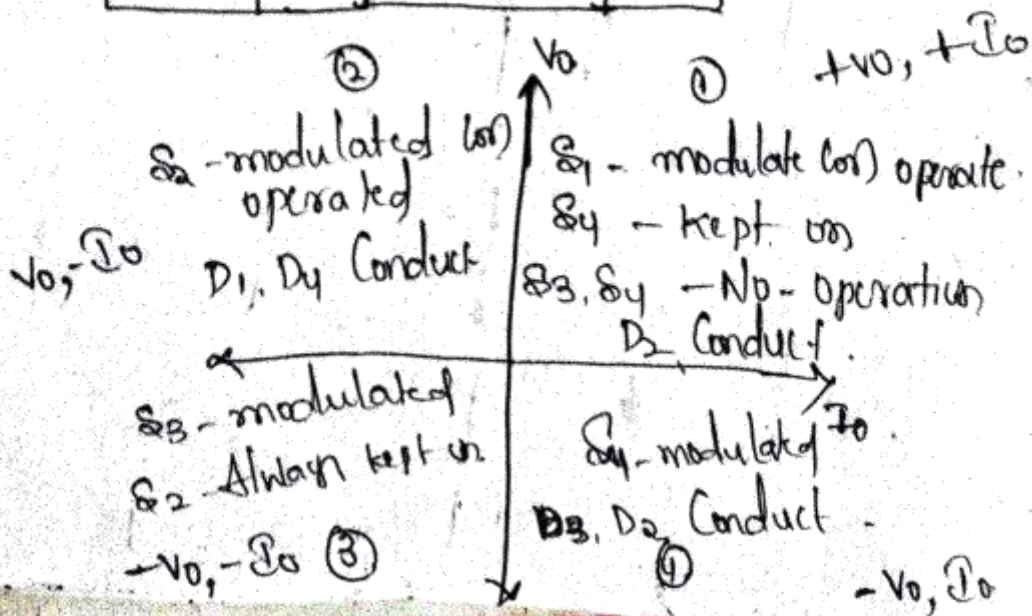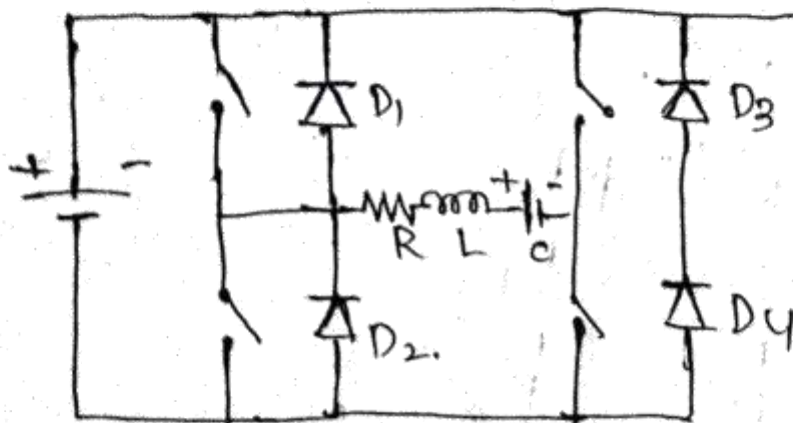
\* Four Quadrant operator chopper or multi quadrant operator chopper:-




\* SMPS [Switch Mode power supply]

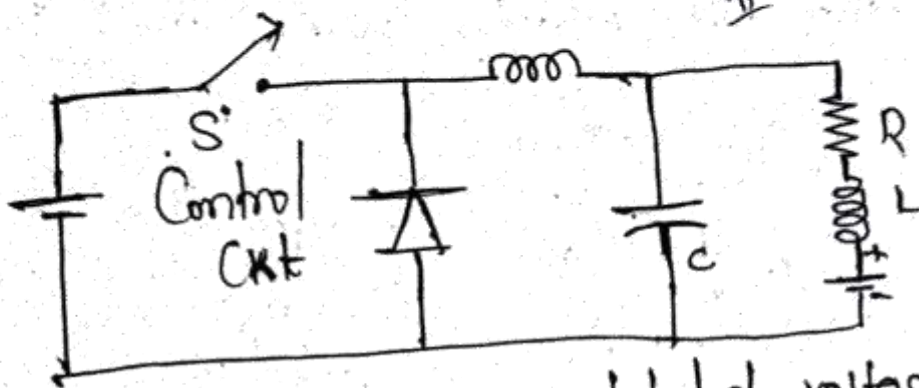(i) Buck Converters:-

I mode  $\rightarrow 0 \leq t \leq t_1$   
 II mode  $\rightarrow t_1 \leq t \leq t_2$



( $V_o$  is regulated o/p voltage).

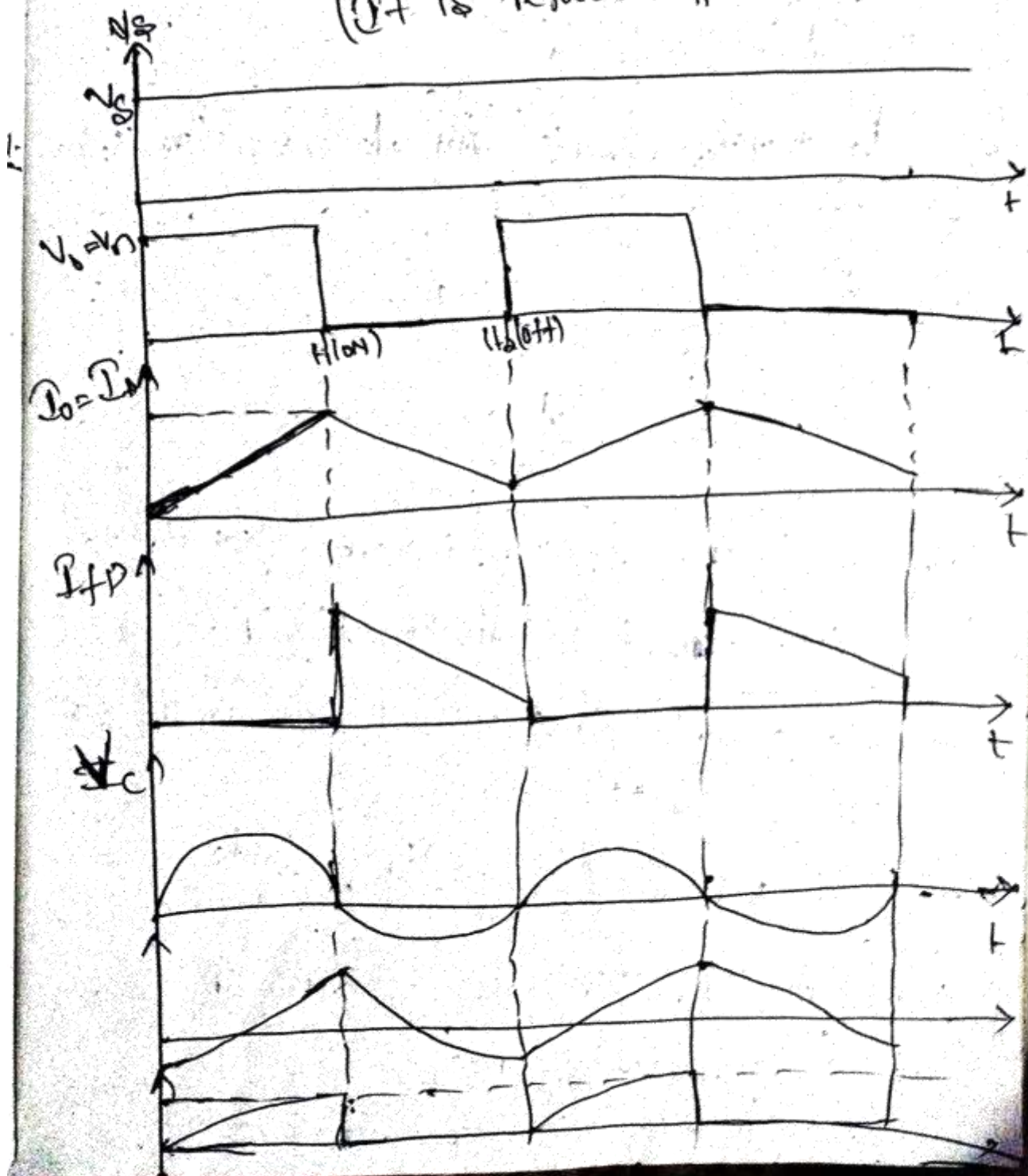

voltage across inductor  $L$ .

$$V_L = L \frac{di}{dt}$$

Assuming that the inductor current rises linearly from  $i_1$  to  $i_2$  in time  $t_1$ .

$$V_S - V_O = \frac{I_2 - I_1}{t_1} = L \cdot \frac{\Delta I}{t_1} \rightarrow (1)$$

$$t_1 = \frac{\Delta I \cdot L}{V_S - V_O} \rightarrow (2)$$

And the inductor current falls linearly from  $i_2$  to  $i_1$  in time  $t_2$ .

$$-V_O = -L \cdot \frac{\Delta I}{t_2} \rightarrow (3)$$

$$t_2 = \frac{\Delta I \cdot L}{V_O} \rightarrow (4)$$

Where,  $\Delta I = I_2 - I_1$  is the peak to peak ripple current of the inductor "L"

→ Equating the values of  $\Delta I$  in Eqn (1) & (2) gives

$$\Delta I = \frac{(V_S - V_O)t_1}{L} = \frac{V_O t_2}{L}$$

Substitute  $t_1 = kT$  and  $t_2 = (1-k)T$

The Average o/p voltage is

$$V_O = V_S \cdot \frac{t_1}{T} = k \cdot V_S \rightarrow (5)$$

Assuming a lossless Circuit

$$V_s I_s = V_a I_a = k V_s I_a$$

and average i/p Current is

$$I_s = k I_a \quad \rightarrow (6)$$

The Switching period 'T' can be expressed as

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I_L}{V_s - V_a} + \frac{\Delta I_L}{V_a}$$

$$T = \frac{1}{f} = \frac{I_L V_s}{V_a (V_s - V_a)} \quad \rightarrow (7)$$

Which gives the peak to peak ripple current.

$$\Delta I = \frac{V_a (V_s - V_a)}{f L V_s} \quad \rightarrow (8)$$

(or)

$$\Delta I = \frac{V_s k (1-k)}{f L} \quad \rightarrow (9)$$

Using Kirchhoff's Current law, Inductor.

Current  $I_L$  is.

$$I_L = i_c + i_o$$

If we assume the load ripple fraction current  $\Delta i_o$  is very small and negligible  $\Delta i_c = \Delta I_L$

$\Rightarrow$  The Average Capacitor Current which flows into for  $t_1/2 + t_2/2 = T/2$ .

$$I_c = \frac{\Delta I}{4}$$

The Capacitor voltage is expressed as

$$V_c = \frac{1}{C} \int i_c dt + V_c(t=0)$$

and the peak to peak ripple voltage of the capacitor is

$$\Delta V_c = V_c - V_c(t=0) = \frac{1}{C} \int_0^{T/2} \frac{\Delta I}{4} dt.$$

$$= \frac{\Delta I T}{8C} = \frac{\Delta I}{8fc} \rightarrow (10)$$


Substituting the values of  $\Delta I$  from Eq (8), (9) & (10).


$$\Delta V_c = \frac{V_a(V_s - V_a)}{8LCf^2V_s} \rightarrow (11)$$

$$\Delta V_c = \frac{V_s k(1-k)}{8LCf^2} \rightarrow (12)$$

17/09/19


Boost Converter :- ( $V_o > V_s$ ).

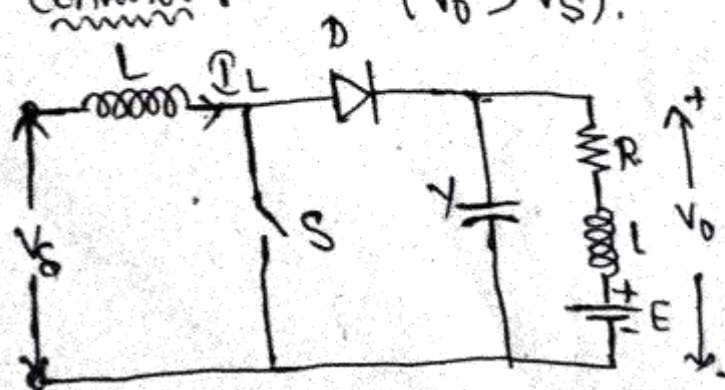

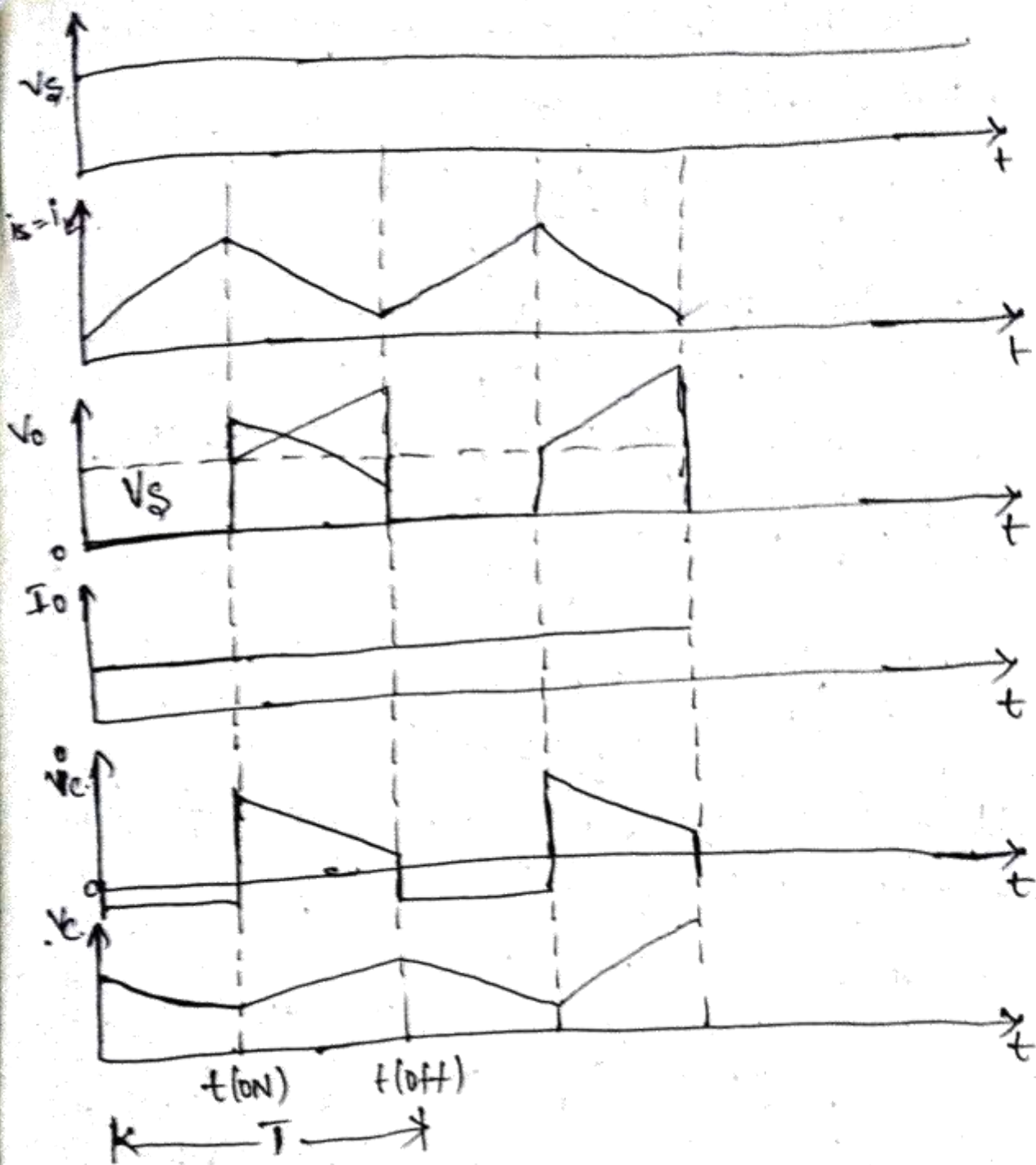

Switch ON


$0 < t < t_1$

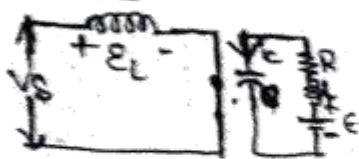

$$k = \frac{t}{T}$$

Switch OFF

$t_1 < t < t_2$

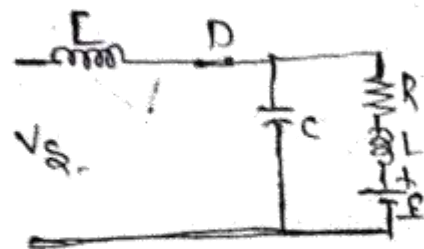

$$k = \frac{1}{1-k}$$

Assume that the inductor current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$ ,

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \rightarrow (1)$$

$$(or) t_1 = \frac{\Delta I L}{V_s} \rightarrow (2)$$

And the inductor current falls linearly from  $I_2$  to  $I_1$  in time  $t_2$ .

$$V_s - V_a = -L \frac{\Delta I}{t_2} \rightarrow (3)$$

$$(or) t_2 = \frac{\Delta I L}{V_a - V_s} \rightarrow (4)$$

Where,  $\Delta I = I_2 - I_1$ , is the peak-to-peak ripple current of inductor 'L'

→ from Eqn (1) & (3)

$$\Delta I = \frac{V_s t_1}{L} = \frac{(V_a - V_s) t_2}{L}$$

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  yield the average of voltage.

$$V_a = V_s \frac{T}{t_1} = V_s (1-k) \rightarrow (5)$$

Which gives  $(1-k) = \frac{V_a}{V_s} \rightarrow (6)$

→ Substituting  $k = \frac{t_1}{T} = t_1 f$  into Eqn (6)

$$t_1 = \frac{V_a - V_s}{V_a \cdot f} \rightarrow (7)$$



Assume lossless Converter,  $V_S I_S = V_O I_O = \frac{V_S I_O}{1-k}$

The average I/p Current is,

$$I_S = \frac{I_O}{1-k} \rightarrow (8)$$

The Switching Period 'T' Can be found.

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I_L}{V_S} + \frac{\Delta I_L}{V_O - V_S}$$

$$T = \frac{\Delta I_L V_O}{V_S (V_O - V_S)} \rightarrow (9)$$

and thus gives the peak to peak ripple Current

$$\Delta I = \frac{V_S (V_O - V_S)}{f \cdot L \cdot V_O} \rightarrow (10)$$

$$\Delta I = \frac{V_S}{f} \cdot \frac{k}{L} \rightarrow (11)$$

When the transistor is ON, the Capacitor supplies the load Current for  $t = t_1$ .

→ The average Capacitor Current during time  $t_1$  is  $I_C = I_O$  and the peak to peak ripple voltage of the Capacitor is.

Changing Capacitor voltage.

$$\Delta V_C = V_C - V_C(t_{20}) = \frac{1}{C} \int_0^{t_1} I_C dt = \frac{1}{C} \int_0^{t_1} I_O dt = \frac{I_O t_1}{C}$$

Substituting  $t_1 = \frac{(V_O - V_S)}{V_O f}$  from Eqn (7) gives

$$\Delta V_c = \frac{I_a (V_a - V_s)}{V_a \cdot f C} \rightarrow (13)$$

(or)

$$\Delta V_c = \frac{I_a k}{f C} \rightarrow (14)$$

Condition for Continuous Inductor <sup>Current</sup> & Capacitor  
- ripple No voltage.

If  $I_L$  is Average inductor Current, the inductor ripple Current

$$\Delta I = Z I_c$$

using Eqn (5) & (11) We get.

$$\frac{k V_s}{f L} = Z I_L = Z I_a = \frac{Z V_s}{(1-k) R}$$

Which gives the Critical value of inductor  $L_c$  is

$$L_c = L = \frac{k(1-k)R}{2f} \rightarrow (15)$$

If  $V_c$  is Average Capacitor voltage, the Capacitor ripple voltage  $\Delta V_c = 2 V_A$ . Using Eqn

(14)

$$\frac{I_a k}{C f} = 2 V_a = 2 I_a R$$

Which gives Critical value of Capacitor.

$$C_c = \frac{k}{2fR} \rightarrow (16)$$

## For Buck Converter:-

⇒ Condition for Continuous inductor Current & Capacitor voltage.


$$L_c = L = \text{Critical value of Inductor} = \frac{(1-k)R}{2f}$$

$$\text{Critical value of Capacitor } C_c = C = \frac{1-k}{16LF^2}$$

## Problem:-

1. The Buck Regulator shown in figure has an i/p voltage of  $V_s = 12V$ . The required average o/p voltage is  $V_a = 5V$ , at  $R = 500\Omega$  and the Peak to peak o/p ripple voltage is ~~with~~ "20mV". The switching frequency is 25 kHz. If the Peak to peak ripple current of the inductor is limited to 0.8 A, Determine the duty cycle (k), the filter inductance (L), (c) the filter Capacitor (C) (d) the Critical values of L and C.

Soln:-

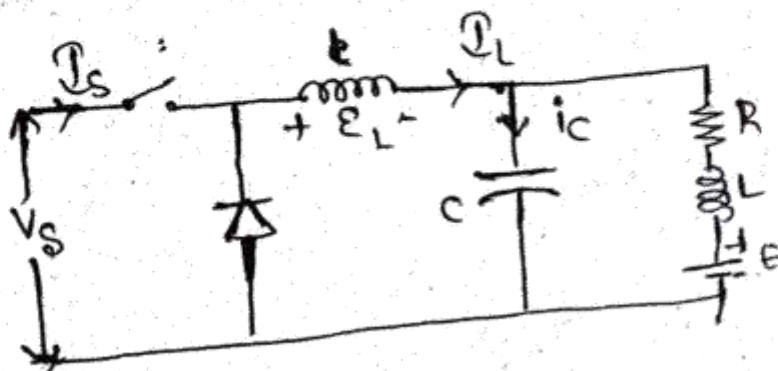

Given data,

$$V_s = 12V, \Delta V_c = 20mV, \Delta I = 0.8A,$$

$$f = 25 \text{ kHz}$$

$$V_a = 5V$$

$$R = 500 \Omega.$$

(a)  $V_a = k \cdot V_s$

$$k = V_a / V_s = 5/12 = 4.16\%$$

(b) peak to peak ripple current.

$$\Delta I = \frac{V_a (V_s - V_a)}{f \cdot L \cdot V_s} = \frac{5(12-5)}{25 \times 10^3 \cdot 12}$$

$$L = \frac{0.8 \times 25 \times 10^3}{5 \times 7} = 145.83 \text{ mH}$$

(c) peak to peak ripple voltage of Capacitor

$$\Delta V_c = \frac{\Delta I}{8 \cdot f \cdot C}$$

$$C = \frac{\Delta I}{8 \cdot f \cdot \Delta V_c} = \frac{0.8}{8 \times 25 \times 10^3 \times 20 \times 10^{-3}}$$

$$= 300 \mu\text{F}$$

(d)  $L_c = \frac{(1-k)R}{2f}$


$$L_c = \frac{(1-0.416) \times 500}{2 \times 25 \times 10^3} = 5.83 \text{ mH}$$

$$C_c = \frac{1-k}{16 L F^2} = \frac{1-0.6}{16 \times 10^{-6} \times 25^2}$$

$$= 4.02 \times 10^{-7} \text{ MF}$$

12/09/19

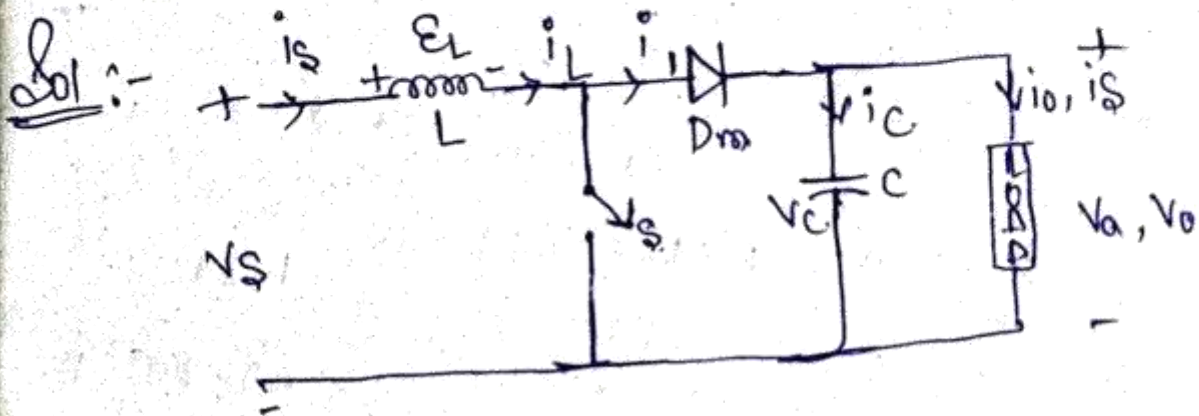1. A Boost Regulator shown in fig on an voltage of  $V_s = 5V$ . The avg op voltage  $V_a = 15V$  and the avg load current  $I_o = 0.5A$ . The switching frequency is  $25 \text{ kHz}$ . If  $L$  is  $150 \mu\text{H}$  and  $C = 220 \mu\text{F}$ . Determine (a) Duty cycle,  $k$  (b) Ripple current of inductor,  $\Delta I$  (c) The peak current of inductor  $I_L$  (d) The ripple voltage of filter capacitor  $\Delta V_c$  and (e) Critical values of  $L$  &  $C$ .



Given data,

$$V_a = 15V, I_o = 0.5A, f = 25 \text{ kHz}, V_s = 5V$$

$$L = 150 \times 10^{-6} \text{ H}, C = 220 \times 10^{-6} \text{ F}$$

(a)  $V_a = V_s \frac{1}{1-k}$

$$15 = \frac{5}{1-k} \Rightarrow k = \frac{2}{3} = 0.667 \text{ (or) } 66.7\%$$

(b)  $\Delta I = \frac{V_s (V_a - V_s)}{f \cdot L \cdot V_a} = \frac{5 (15 - 5)}{25 \times 10^3 \times 150 \times 10^{-6} \times 15} = 0.89 \text{ A}$

$$(c) \cdot I_s = \frac{I_a}{1-k} = \frac{0.5}{1-0.667} = 1.5 \text{ A Peak inductor current}$$

$$I_2 = I_s + \frac{\Delta I}{2} = 1.5 + \frac{0.89}{2} = 1.945 \text{ A}$$

$$(d) \Delta V_c = \frac{I_a k}{f \cdot C} = \frac{0.5 \times 0.667}{25000 \times 220 \times 10^{-6}} = 60.6 \text{ mV}$$


$$(e) L_c = \frac{k(1-k) \cdot R}{2f}$$

$$R = \frac{V_a}{I_a} = \frac{15}{0.5} = 30$$

$$= \frac{0.667(1-0.667) \cdot 30}{2 \times 25000} = 1.33 \times 10^{-4} = 0.000133 \text{ H} = 133 \text{ } \mu\text{H}$$


$$(f) C_c = \frac{k}{2fR} = \frac{0.667}{2 \times 25000 \times 30} = 0.44 \text{ } \mu\text{F}$$

# Buck-Boost Converter:-

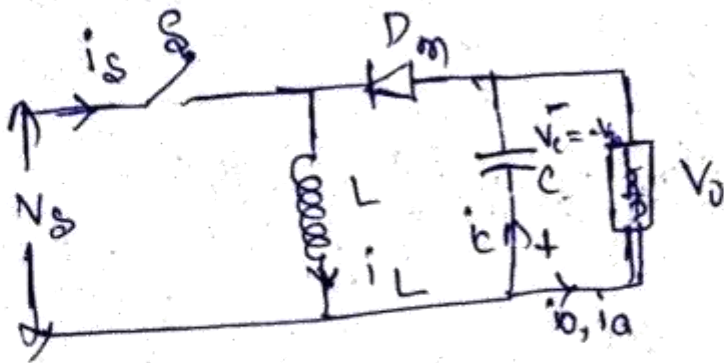



Mode-I

$$0 \leq t \leq t_1$$

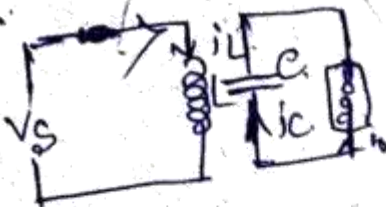

Mode-II

$$t_1 \leq t \leq t_2$$

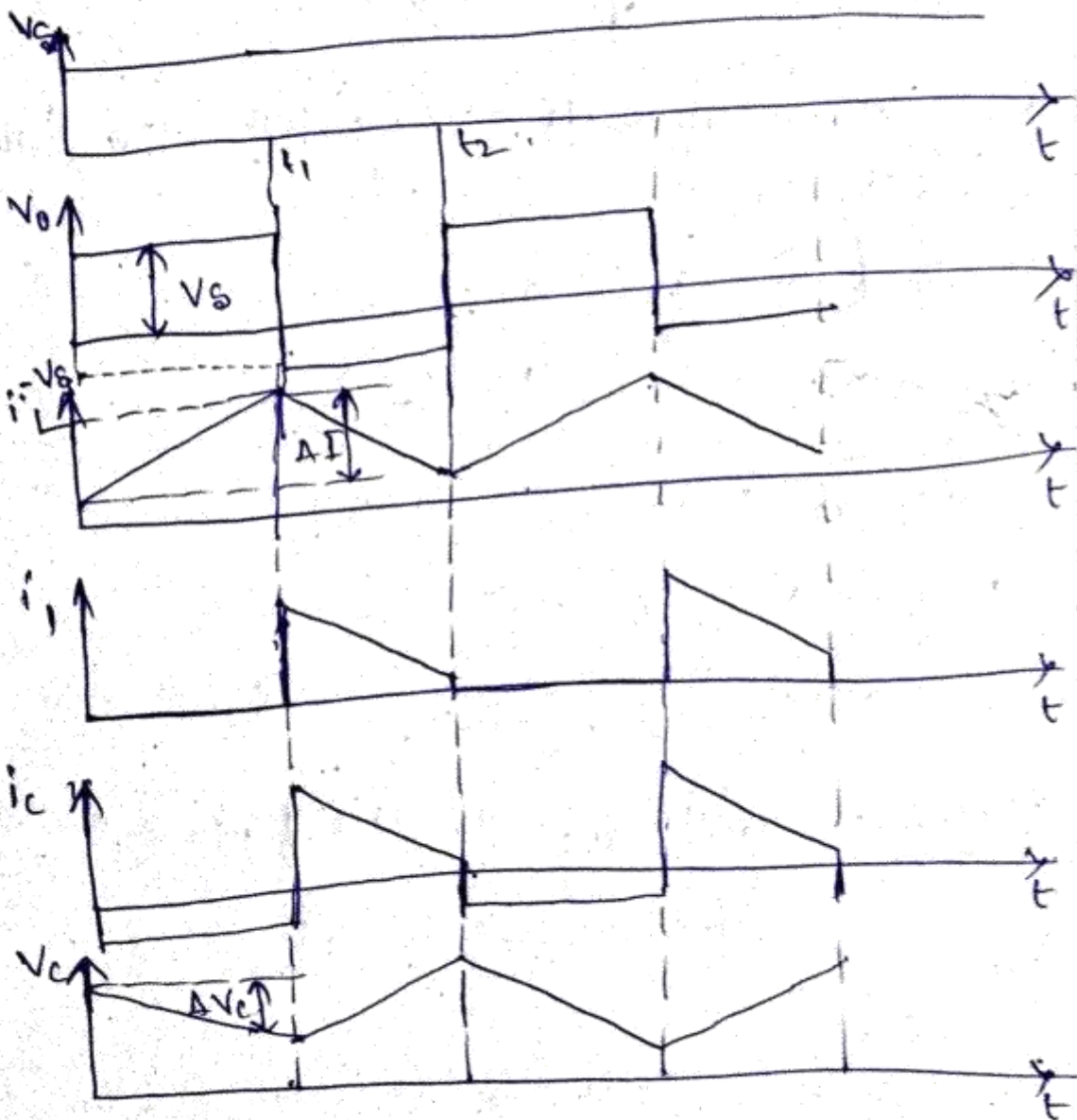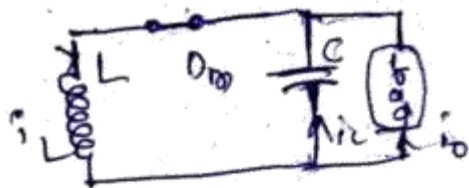

19/09/19

Assuming that the induction current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$ .

$$V_s = L \cdot \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1} \rightarrow (1)$$

(or)

$$t_1 = \frac{\Delta I L}{V_s} \rightarrow (2)$$

and the induction current falls linearly from  $I_2$  to  $I_1$  in time  $t_2$ .

$$V_0 = -L \frac{\Delta I}{t_2} \rightarrow (3)$$

(or)

$$t_2 = -\frac{\Delta I L}{V_0} \rightarrow (4)$$

Where  $\Delta I = I_2 - I_1$  is the peak to peak ripple current of inductor 'L'.

From Eq (1) and (3)

$$\Delta I = \frac{V_s t_1}{L} = \frac{-V_0 t_2}{L}$$

Substituting  $t_1 = kT$  &  $t_2 = (1-k)T$ .

The average o/p voltage is,

$$V_0 = -\frac{V_s k}{1-k} \rightarrow (5)$$

Substituting  $t_1 = kT$  and  $t_2 = (1-k)T$  into Eq (5) yields

$$(1-k) = \frac{-V_s}{V_0 - V_s} \rightarrow (6)$$

Substituting  $t_2 = (1-k)T$  and  $(1-k)$  from Eq (6) in Eq (5) yields



$$t_1 = \frac{V_o}{(V_o - V_s)f} \rightarrow (7)$$

Assume buck converter circuit,  $V_s I_s = V_o I_o = \frac{V_s I_o}{1-k}$  and the average input current  $I_s$  is related to the average output current  $I_o$  by.

$$I_s = \frac{I_o k}{1-k} \rightarrow (8)$$

The switching period 'T' can be found from

$$T = \frac{1}{f} = t_1 + t_2 = \frac{\Delta I_L}{V_s} + \frac{\Delta I_L}{V_o} = \frac{\Delta I_L (V_o - V_s)}{V_s V_o} \rightarrow (9)$$

The peak-to-peak ripple current from Eqn (9)

$$\Delta I = \frac{V_s \cdot V_o}{fL(V_o - V_s)} \rightarrow (10)$$

$$\text{or } \Delta I = \frac{V_s k}{fL}$$

When switch is on, the filter capacitor supplies the load current for  $t = t_1$ . The average discharging current of capacitor is  $I_c = I_o$  and the peak-to-peak ripple voltage of capacitor is.

$$\Delta V_c = \frac{1}{C} \int I_c dt = \frac{1}{C} \int I_o dt = \frac{I_o t_1}{C} \rightarrow (11)$$

Substituting  $t_1 = \frac{V_o}{(V_o - V_s)f}$  from Eqn (7) becomes

$$\Delta V_c = \frac{I_o \cdot V_o}{(V_o - V_s) \cdot f \cdot C} \rightarrow (12)$$

$$\text{or } \Delta V_c = \frac{I_o k}{f \cdot C} \rightarrow (13)$$

Condition for Continuous inductor Current and Capacitor voltage is

If  $I_L$  is the average inductor current, Inductor ripple Current

$\Delta I = 2I_L$  using Eqn (5) and Eqn (11), we get.

$$\frac{k \cdot V_s}{fL} = 2I_L = 2I_a = \frac{2kV_s}{(1-k)R}$$

Which gives the critical value of inductor  $L_c$

$$L_c = L = \frac{(1-k)R}{2f} \rightarrow (15)$$


If  $v_c$  is the average, the Capacitor ripple voltage  $\Delta v_c = \Delta v$  using Eqn (14) we get.

$$\frac{I_a k}{2f} = 2v_c = 2I_a R$$


Which gives the critical value of Capacitor  $C_c$  is.

$$C_c = C = \frac{k}{2fR} \rightarrow (16)$$

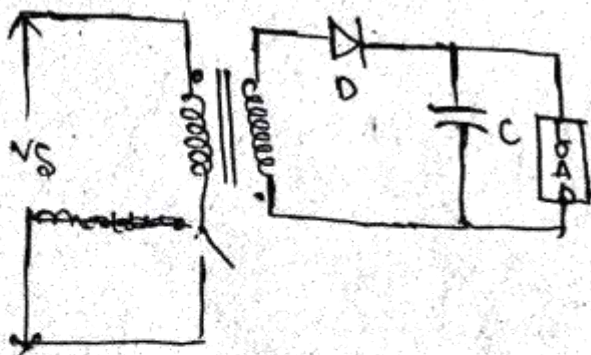
\* Fly Back Converter can forward back:- IMP









Mode - I ON

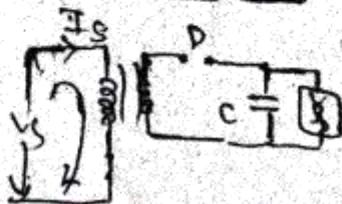

OFF

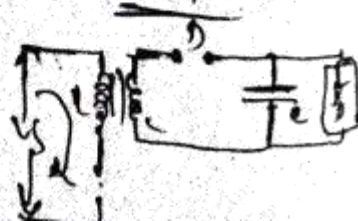

21/09/19

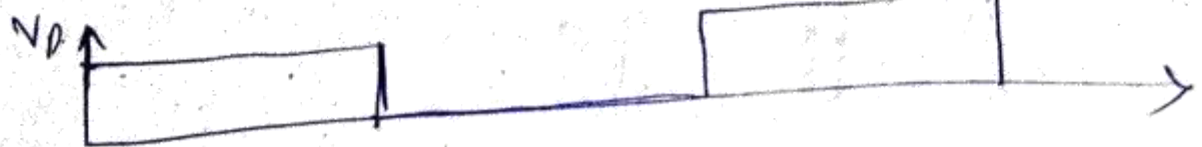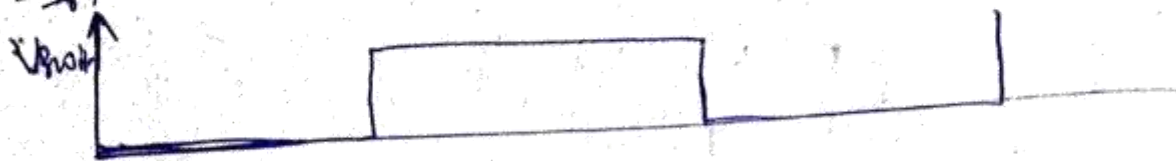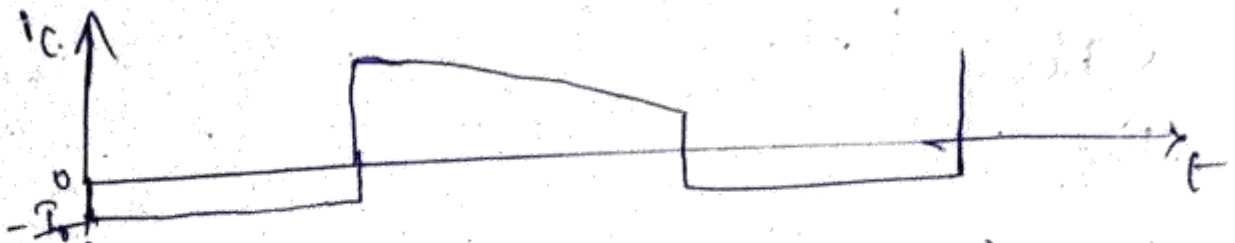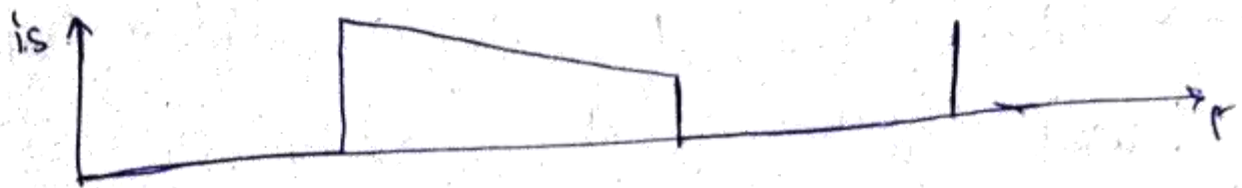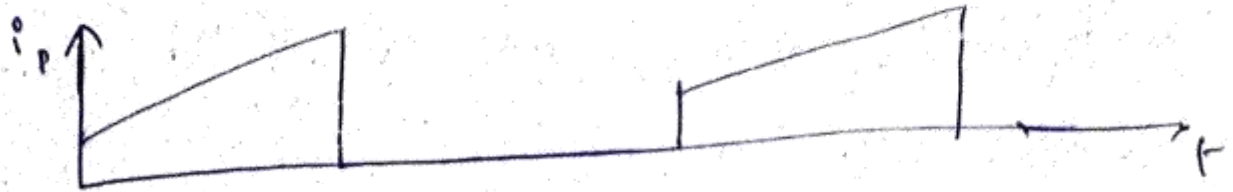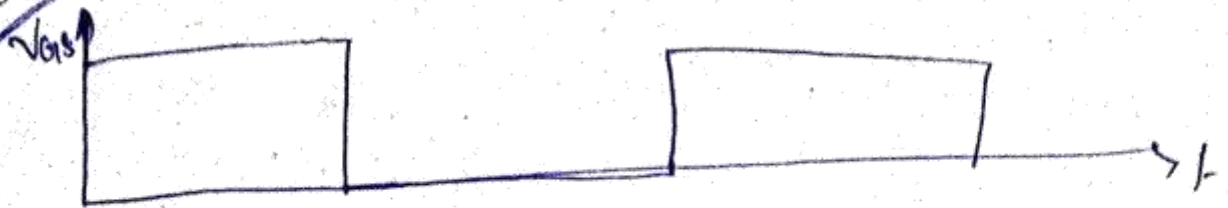

$$V_0 = \frac{k}{1-k} V_s \rightarrow \text{Buck Boost}$$

$$V_0 = \frac{N_2}{N_1} \cdot \frac{k}{1-k} V_s \Rightarrow \text{Fly back Converter}$$

$$V_o = \frac{K}{1-K} V_s \rightarrow \text{BUCK Boost}$$


$$V_o = \frac{N_2}{N_1} \frac{K}{1-K} V_s \rightarrow \text{Fly back Converter}$$

→ BUCK Boost Converter & fly back Converter is only one difference.


— isolation
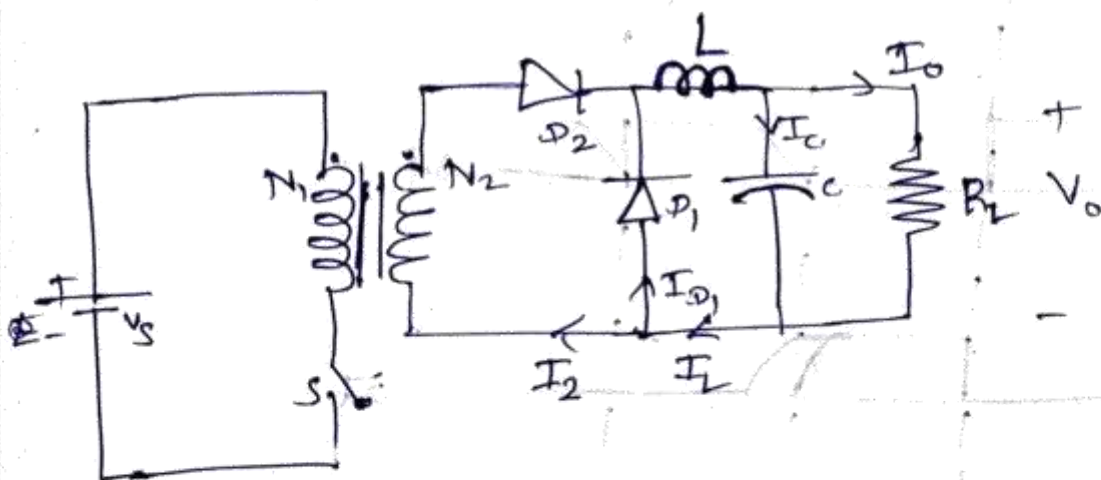
### \* Forward Converter :-

→ Forward Converter is derived from BUCK Converter



Switch ON  
( $0 \leq t \leq t_1$ )

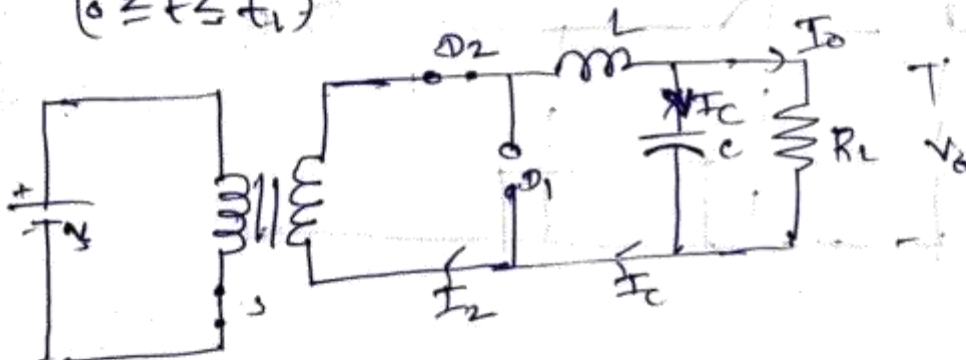

Switch off :-

$t_1 \leq t \leq t_2$

