


Date
23/09/19

UNIT - IV

A.c to A.c Controlled Converter

→ transformer ~~to~~ Converts fixed A.c to variable ~~A.c~~ (frequency is same).



→ Auto transformer, tap changer, Saturable react used fixed A.c to variable D.C.


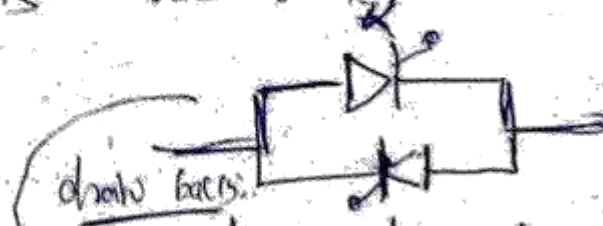
→ Here dis Advantages are more, by Avoiding this we use  (Advanced device)

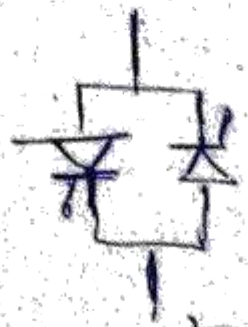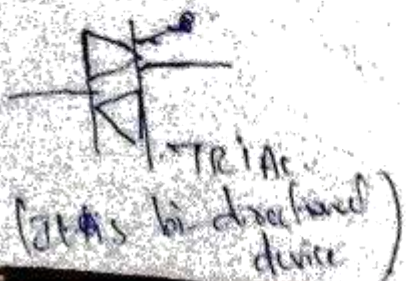(i) device temperature increases, the device may be damaged


Applications

- Speed Control of ac drives
- furnaces → induction yield.
- static VAR Compensators.



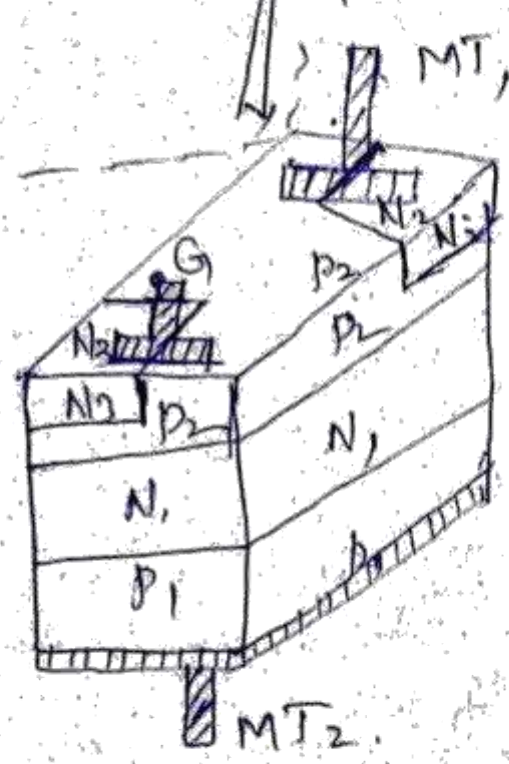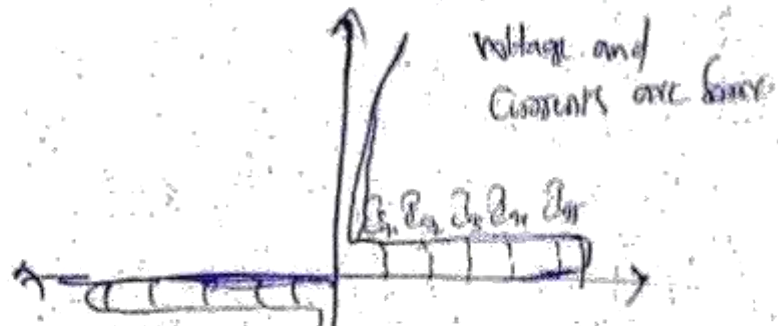

represented by

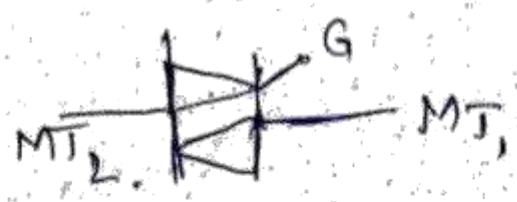

Operation:-

→ It can be operated by "4" modes

Mode-1:-

→ MT_1 terminal +ve w.r.t MT_2 & Gate terminal is positive.


Mode-2:-

MT_2 is +ve and Gate is Negative.

mode-3:- MT_2 is -ve and Gate is +ve.

mode-4:- MT_1 is -ve and Gate is -ve.

Mode (i):

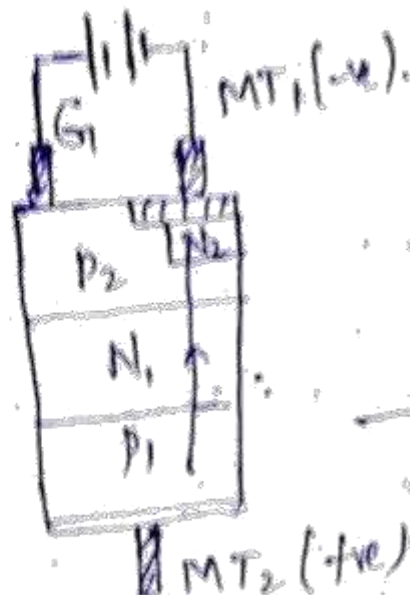


T_1, T_2 are forward bias
 T_2 are reverse bias

→ There is no flow of current.

→ The device is very sensitive to operate.

Mode (ii):

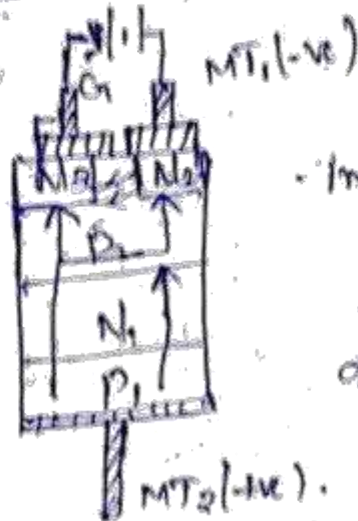Gate is Applied
 poles are injected
 to N_2 .




Initial current path is
 P_1, N_1, P_2, N_2
 due to potential
 difference the current
 is diverted to N_2 to N_1 .

Final Conduction P_1, N_1, P_2, N_2 .

→ In this mode the device is Not sensitive.



Mode (iii):

The device is
 not more
 sensitive.

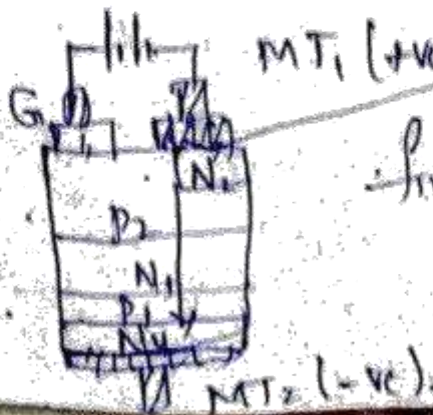

→ Poles are injected.
 Final Conduction path
 is P_2, N_2, P_1, N_1 .




24/09/19
Mode IV :-

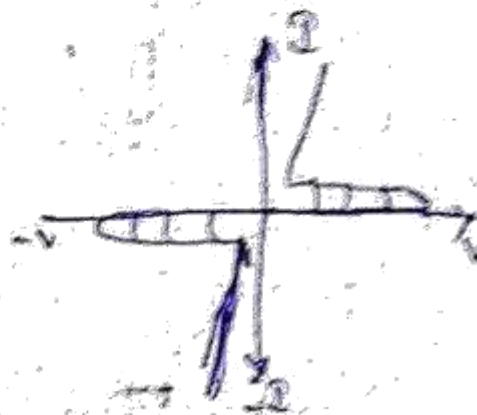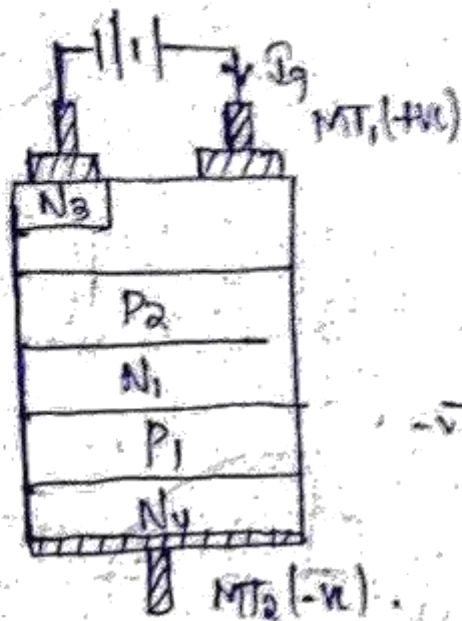


- The device is operated sensitively.
- TRIAC is operated in 1st mode & 4th mode.
- Diode is uncontrolled devices.

* Control techniques of TRIAC:

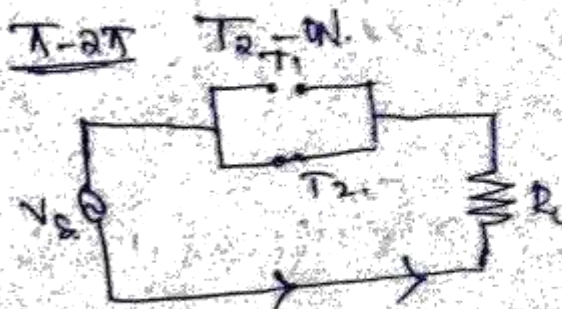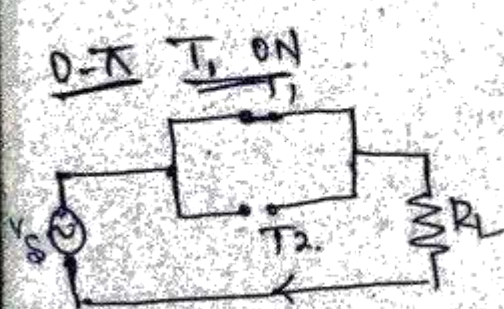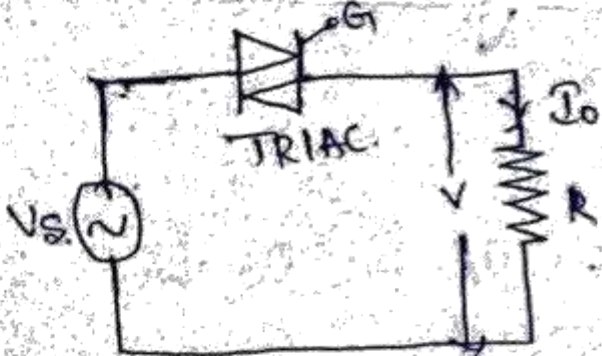(i) Phase Control (or) 1-φ AC voltage Control With R-L :-



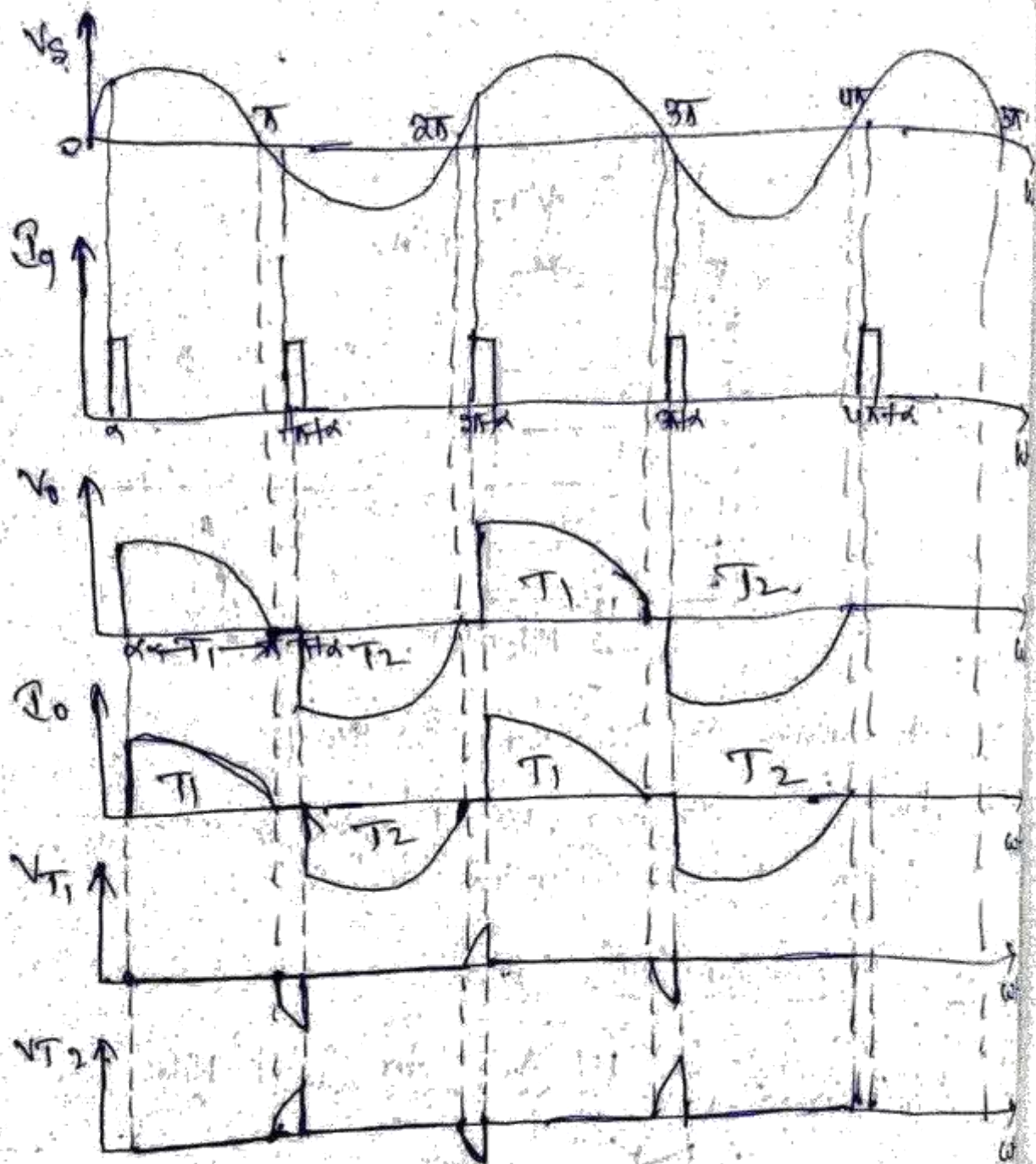

26/09/19

The average value of the sine wave form is always zero.
 The rms value of o/p voltage is

$$V_{\text{rms}} = \left[\frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t \right]^{1/2}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \left[\frac{1}{\pi} (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R}$$

The average power delivered to load,

$$P = \frac{V_{\text{orms}}^2}{R} = I_{\text{orms}}^2 R.$$

$$= \frac{V_m^2}{2R} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right].$$

$$= \frac{V_s^2}{R} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right].$$

Where $V_m = \sqrt{2} V_s$

maximum power is delivered to load ' $\alpha = 0$ '.

i.e., $P_{\text{max}} = \frac{V_s^2}{R}$.

$$\text{power factor} = \frac{\text{Real power}}{\text{Apparent power}} = \frac{V_s I_1 \cos \phi_1}{V_s I_{\text{rms}}}$$

$$= \frac{I_1 \cos \phi_1}{I_{\text{rms}}}$$

$$I_1 = \frac{I_{\text{rms}}}{\sqrt{2}} = \text{r.m.s value of fundamental}$$

Component of load current.

$I_{\text{r.m.s}} = I_{\text{orms}} = \text{r.m.s value of load (or source) current.}$


$$\text{Real power delivered to load} = \frac{V_{\text{orms}}^2}{R}.$$

Apparent power delivered to load = $V_s I_{rms}$
 $= V_s \cdot I_{rms} = V_s \cdot \frac{V_{rms}}{R}$

D.f = $\frac{V_{rms}/R}{V_s \cdot V_{rms}/R} = \frac{V_{rms}}{V_s}$

Integral Area Control

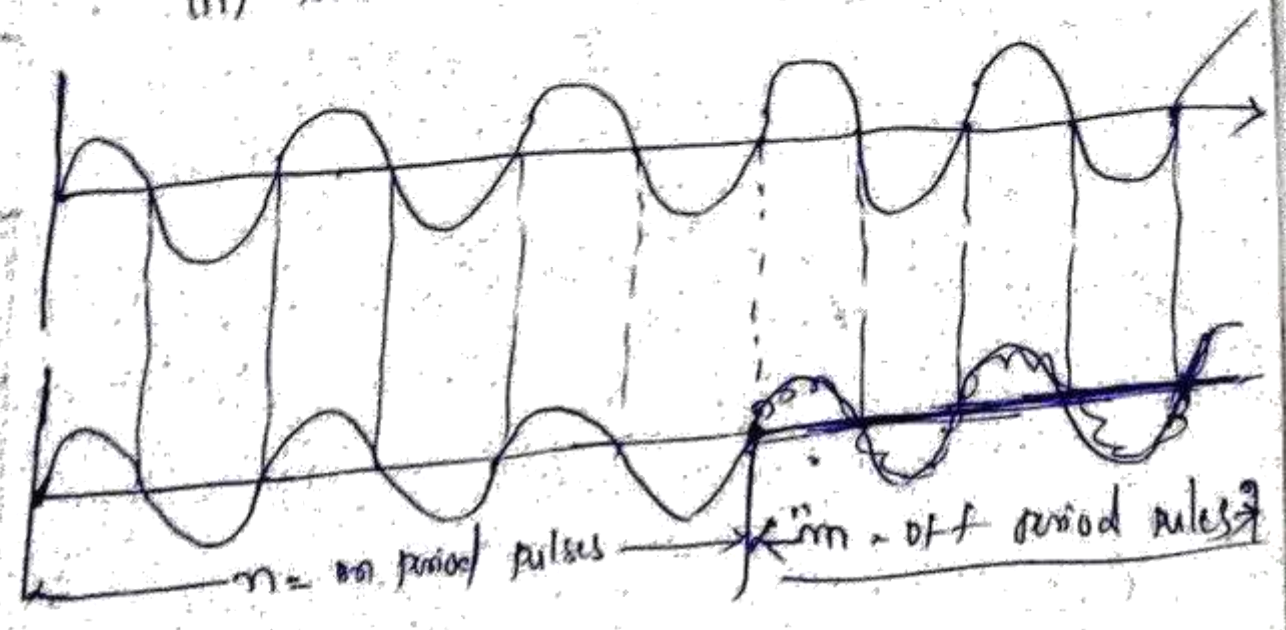→ These Applications are used in machine time constant
 (ii) Thermal time constant.



Rms value of op voltage V_{rms}

$$V_{rms} = \frac{1}{\text{periodicity}} \left(\int_0^{2\pi} V_m^2 \sin^2 \omega t \, d\omega t \text{ for } 1^{\text{st}} \text{ cycle} \right. \\ \left. + \int_0^{2\pi} V_m^2 \sin^2 \omega t \, d\omega t \text{ for } 2^{\text{nd}} \text{ on cycle} \right)$$

∫₀^{2π} V_m² sin² ωt dt for nth on cycle.

$$V_{\text{rms}} = \left[\frac{1}{2\pi(nT_m)} \int_0^{2\pi} V_m^2 \sin^2 \omega t dt \right]^{1/2}$$

$$V_{\text{rms}} = \left[\frac{n V_m^2}{4\pi(nT_m)} \int_0^{2\pi} (1 - \cos 2\omega t) dt \right]^{1/2}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{n}{nT_m}} = V_s \cdot \sqrt{\frac{n}{nT_m}}$$

$$= V_s \cdot \sqrt{k}$$

where,

k = duty cycle of AC voltage control.

$$\text{power delivered to load } P = \frac{V_{\text{rms}}^2}{R} = \frac{V_s^2}{R} \left(\frac{n}{nT_m} \right)$$

$$= \frac{k \cdot V_s^2}{R}$$

RMS value of i_p current I_s = R.M.S value of load current

$$\text{i/p } V_A = V_s \quad (\text{rms value of source current})$$

$$= V_s I_s = V_s \cdot I_{\text{rms}} = V_s \cdot \frac{V_{\text{rms}}}{R}$$

power delivered to load = i/p V_A × P.f



$$\text{i/p } P.f = \frac{V_{\text{rms}}}{R} \cdot \frac{R}{V_s \cdot V_{\text{rms}}}$$

$$= \frac{V_{\text{rms}}}{V_s} = \sqrt{\frac{n}{nT_m}} = \sqrt{k}$$


$$\text{Thyristor Current (ITM)} = \frac{k \cdot I_m}{\pi}$$

$$\text{RMS Thyristor Current (ITR)} = \frac{I_m \sqrt{k}}{2}$$

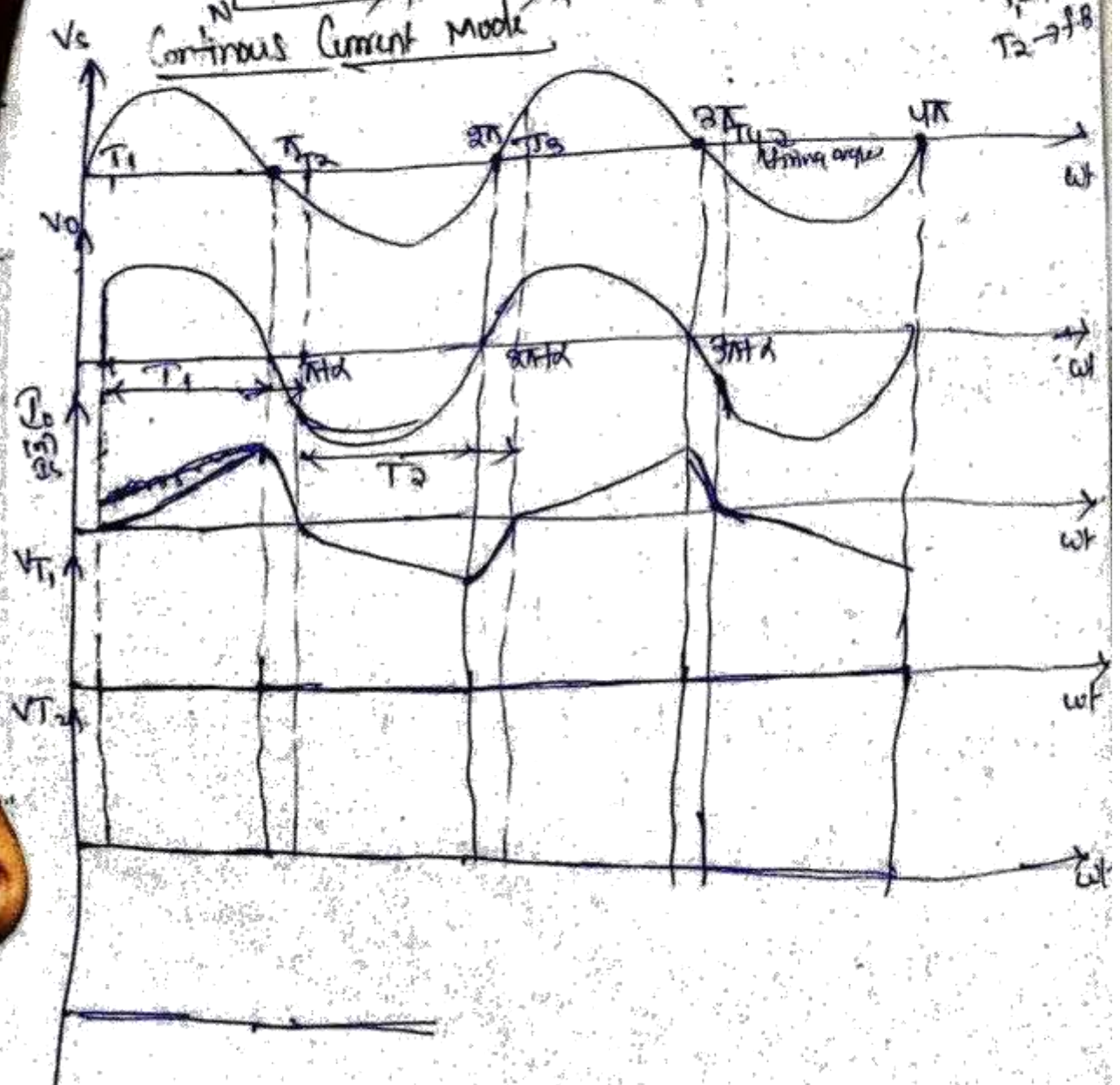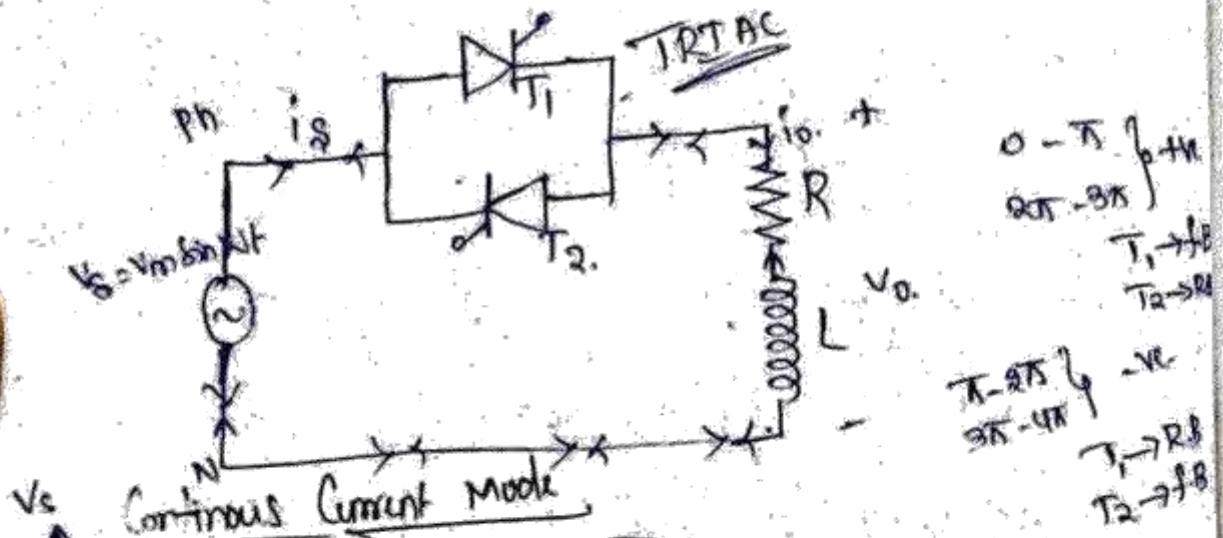* 1- ϕ A.c Voltage Controlled with R-L Load



Discontinuous Current mode:-

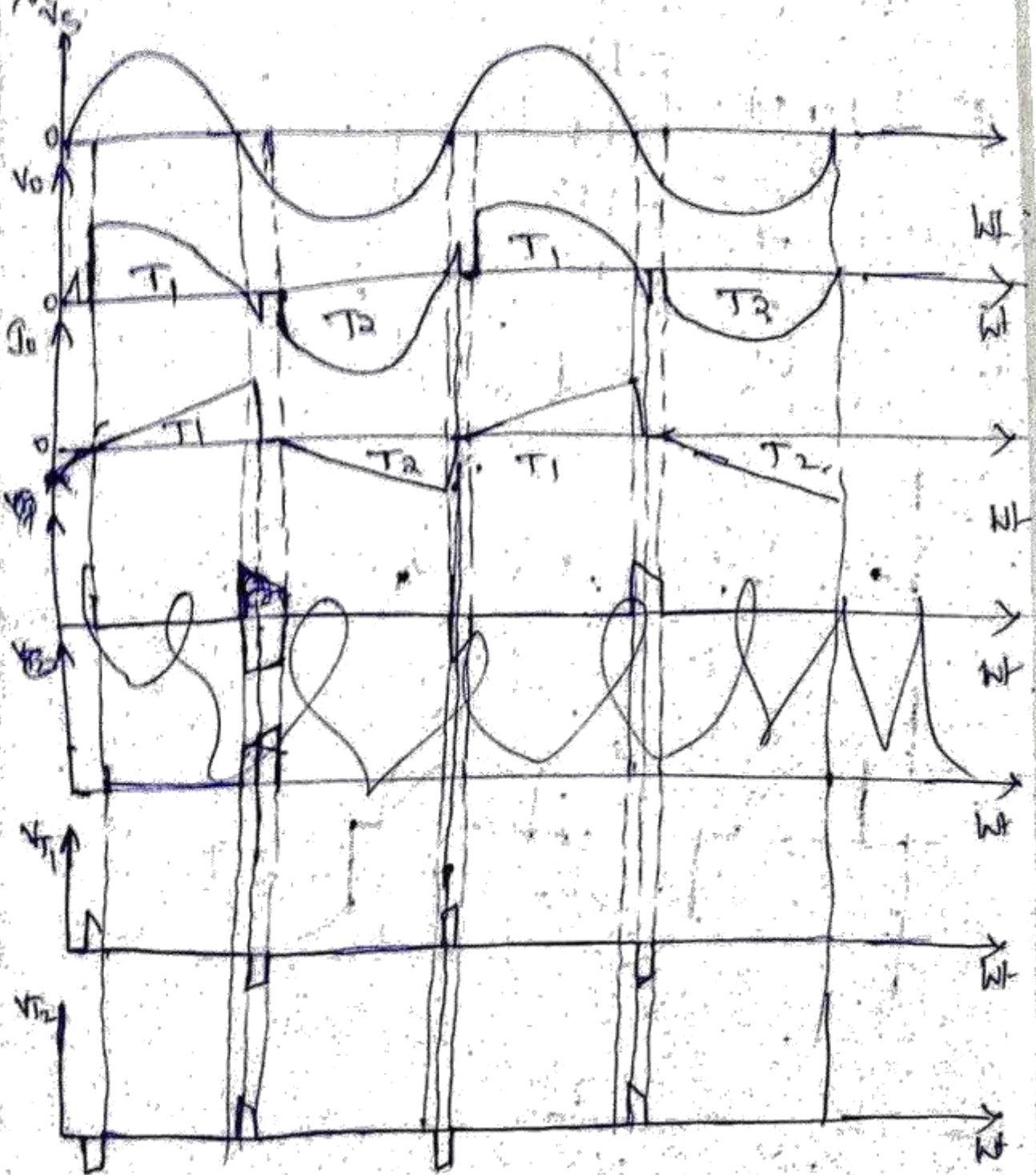



27 log 19

$$V_{rms} = \left[\frac{1}{\pi} \int_0^{\pi} V_m \sin^2 \omega t \, d\omega t \right]^{1/2}$$


$$V_{rms} = \frac{V_m}{\sqrt{2}} = V_s$$

$$I_{rms} = \frac{V_{rms}}{R}$$


Tap Changing Transformer:

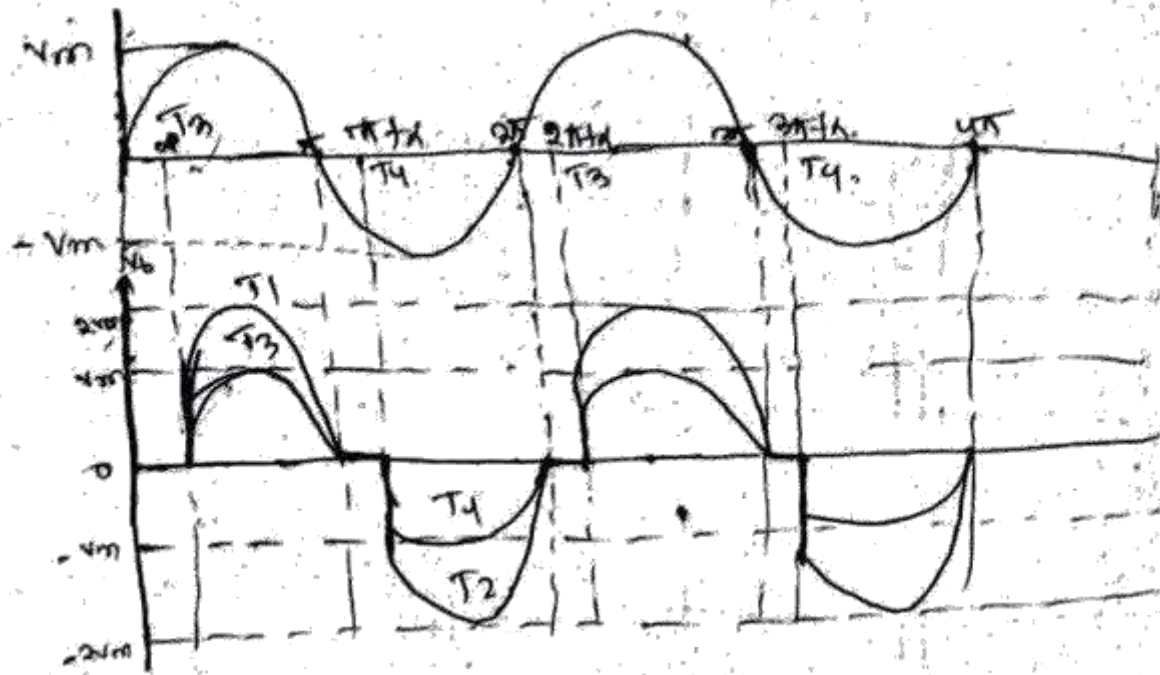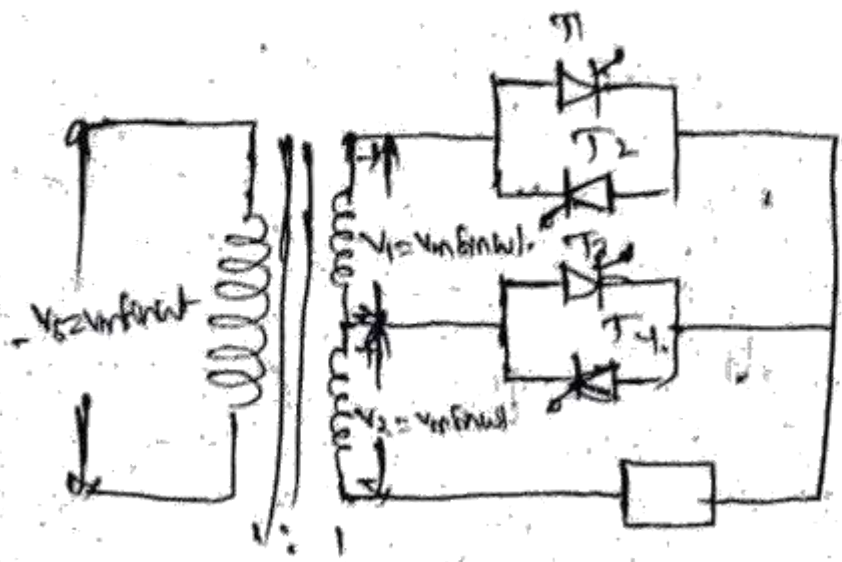

3-d AC voltage Control:

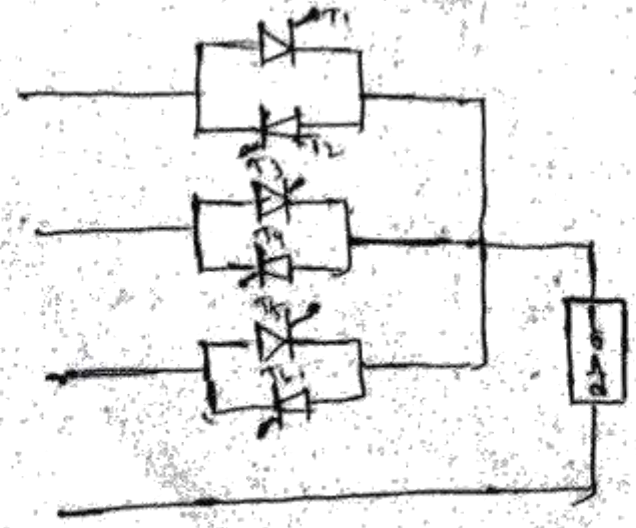

Cycle Converter

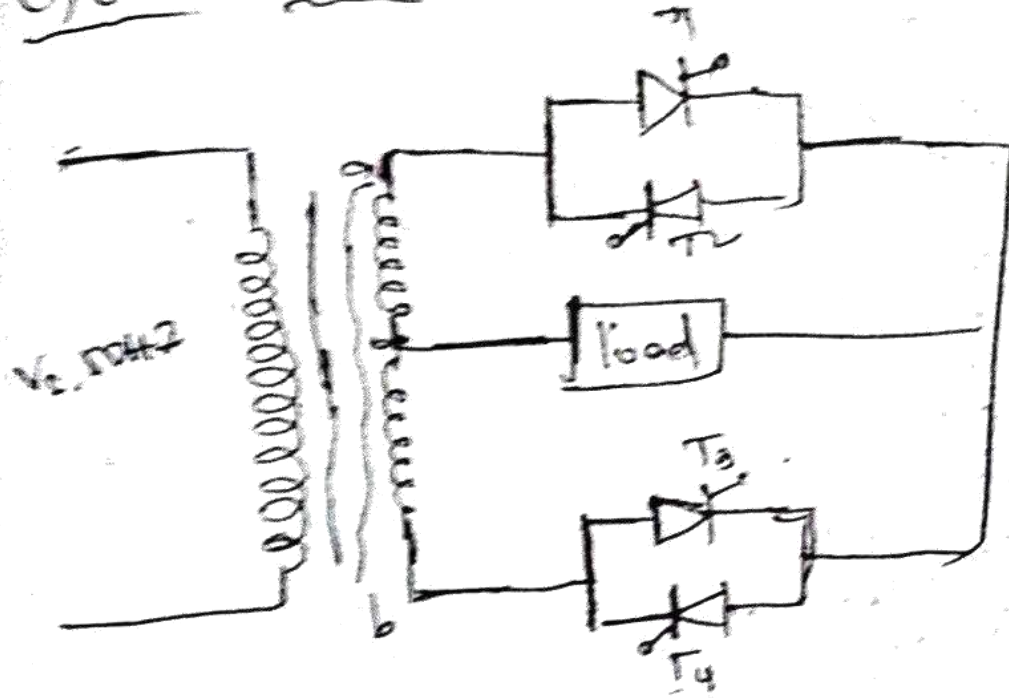

⇒ Step down Converter ⇒ Line Commutation method.
Step up Converter ⇒ forced Commutation method.