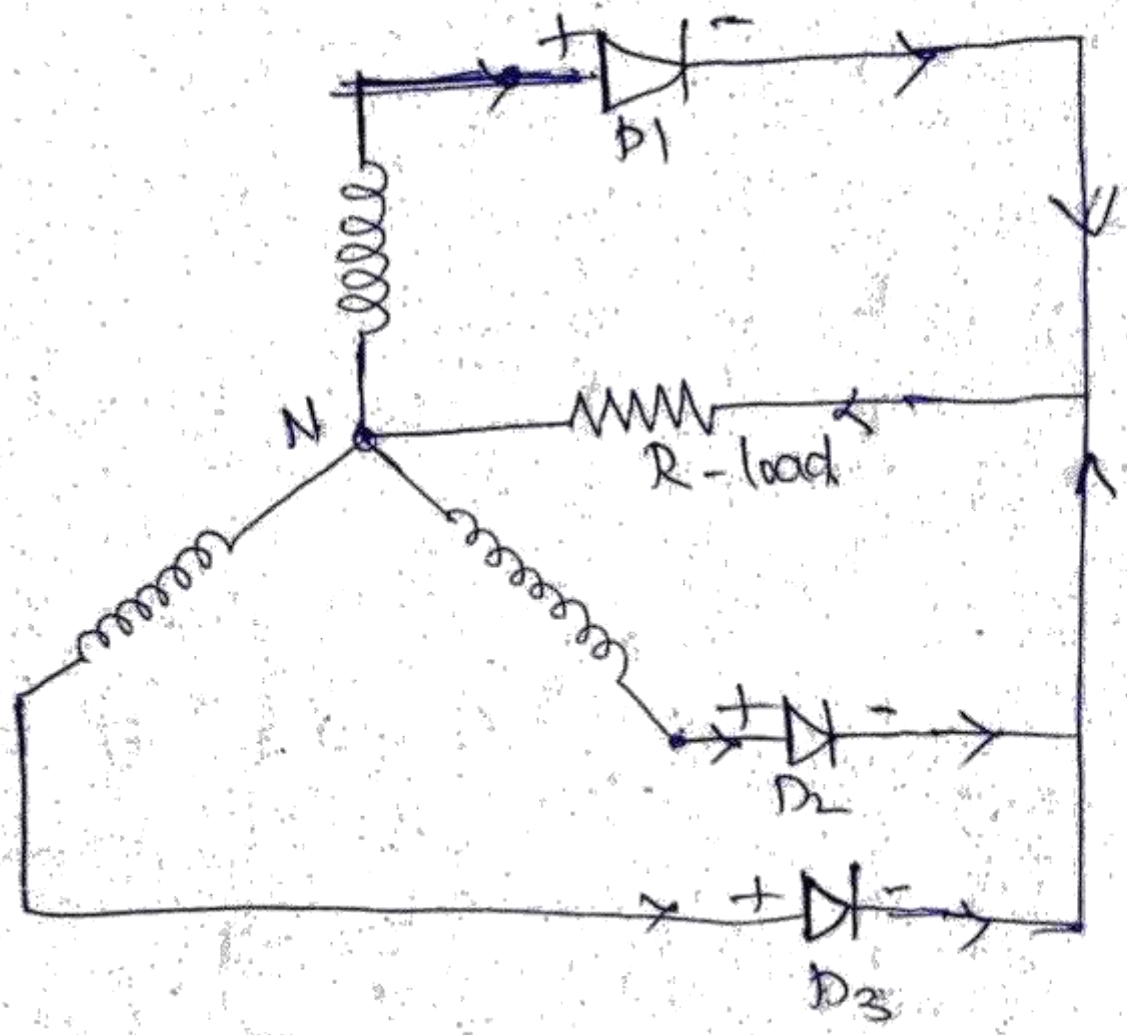


17/08/19
UNIT-3

Three phase Rectifier



* 3- ϕ Half Wave Rectifier with R-load





- Each angle is displaced by 120°
- There is no voltage drop.

21/08/19

2- ϕ Half wave Converter with R-load :-

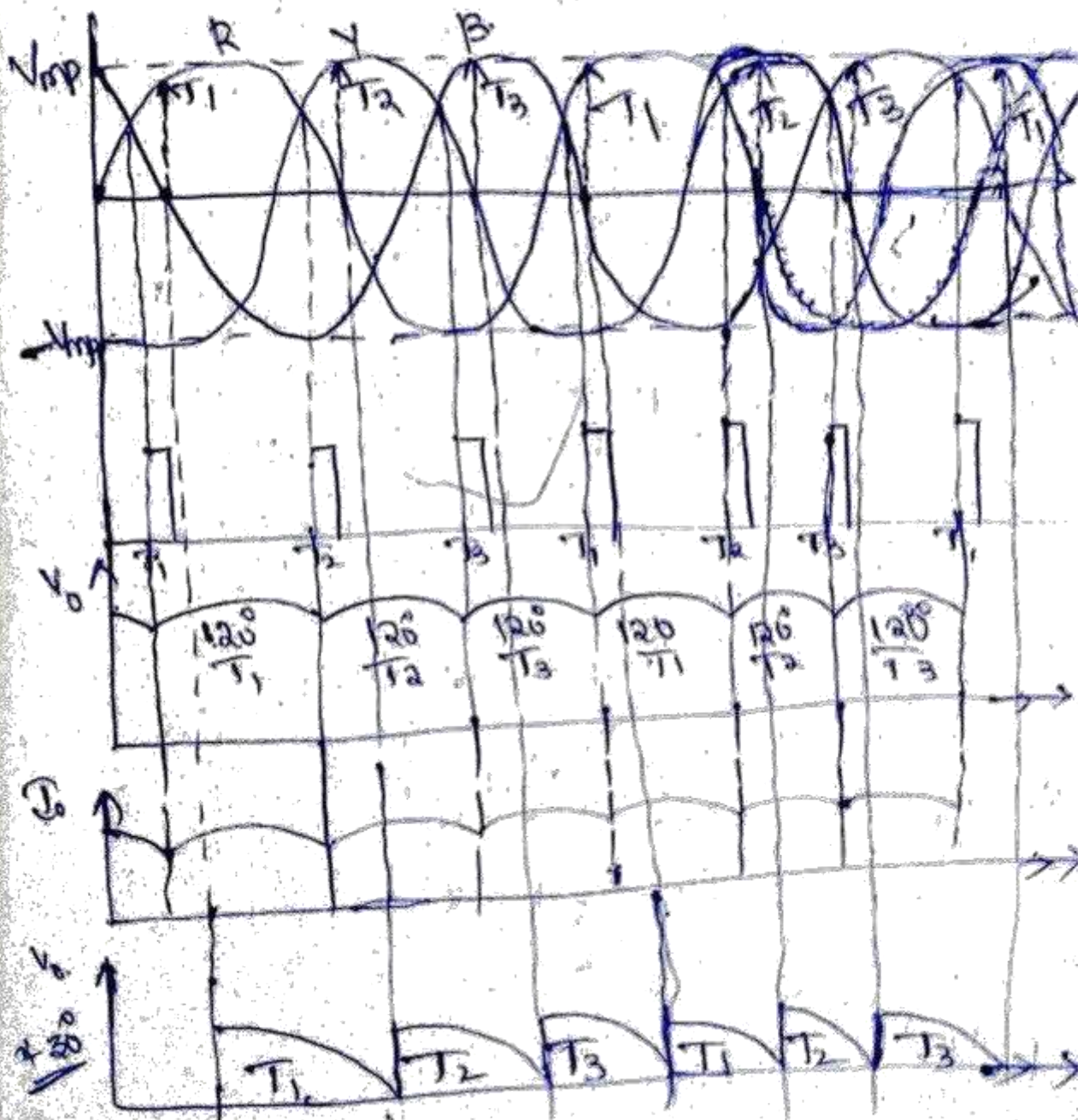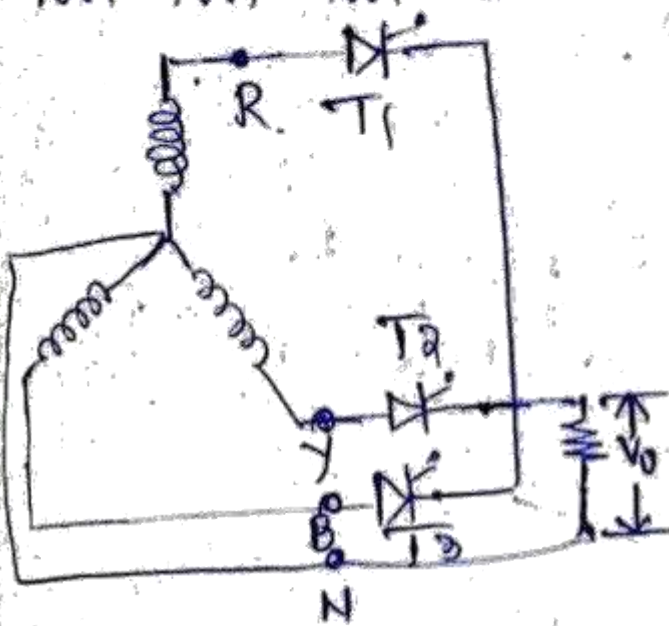

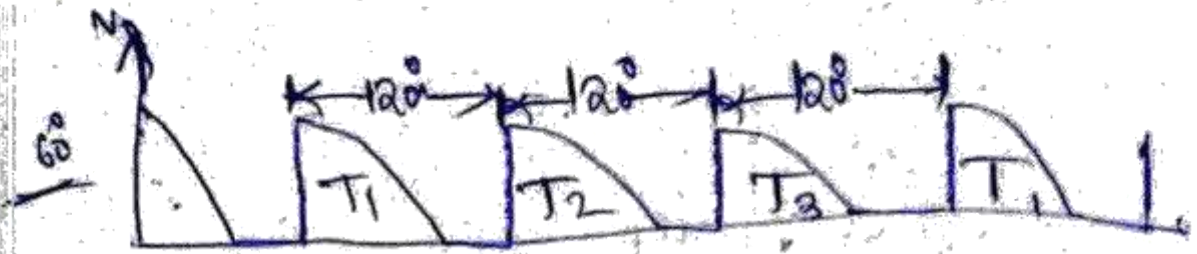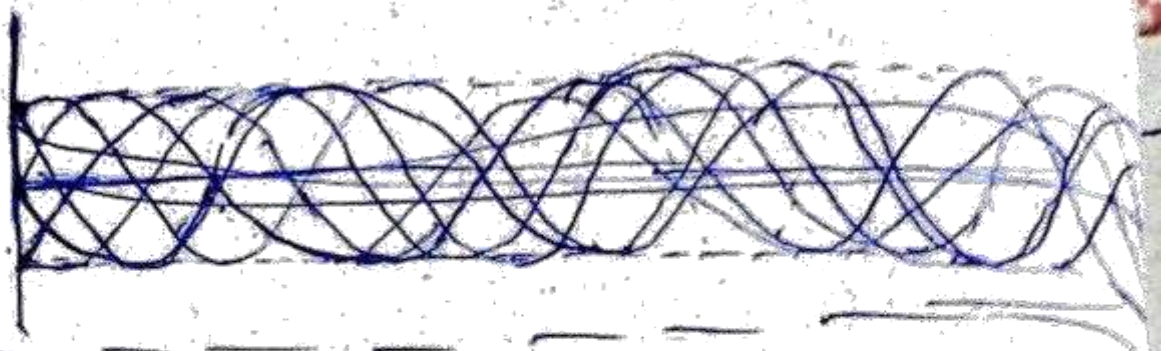

22/08/19

$$0 \leq \alpha \leq 30^\circ$$

for Continuous, Current Mode :-

$$V_{omms} = \left[\frac{3}{2\pi} \int_{\pi/6 + \alpha}^{\pi/6 + \alpha + \pi/6} V_{mp} \sin \omega t d\omega t \right]^{1/2}$$

$$= \frac{3V_{mp}}{4\pi} \left[\int_{\alpha + \pi/6}^{\alpha + \pi/6 + \pi/6} \sin \omega t d\omega t - \left[\frac{\sin 2\omega t}{2} \right]_{\alpha + \pi/6}^{\alpha + \pi/6 + \pi/6} \right]^{1/2}$$

$$= \frac{3V_{mp}}{4\pi} \left[\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos \alpha \right]^{1/2}$$

$$= V_{mp} \left[\frac{1}{2} + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$V_{omms} = \sqrt{3} V_{mp} \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$= V_{me} \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$$E_{omms} = \frac{V_{omms}}{2}$$

for Discontinuous Current Mode :- $30^\circ \leq \alpha \leq 180^\circ$.

$$V_o = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_{mp} \sin \omega t \, d\omega t$$

$$V_o = \frac{3V_{mp}}{2\pi} \left[1 + \cos(\alpha + 30^\circ) \right]$$

$$V_{rms} = \left[\frac{3}{2\pi} \int_{\pi/6+\alpha}^{\pi} V_{mp}^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$= \frac{\sqrt{3} V_{mp}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \ln \left(\frac{2\alpha + \pi/3}{3} \right) \right]^{1/2}$$

$$= \frac{V_m}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \ln \left(\frac{2\alpha + \pi/3}{3} \right) \right]^{1/2}$$

R-l load :-

Continuous :-

$$V_o = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_{mp} \sin \omega t \, d\omega t$$

$$= \frac{3\sqrt{3} V_{mp}}{2\pi} \cos \alpha \quad (\text{or})$$



$$= \frac{3V_{m1}}{2\pi} \cos \alpha$$

$$I_o = V_o / R$$


3- ϕ Full wave Converter Rectifiers




- 1) Center-tapped Full wave rectifiers
- ii) Bridgeten full wave rectifiers

ii) Mid point Configuration

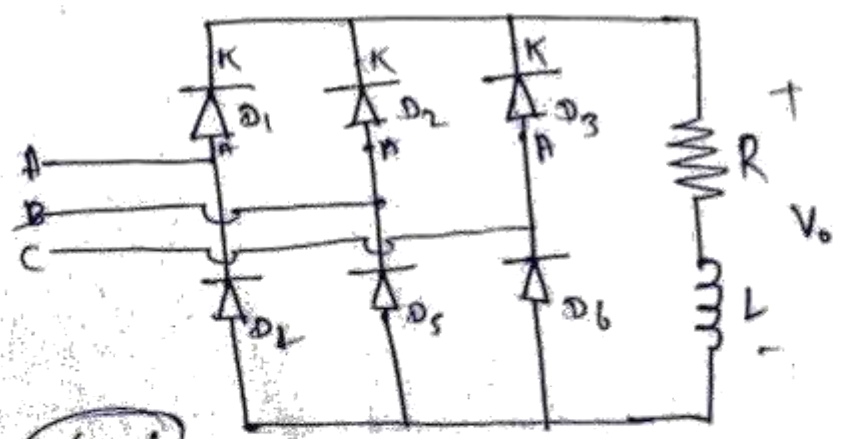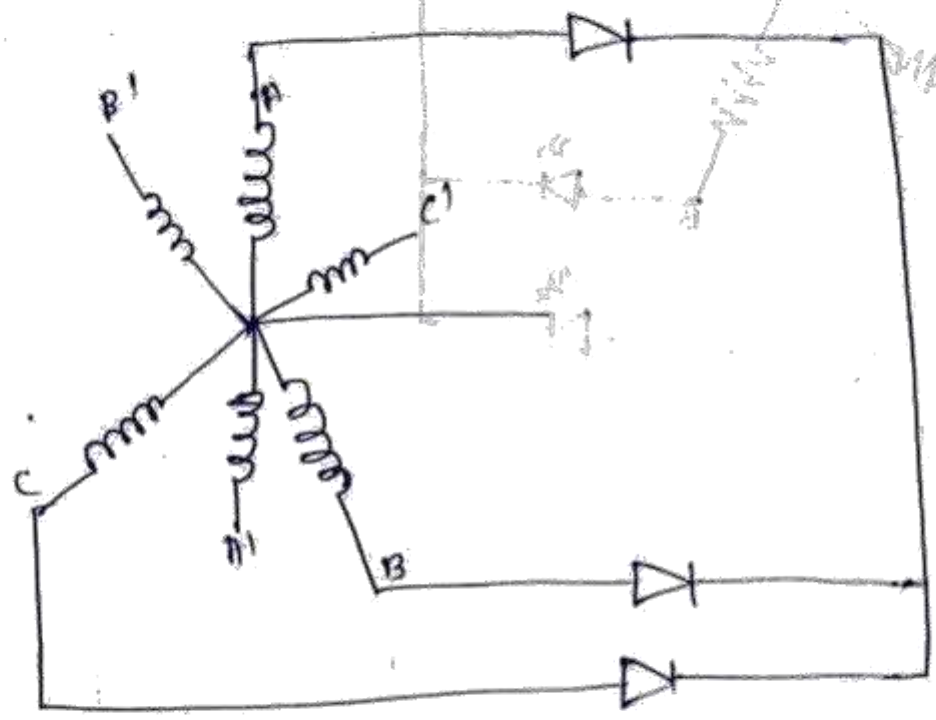

$T = 120^\circ$

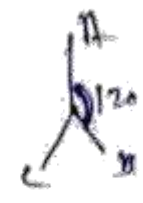

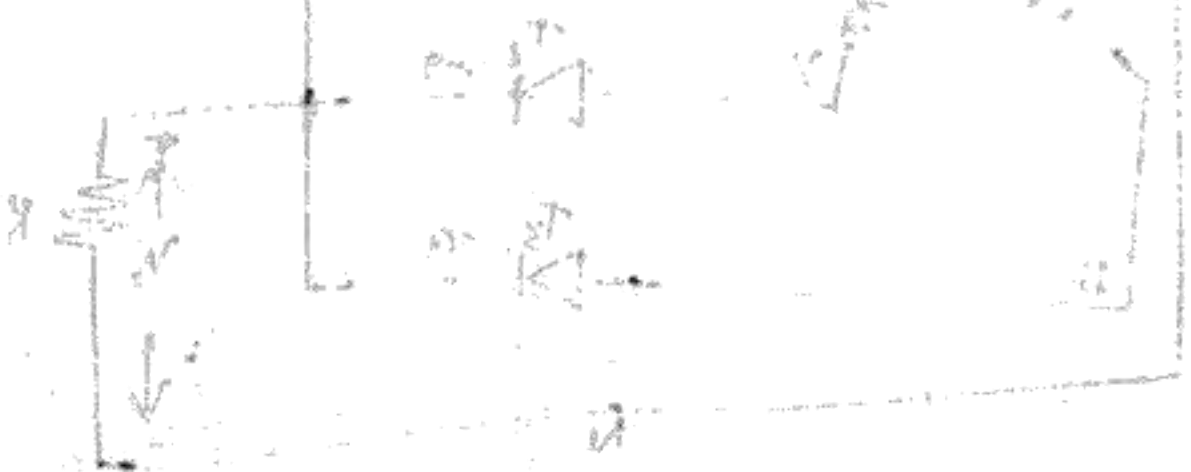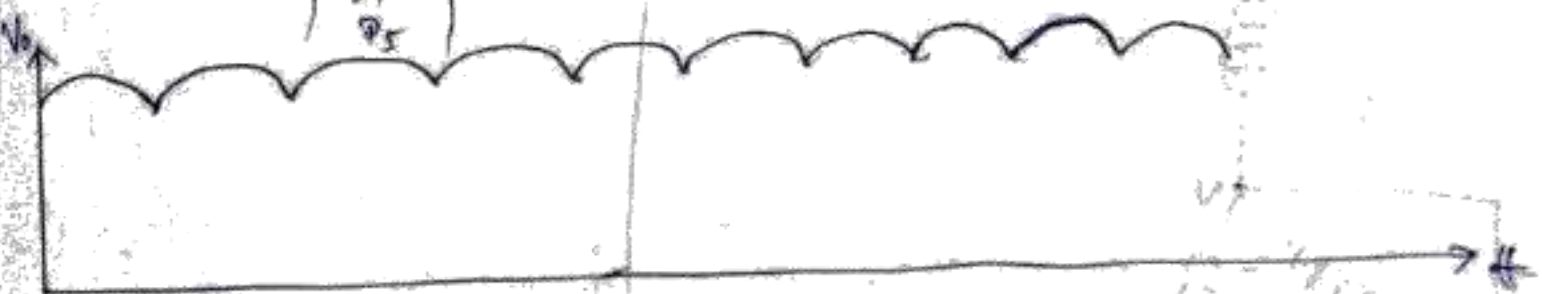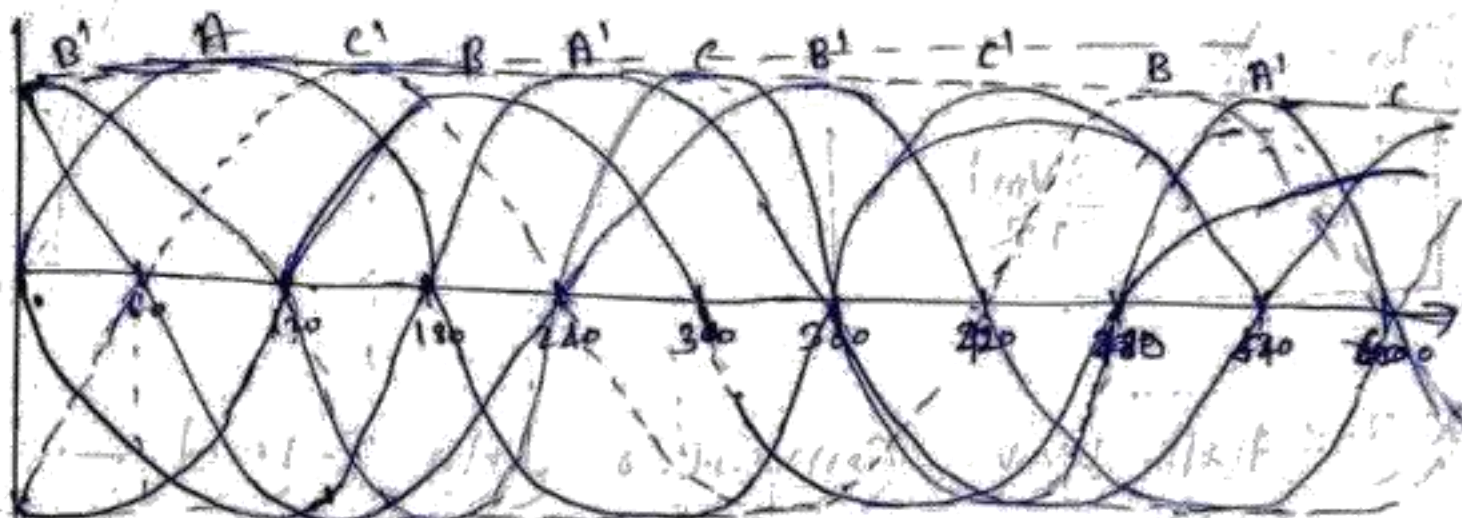

$$V_o = \frac{6}{2\pi} \int_{\pi/2}^{\pi/3} V_m \sin \omega t \, d\omega t$$

$$= \frac{6V_m}{2\pi} \left[-\cos \omega t \right]_{\pi/2}^{\pi/3} = \frac{3V_m}{\pi} \left[\cos\left(\frac{2\pi}{3}\right) + \cos\left(\frac{\pi}{2}\right) \right]$$


$$= \frac{3V_m}{\pi} \left[\cos\left(\frac{2\pi}{3}\right) + \cos\left(\frac{\pi}{2}\right) \right]$$





$$V_o = \frac{3V_m}{\pi}$$

$$I_o = \frac{V_o}{R}$$

$$I_o = \frac{3V_m}{\pi R}$$


* 3- ϕ Half wave Converter with R-Load

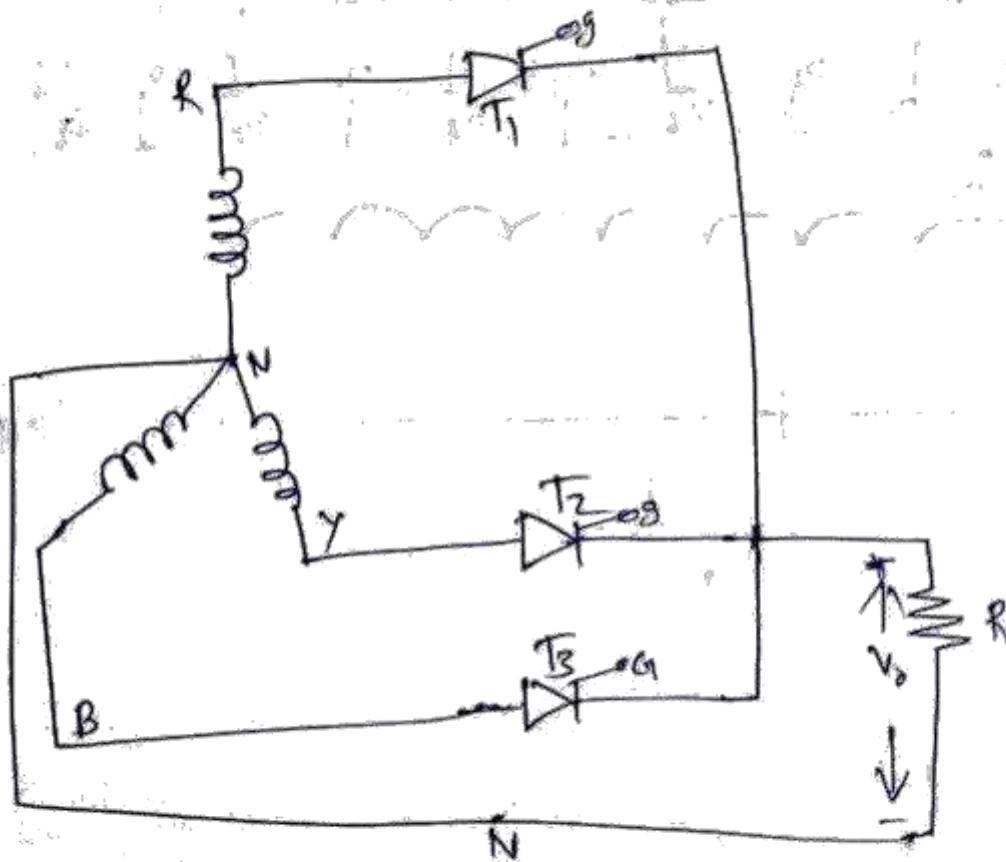

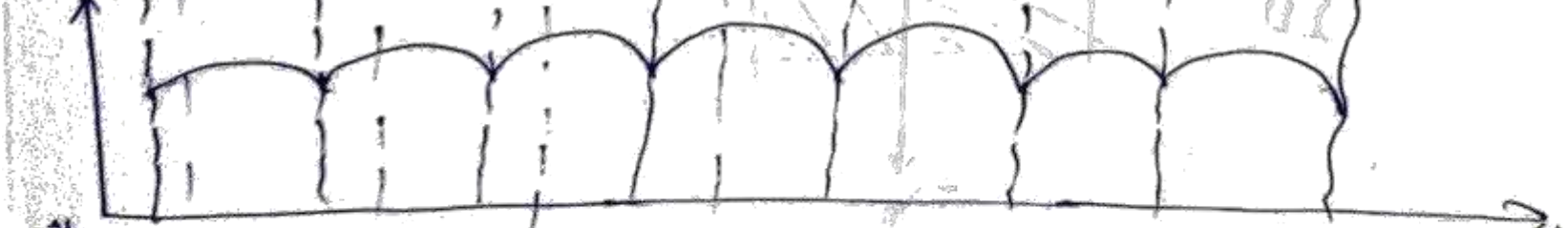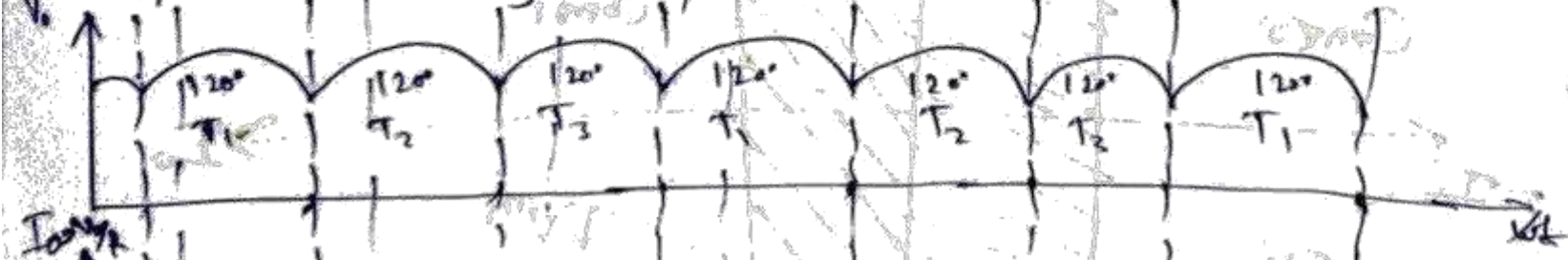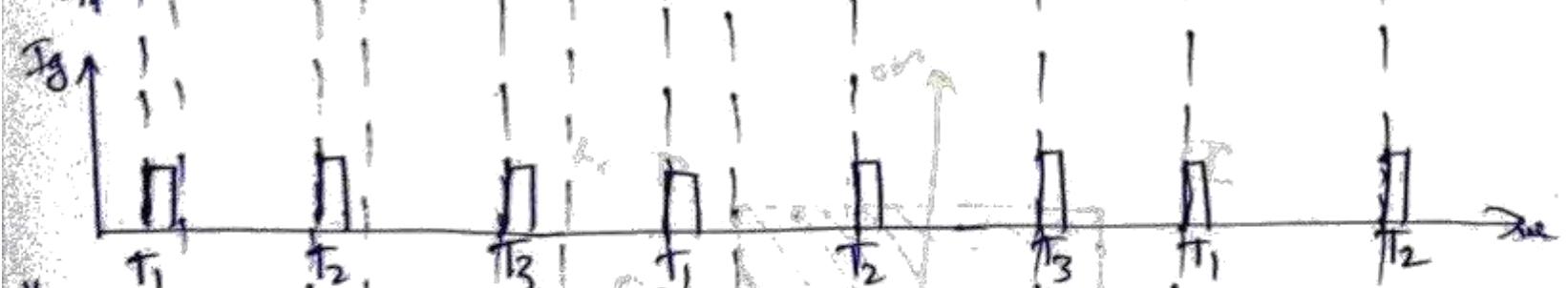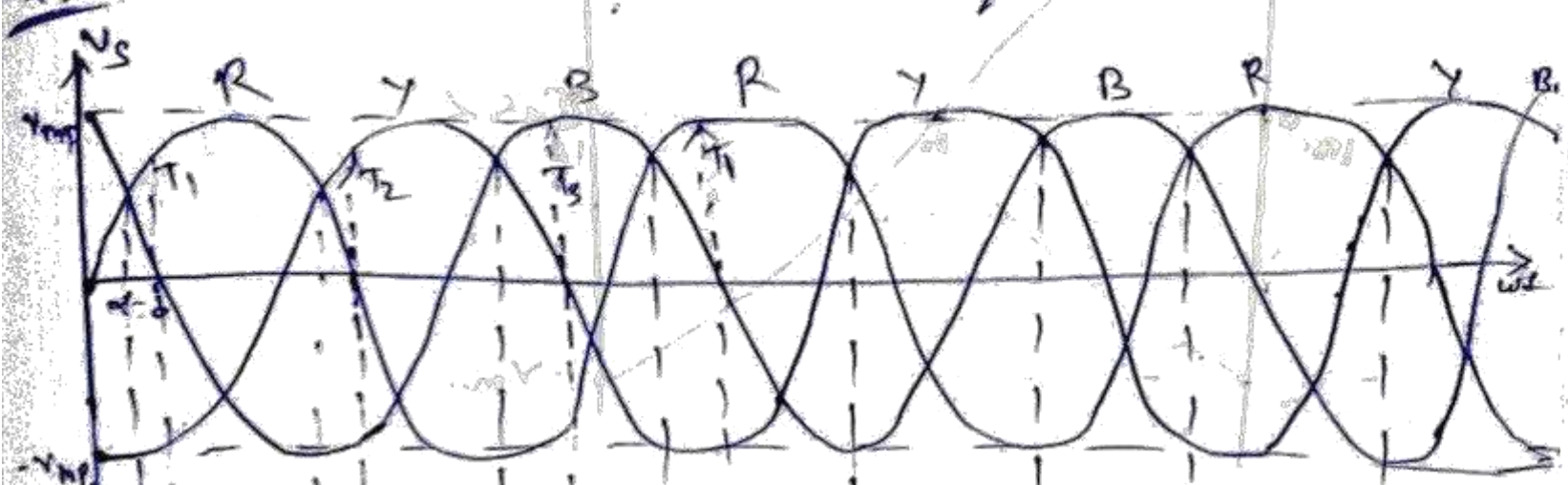



$$\Delta V_C = \frac{2\pi I}{F \cdot C} = \frac{2\pi \cdot 100 \text{ A}}{2500 \text{ Hz} \cdot 1000 \text{ F}} = 0.0004 \text{ V}$$

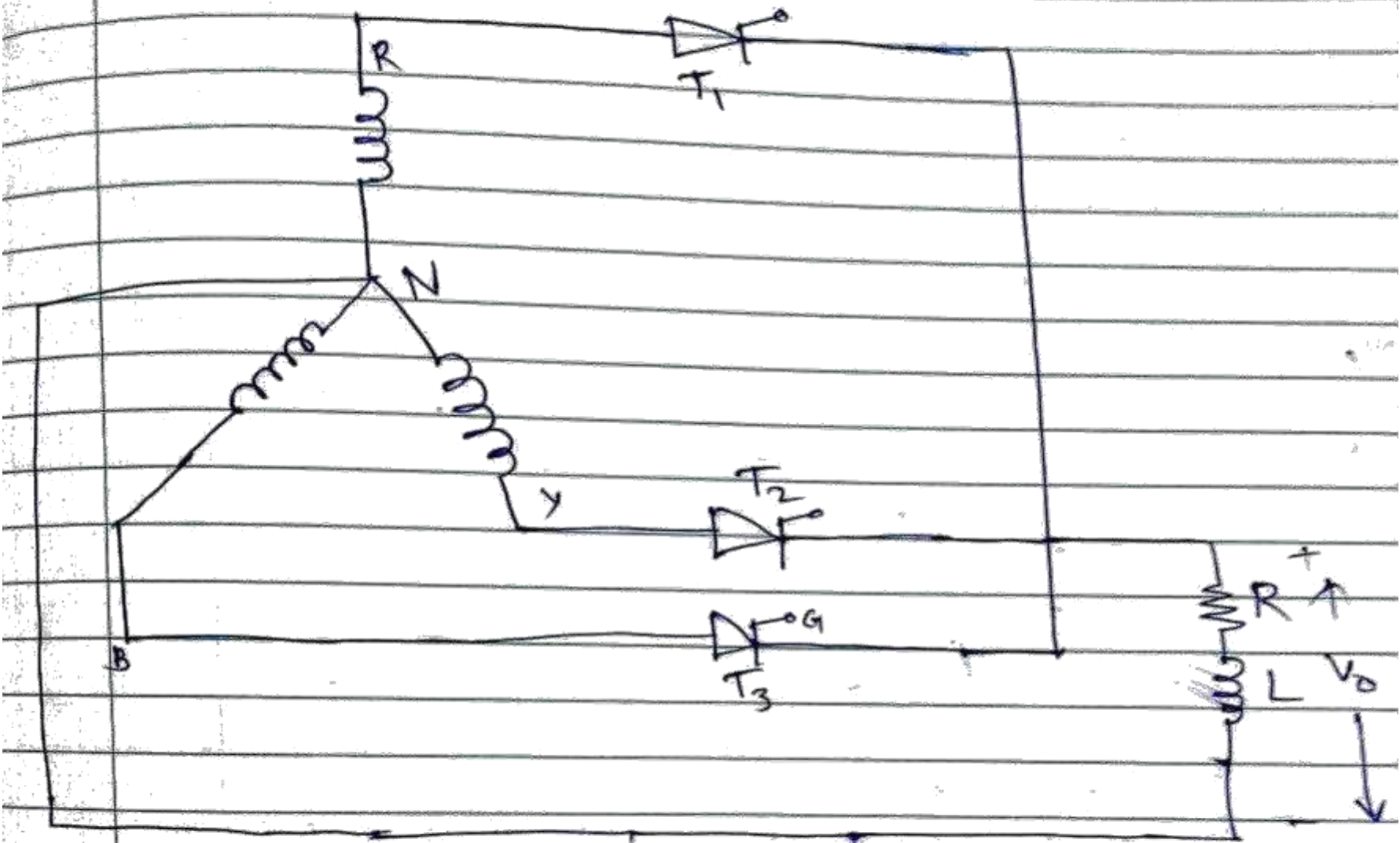* 3- ϕ half wave Converter with R-L Load :-



Teacher's Signature _____

$\alpha = 60$

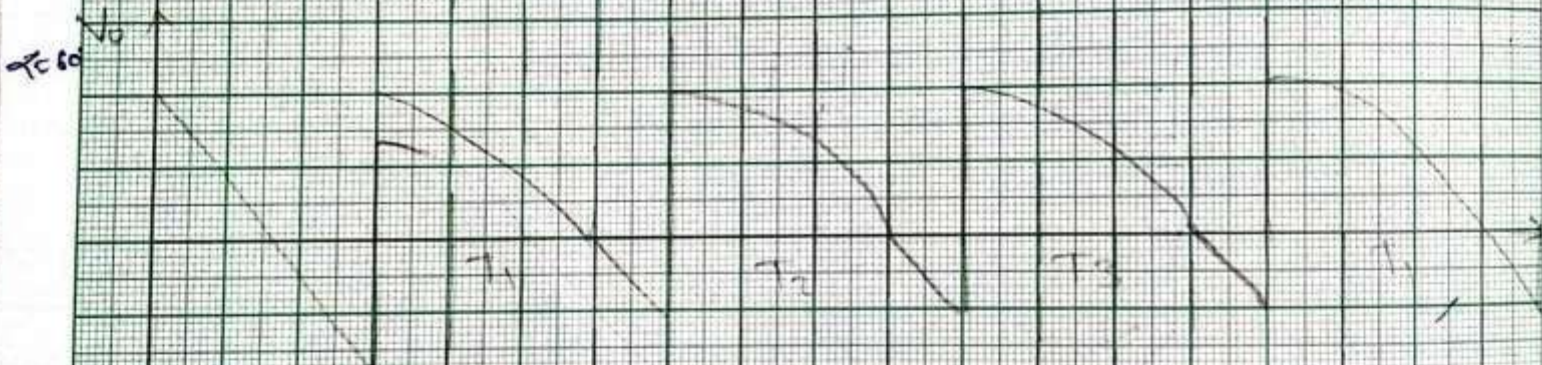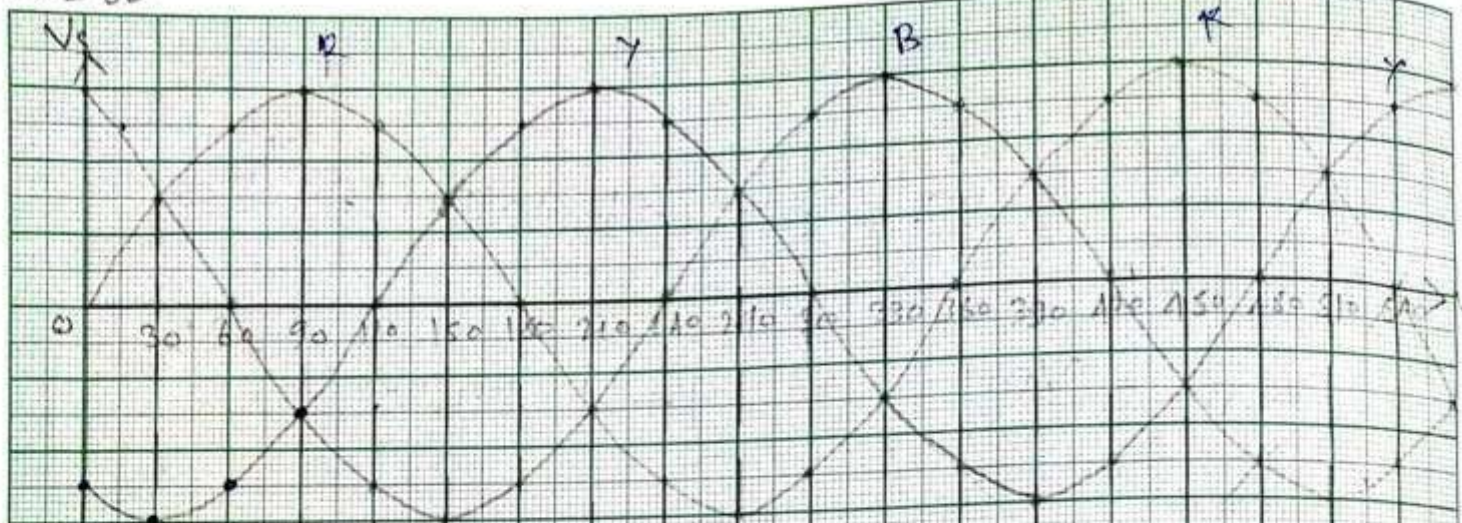

Average o/p Voltage :-

$$V_o = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_{mp} \sin \omega t \, d\omega t$$



$$= \frac{3\sqrt{3} V_{mp}}{2\pi} \cos \alpha \quad (\text{or})$$

$$V_o = \frac{3V_{ml}}{2\pi} \cos \alpha$$

$$I_o = \frac{V_o}{R}$$

3- ϕ half wave converter with R-L Load with Free wheeling


Date _____

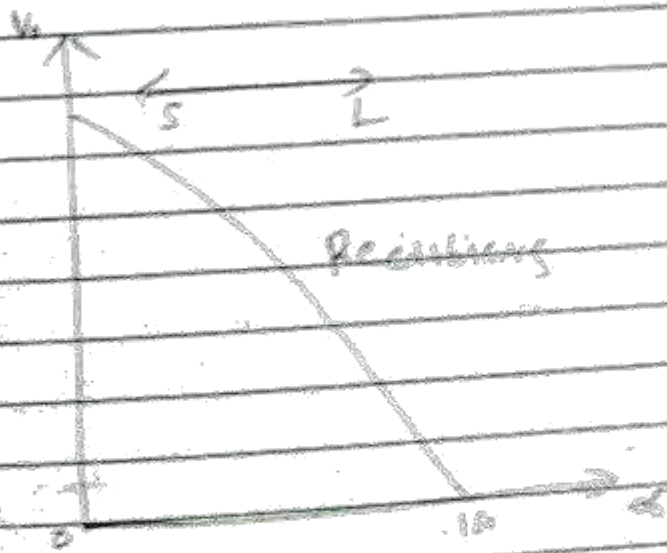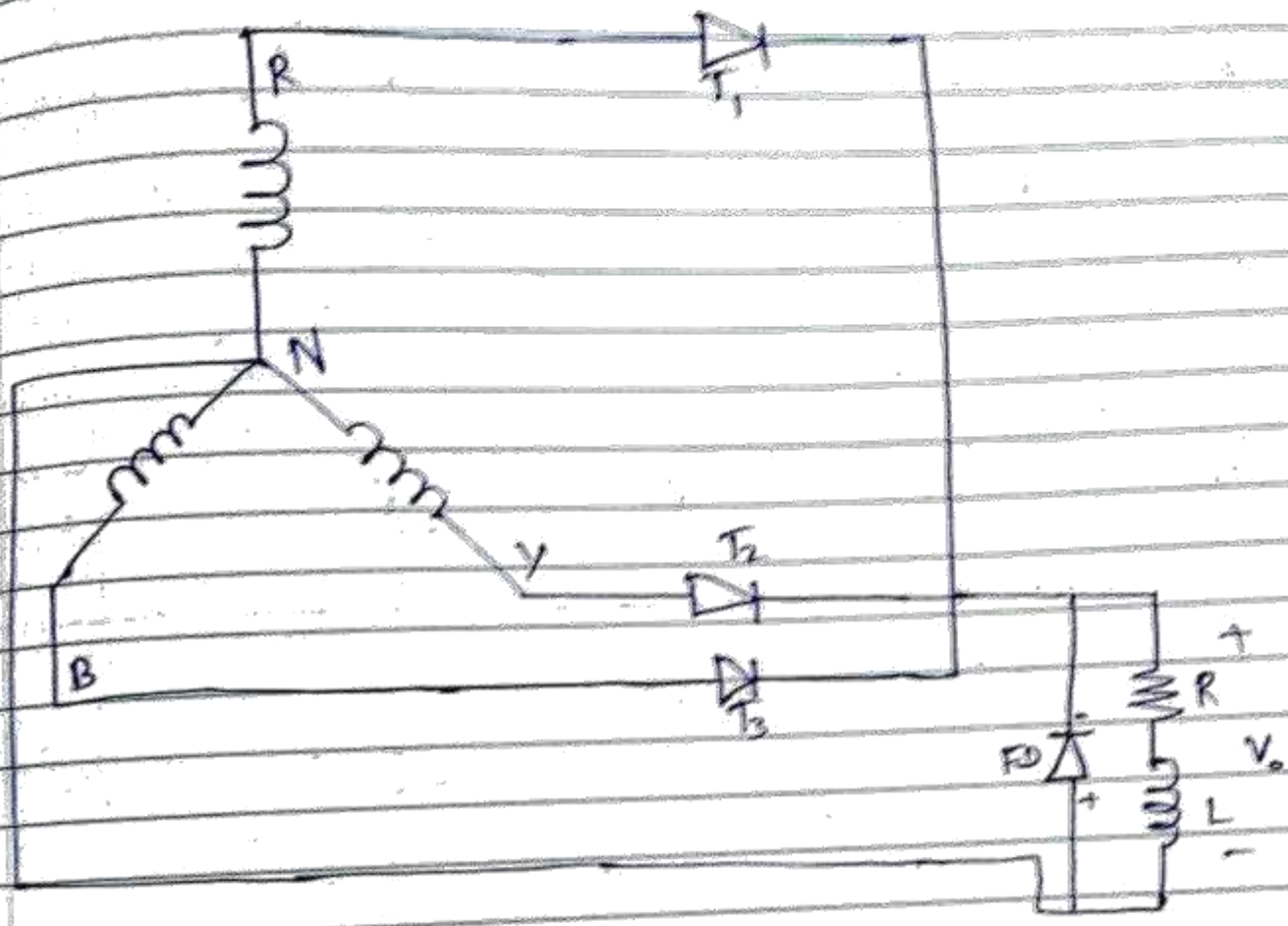

$$V_o = \frac{3\sqrt{3} V_{ms}}{2\pi} (1 + \cos \alpha)$$


Teacher's Signature _____

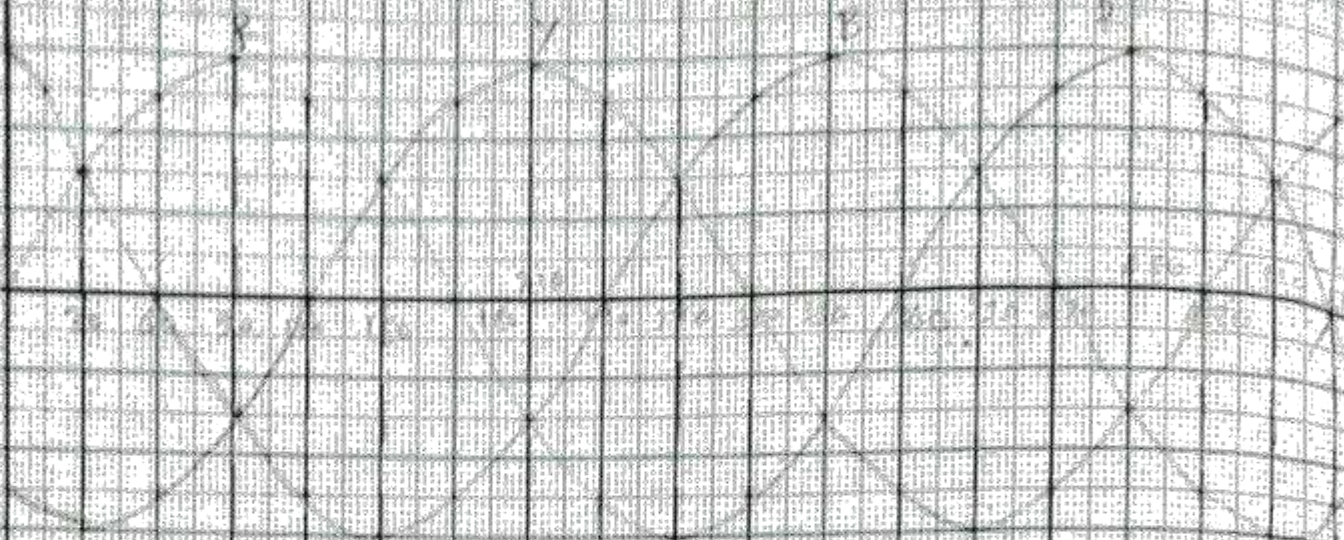3- ϕ , 120° with R-L load & free wheeling Diode



3-Phase Fully Controlled Converter with R Load

Date _____

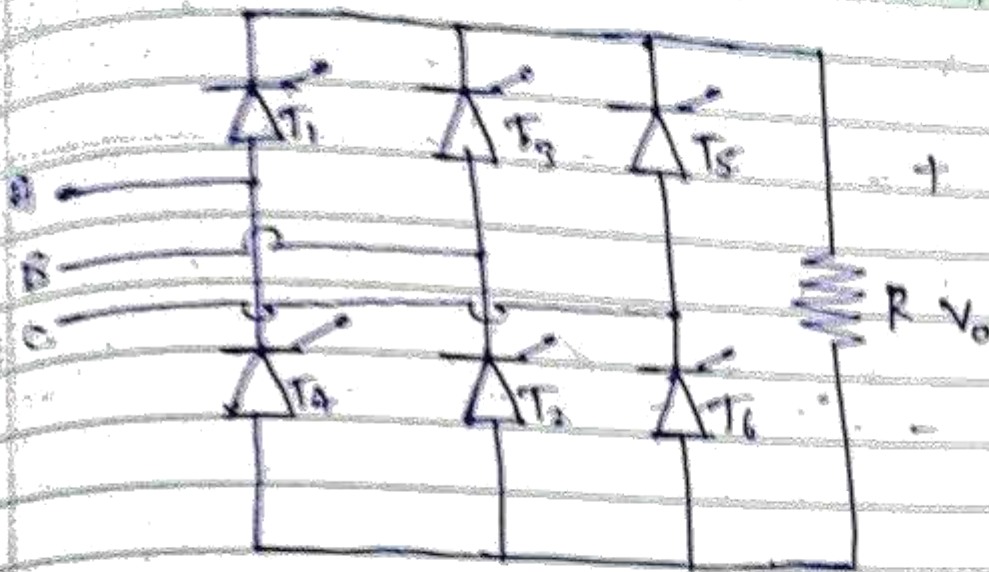

$$V_o = \frac{6}{2\pi} \int_{\pi+\pi/3}^{\pi+2\pi/3} V_m \sin \omega t \, d\omega t$$

$$= \frac{3V_m}{\pi} \left[\cos(\pi + \pi/3) - \cos(\pi + 2\pi/3) \right]$$

$$V_o = \frac{3V_m}{\pi} \cdot 0.866$$

$$I_o = \frac{V_o}{R}$$

$$I_o = \frac{V_o}{R}$$





$$V_{o, \text{RMS}} = \left[\frac{6}{2\pi} \int_{\pi+\pi/3}^{\pi+2\pi/3} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$= \frac{3V_m}{\sqrt{\pi}} \left[\int_{\pi+\pi/3}^{\pi+2\pi/3} \frac{1 - \cos 2\omega t}{2} \, d\omega t \right]^{1/2}$$

$$= \frac{3V_m}{\sqrt{\pi}} \left[\left(\frac{\pi}{3} \right) - \frac{1}{2} \sin 2\pi \right]^{1/2}$$


Teacher's Signature _____

S.C.M

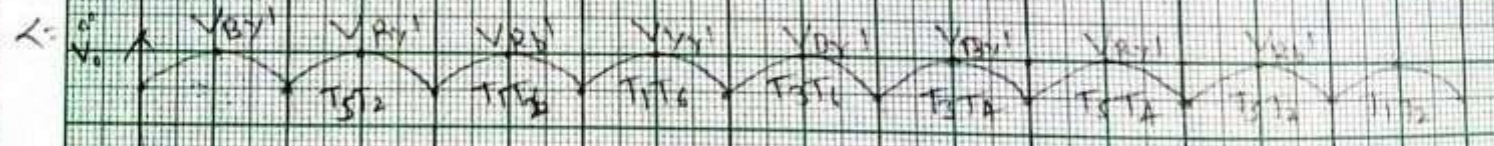
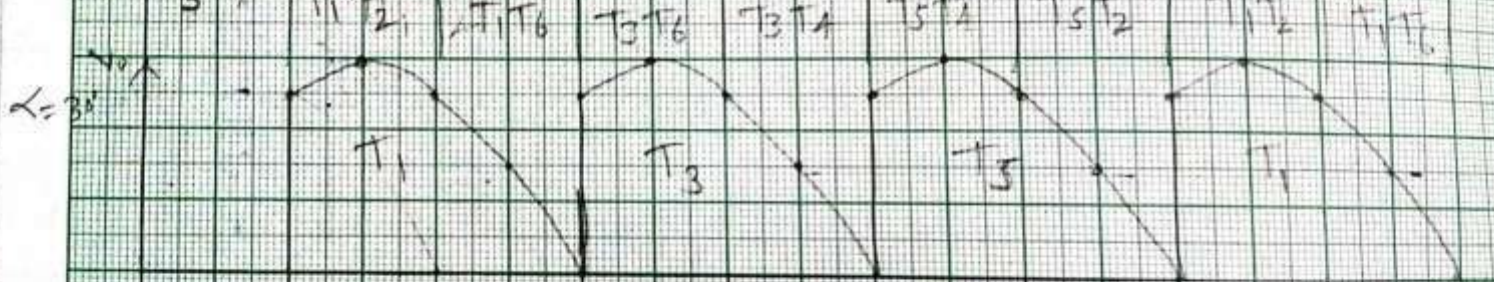
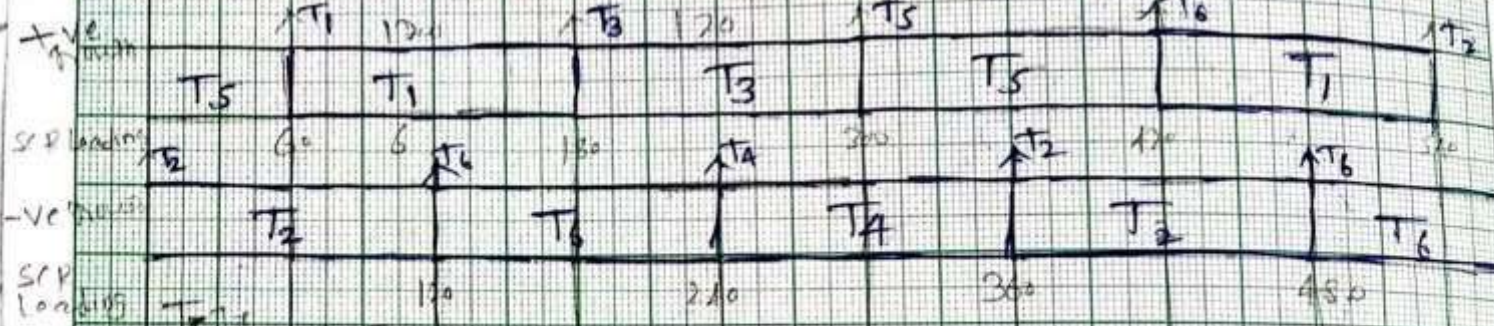
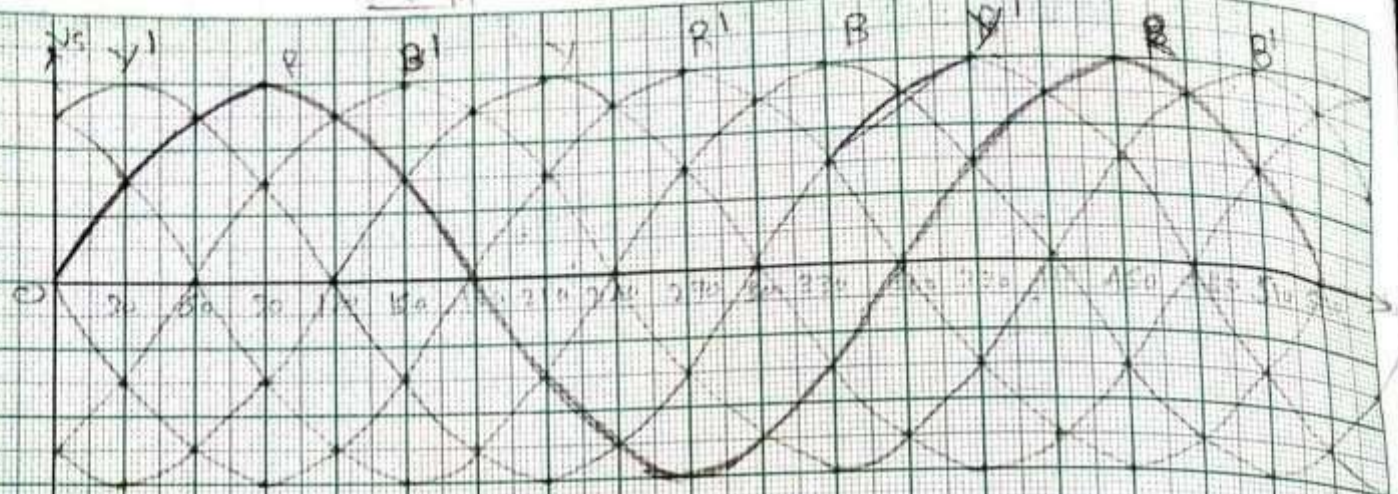


3- ϕ Fully Controlled Converter with R-L Load


Date _____

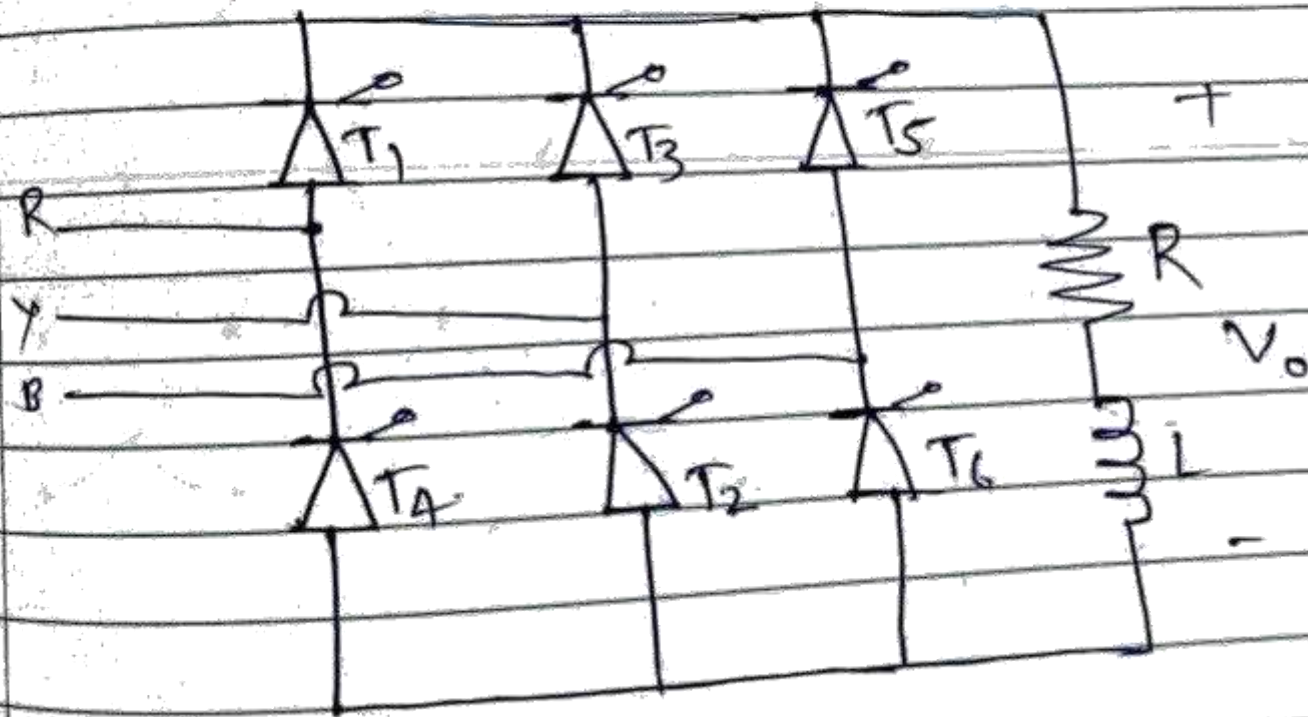

$\alpha = 90 + 60 = 150^\circ$, D.C.M

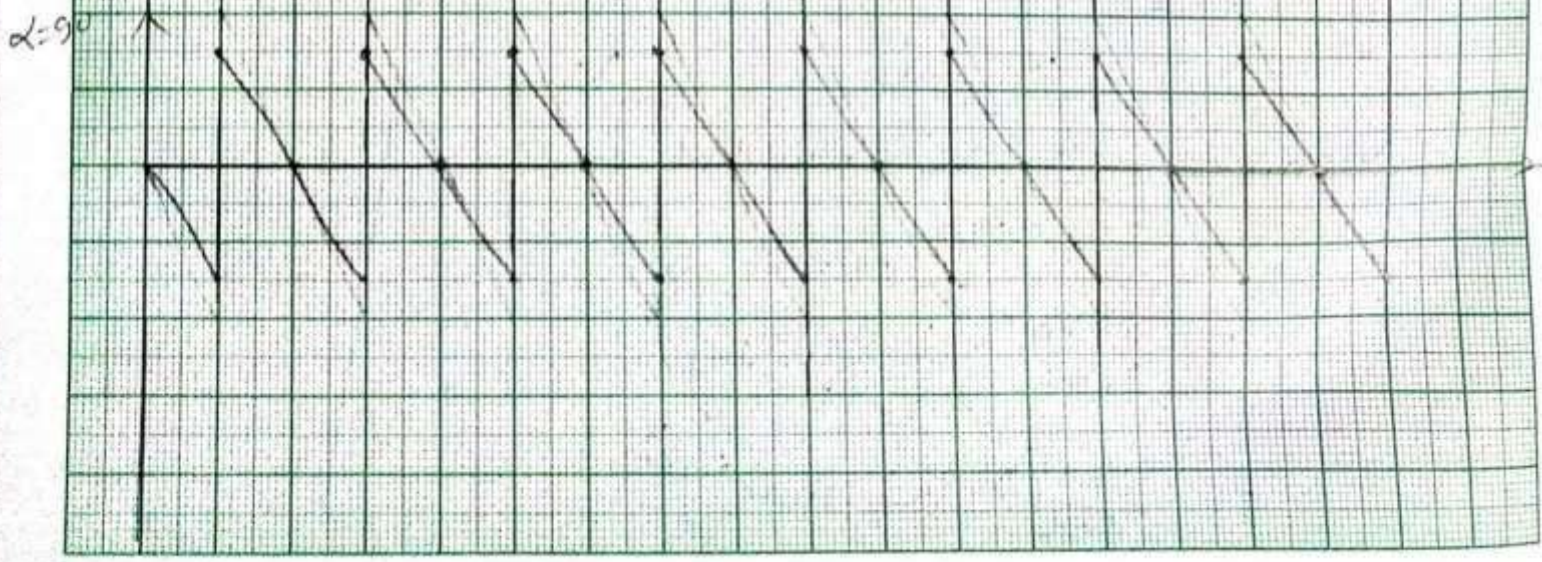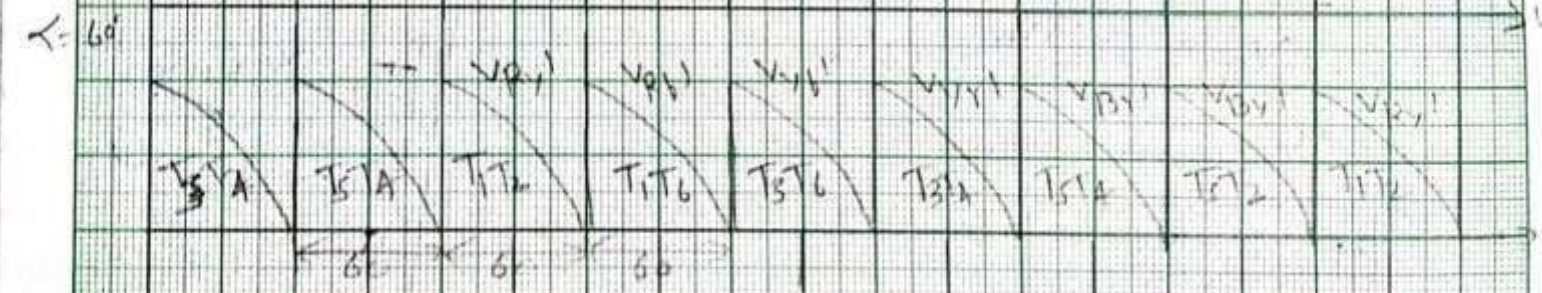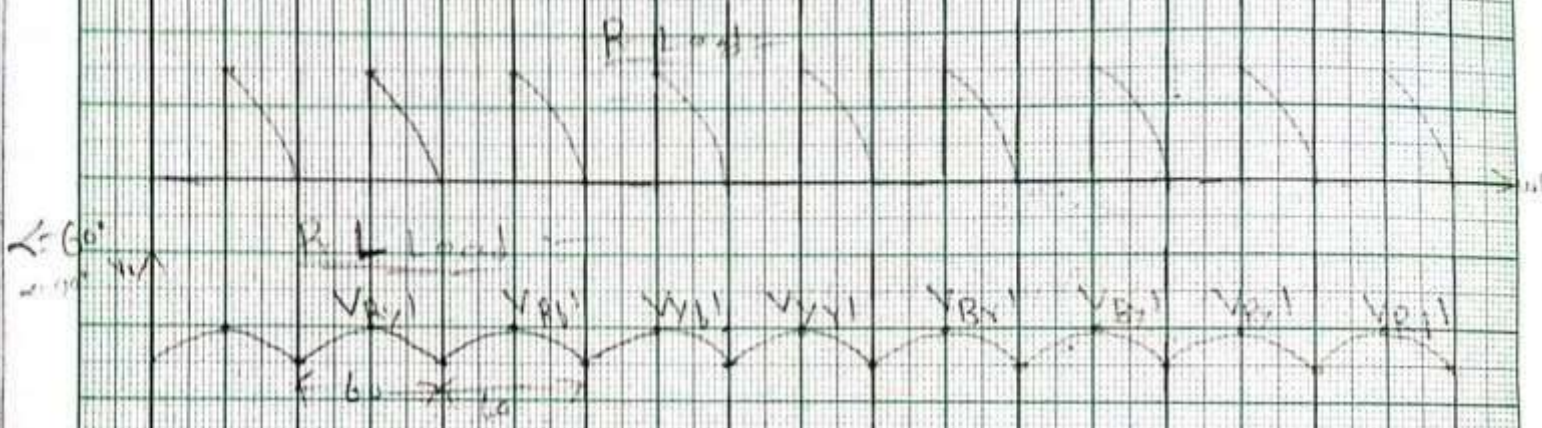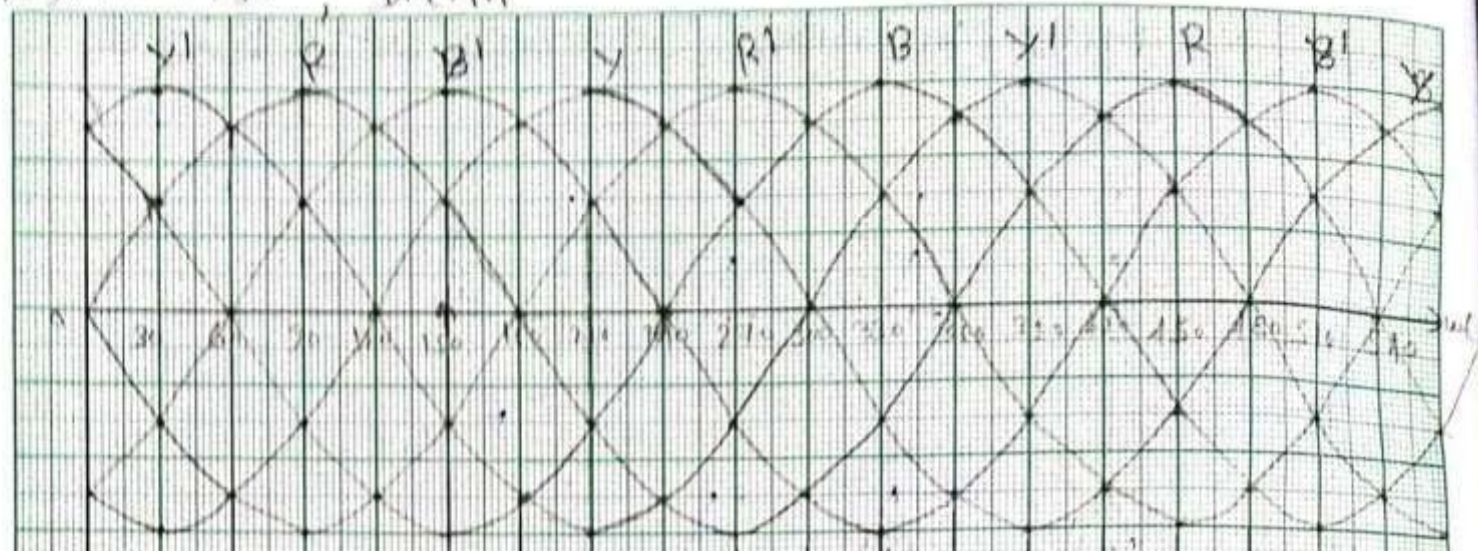


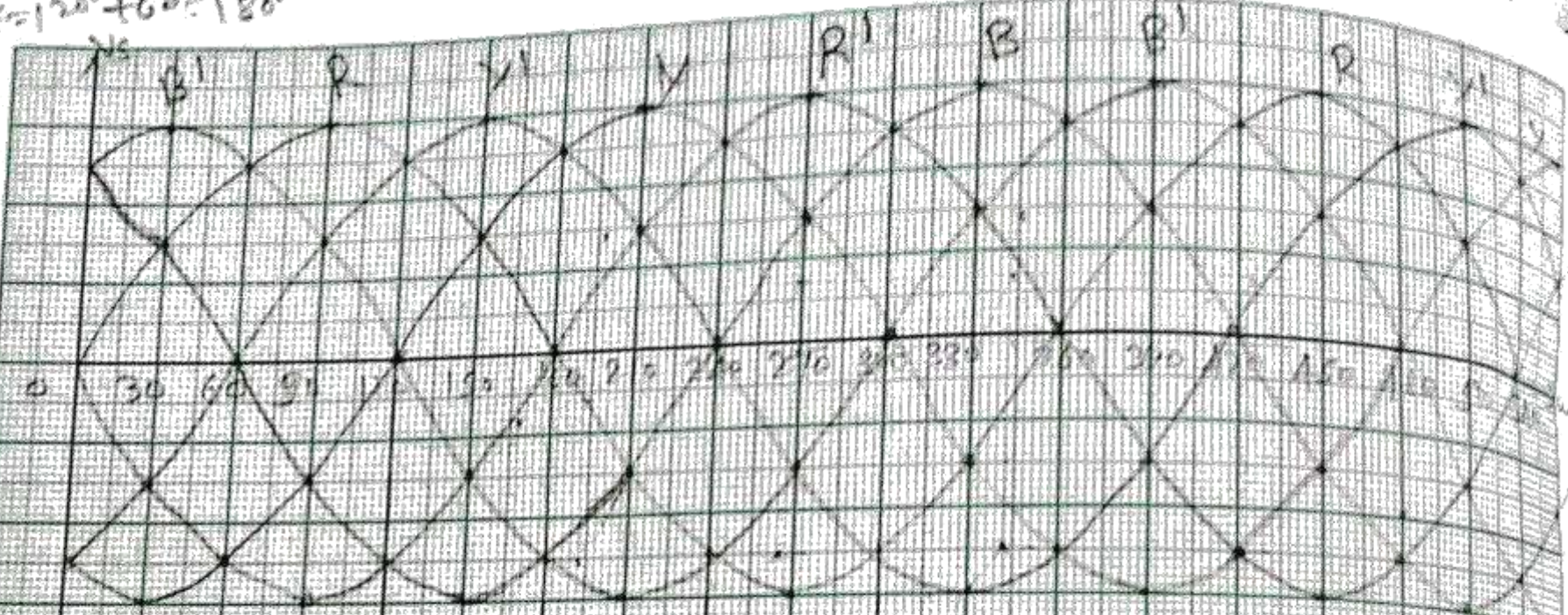$\text{width} = 120^\circ + 60^\circ = 180^\circ$



\angle




$\leftarrow 180 \rightarrow$

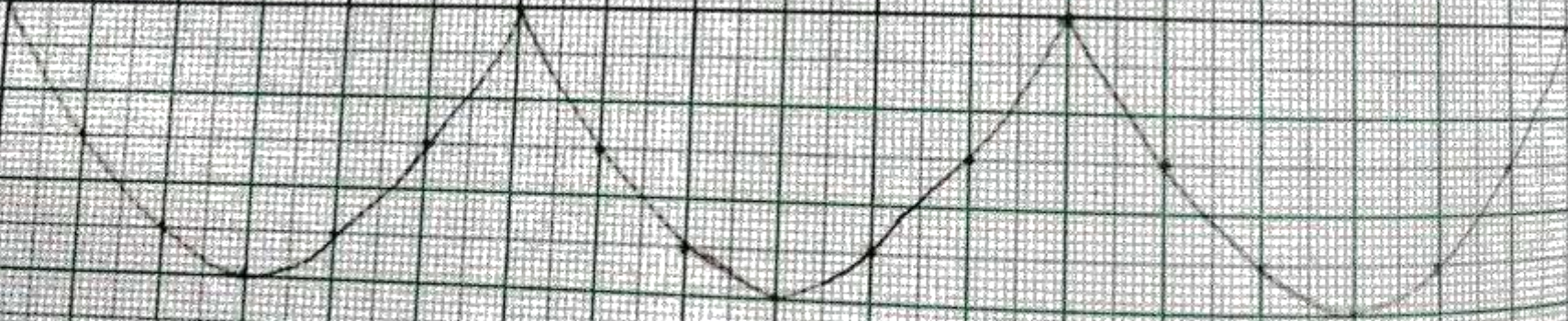


6
30
30
90

Dual Converter



1-8 (or) 3-6 Fully Controlled Converters

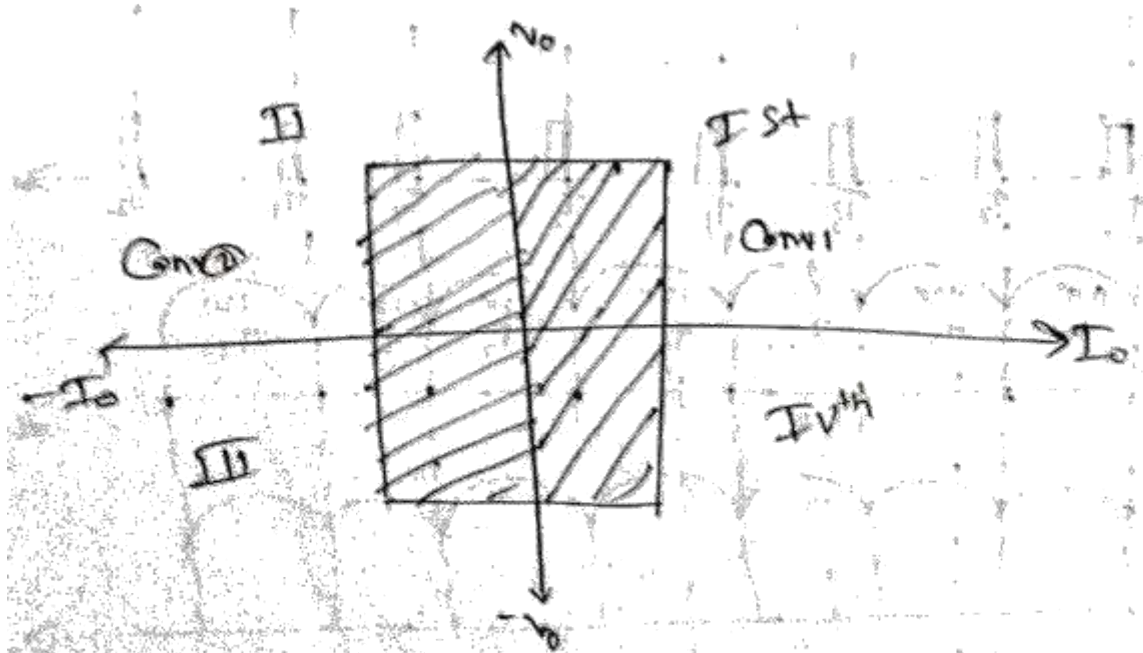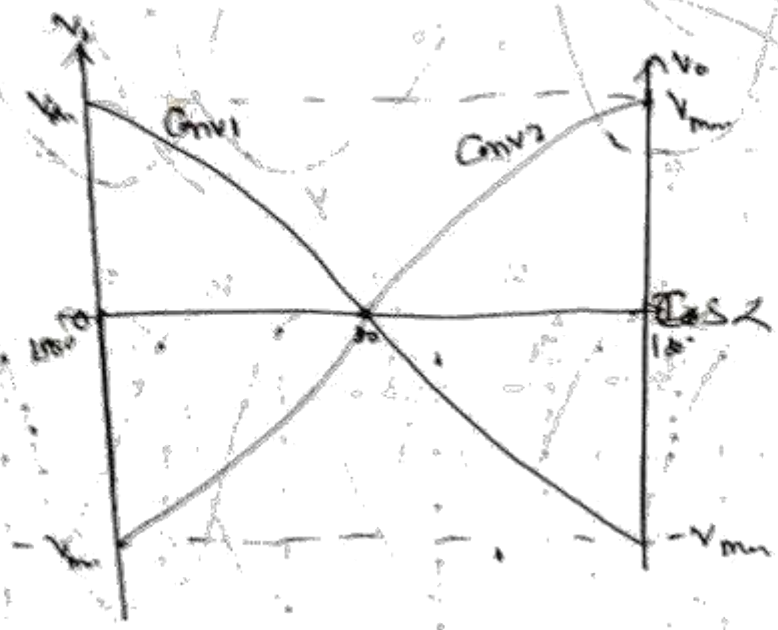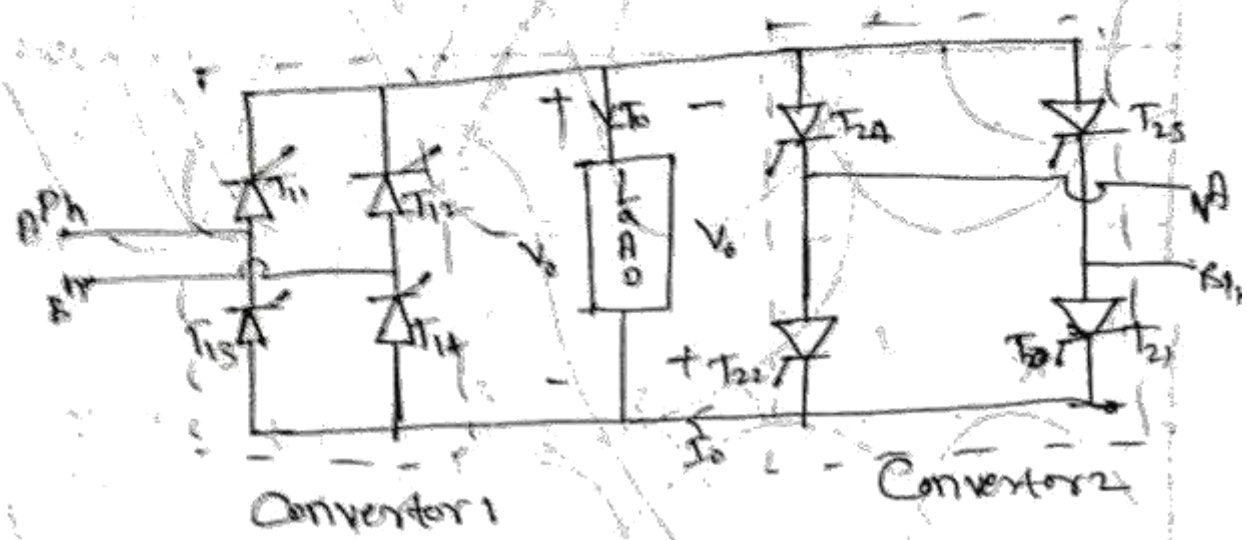

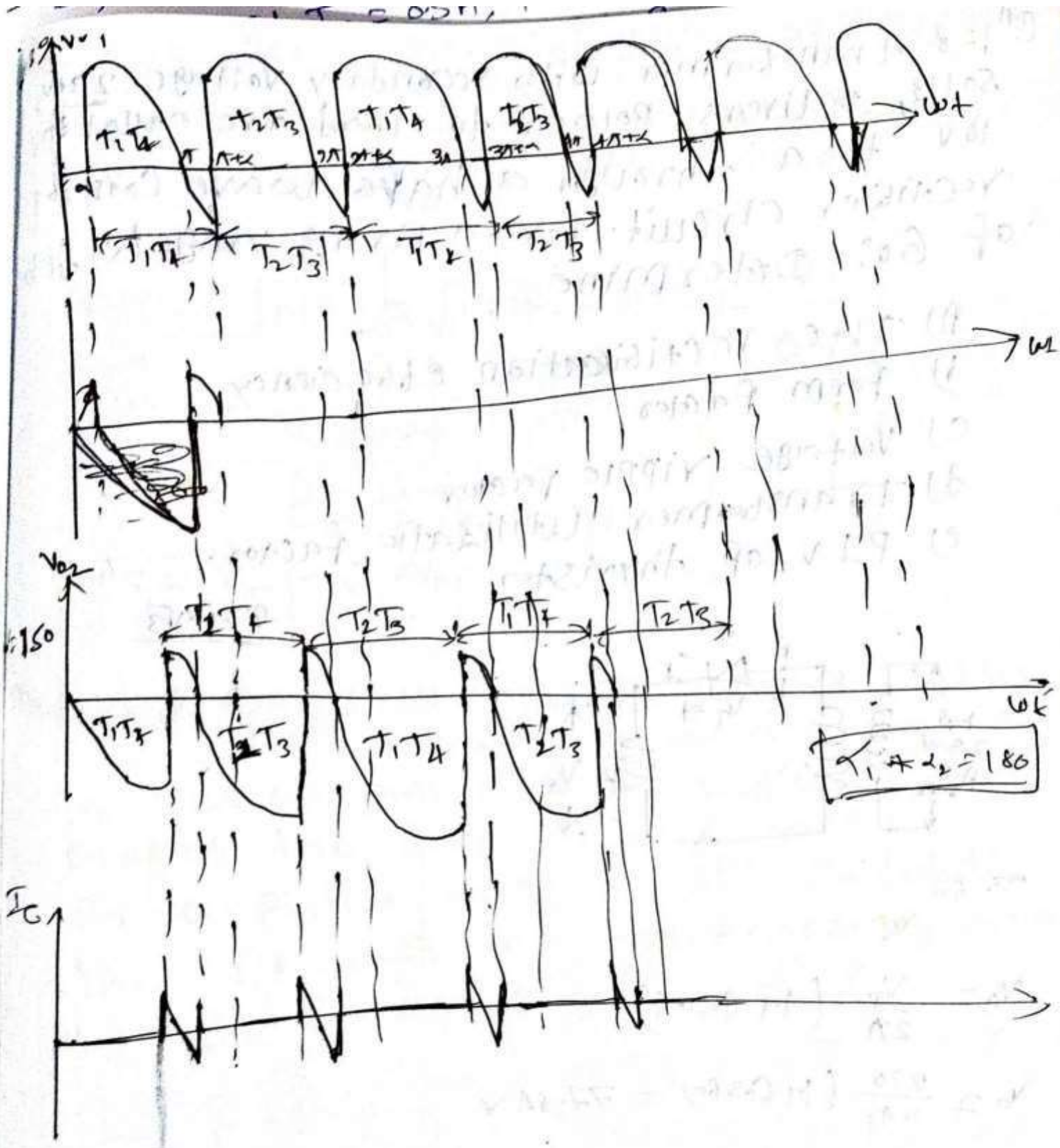

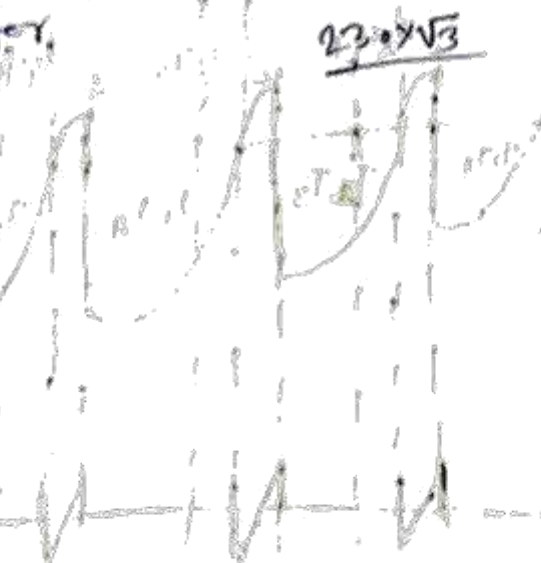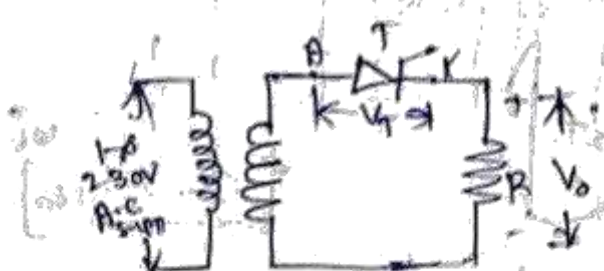Q1) A transformer with secondary voltage 230V, 50Hz, delivers power to load ac called to 10V through a half wave controlled rectifier circuit. For a firing angle delay of 60° . Determine

- The rectification efficiency
- Form factor
- Voltage ripple factor
- Transformer utilization factor.
- PIV of thyristor.



$T = 60$

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$V_o = \frac{230}{2\pi} (1 + \cos 60) = 77.64 \text{ V}$$

$$I = \frac{V_o}{R} = \frac{77.64}{10} = 7.7 \text{ A}$$

out put ac power (P_{ac}) = $V_{orms} \times I_{orms}$

$$V_{orms} = \frac{V_m}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$= \frac{\sqrt{2} \times 230}{2\sqrt{\pi}} \left[(\pi - \pi/3) + \frac{1}{2} \sin 120 \right]^{1/2}$$

$$= 145.86 \text{ V}$$

$$I_{orms} = \frac{V_{orms}}{R} = \frac{145.86}{10} = 14.58 \text{ A}$$

$$P_{ac} = 145.86 \times 14.58 = 602.8 \text{ W}$$

$$\eta = \frac{P_{ac}}{P_{dc}} = \frac{V_o I_o}{V_{rms} I_{rms}} = \frac{602.86}{2127.8} = 0.283 = 28.35\%$$

$$\text{Form Factor} = \frac{V_{rms}}{V_o} = \frac{145.87}{97.64} = 1.49$$


$$VRF = \sqrt{FF^2 - 1} = \sqrt{1.829^2 - 1} = 1.5$$

$$TUF = \frac{V_o I_o}{V_s I_{s(rms)}} = \frac{602.86}{230 \times 14.54} = 0.17$$

$$I_s = I_{rms}$$

$$PIV = V_m = \sqrt{2} \times V_{rms} = 325$$

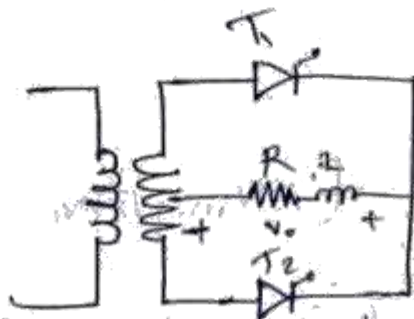Q. A 1- ϕ Conv Full Converter connected to 230V, 50Hz source is leading a load equal to 10Ω in series with a large inductor, that makes the load current ripple. For a firing angle of 45° , calculate the i/p and o/p performance parameters of this converter.



$$V_o = \frac{2V_m}{\pi} \cos \alpha = \frac{2 \times \sqrt{2} \times 230}{\pi} \cos(45^\circ) = 146.42V$$

$$I_o = \frac{V_o}{R} = \frac{146.42}{10} = 14.64A$$

$$V_{o(rms)} = \frac{V_m}{\sqrt{\pi}} \left[(\pi) + \frac{1}{2} \sin 2(\pi + \alpha) \right]^{1/2}$$

$$= \frac{230 \times \sqrt{2}}{\sqrt{\pi}} \left[(\pi) + \frac{1}{2} \sin 2(\pi + 45^\circ) \right]^{1/2}$$

$$V_{o(rms)} =$$

$$I_{o(rms)} = \frac{V_{o(rms)}}{R} = 14$$

$$\gamma = \frac{P_{dc}}{P_{a.c.}} = \frac{V_o I_o}{V_{rms} I_{rms}}$$

$$FF = \frac{V_{o,rms}}{V_o} = 1.57$$

$$VRV = \sqrt{FF^2 - 1} = \sqrt{1.57^2 - 1} = 1.21$$

$$TUF = \frac{V_o I_o}{V_s I_s} = \frac{116.42 \times 14.64}{230 \times 14.64}$$

CRF (Current ripple factor) = 0

$$I_s = \frac{2\sqrt{2} I_o}{\pi} = 13.18$$

$$\theta_1 = -\alpha, \theta_2 = -145^\circ$$

Displacement factor = $\cos \alpha = 0.707$

Total input current

$$I_s = I_o = 14.64 \text{ A}$$

Active power (P) = $V_o I_o$

$$P = V_s I_s \cos \phi$$

$$= V_s \left(\frac{2\sqrt{2} I_o}{\pi} \right) \cos \alpha$$

$$= \frac{2V_m I_o}{\pi} \cos \alpha$$

$$= V_o I_o$$

$$= 2143.7 \text{ W}$$

Reactive power = $\frac{2V_m}{\pi} I_o \sin \alpha$

$$Q = V_s I_s \sin \alpha$$

$$Q = V_s \left(\frac{2\sqrt{2} I_o}{\pi} \right) \sin \alpha$$

$$= V_s \frac{2V_m}{\pi} I_o \sin \alpha = 4910.42 \text{ W}$$

$$= V_o I_o \sin \alpha$$